

Project 2: Digital Electronics using HDL

Nahin Ul Sadad
Lecturer
CSE, RUET

প্রশ্নঃ Real life এ Digital IC (like
Microprocessor/Network Switch) কিভাবে
ডিজাইন করা হয়?

উত্তরঃ HDL এ Code করে Digital IC ডিজাইন করা হয়। কারণ হাতে Schematics draw/Breadboard এ Prototype করা impractical।

প্রশ্ন: HDL কি?

উত্তরঃ In computer engineering, a hardware description language (HDL) is a specialized computer language used to describe the structure and behavior of electronic circuits, and most commonly, digital logic circuits. - Wikipedia

প্রশ্নঃ HDL এবং High level programming language যেমন C এর মধ্যে পার্থক্য কি?

উত্তরঃ HDL is not a programming language. It just describes logic circuits. But C itself a programming language.

HDL code works concurrently. But C code works sequentially.

প্রশ্নঃ HDL শিখার সুবিধা কি?

উত্তরঃ Knowing HDL is the first requirement of almost every hardware engineer job.

প্রশ্নঃ HDL code এ লিখা digital circuit
সরাসরি run করার উপায় আছে?

উত্তৰঃ হ্যা আছে। FPGA ব্যৱহাৰ কৰে।

প্রশ্ন: FPGA কাকে বলে?


উত্তরঃ A field-programmable gate array (FPGA) is an integrated circuit designed to be configured by a customer or a designer after manufacturing – hence the term "field-programmable".

The FPGA configuration is generally specified using a hardware description language (HDL).

– Wikipedia


Field-Programmable Gate Array (FPGA)

 - ◆ First introduced by Xilinx in 1985
- ◆ Arrays of logic blocks (to implement logic functions)
- ◆ Lots of programmable wiring in routing channels
- ◆ Very flexible I/O interfacing logic core to outside world
- ◆ Two dominant FPGA makers:
 - Xilinx and Altera
- ◆ Other specialist makers e.g. Actel and Lattice Logic




Configurable Logic Block (CLB)

 - ◆ Based around Look-up Tables (LUTs), most common with 4-inputs
- ◆ Optional D-flipflop at the output of the LUT
- ◆ 4-input LUT can implement ANY 4-input Boolean equation (truth-table)
- ◆ Special circuits for cascading logic blocks (e.g. carry-chain of a binary adder)





Logic Element
(LE)

 

- ◆ Each logic block has pins located for easy access:


Programmable Routing

  - ◆ Between rows and columns of logic blocks are wiring channels
- ◆ These are programmable – a logic block pin can be connected to one of many wiring tracks through a programmable switch
- ◆ Xilinx FPGAs have dedicated switch block circuits for routing (more flexible)
- ◆ Each wire segment can be connected in one of many ways:




The idea of configuring FPGA

- ◆ Programming an FPGA is NOT the same as programming a microprocessor
- ◆ We download a **BITSTREAM** (not a program) to an FPGA
- ◆ Programming an FPGA is known as **CONFIGURATION**
- ◆ All LUTs are configured using the BITSTREAM so that they contain the correct values to implement the Boolean logic
- ◆ Shown here is a typical implementation of a 4-LUT circuit
 - ABCD are the FOUR inputs
 - There is four level of 2-to-1 multiplexer circuits
 - The 16-inputs to the mux tree determine the Boolean function to be implemented as in a truth-table
 - These 16 binary values are stored in registers (DFF)
 - Configuration = setting the 16 registers to 1 or 0

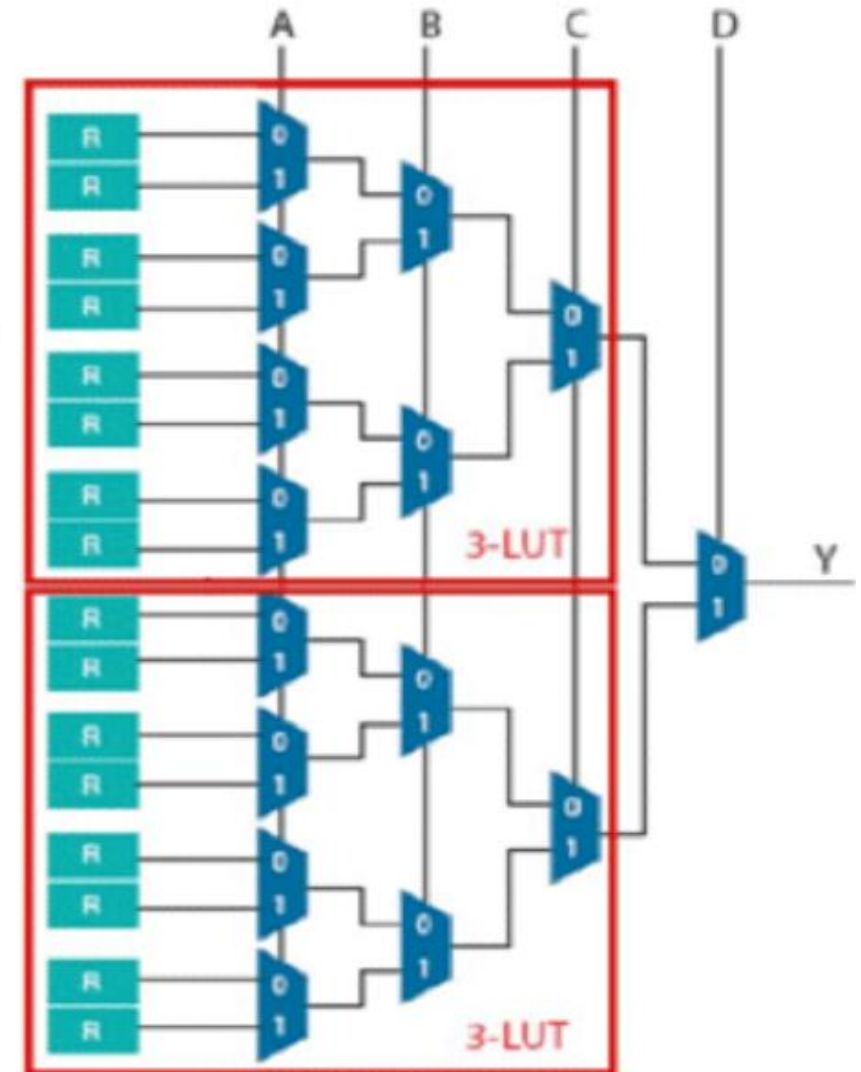

Typical VLSI Design Flow

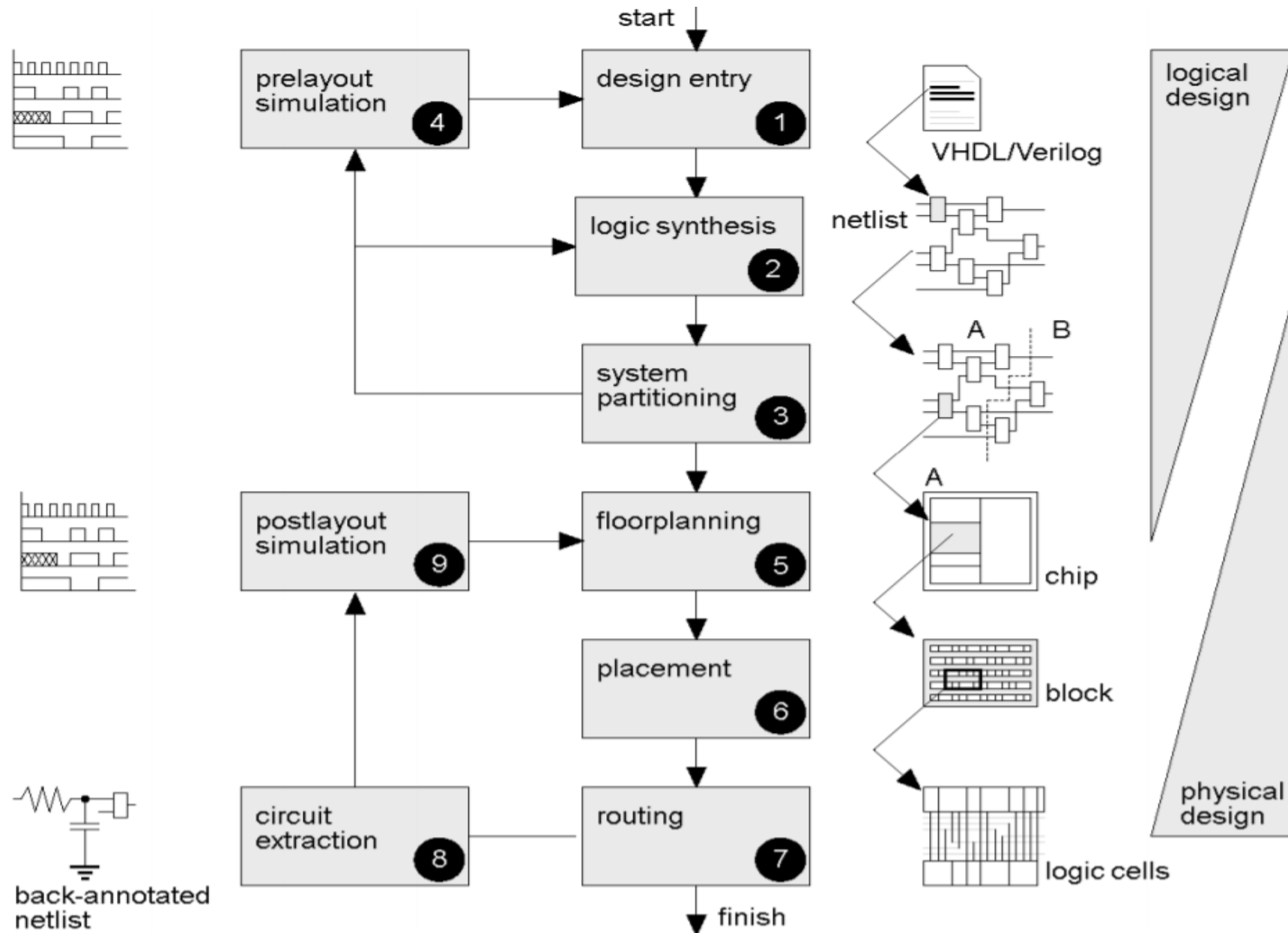

প্রশ্ন: What are names of some HDL
language?

উত্তর: Verilog, VHDL etc.

প্রশ্নঃ How to install Verilog?

উত্তরঃ To download and install Iverilog, Goto this site:
<http://bleyer.org/icarus/>

Follow this YouTube tutorial:
https://www.youtube.com/watch?v=hg9splN_83Y

Make sure to click “Add Icarus Verilog executables
folder to the system PATH”

উত্তরঃ For Linux installation,

```
sudo apt-get update
```

```
sudo apt-get install iverilog
```

```
sudo apt-get install gtkwave
```

প্রশ্ন: What should be IDE to write Verilog code?

উত্তরঃ My suggestion is VSCode. Goto to this link to download:

<https://code.visualstudio.com/download>

Follow this YouTube tutorial:


<https://www.youtube.com/watch?v=rwVFDfy2xVI>

Make sure to install Verilog addon for syntax highlighting.

প্রশ্নঃ Write a simple comparator logic circuit in Verilog?

Input x	Input y	Output z
0	0	1
0	1	0
1	0	0
1	1	1

উত্তরঃ

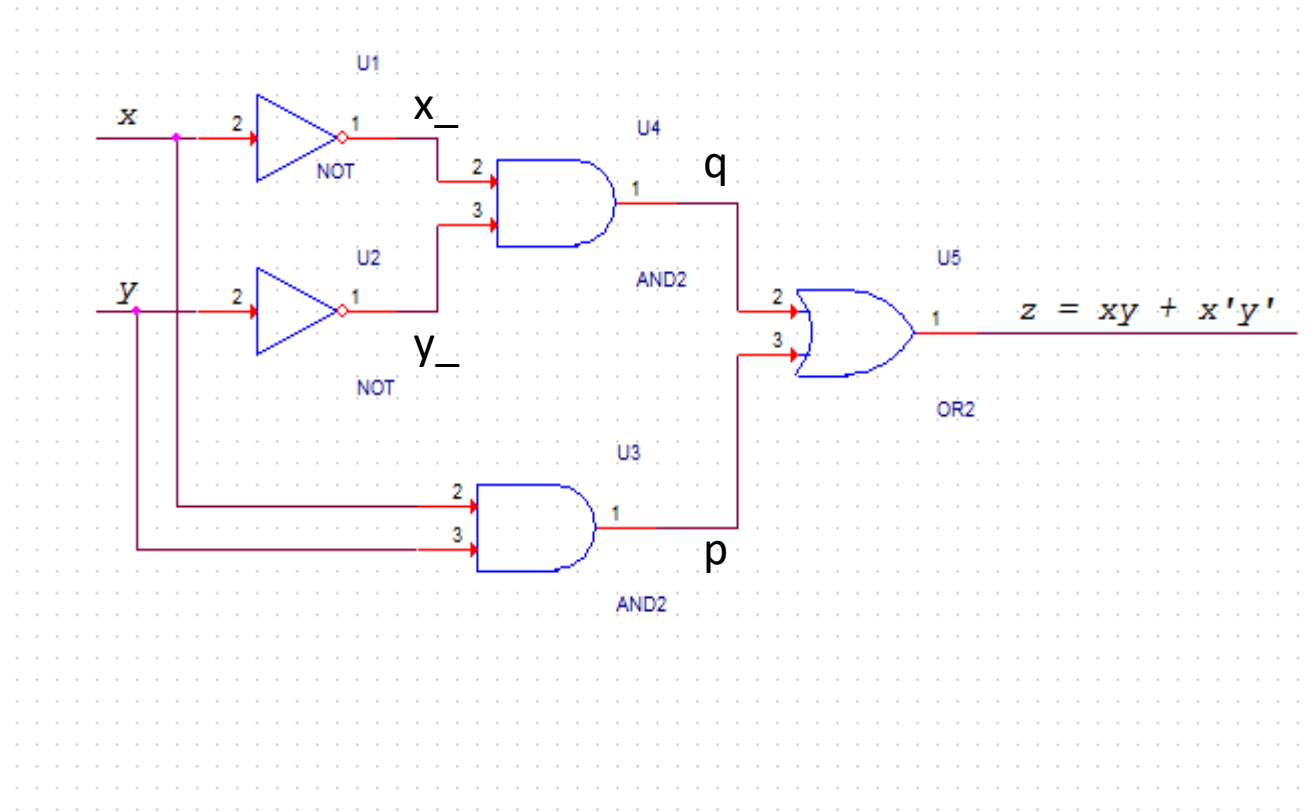

উত্তরঃ

```
module comparator
(
input x,
input y,
output z
);

wire x_, y_, p, q;
not(x_, x);
not(y_, y);
and(p, x, y);
and(q, x_, y_);
or(z, p, q);

endmodule
```

comparator.v

উত্তরঃ

```
module comparator
(
input x,
input y,
output z
);

wire x_, y_, p, q;
not(x_, x);
not(y_, y);
and(p, x, y);
and(q, x_, y_);
or(z, p, q);

endmodule
```

Logic function name

Input port names

Output port names

Internal wires

NOT/AND/OR gate (output, input)

Here we have used Gate Level Modelling.

**প্রশ্নঃ Verify a simple comparator logic circuit
written in Verilog?**

Input x	Input y	Output z
0	0	1
0	1	0
1	0	0
1	1	1

উত্তরঃ Verilog এ লেখা কোড verify করতে আমরা test bench লিখি।

```
`timescale 1ns / 1ps
module stimulus;
// Inputs
reg x;
reg y;
// Outputs
wire z;
// Instantiate the
//Unit Under Test
//(UUT)
comparator uut
(
.x(x),
.y(y),
.z(z)
);
```

```
initial begin
    // Initialize Inputs
    x = 0;
    y = 0;

    #20 x = 1;
    #20 y = 1;
    #20 y = 0;
    #20 x = 1;
    #40;
end
```

```
initial begin
    $monitor("x=%d,y=%d,z=%d \n",x,y,z);
end
```

```
endmodule
```

stimulus.v

উত্তরঃ Verilog এ লেখা কোড verify করতে আমরা test bench লিখি। এই test benchকে পরে simulation করা হয়।

Timescale

Simulation will run in steps of 1ns and has a precision value of 1ps.

Test bench name

Register

Inputs will be defined as reg.

Instantiation

It creates an instance of the comparator module.

```
`timescale 1ns / 1ps
module stimulus;
  // Inputs
  reg x;
  reg y;
  // Outputs
  wire z;
  // Instantiate the
  //Unit Under Test
  //(UUT)
  comparator uut
  (
    .x(x),
    .y(y),
    .z(z)
  );
```

initial begin

// Initialize Inputs

x = 0;

y = 0;

#20

x = 1;

#20

y = 1;

#20

y = 0;

#20

x = 1;

#40;

end

initial begin

\$monitor("x=%d,y=%d,z=%d \n",x,y,z);

end

endmodule

Initializing inputs at the beginning of simulation.

20 means
Wait for 20ns.

x = 1 means
X value will be
changed to 1 after
waiting 20ns.

\$monitor means
It will display the
values of x, y and z.

প্রশ্নঃ How to simulate Verilog program with test bench.

উত্তর: Go to terminal in VSCode and write:

```
iverilog -o out.vvp comparator.v stimulus.v  
# comment: out.vvp is the name output file after  
# compilation. "-o" defines output parameter.  
vvp out.vvp  
# comment: Show the output of the stimulus
```

```
#output:  
x=0,y=0,z=1  
x=1,y=0,z=0  
x=1,y=1,z=1  
x=0,y=1,z=0
```

প্রশ্নঃ How to show graphical
simulation/waveforms of Verilog program with
test bench.

উত্তর: We will be using gtkwave.

First, add these two new lines in test bench:

```
`timescale 1ns / 1ps
module stimulus;
// Inputs
reg x;
reg y;
// Outputs
wire z;
// Instantiate the
//Unit Under Test
//(UUT)
comparator uut
(
.x(x),
.y(y),
.z(z)
);
```

```
initial begin
$dumpfile("test.vcd");
$dumpvars(0,stimulus);
// Initialize Inputs
x = 0;
y = 0;

#20 x = 1;
#20 y = 1;
#20 y = 0;
#20 x = 1;
#40;
end

initial begin
$monitor("x=%d,y=%d,z=%d \n",x,y,z);
end


endmodule
```

stimulus.v


উত্তর: Go to terminal in VSCode and write:

```
iverilog -o out.vvp comparator.v stimulus.v  
# comment: out.vvp is the name output file after  
# compilation. "-o" defines output parameter.  
vvp out.vvp  
# comment: Show the output of the stimulus  
gtkwave test.vcd &  
# It will show graphical simulation.
```


উত্তরঃ

 


উত্তরঃ

 


উত্তরঃ

 


উত্তরঃ

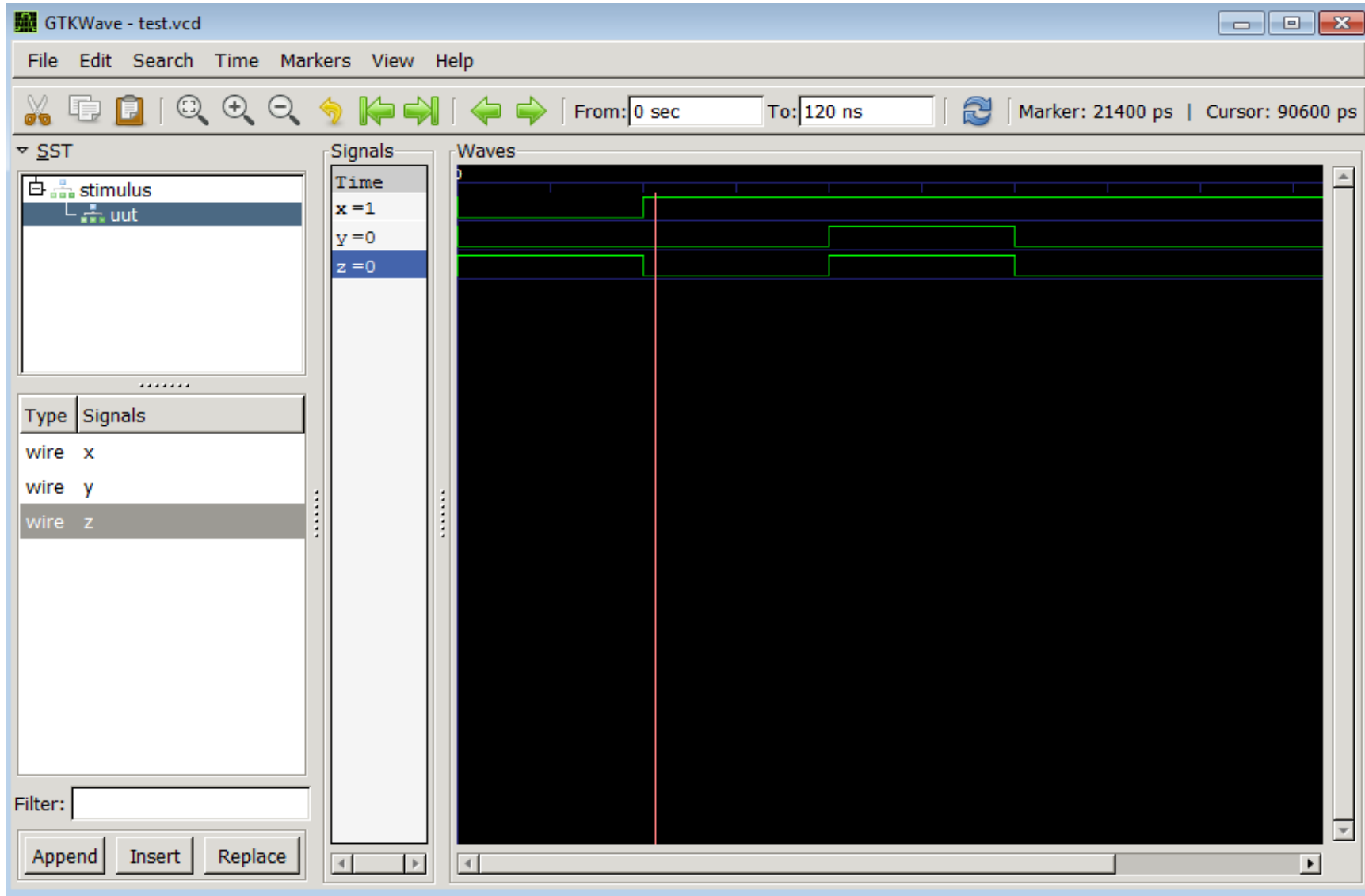

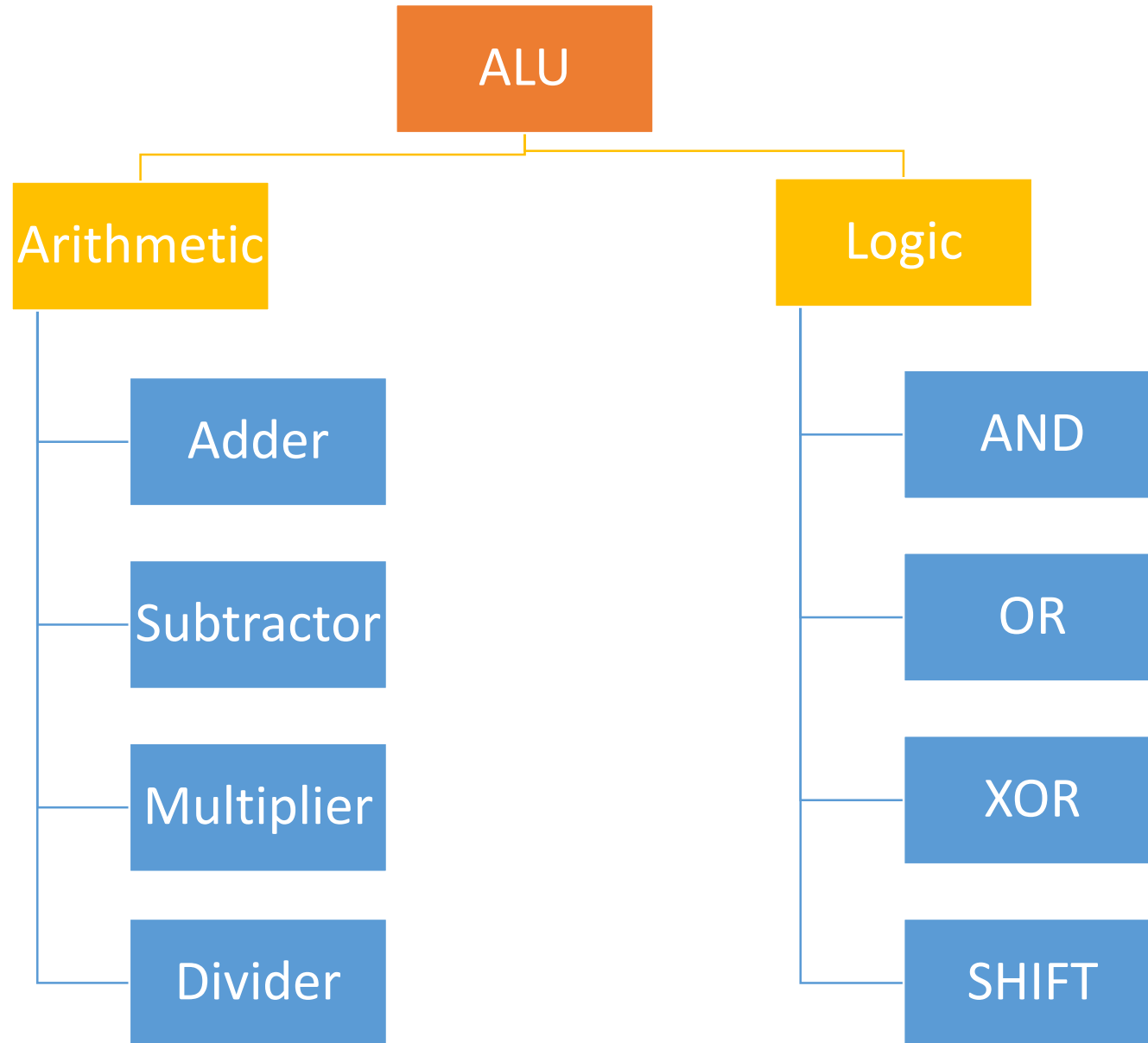Next Day:
ALU Design I: Shifter &
Multiplier



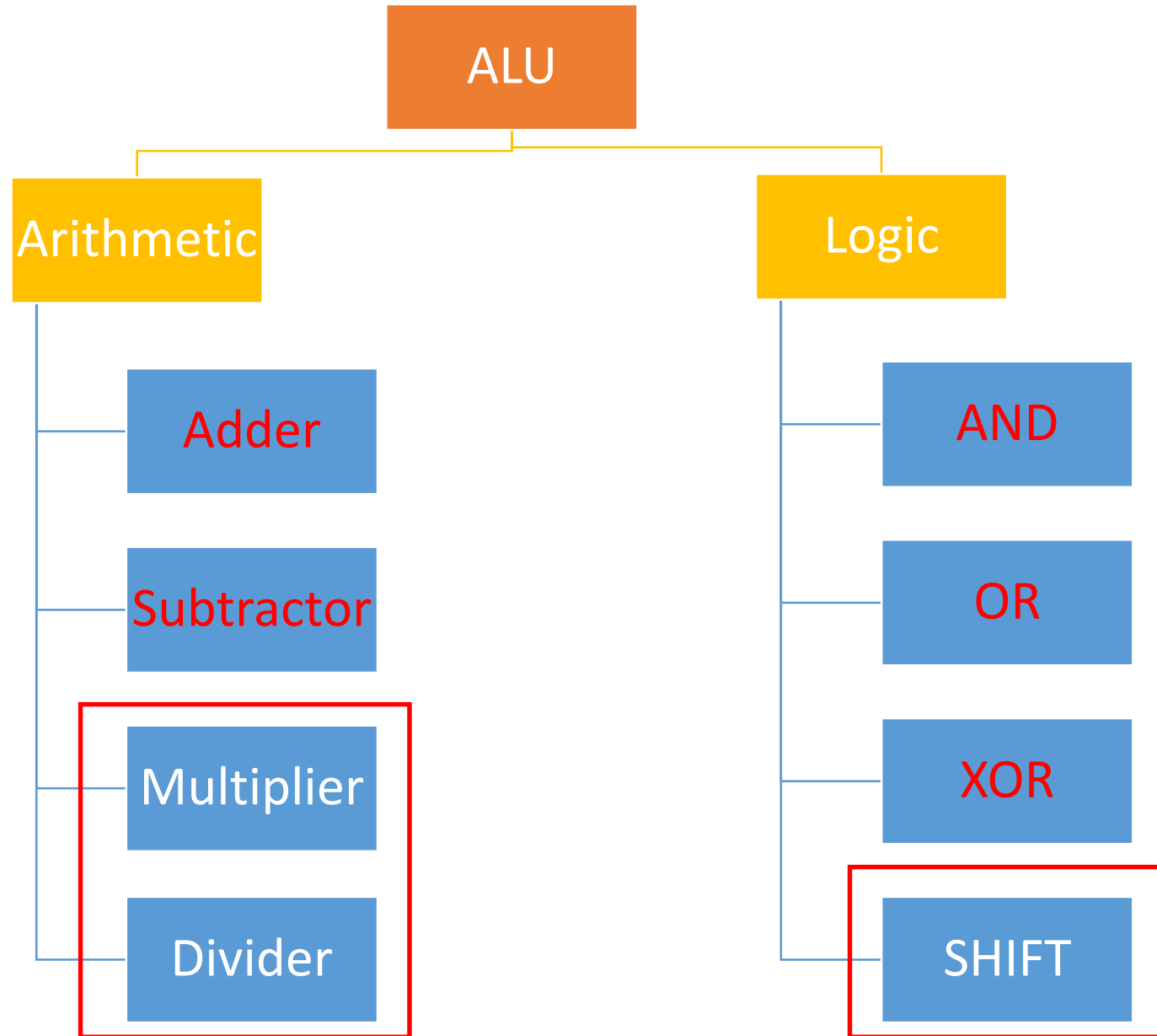

Thank You 😊