

Pull-Up and Pull-Down Networks

Mahit Kumar Paul
Assistant Professor, Dept. of CSE
RUET, Rajshahi-6204

mahit.cse@gmail.com

mahit@cse.ruet.ac.bd

Pull-Up and Pull-Down Networks

- A **CMOS** gate is a combination of two networks: the Pull Up Network (PUN) and the Pull Down Network (PDN).


 


Fig1. CMOS Inverter

 


Pull-Up and Pull-Down Networks...

- Normally the PDN is consisting of **NMOS** devices whereas PUN is consisting of **PMOS** devices.
- The function of PUN is to provide a connection between **VDD** and **Vout** to pull **Vout** to logic '1' whereas the function of PDN is to provide connection between **GND** and **Vout** to pull **Vout** to logic '0'.
- Using this CMOS logic, many circuits can be developed.
Such as NAND, NOR, XNOR etc.

Pull-Up and Pull-Down Networks...


Binary logic values represented by voltages:

 "High" = Supply Voltage, "Low" = Ground Voltage




PFET connects
S and D when
 $G = \text{"low"} = 0V$


Supply Voltage = V_{DD}

 

PFET only good
at pulling up

 

 
NFET connects
D and S when
 $G = \text{"high"} = V_{DD}$



NFET only good
at pulling down

Ground = GND = 0V

Pull-Up and Pull-Down Networks...

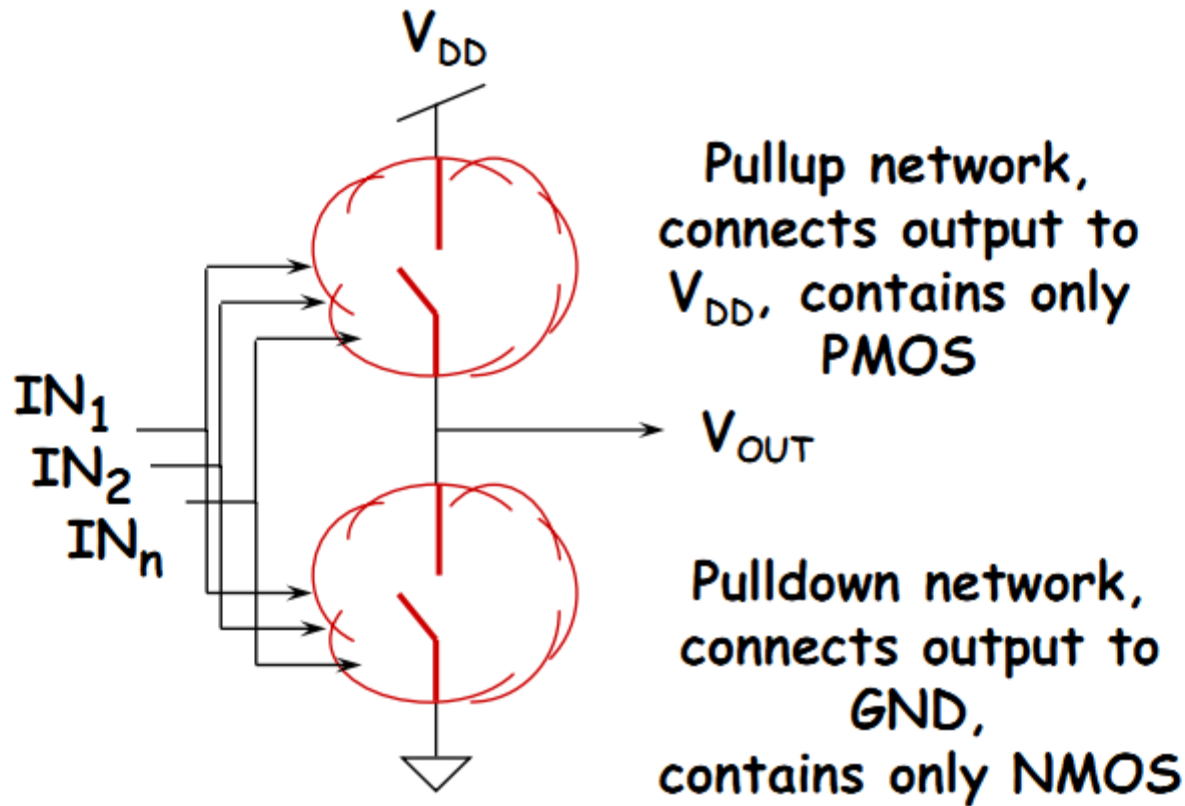

For every set of input logic values, either pullup or pulldown network makes connection to V_{DD} or GND

- If both connected, power rails would be shorted together
- If neither connected, output would float (tristate logic)

Pull-Up and Pull-Down Networks...

Pull up network should connect output to V_{DD} when
 $f(x_1, x_2, \dots) = 1$

Pull down network should connect output to GND
when $\overline{f}(x_1, x_2, \dots) = 1$

Because PMOS is conducting with low inputs, useful
to write pullup as function of inverted inputs

$$p(\overline{x}_1, \overline{x}_2, \dots) = f(x_1, x_2, \dots)$$

Pull-Up Is Dual of Pull-Down Network

For NAND gate, $f = \overline{A.B}$

Pulldown $\bar{f} = A.B$



Pullup $p = f = \overline{A.B}$
 $= \bar{A} + \bar{B}$

(De Morgan's Laws)

For NOR gate, $f = \overline{A+B}$


Pulldown $\bar{f} = A+B$

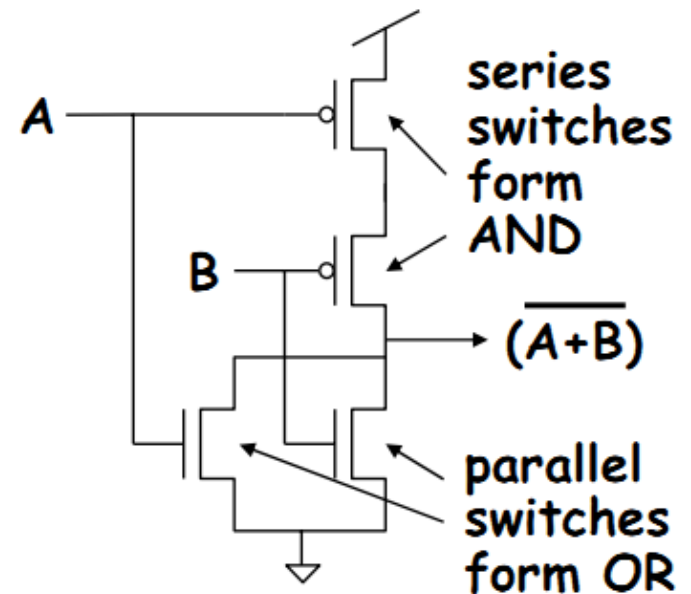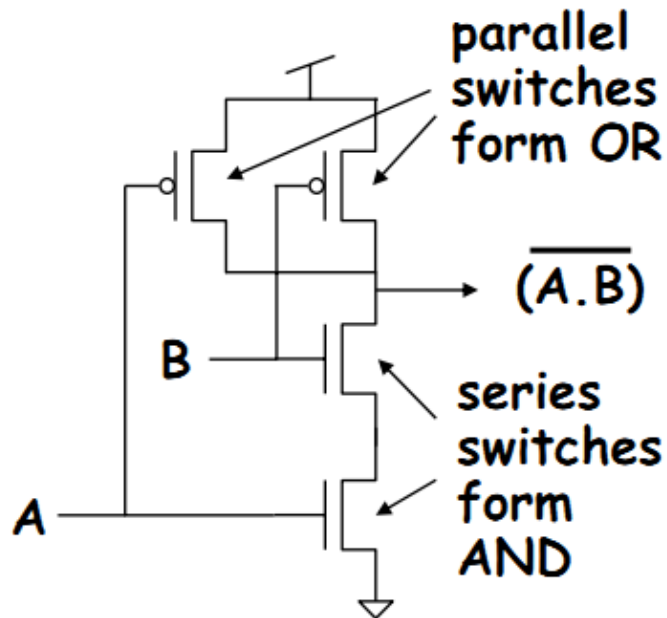Pullup $p = f = \overline{A+B}$
 $= \bar{A} . \bar{B}$



More Examples

$$f = \overline{(A+B).C}$$

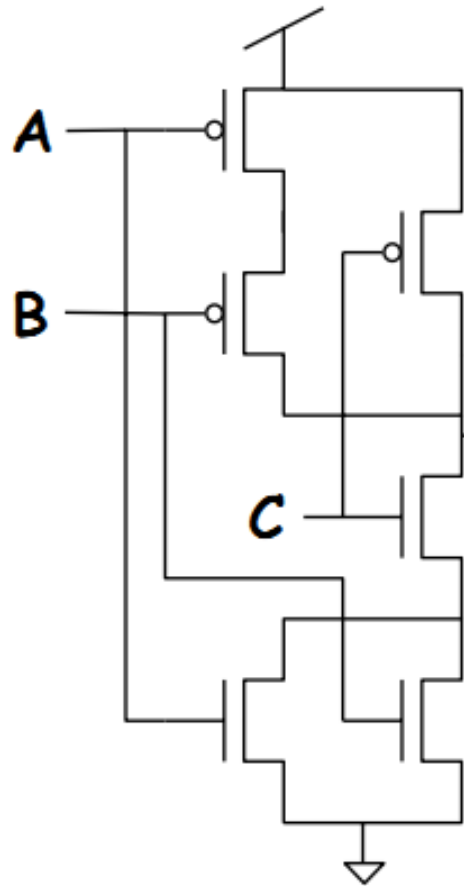


$$\begin{aligned}\text{pullup } p &= \overline{(A+B).C} \\ &= \overline{(A+B)} + \overline{C} \\ &= (\overline{A}.\overline{B}) + \overline{C}\end{aligned}$$

$$\text{pulldown } \overline{f} = (A+B).C$$


More Examples...

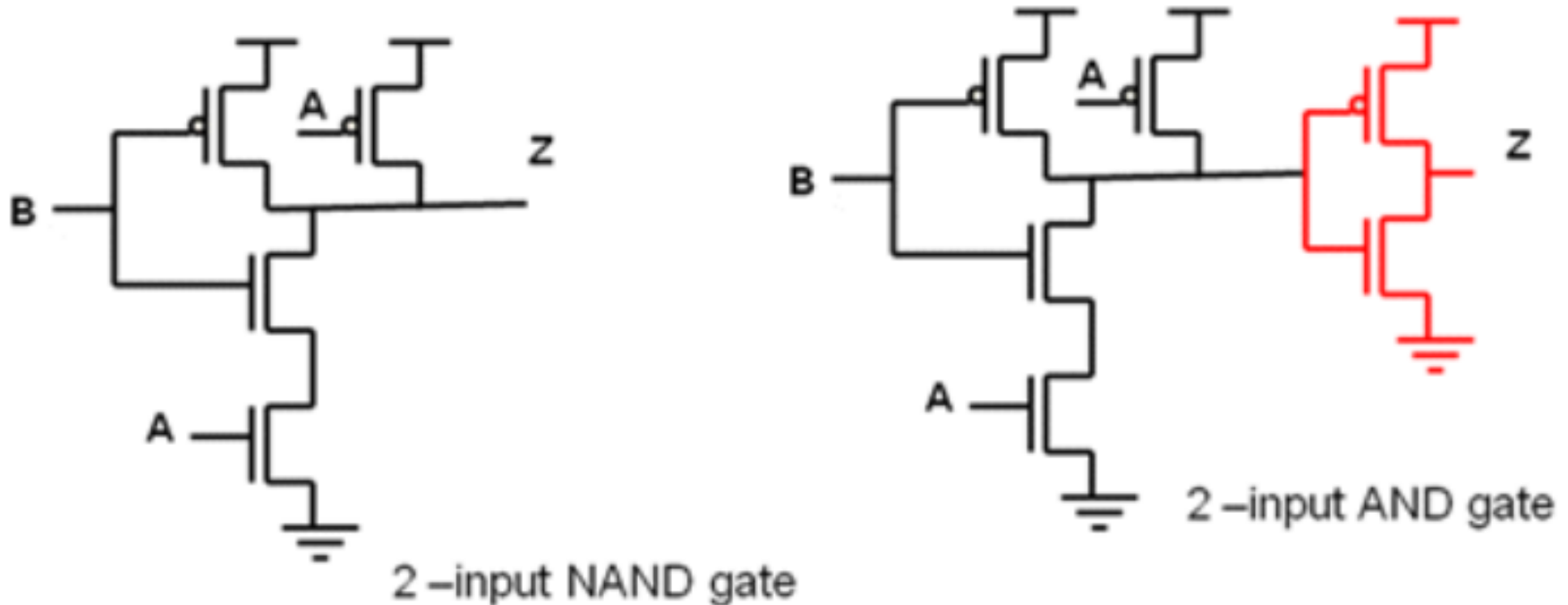CMOS always ought to provide INVERTED outputs like Inverter, NAND, NOR, XNOR etc. Sometimes a non-inverting function is required, in which case it's just as easy to implement it with a final inverter or with a non-inverting function like AND, OR as also shown in the below Fig



More Examples...


$$f = (A'B + AB')'$$

 

2 input XNOR gate

More Examples...

$$f = A'B + AB'$$

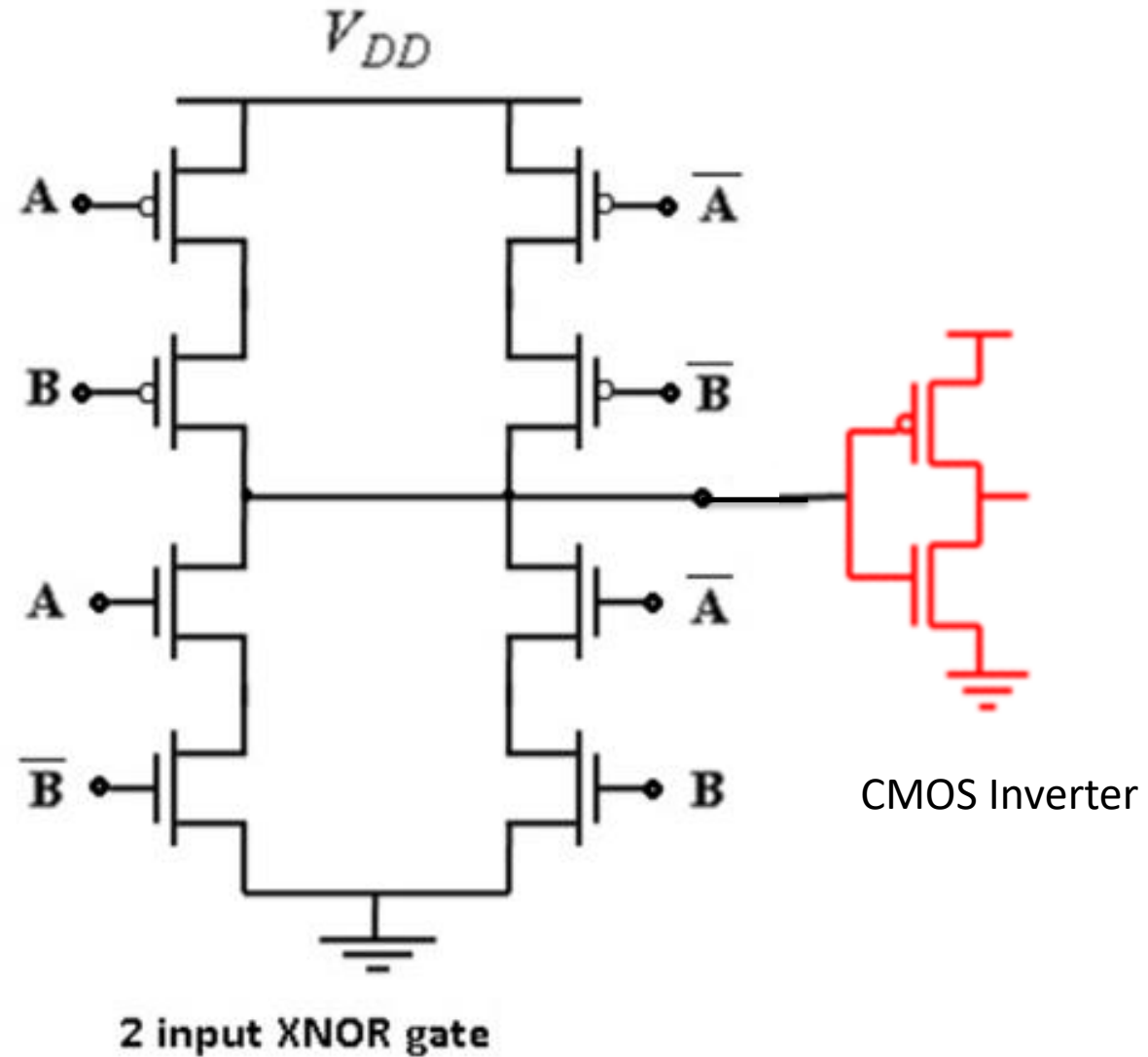

References

- [1] <https://www.electronics-tutorial.net/Digital-CMOS-Design/CMOS-Logic-Gates/Pull-up-and-Pull-Down-Networks/>
- [2] https://ocw.mit.edu/courses/electrical-engineering-and-computer-science/6-884-complex-digital-systems-spring-2005/lecture-notes/103_cmos_gates.pdf

Thank You