
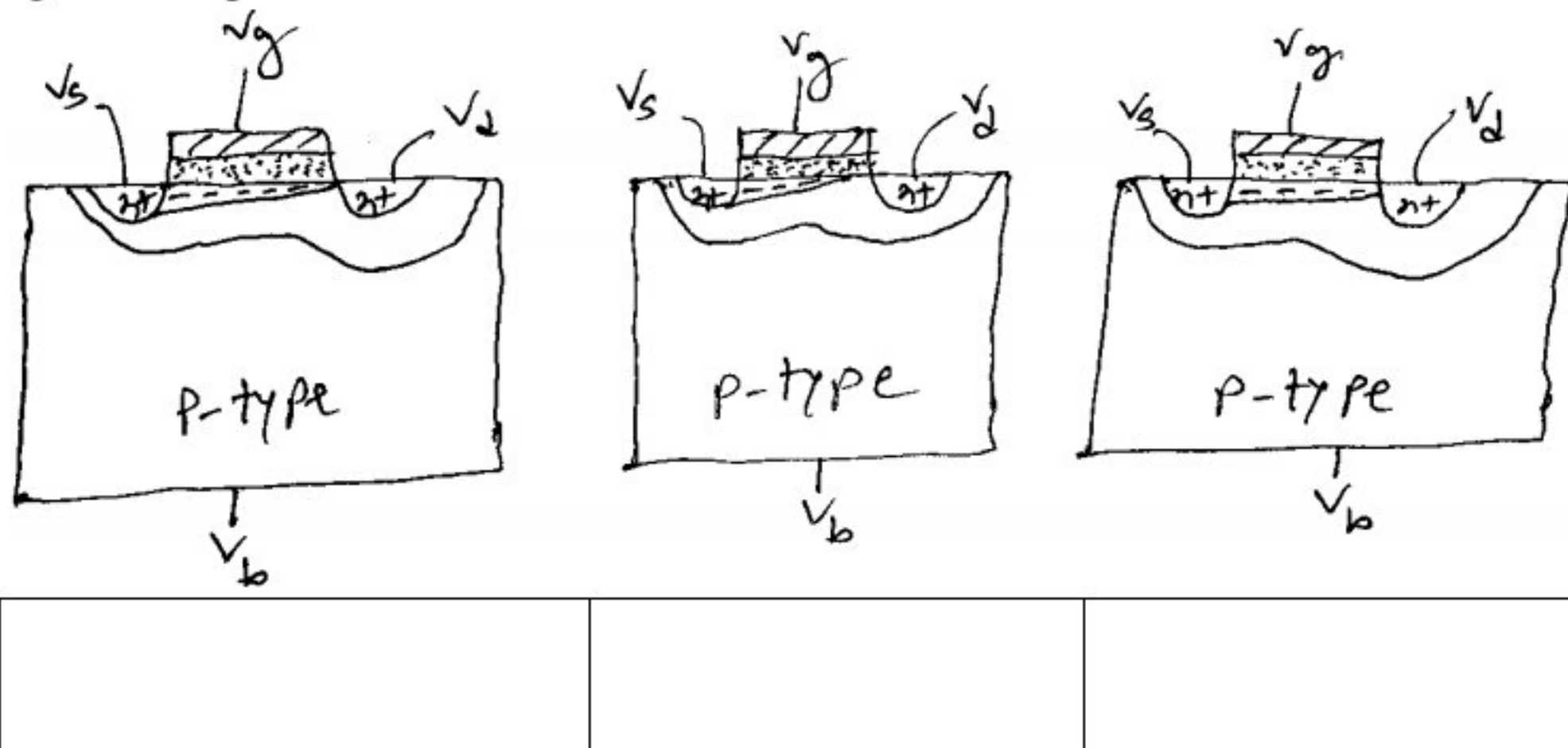


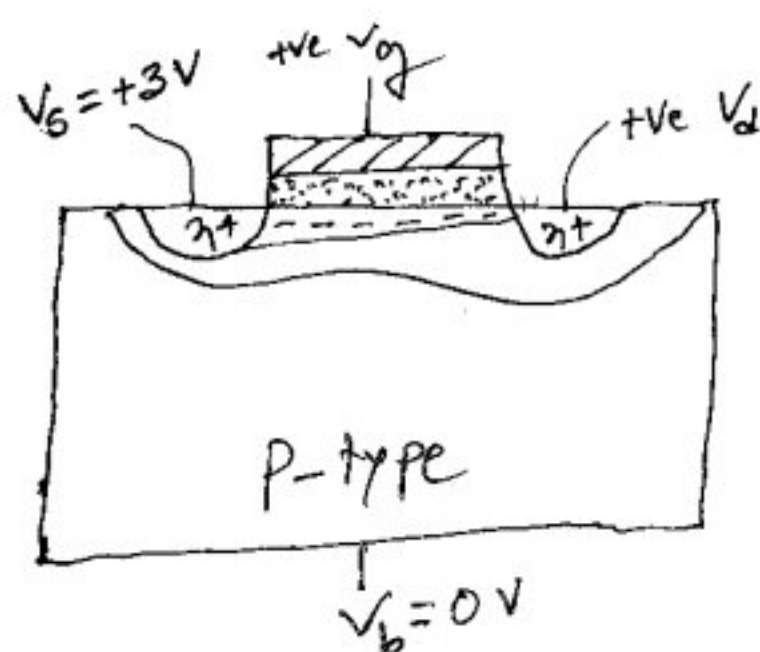- Q1. Mention the working state of each of the MOSFET in the blank box beneath each of the 3 figures. Be specific. 3



- Q2. Draw the typical I_{ds} versus V_{ds} characteristics curve of an enhancement mode NMOS for a constant V_{gs} . 4

- Q3. Determine the threshold voltage of the following NMOS considering the body-effect where initial threshold is 0.8V. Consider that except the necessary parameters all others are constant. 5



Solution:


- Q4. Consider an enhancement mode NMOS where $W:L=1:1$. The gate input is 2V; source, drain, and body are connected to 1V, 2V, and 0V respectively, and threshold is 1V. Now determine the current through the NMOS. (You can use opposite page if necessary). 8

- Q1. Derive the characteristics equation that indicates the behavior of body effect for an inverter having n-channel enhancement mode MOSFET as driver with same as the load. Conclude whether the behavior is linear or non-linear. 10
- Q2. Given $V_{gs} = 0V$, $V_{ld} = -4V$, $W_2/L_2 = 1:1$; Now derive the approximation of R (resistance) to calculate the rising time for an NMOS inverter with depletion load and enhancement driver. Finally determine the value of R in $M\Omega$ from your derived approximation using the given values. 10

Q1. For a CMOS inverter $W_1:L_1=1:1$, $W_2:L_2=2:1$, $V_{te} = V_{tep} = 1V$, $\frac{\epsilon\mu_n}{D} = 3 \times 10^{-8} \frac{mA}{mV^2}$, $\frac{\epsilon\mu_p}{2D} = 0.75 \times 10^{-11} \frac{A}{mV^2}$. Now if $V_{sg} = V_{gs} = 3.3V$ then find out the followings (a-d) for both load and driver transistors: (You must specify the necessary equations clearly).

- Pinch-off voltages
- Input voltages
- Output voltages
- Saturation currents
- Finally find out the current flow throughout the CMOS inverter.

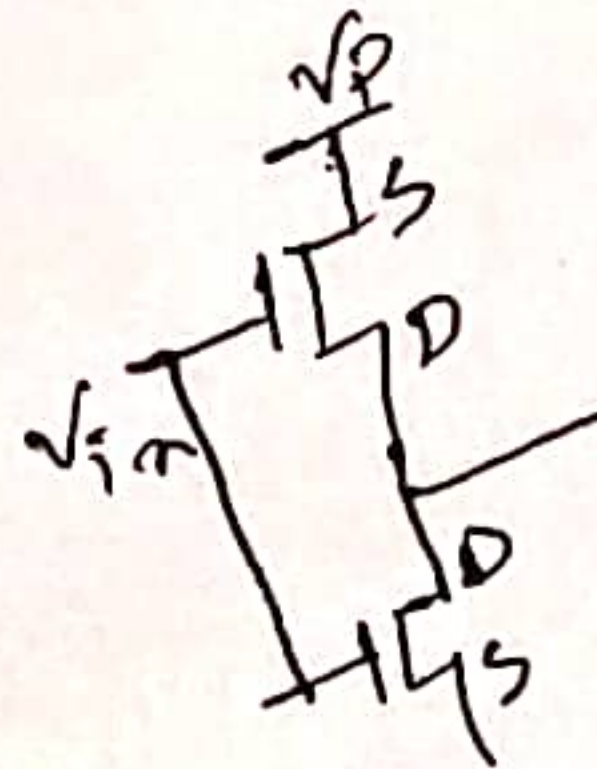Q2. Briefly explain the operating principle of CMOS transmission gate with necessary diagram.



$$V_{gs} = V_p - V_g = V_p - V_{in}$$

$$\Rightarrow V_{gs}^2 = V_p - V_{out}$$

$$V_{out} = V_p - V_{gs}^2$$

Q1

Mention the name of each of the routing models beneath the individual figures.

4




| | |
|--|--|
| | |
|--|--|

Q2

Mention the name of each of the routing technique used beneath the individual figures.

4

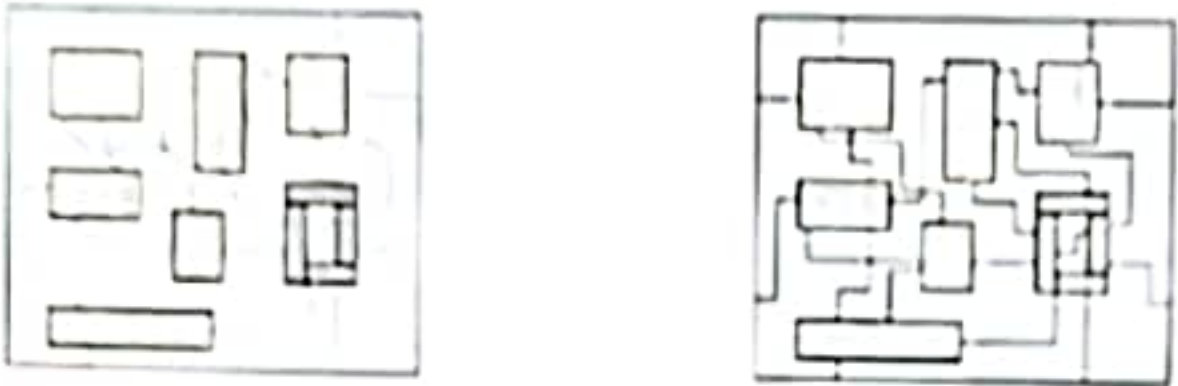


| | |
|--|--|
| | |
|--|--|

Q3

Mention the name of each of the channel junction created beneath the individual figures.

6

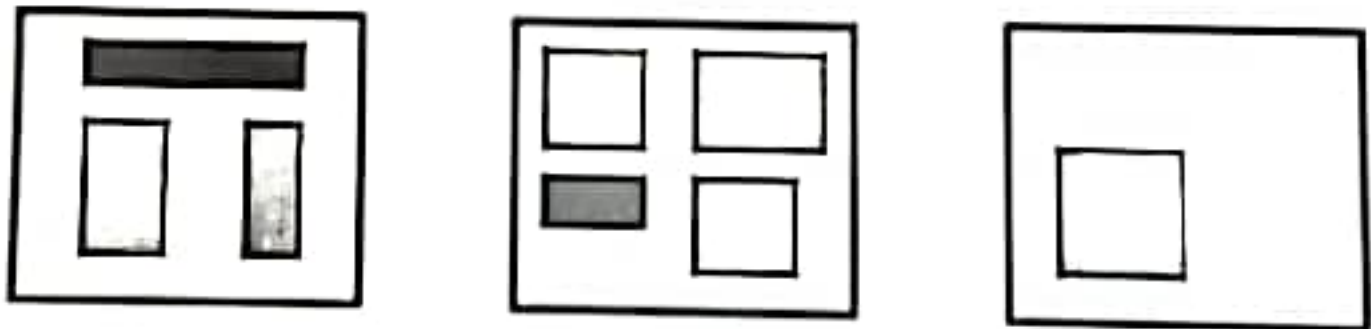


| | | |
|--|--|--|
| | | |
|--|--|--|

Q4

Mention the name of each of the routing regions created beneath the individual figures.

6

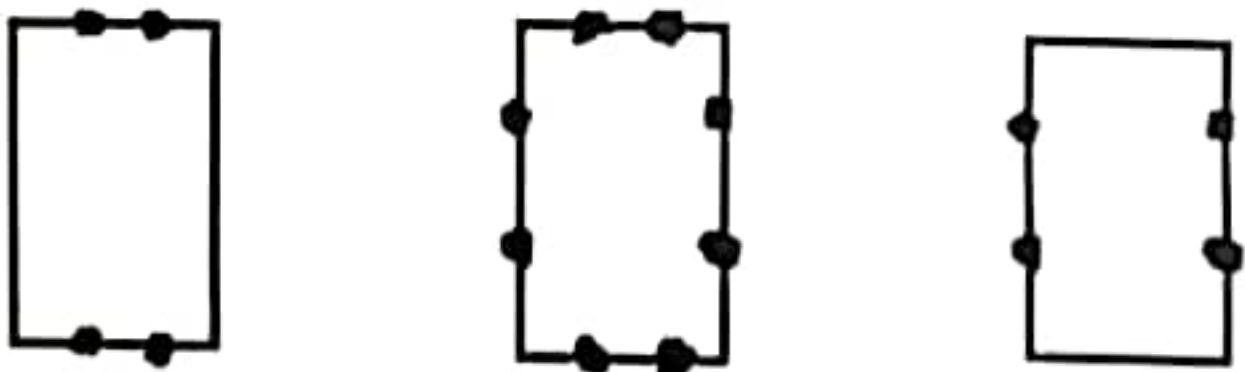

| | | |
|--|--|--|
| | | |
|--|--|--|