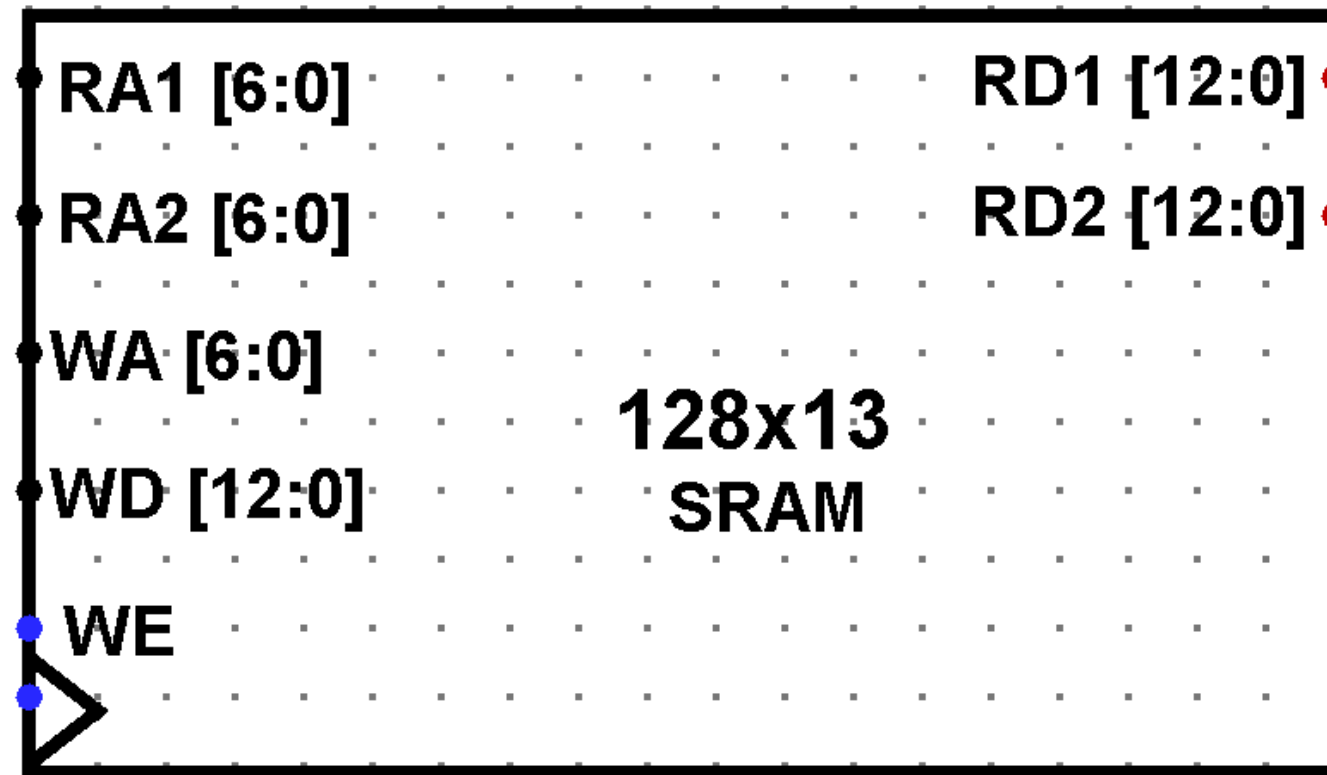


Final Main Memory (RAM) Design

Nahin Ul Sadad
Lecturer
CSE, RUET

Main Memory (SRAM)

RAM chip is shown below:



Here,
RA1 = Read Address 1
RA2 = Read Address 2
RD1 = Read Data 1
RD2 = Read Data 2
WA = Write Address
WD = Write Data
WE = Write Enable


Figure: RAM chip (128x13)

Size of RAM = 128. It can store 128 instructions/data.

Word Size of RAM = 13. It can store 13bit instruction/data in every address.

1x1 Static RAM (SRAM) Cell

1x1 SRAM

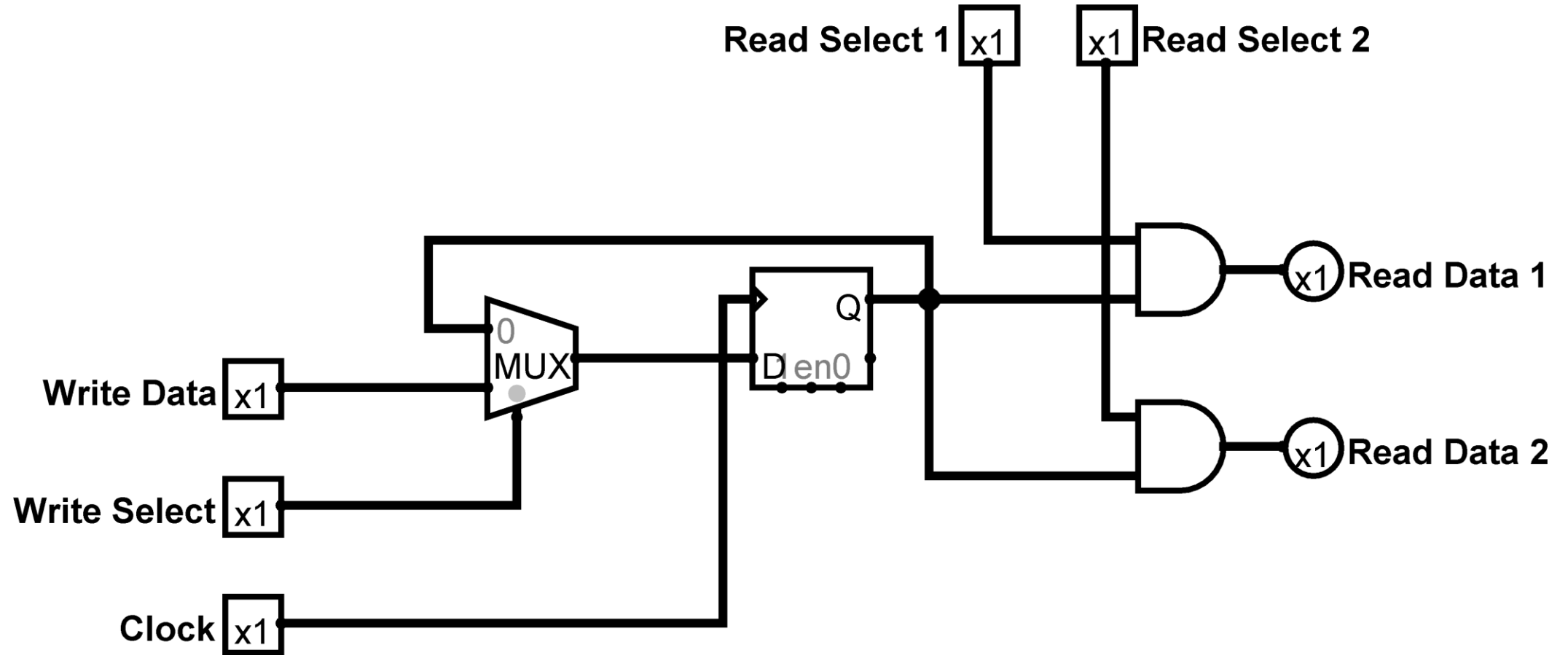

1x1 SRAM


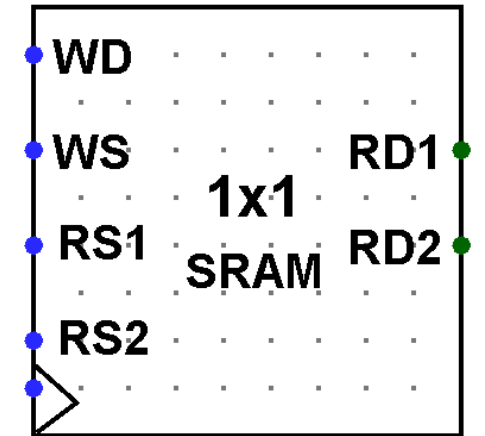
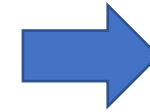
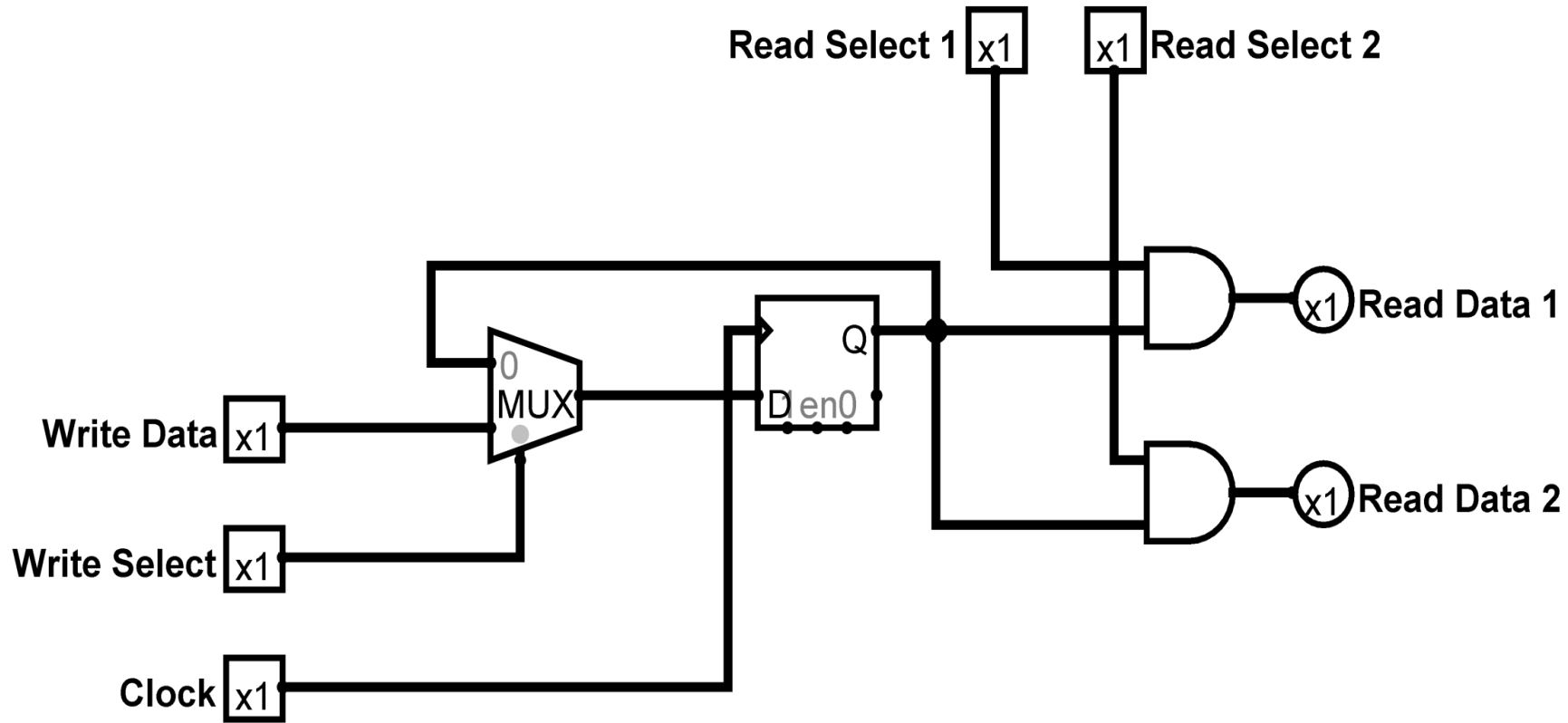



Figure: 1x1 SRAM Chip

1x3 Static RAM (SRAM) Cell

1x3 SRAM

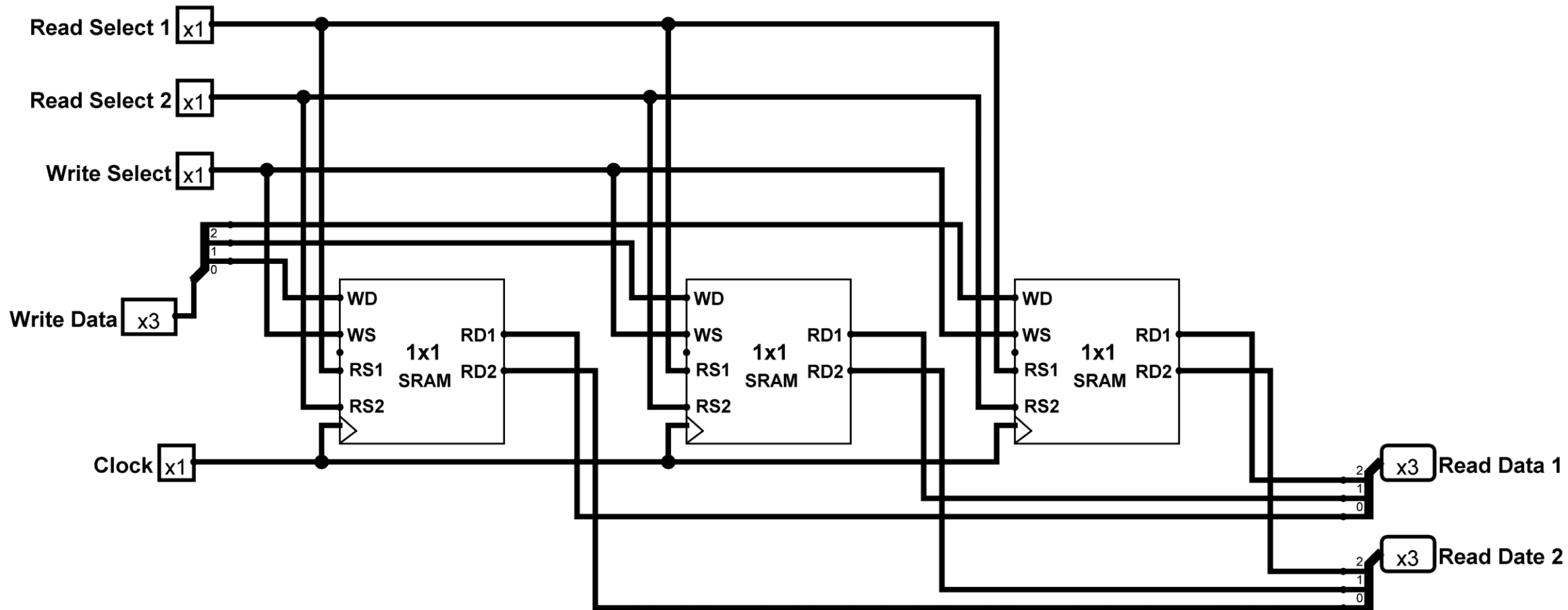


1x3 SRAM


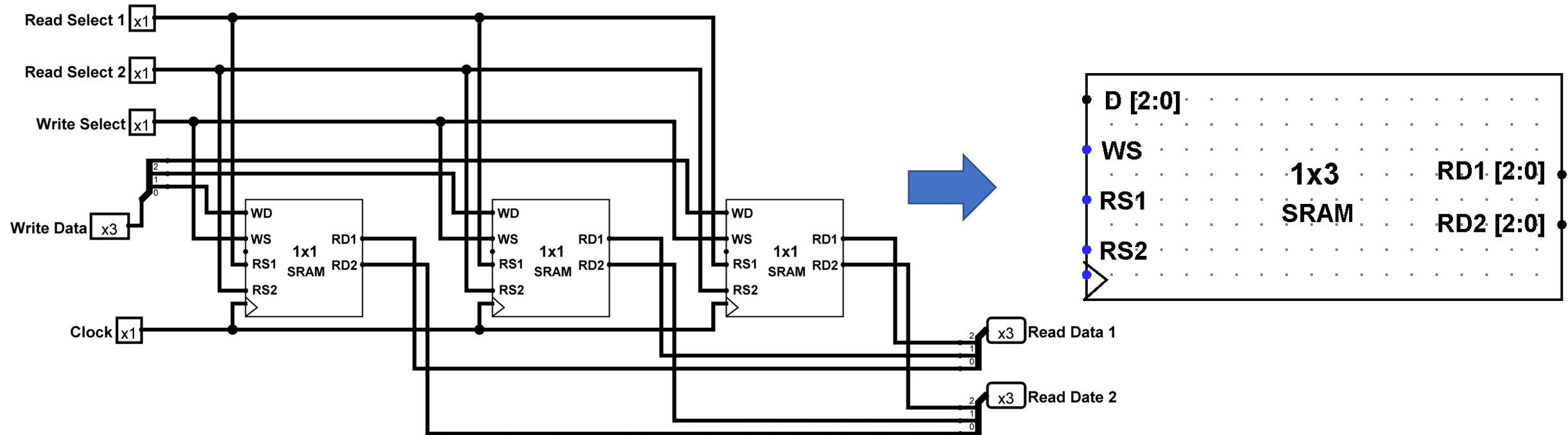


1x13 Static RAM (SRAM) Cell

1x13 SRAM

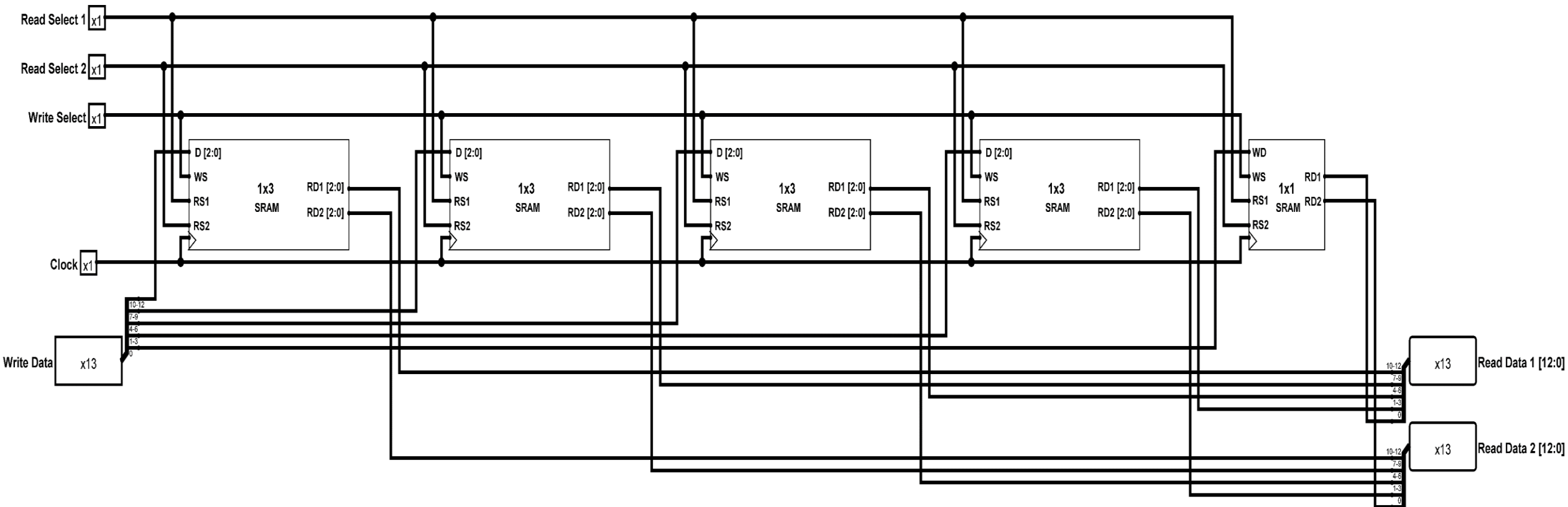


1x13 SRAM


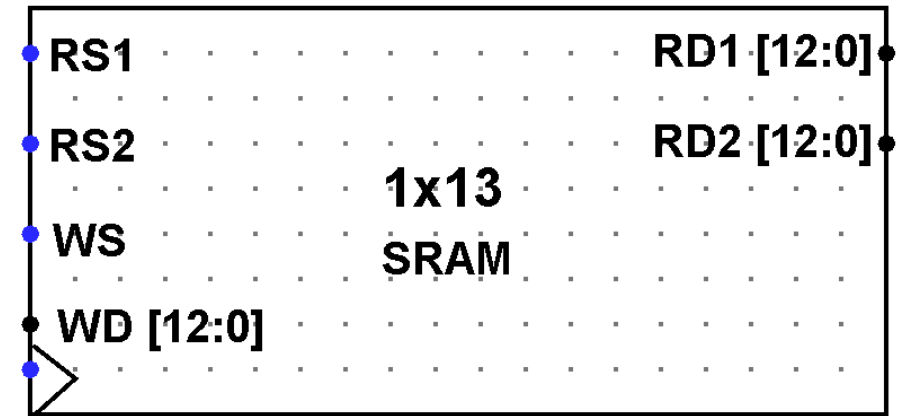
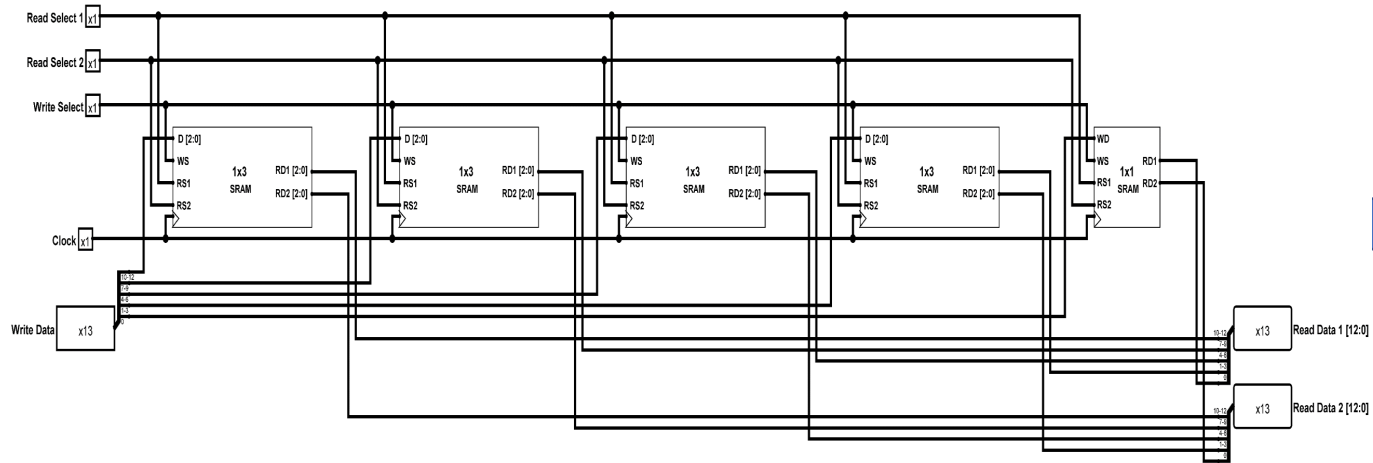


4x13 Static RAM (SRAM) Cell

4x13 SRAM















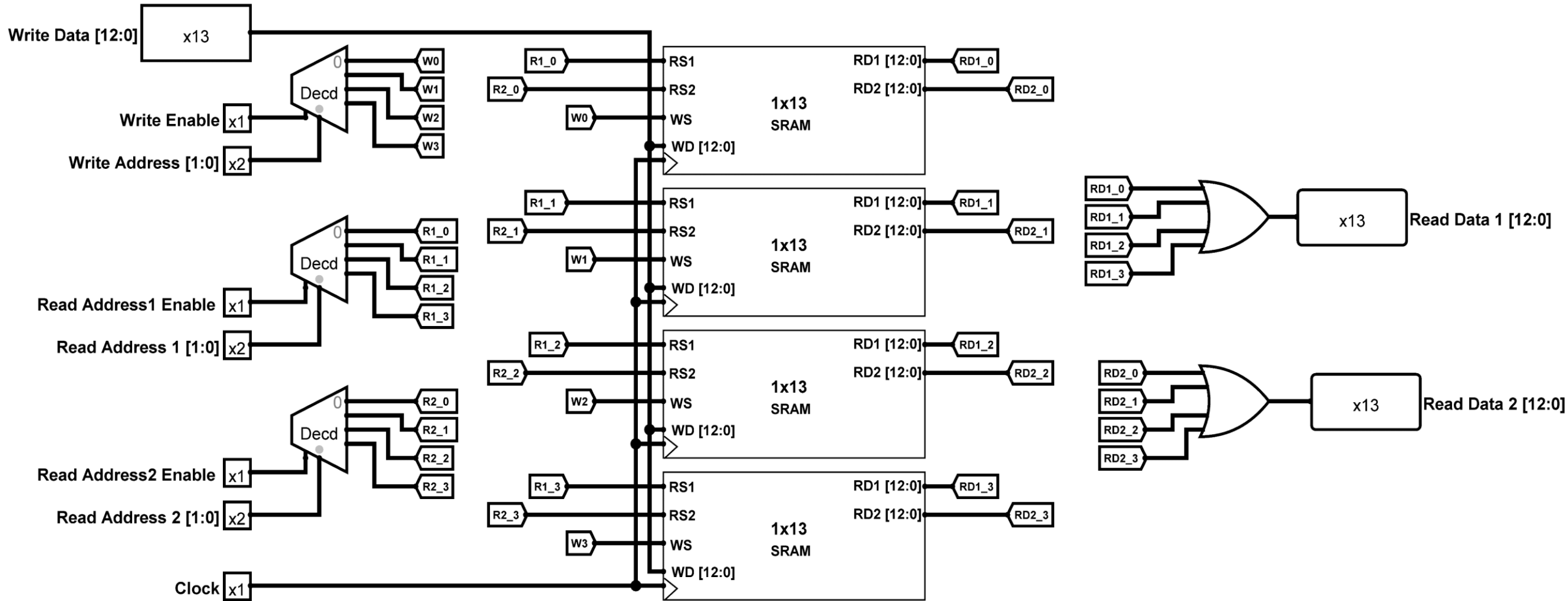


4x13 SRAM

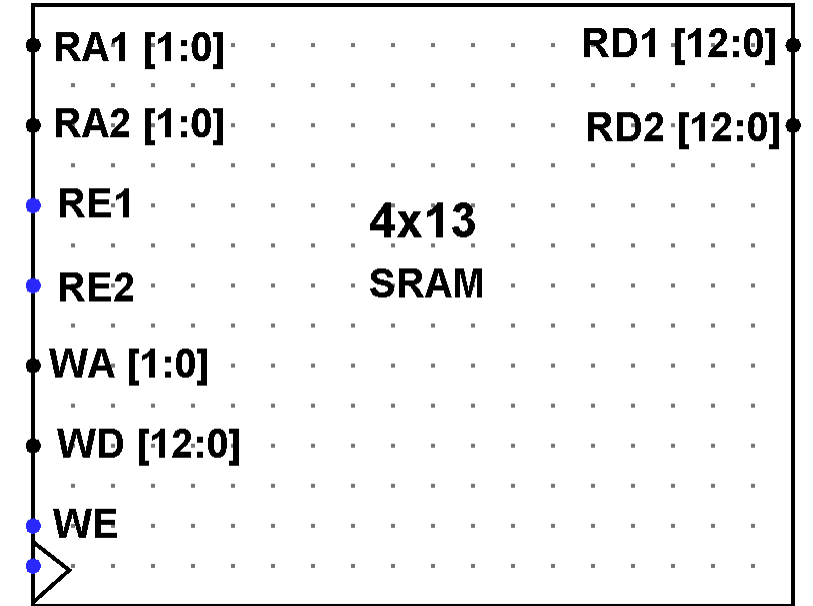
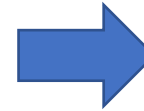
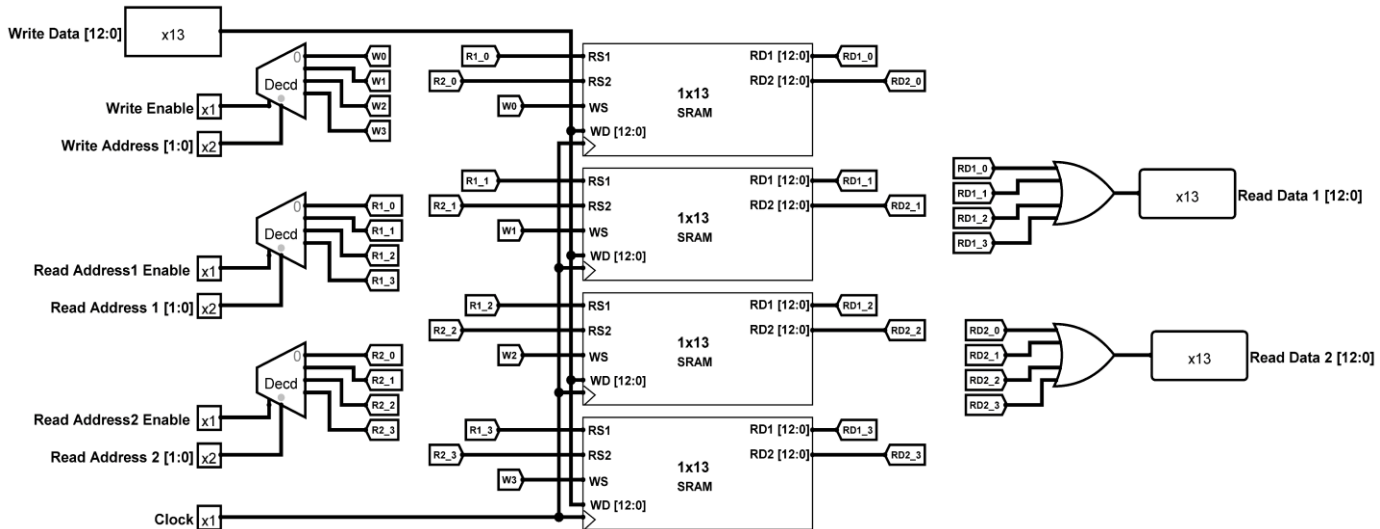


16x13 Static RAM (SRAM) Cell

16x13 SRAM

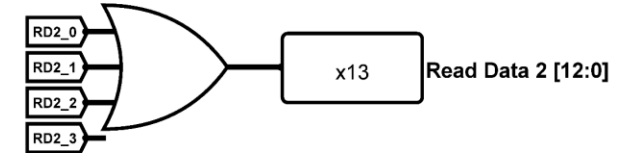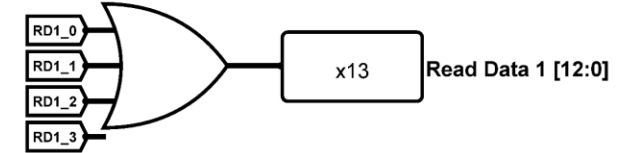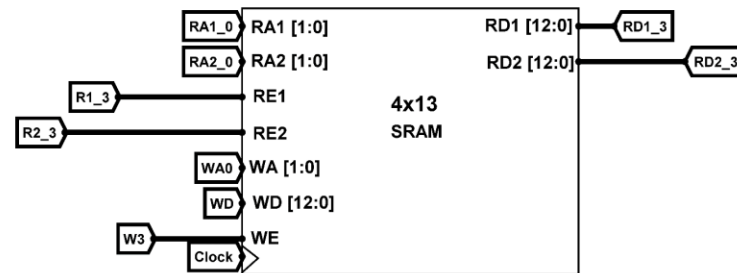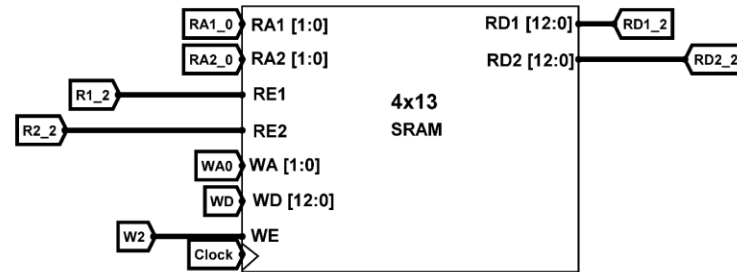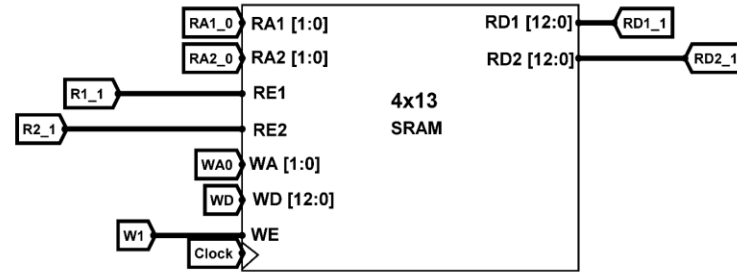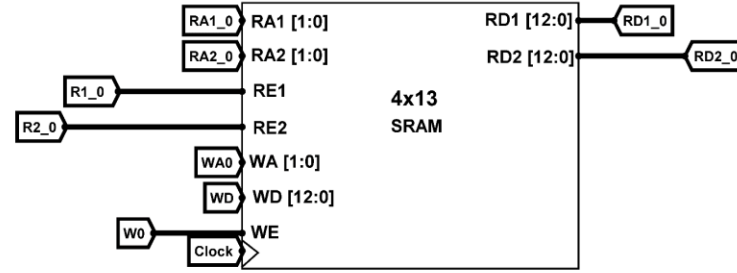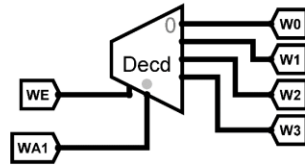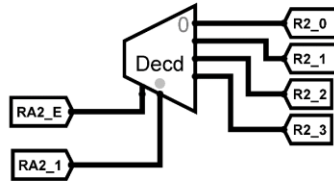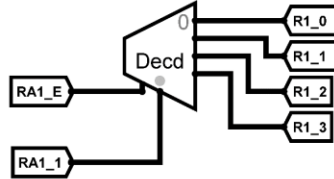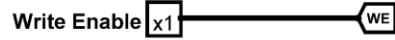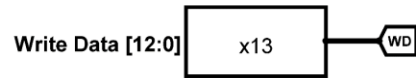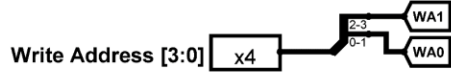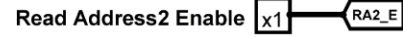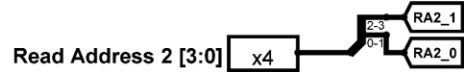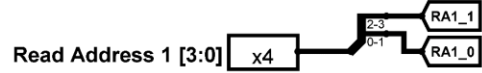


16x13 SRAM

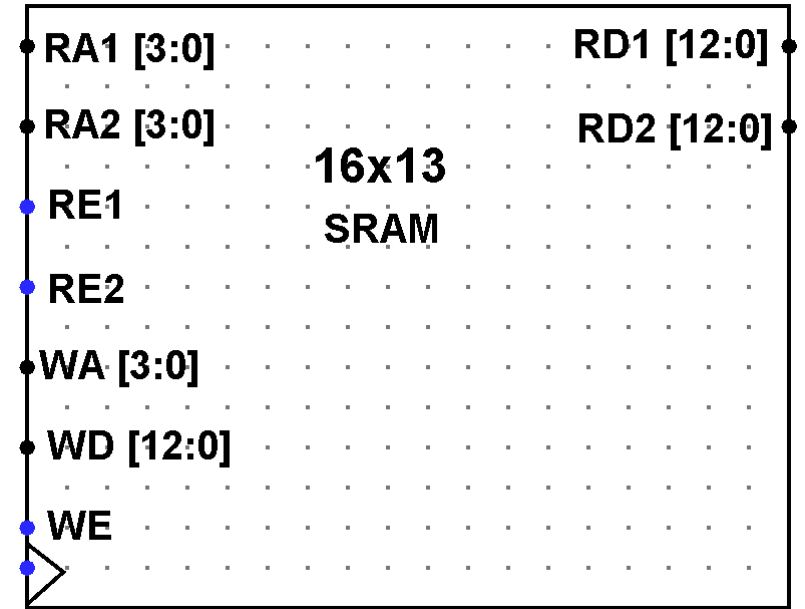
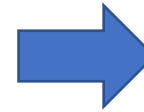
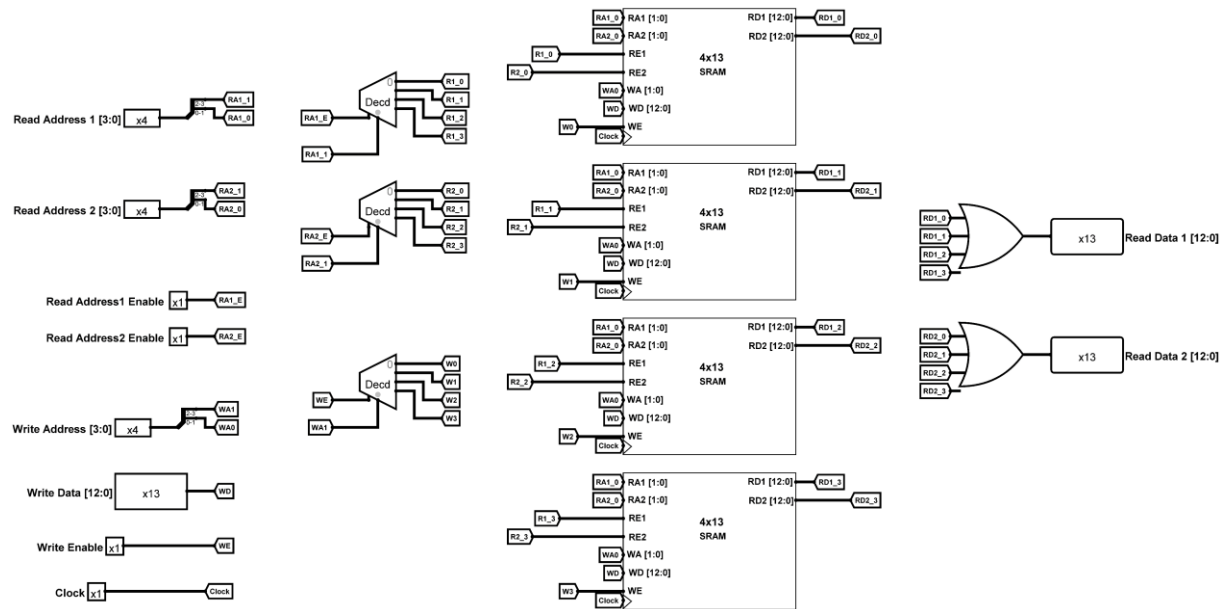


64x13 Static RAM (SRAM) Cell

64x13 SRAM

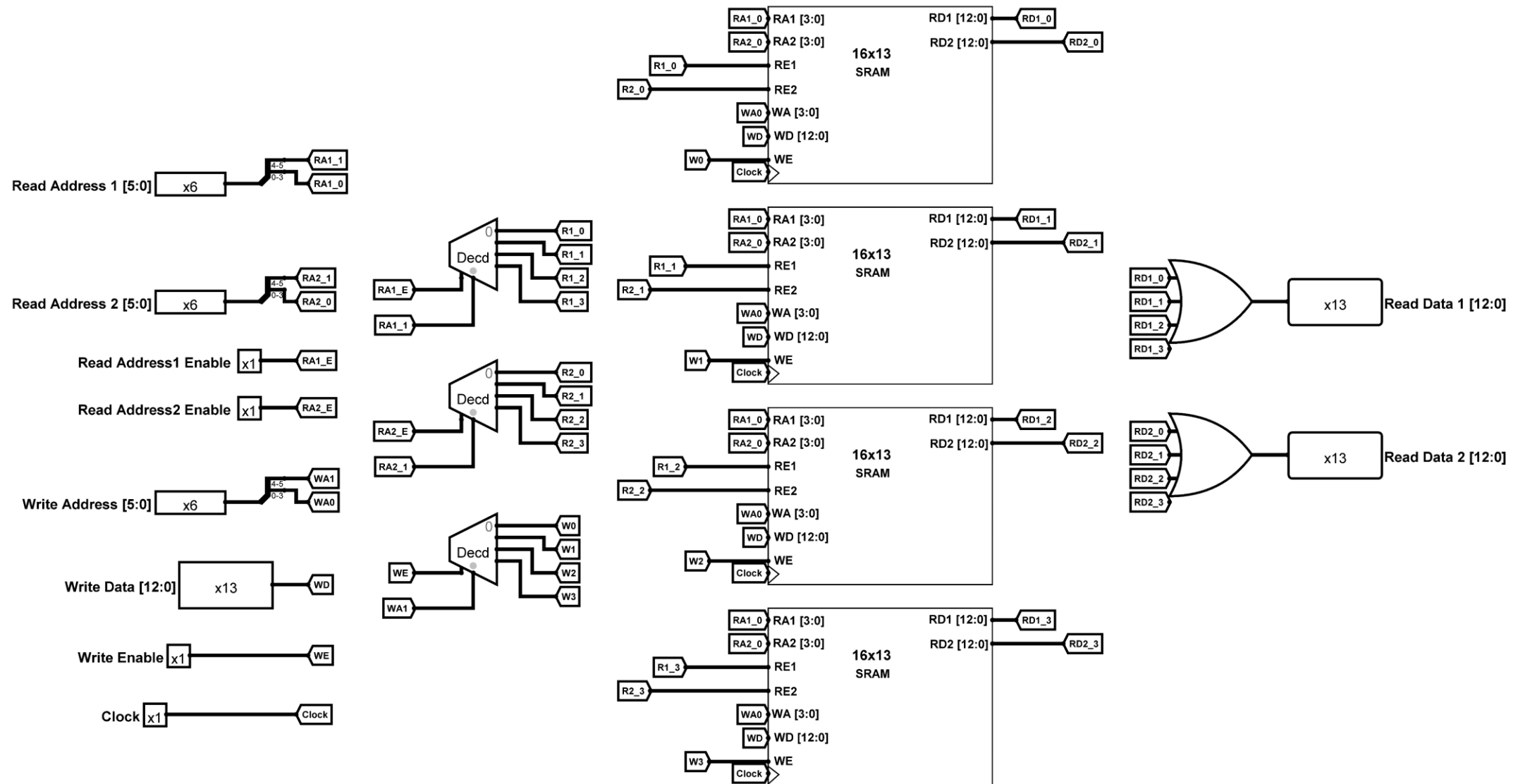


64x13 SRAM

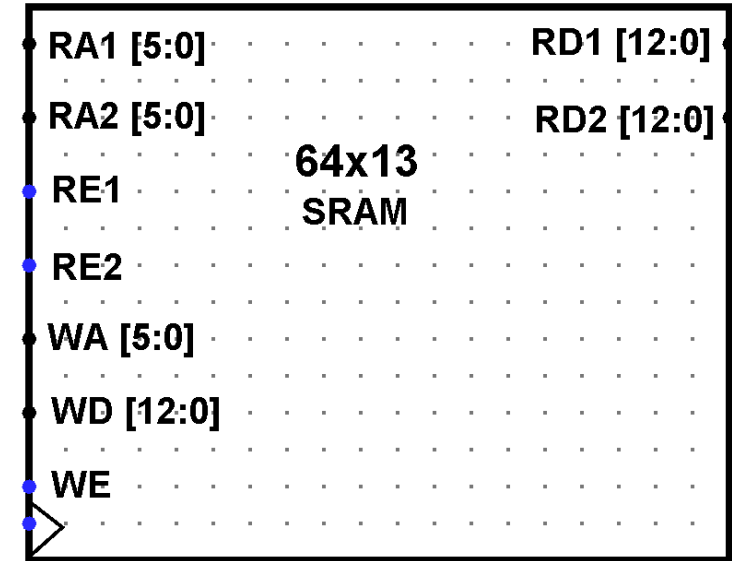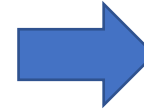
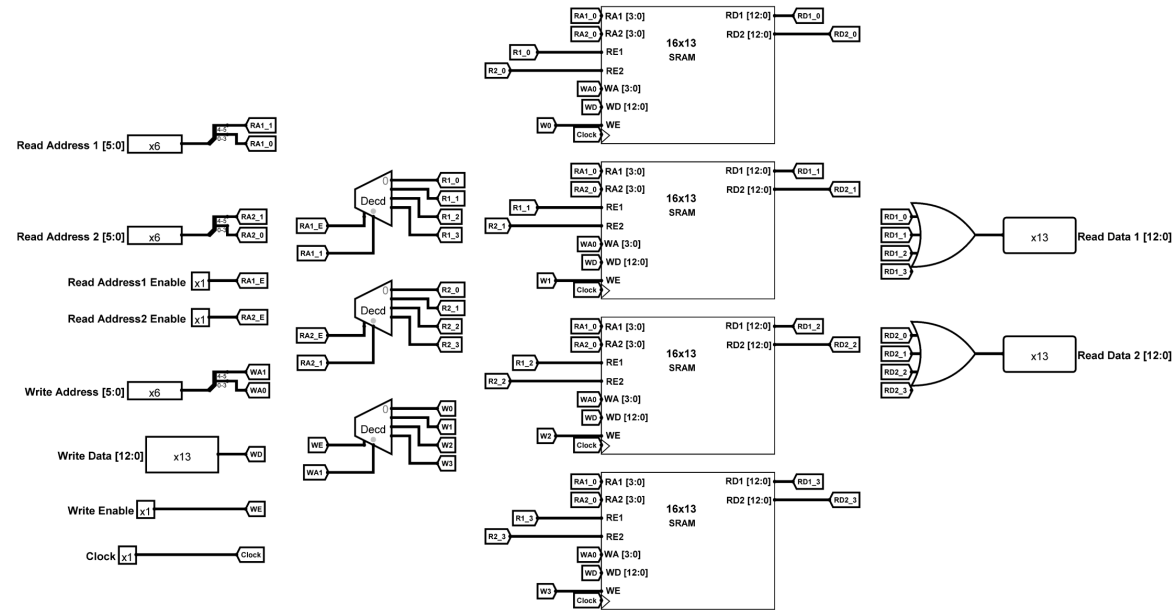


128x13 Static RAM (SRAM) Cell

128x13 SRAM

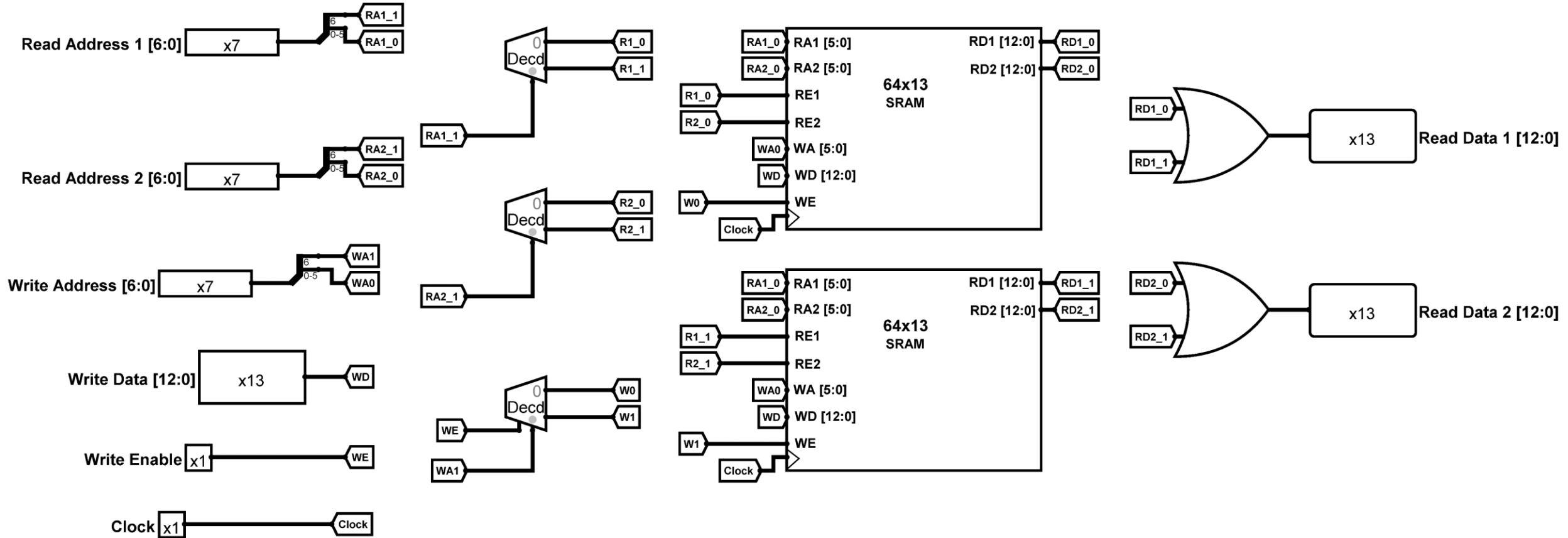

128x13 SRAM

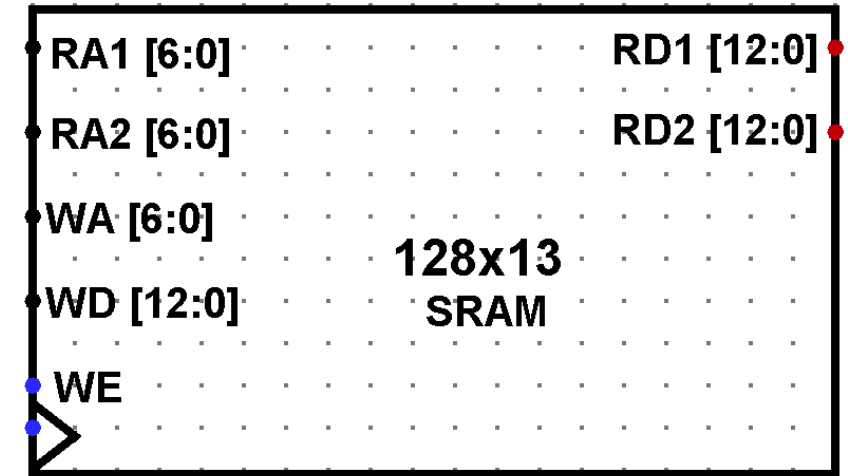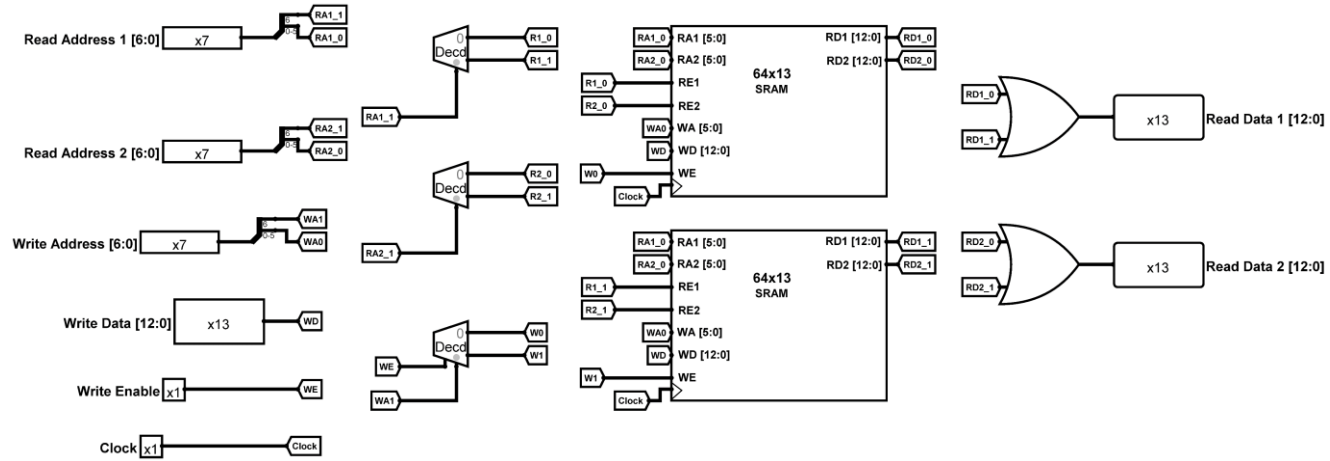

Thank You 😊