

# **Memory Hierarchy & Register Set Design I**

# Memory Hierarchy

# Memory Technologies

	Capacity	Latency	Cost/GB
<b>Register</b>	1000s of bits	20 ps	\$\$\$\$
<b>SRAM</b>	~10 KB-10 MB	1-10 ns	~\$1000
<b>DRAM</b>	~10 GB	80 ns	~\$10
<b>Flash (SSD)*</b>	~100 GB	100 us	~\$1
<b>Hard disk*</b>	~1 TB	10 ms	~\$0.10

# Memory Hierarchy

	Capacity	Latency	Cost/GB
Register	1000s of bits	20 ps	\$\$\$\$
SRAM	~10 KB-10 MB	1-10 ns	~\$1000
DRAM	~10 GB	80 ns	~\$10
Flash (SSD)*	~100 GB	100 us	~\$1
Hard disk*	~1 TB	10 ms	~\$0.10



Capacity  
Decrease



Speed  
Increase



Cost  
Increase


# Memory Hierarchy

	Capacity	Latency	Cost/GB
Register	1000s of bits	20 ps	\$\$\$\$
SRAM	~10 KB-10 MB	1-10 ns	~\$1000
DRAM	~10 GB	80 ns	~\$10
Flash (SSD)*	~100 GB	100 us	~\$1
Hard disk*	~1 TB	10 ms	~\$0.10

**We want large, fast and cheap memory. But**

**Large memories are slow!**

**Fast memories are expensive!**

 


# Memory Hierarchy

**Idea: Can we use a hierarchal system of memories with different tradeoffs to emulate a large, fast, cheap memory?**

# Memory Hierarchy

- Programming model: Single memory, single address space
- Machine transparently stores data in fast or slow memory, depending on usage patterns.

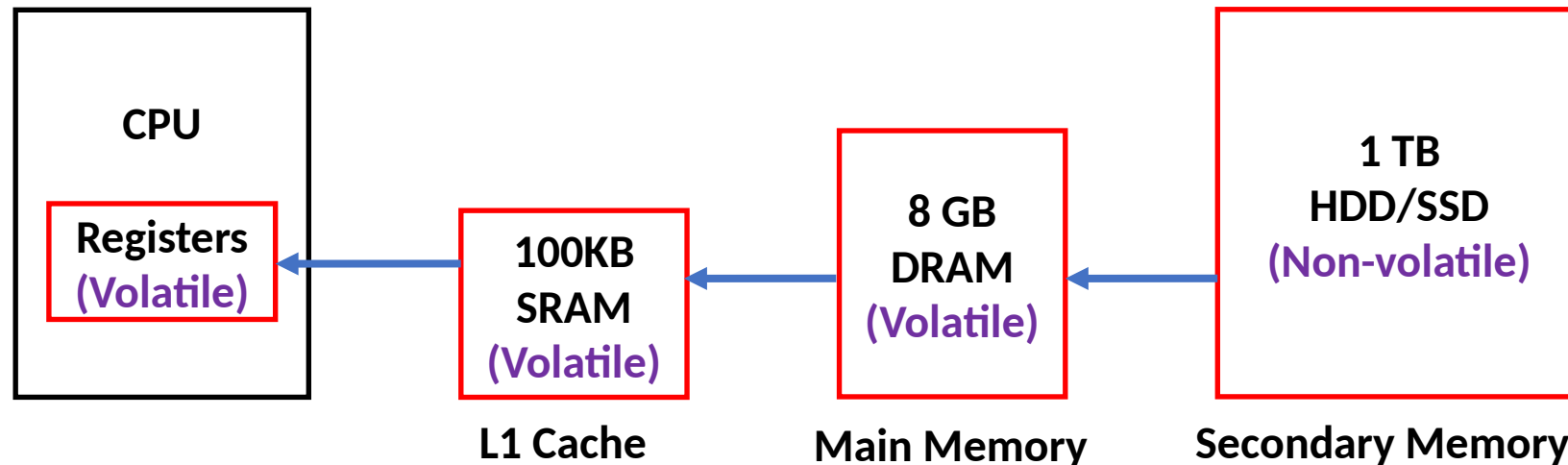

**Figure: Memory Hierarchy**

**Volatile Memory** = It only contains data when it is powered ON.  
It will lose its contents after power off.

**Non-volatile Memory** = It contains data even after power off.

# Memory Hierarchy

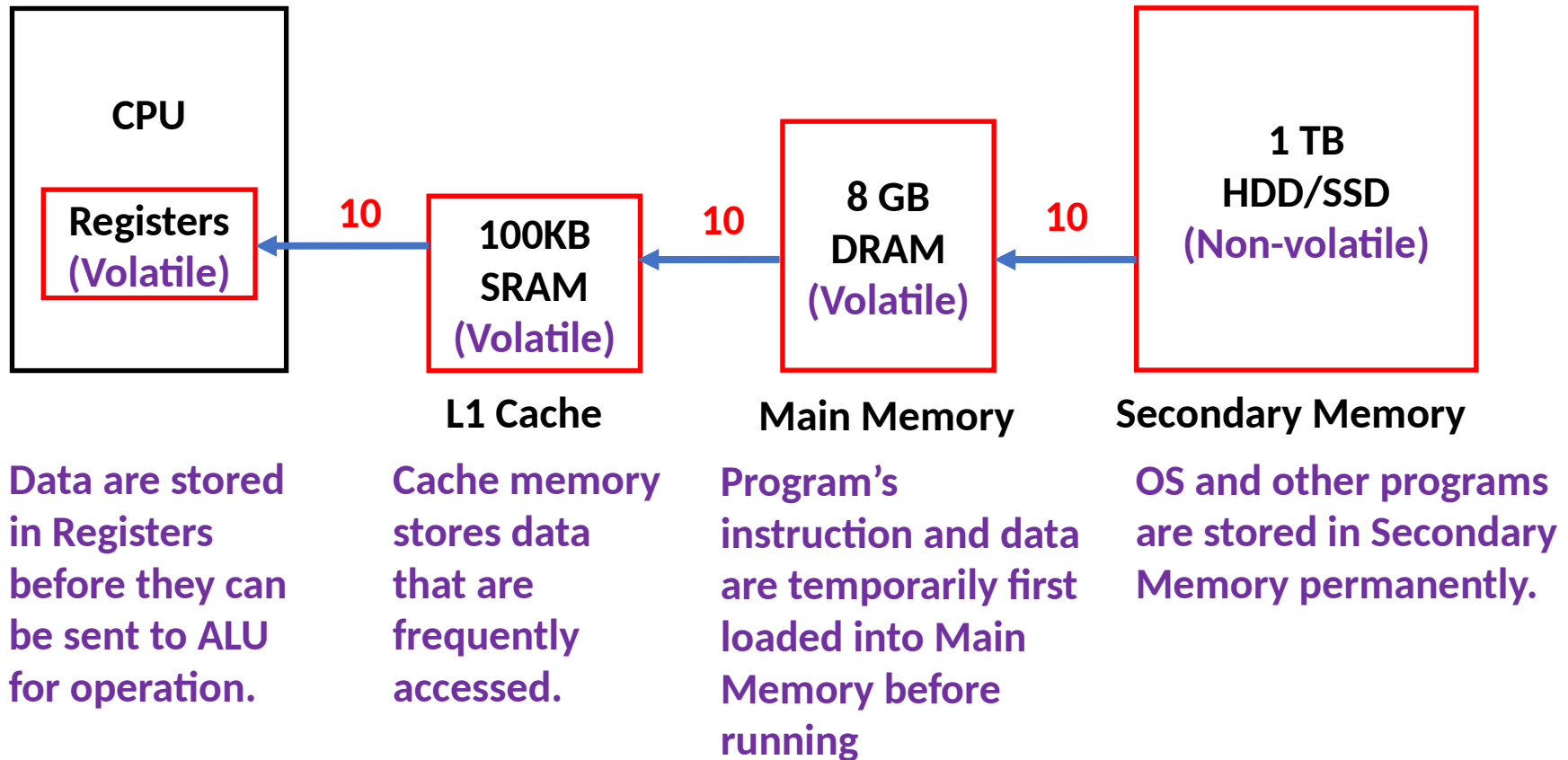


Figure: How Memory Hierarchy works



# Registers

# D Flip-flop

D	Q(t + 1)
0	0
1	1

Fig: D Flip-flop truth table

 



Fig: D Flip-Flop

# D Flip-Flop


Assume,  $Q=0$  which means D-FF has 0 value stored.

D	$Q(t + 1)$
0	0
1	1

Fig: D Flip-flop truth table

 

At Negative Clock Edge

 

At Positive Clock Edge


Fig: How D Flip-Flop works.

# D Flip-Flop

Assume,  $Q=0$  which means D-FF has 0 value stored.


D	$Q(t + 1)$
0	0
0	1

Fig: D Flip-flop truth table

 

At Negative Clock Edge

 D Flip-flop will not update its content because clock is not on positive edge.



At Positive Clock Edge


Fig: How D Flip-Flop works.

# D Flip-Flop

Assume,  $Q=1$  which means D-FF has 1 value stored.


D	$Q(t + 1)$
0	0
0	1

Fig: D Flip-flop truth table

 

At Negative Clock Edge

 D Flip-flop will not update its content because clock is not on positive edge.



At Positive Clock Edge


Fig: How D Flip-Flop works.

# D Flip-Flop

Assume,  $Q=1$  which means D-FF has 1 value stored.


D	$Q(t + 1)$
0	0
0	1

Fig: D Flip-flop truth table

 

At Negative Clock Edge

 D Flip-flop will not update its content because clock is not on positive edge.




At Positive Clock Edge

D Flip-flop will update its content because clock is on positive edge.

Fig: How D Flip-Flop works.

# 1-bit Register

 

Sel	Z
0	A
1	B

$$Z = \text{Sel}' \cdot A + \text{Sel} \cdot B$$


 


Fig: 1-bit Register

# 1-bit Register

 


At negative clock cycle,  
D Flip-flop will not update its  
content regardless of and value.

Fig: How 1-bit Register Works



# 1-bit Register

 


At positive clock cycle,  
D Flip-flop will update its content.

When  
So, Data will remain same in D-FF.

Fig: How 1-bit Register Works


# 1-bit Register

 

At positive clock cycle,  
D Flip-flop will update its content.

When  
So, Data will be updated in D-FF.

# 1-bit Register

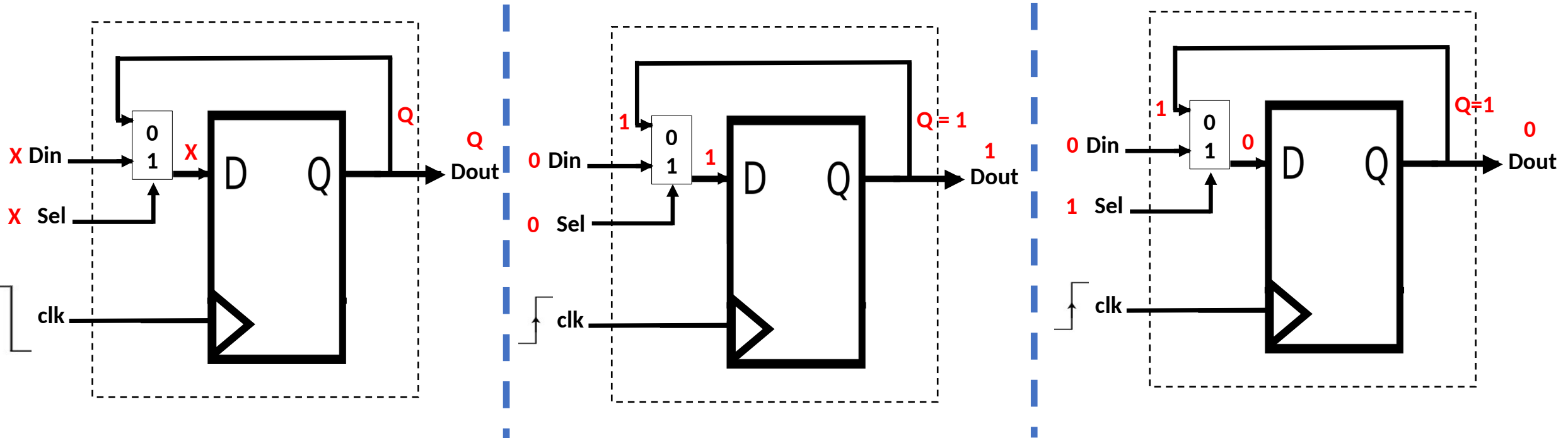

At negative clock cycle,  
D Flip-flop will not update its  
content regardless of and value.

At positive clock cycle,  
D Flip-flop will update its content.

When  
So, Data will remain same in D-FF.

At positive clock cycle,  
D Flip-flop will update its content.

When  
So, Data will be updated in D-FF.

Fig: How 1-bit Register Works

# 1-bit Register

 


Fig: 1-bit Register

 
 


Figure: 1 bit register chip

# 2-bit Register

 


Figure: 2 bit Register

# 2-bit Register

 


Figure: How 2 bit Register Works

# 2-bit Register

 


Figure: 2 bit Register

 
 


Figure: 2 bit register chip

# 2-bit Register

 


Figure: 2 bit Register


 


Figure: 2 bit register chip

 


**Homework:**  
**Similarly Design 3bit/4bit Register**



# Register Set Design I

# 1-bit CPU

## Program Counter (PC)

 


## RAM (Main Memory)

  


## Control Unit (CU)

## Register File

 

$alu[1]$   $alu[0]$

 

## Arithmetic and Logic Unit (ALU)

Figure: 1-bit CPU

# Register Set Design

In Assembly Language,

Suppose **ADD R0, R1 (R0 = R0 + R1)**

Here, We will be adding contents of **R0** and **R1** and store that result in **R0**. It depends on design.

In order to do this, We first have to select:

**Registers to be read: R0 and R1**

**Register to be written: R0**

# Register Set Design

**ADD R0, R1**


**Registers to be read: R0 and R1**

**Register to be written: R0**

**Ra and Rb will select registers  
whose data to be read.**

**Wr will select register to be written.  
Wrd is data to be written in register  
selected by Wr.**

**Value within register R0 will be sent to a.  
Value within register R1 will be sent to b.**

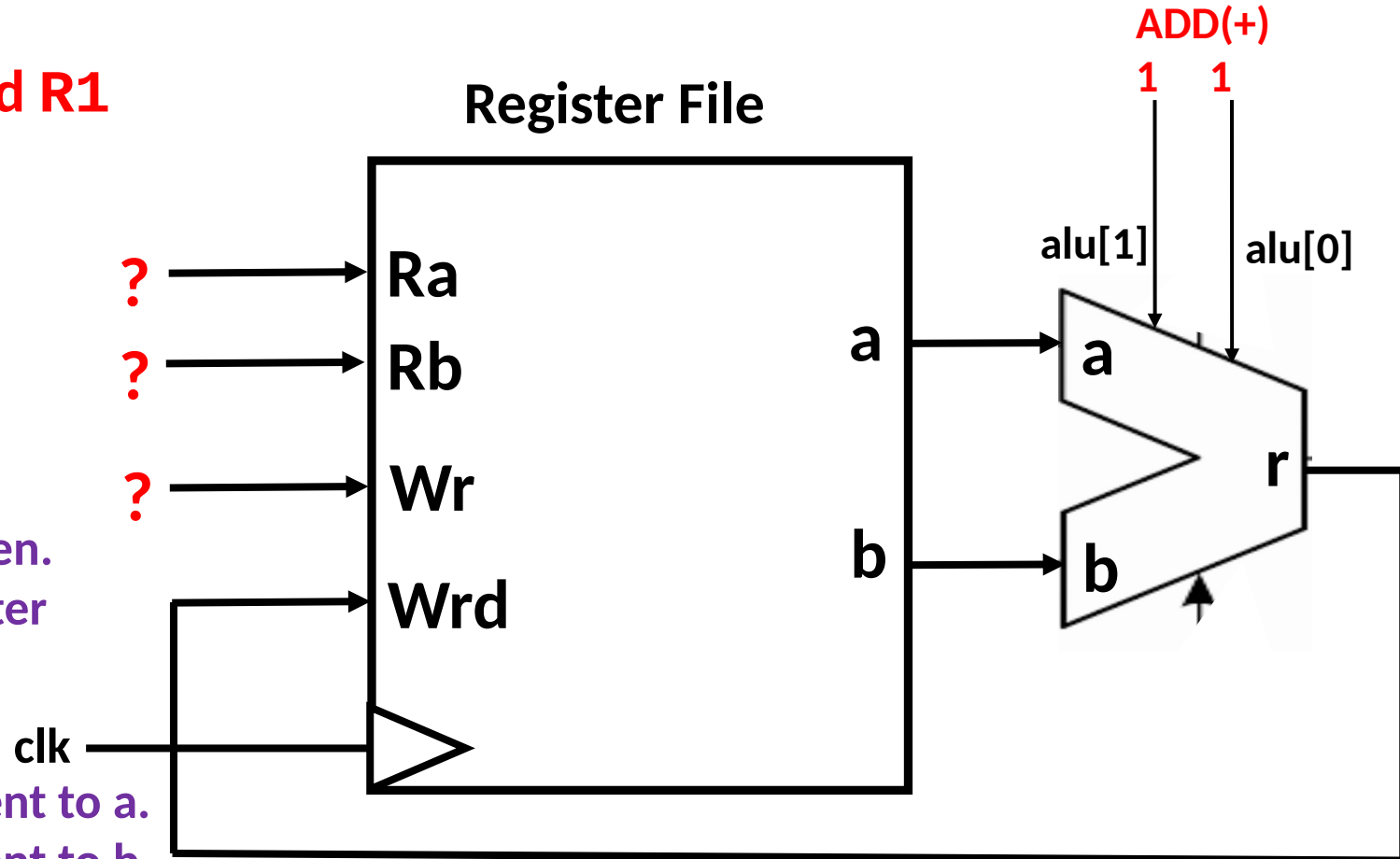

**Figure: How Register set operates in CPU**

# Register Set Design

**ADD R0, R1 (R0 = R0 + R1)**


**Registers to be read: R0 and R1**

**Register to be written: R0**

Ra and Rb will select registers  
whose data to be read.

Wr will select register to be written.  
Wrd is data to be written in register  
selected by Wr.

Value within register R0 will be sent to a.  
Value within register R1 will be sent to b.

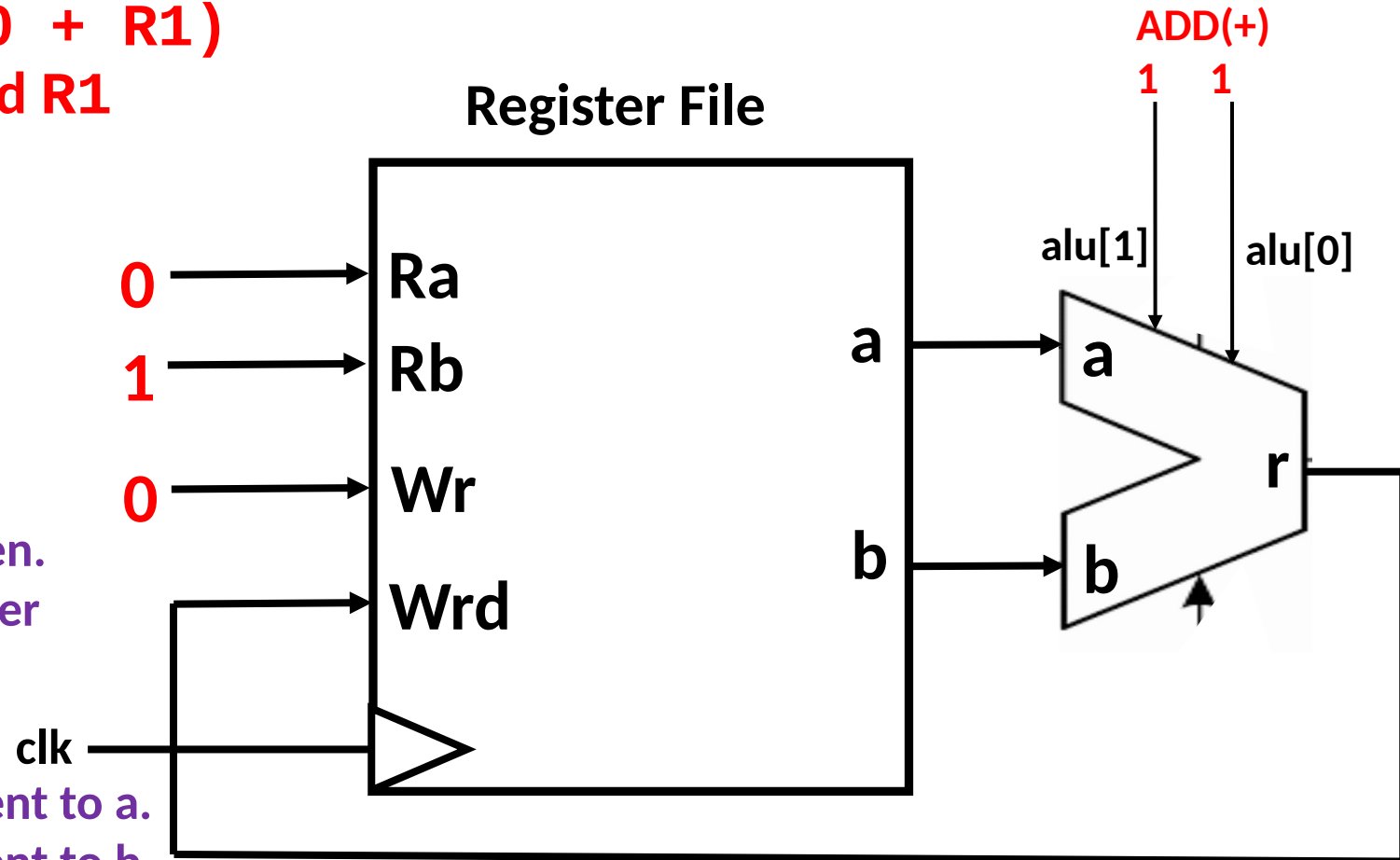

**Figure: How Register set operates in CPU**

# Register Set Design

**ADD R0, R1 (R0 = R0 + R1)**


**Registers to be read: R0 and R1**

**Register to be written: R0**

Ra and Rb will select registers  
whose data to be read.

Wr will select register to be written.  
Wrd is data to be written in register  
selected by Wr.

Value within register R0 will be sent to a.  
Value within register R1 will be sent to b.

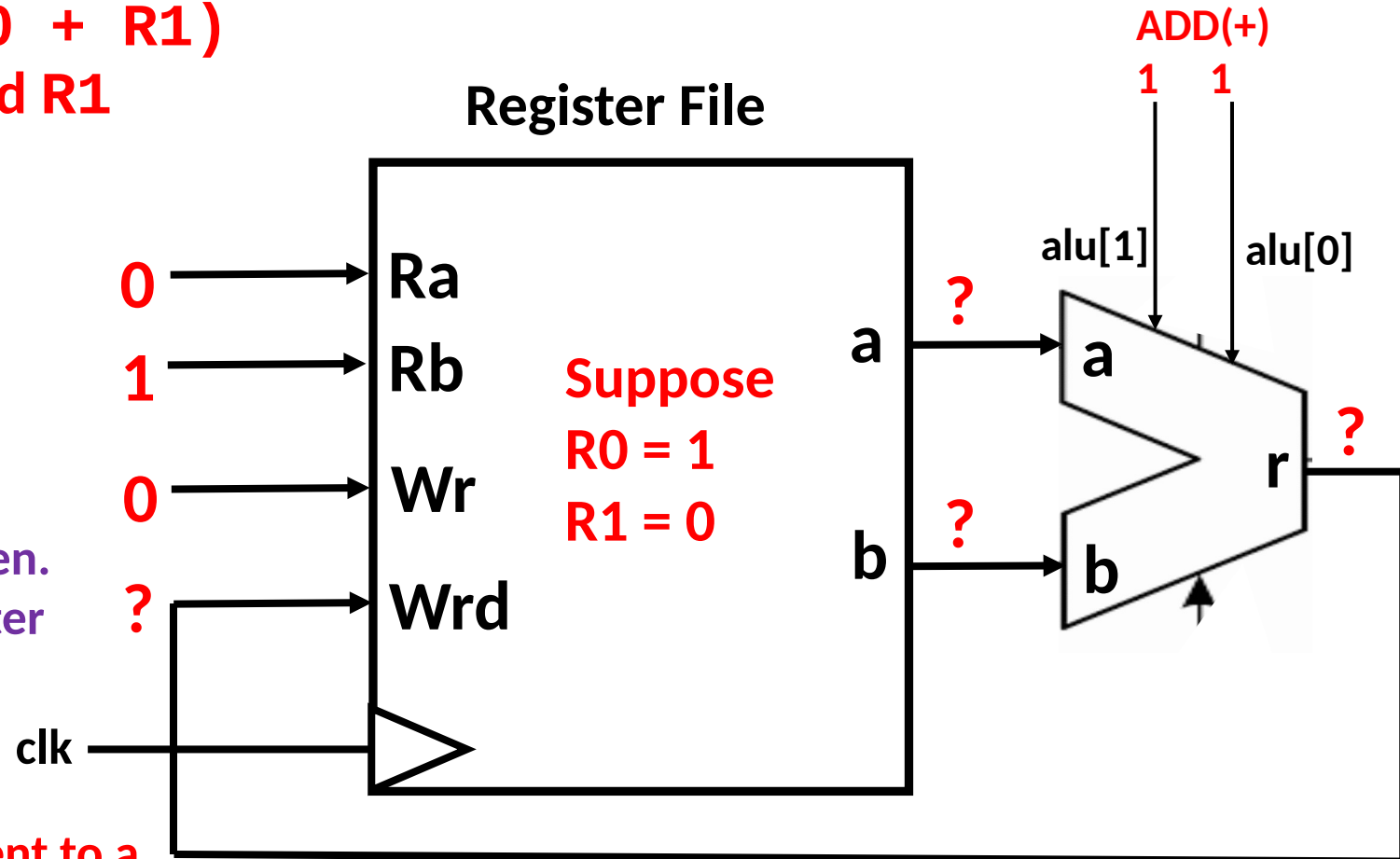

**Figure: How Register set operates in CPU**

# Register Set Design

**ADD R0, R1 (R0 = R0 + R1)**


**Registers to be read: R0 and R1**

**Register to be written: R0**

Ra and Rb will select registers  
whose data to be read.

Wr will select register to be written.  
Wrd is data to be written in register  
selected by Wr.

Value within register R0 will be sent to a.  
Value within register R1 will be sent to b.

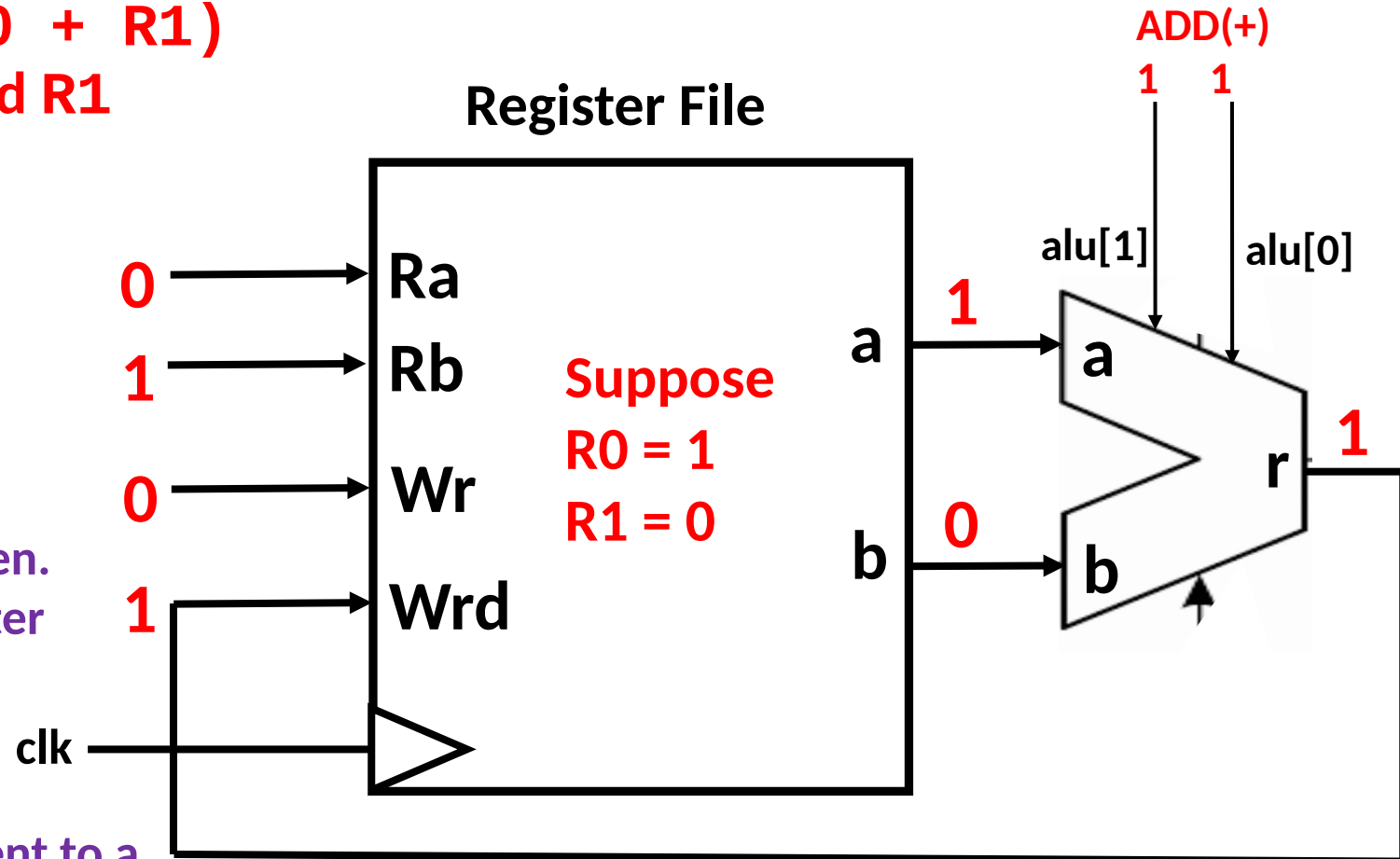


**Figure: How Register set operates in CPU**

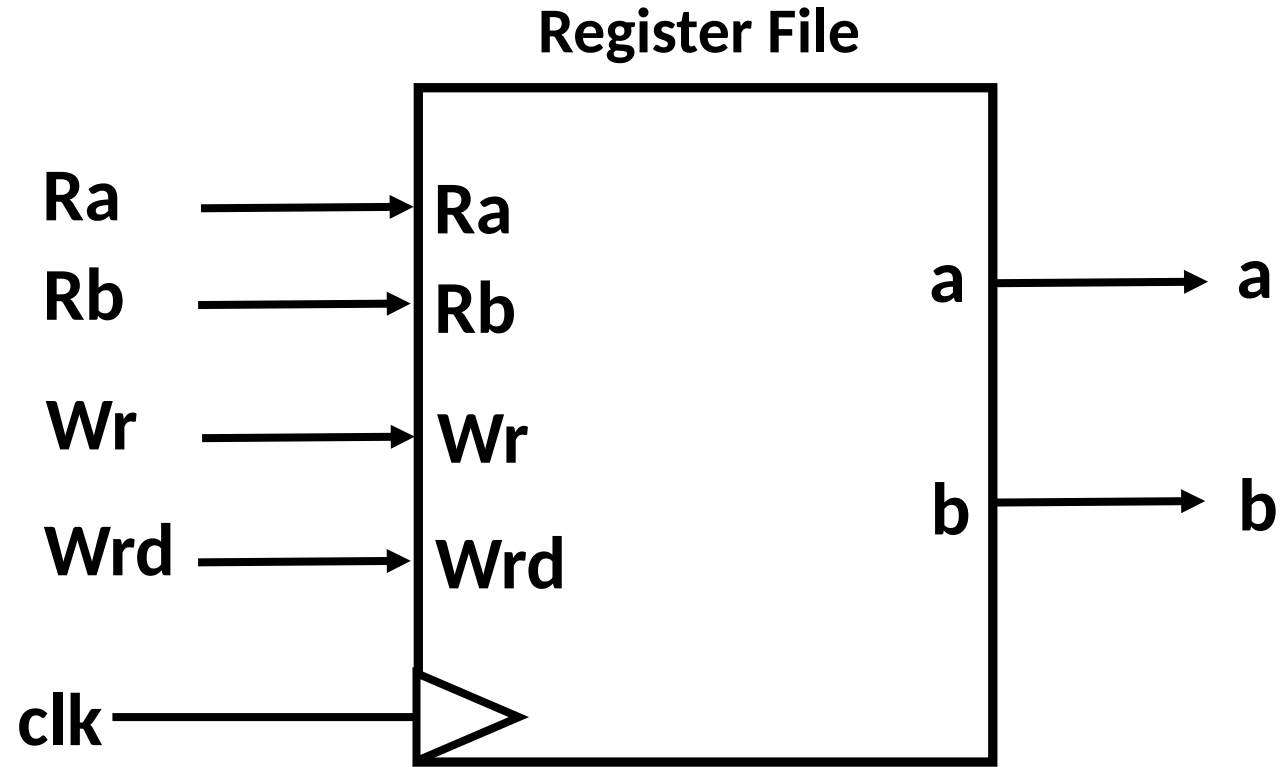

# Register Set Design

## 1bit Register Set with 2 1bit registers



**We will be designing this Register File!**

# Register Set Design


## 1bit Register Set with 2 1bit registers

Suppose we have 2 1-bit registers: R0 and R1.

Ra  
Rb

First, we have to select registers which will be defined by Ra and Rb.

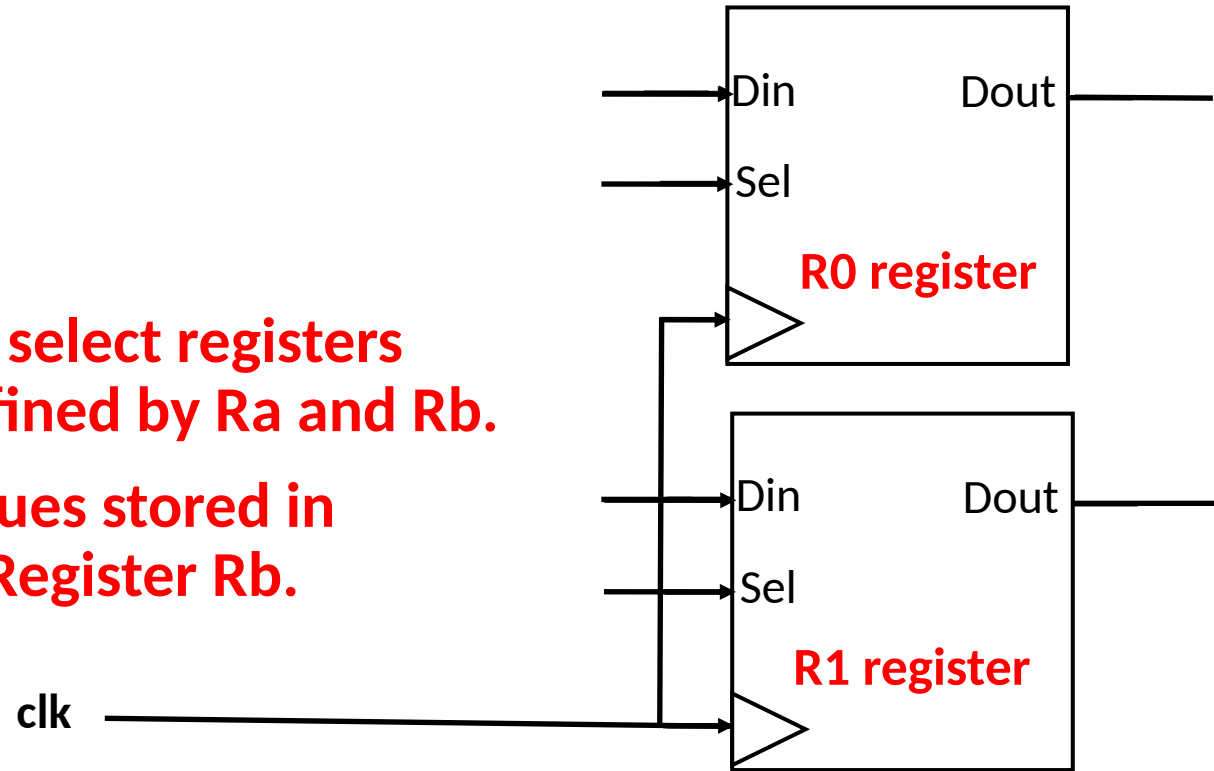We just need values stored in Register Ra and Register Rb.



# Register Set Design


## 1bit Register Set with 2 1bit registers

Suppose we have 2 1-bit registers: R0 and R1.

Ra  
Rb

First, we have to select registers which will be defined by Ra and Rb.

 We just need values stored in Register Ra and Register Rb.



a  
b

Then, We will have to send data of selected register to a (Ra) and b (Rb).

# Register Set Design


## 1bit Register Set with 2 1bit registers

Suppose we have 2 1-bit registers: R0 and R1.

Ra  
Rb

First, we have to select registers which will be defined by Ra and Rb.

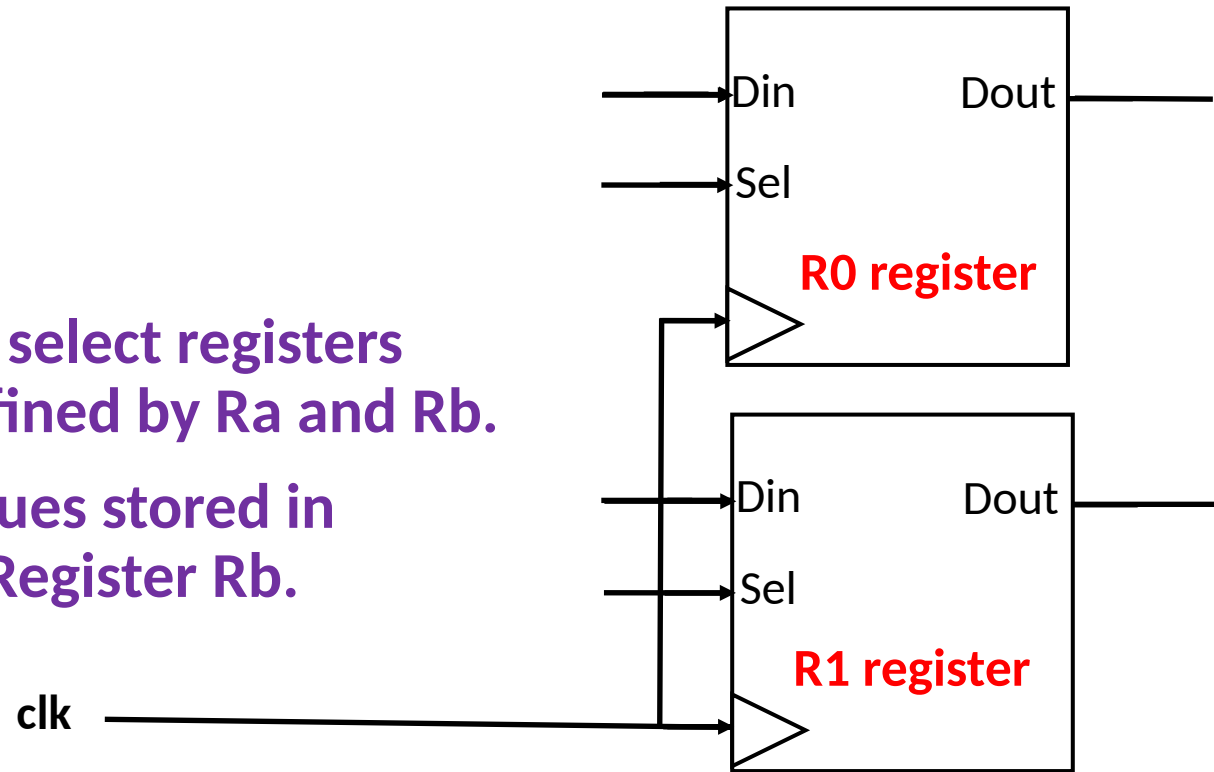We just need values stored in Register Ra and Register Rb.



Then, We will have to send data of selected register to a (Ra) and b (Rb).


# Register Set Design

## 1bit Register Set with 2 1bit registers

Suppose we have 2 1-bit registers: R0 and R1.

**Ra**  
**Rb**

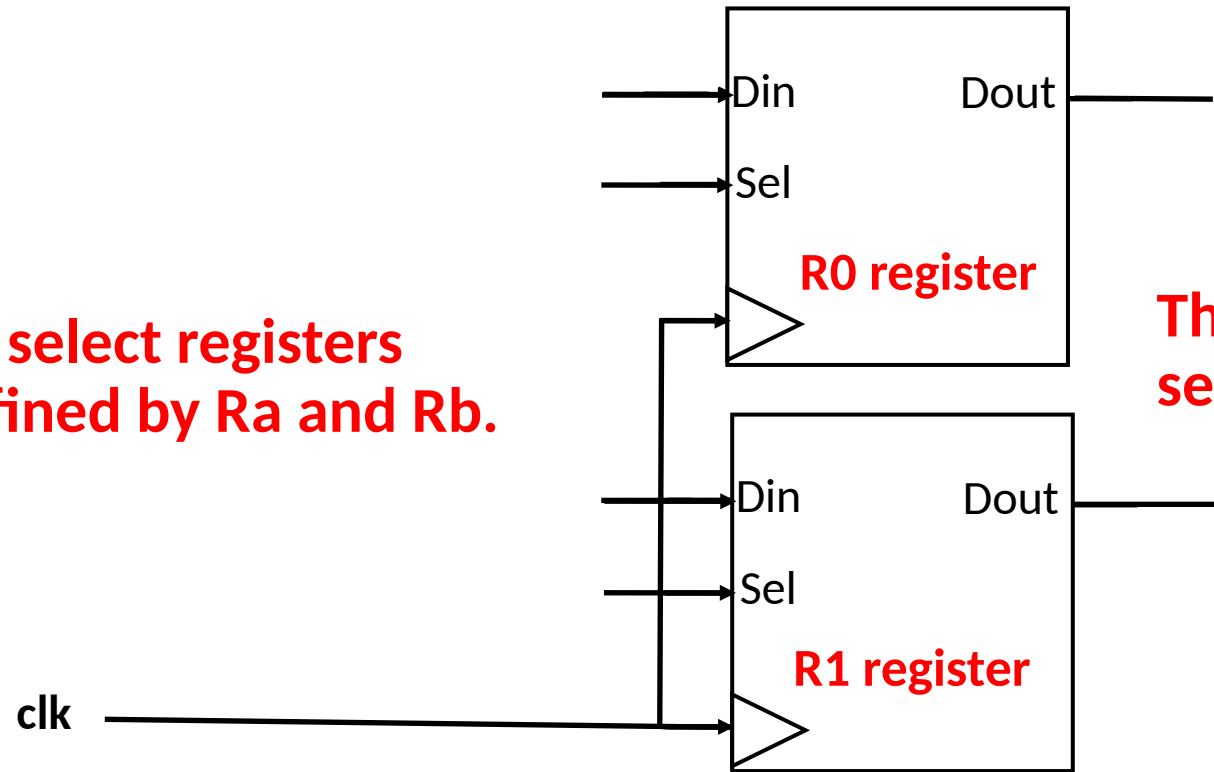
First, we have to select registers which will be defined by Ra and Rb.



Then, We will have to send data of selected register to a and b

# Register Set Design
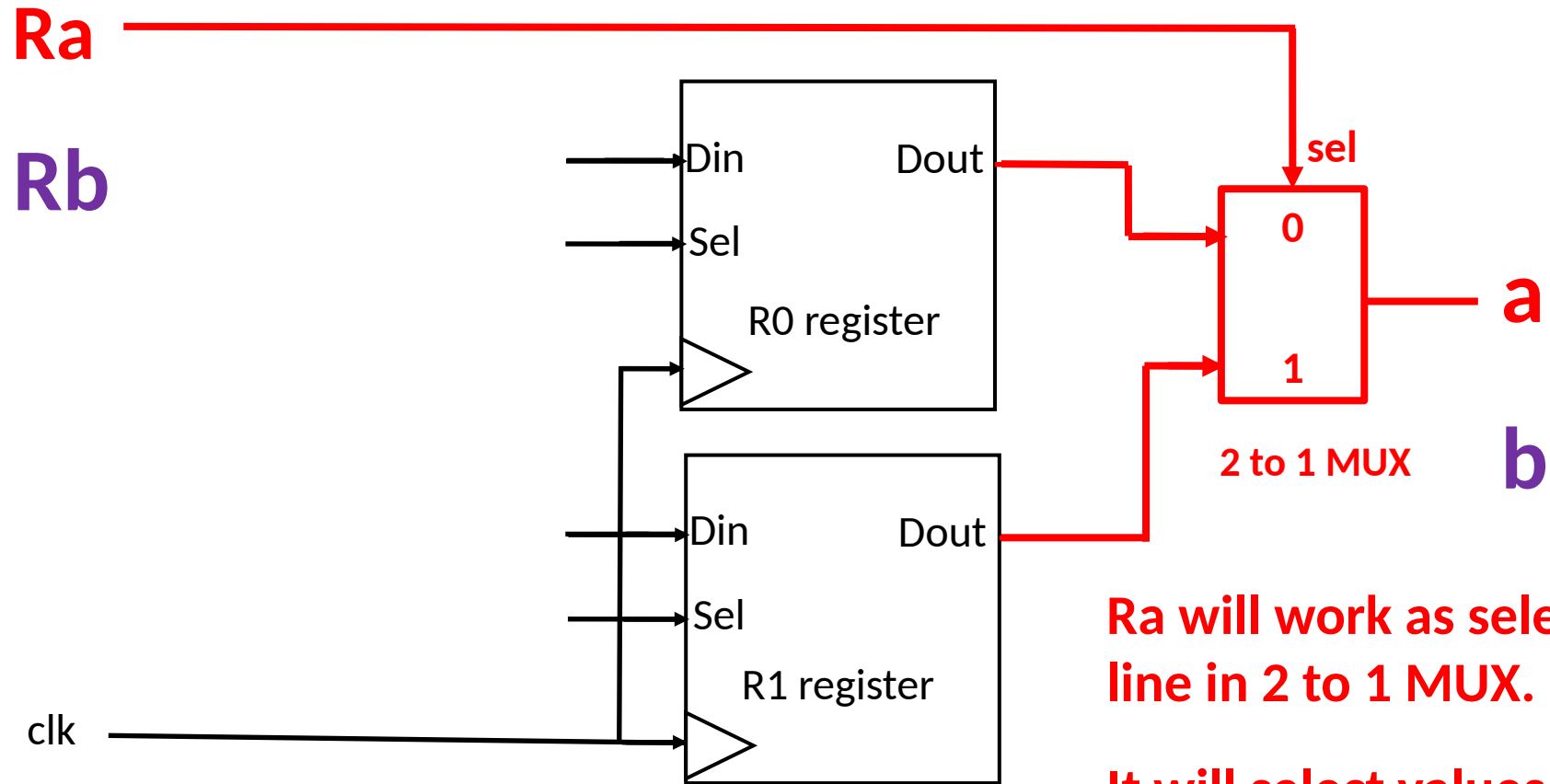
## 1bit Register Set with 2 1bit registers



**Ra will work as selection line in 2 to 1 MUX.**

**It will select values of one of registers selected by Ra.**

# Register Set Design

## 1bit Register Set with 2 1bit registers

**Ra = 0**

**Rb**


**Suppose**

**R0 = 1**

**R1 = 0**

**It means R0 contains 1 value.**

**And R1 contains 0 value.**

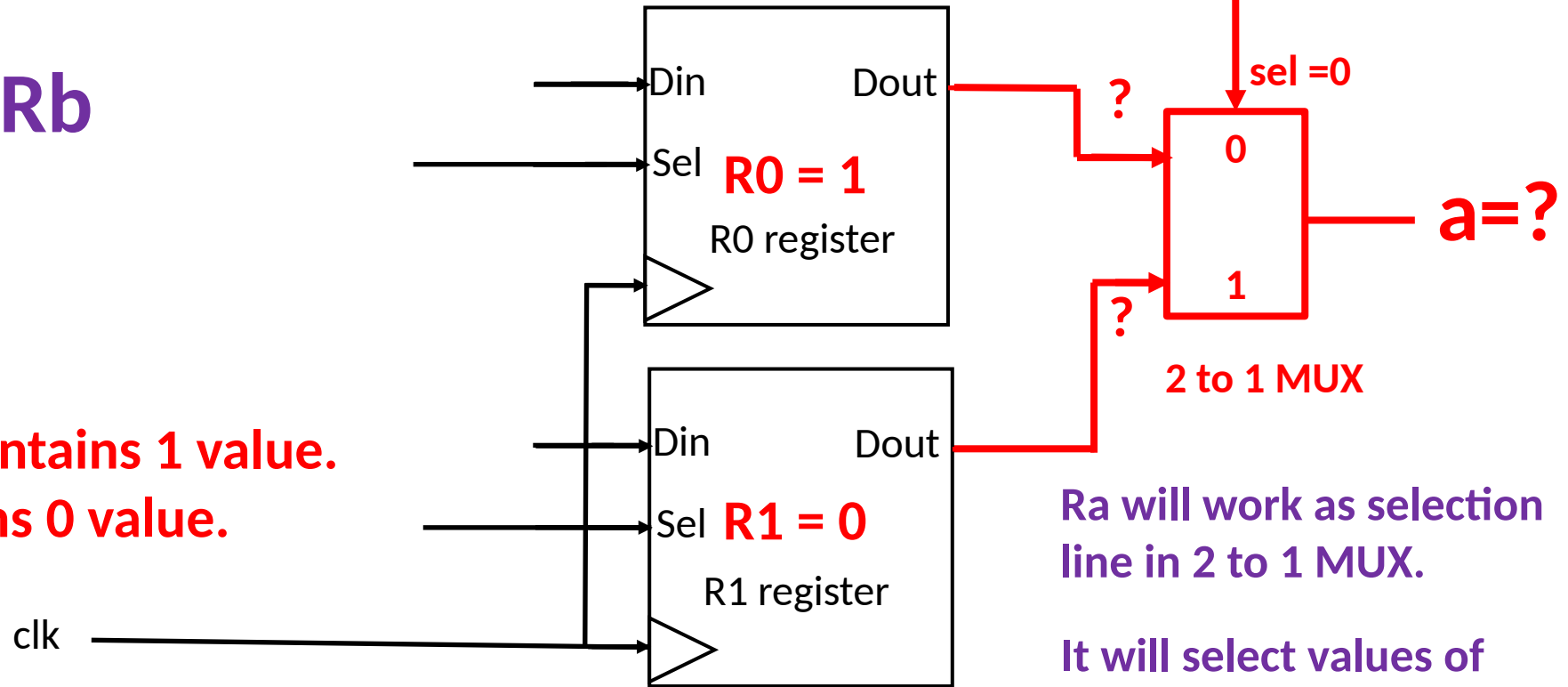

# Register Set Design

## 1bit Register Set with 2 1bit registers

**Ra = 0**

**Rb**


Suppose

**R0 = 1**

**R1 = 0**

It means R0 contains 1 value.


And R1 contains 0 value.

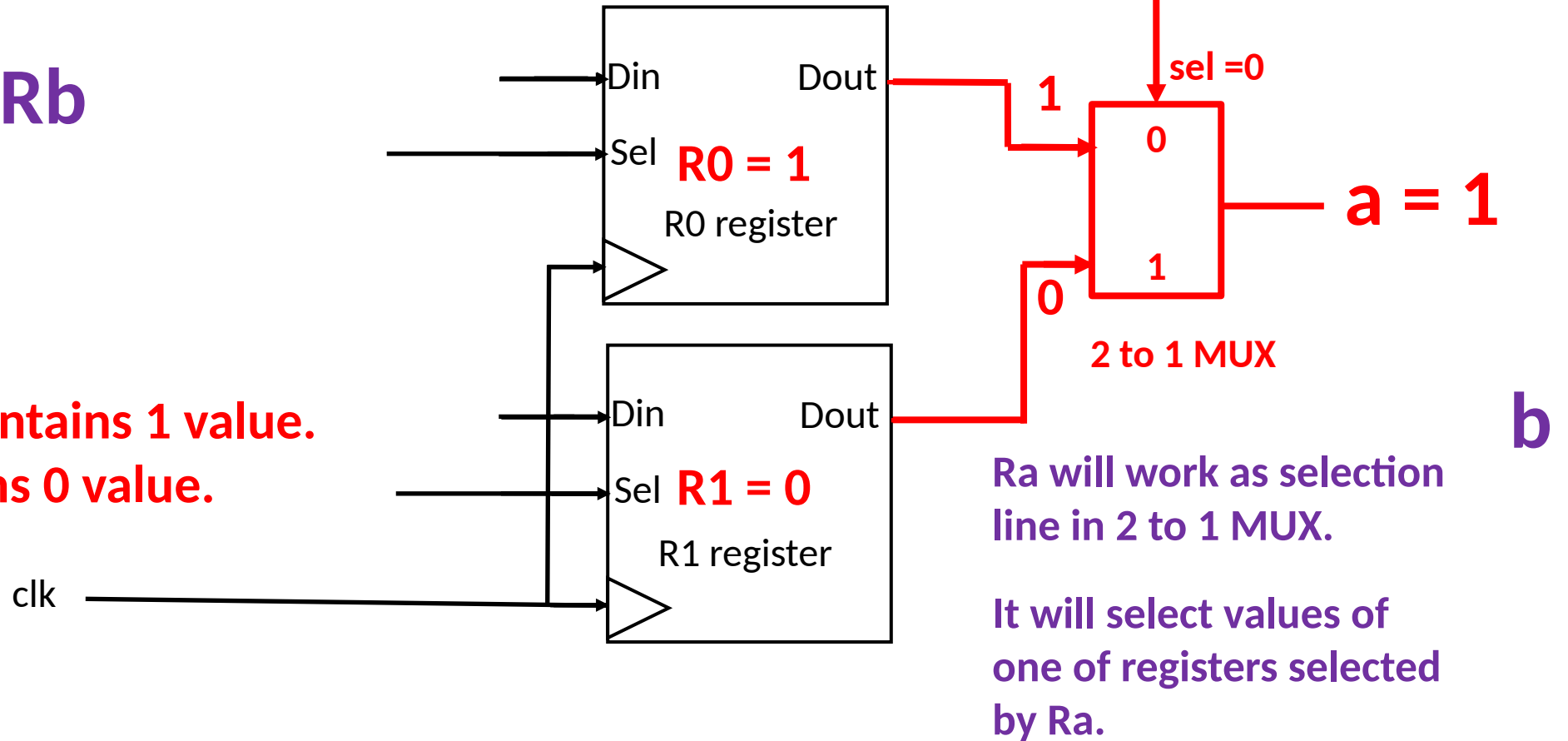



# Register Set Design
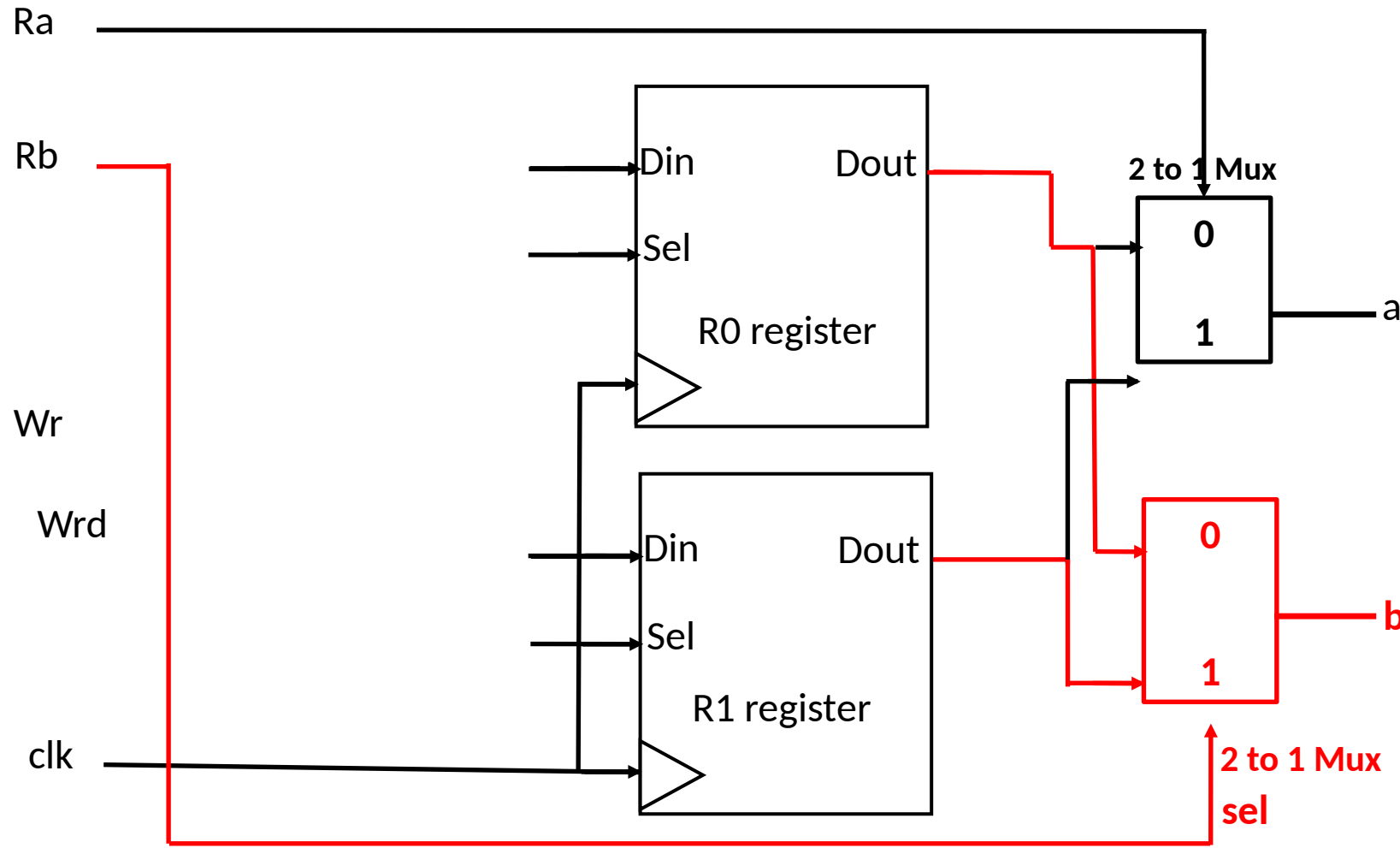
## 1bit Register Set with 2 1bit registers




Similarly, Rb will work as selection line in 2 to 1 MUX.

It will select values of one of registers selected by Rb.

# Register Set Design

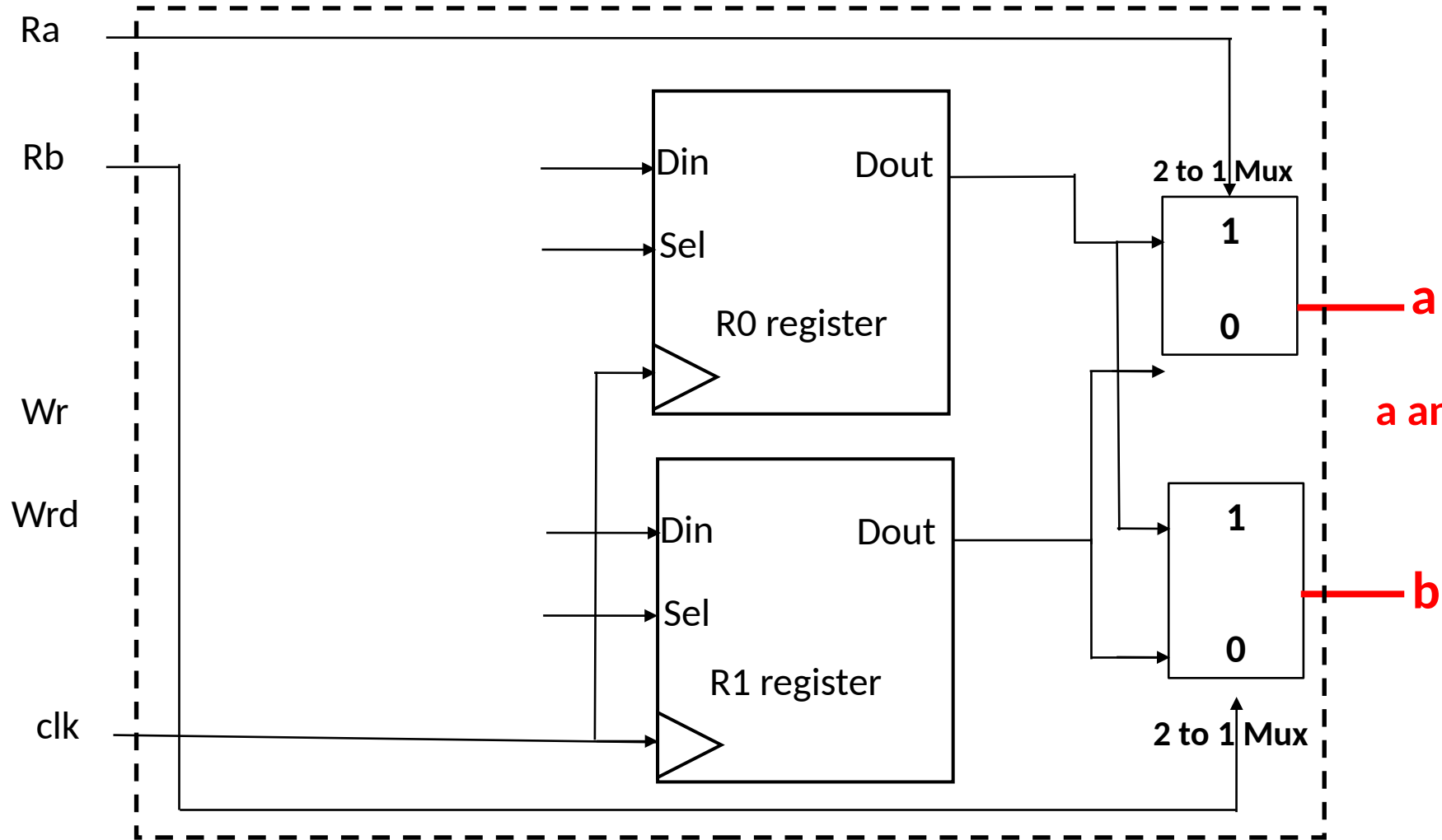
## 1bit Register Set with 2 1bit registers



**a and b will be connected to ALU.**


# Register Set Design
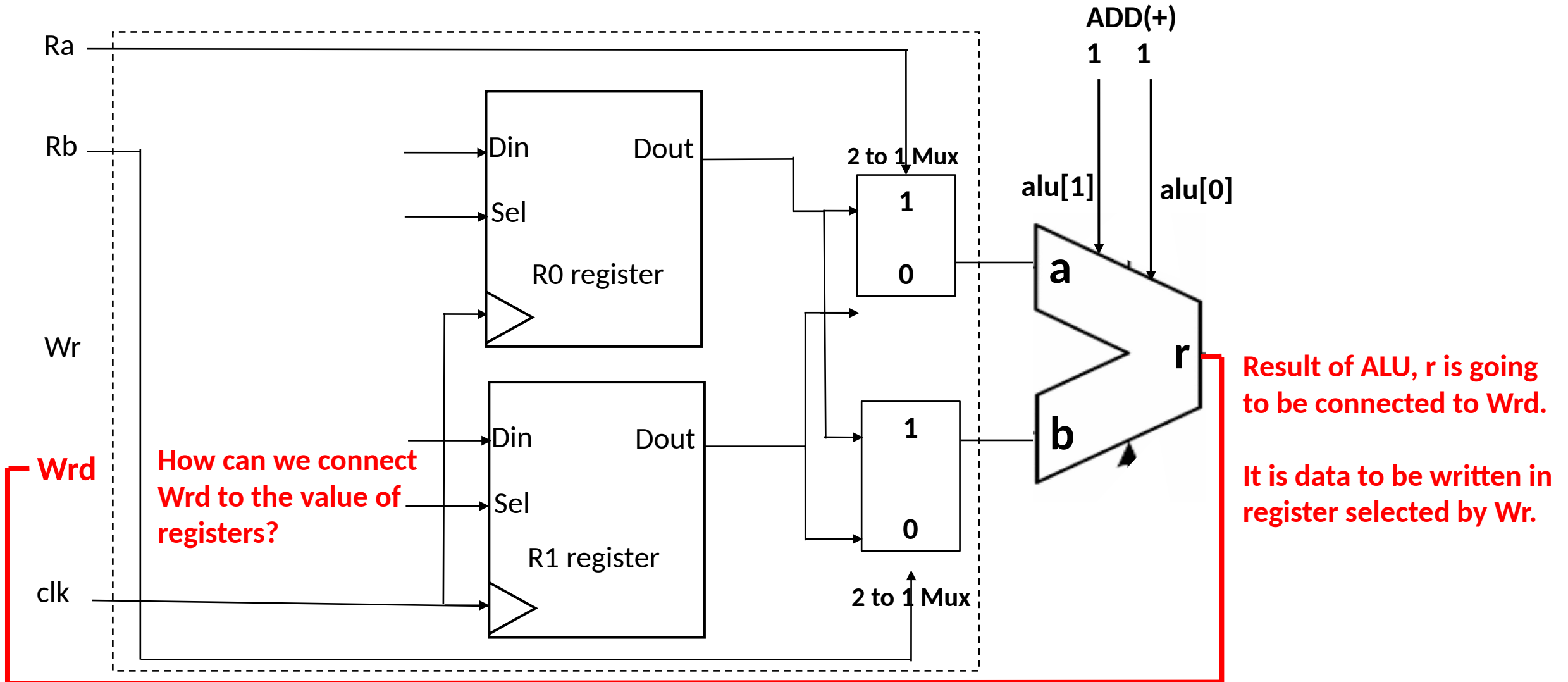
## 1bit Register Set with 2 1bit registers



# Register Set Design
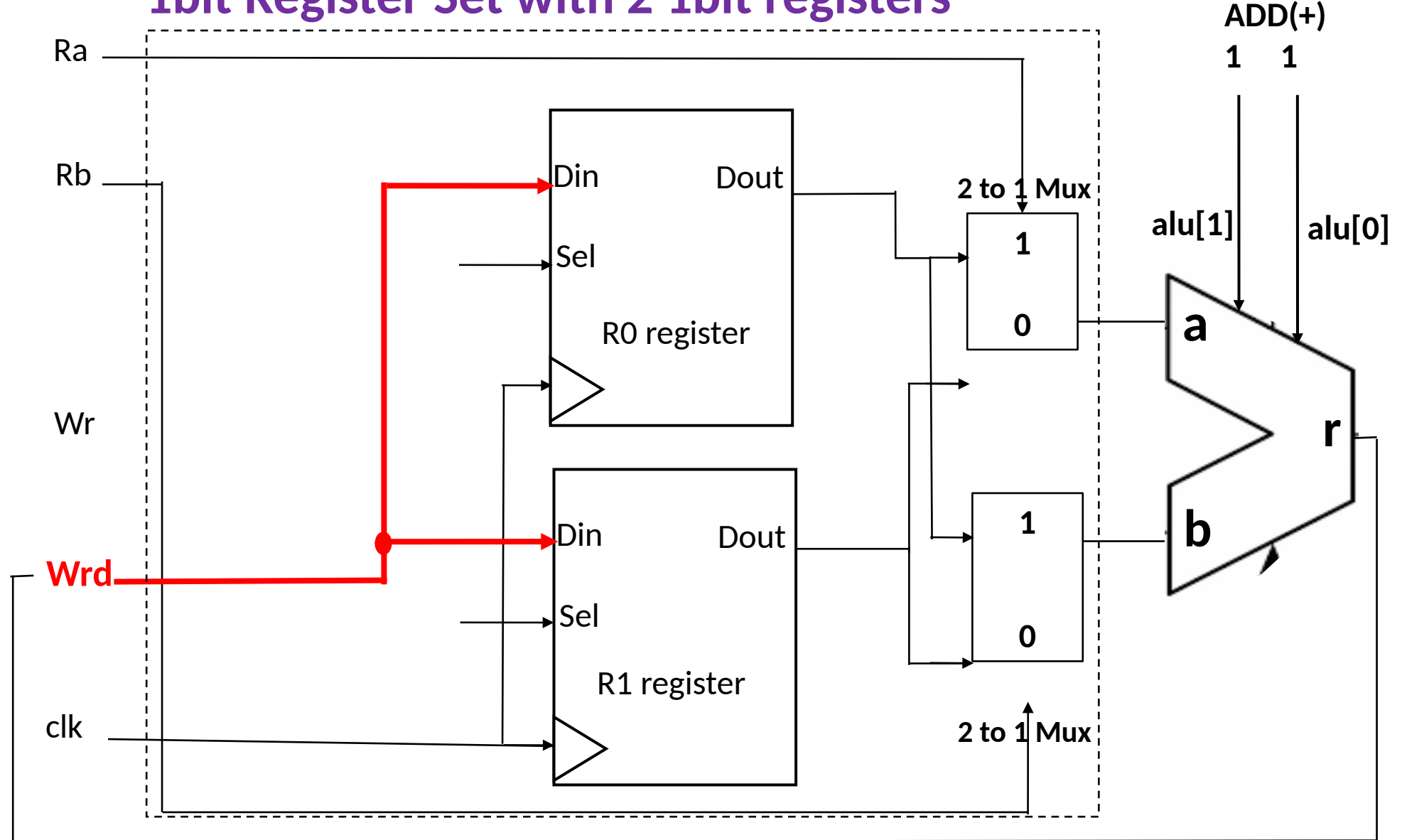
## 1bit Register Set with 2 1bit registers




We will directly connect Wrd to Din pin of each register.

Even though Wrd is connected to Din, It cannot update data in register UNLESS Sel = 1 AND CLOCK IS POSITIVE EDGE.


# Register Set Design
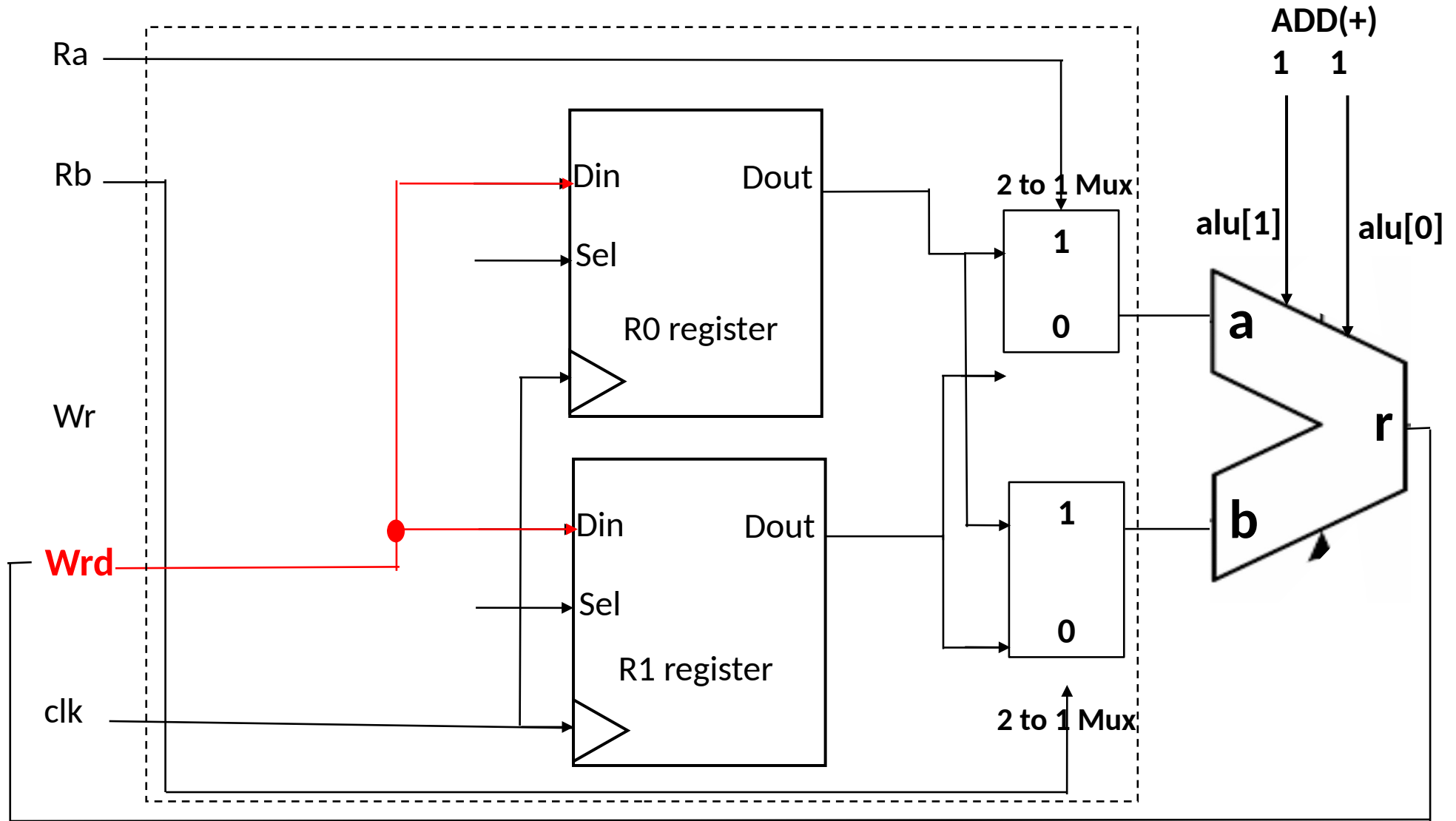
## 1bit Register Set with 2 1bit registers



How are we going to select one of registers defined by  $Wr$ ?

### 1 to 2 Decoder

 


S	A	B
0	1	0
1	0	1

**A** = **\$**  
**B** = **\$**

We can use a 1 to 2 decoder to select one of register.

## Register Set Design

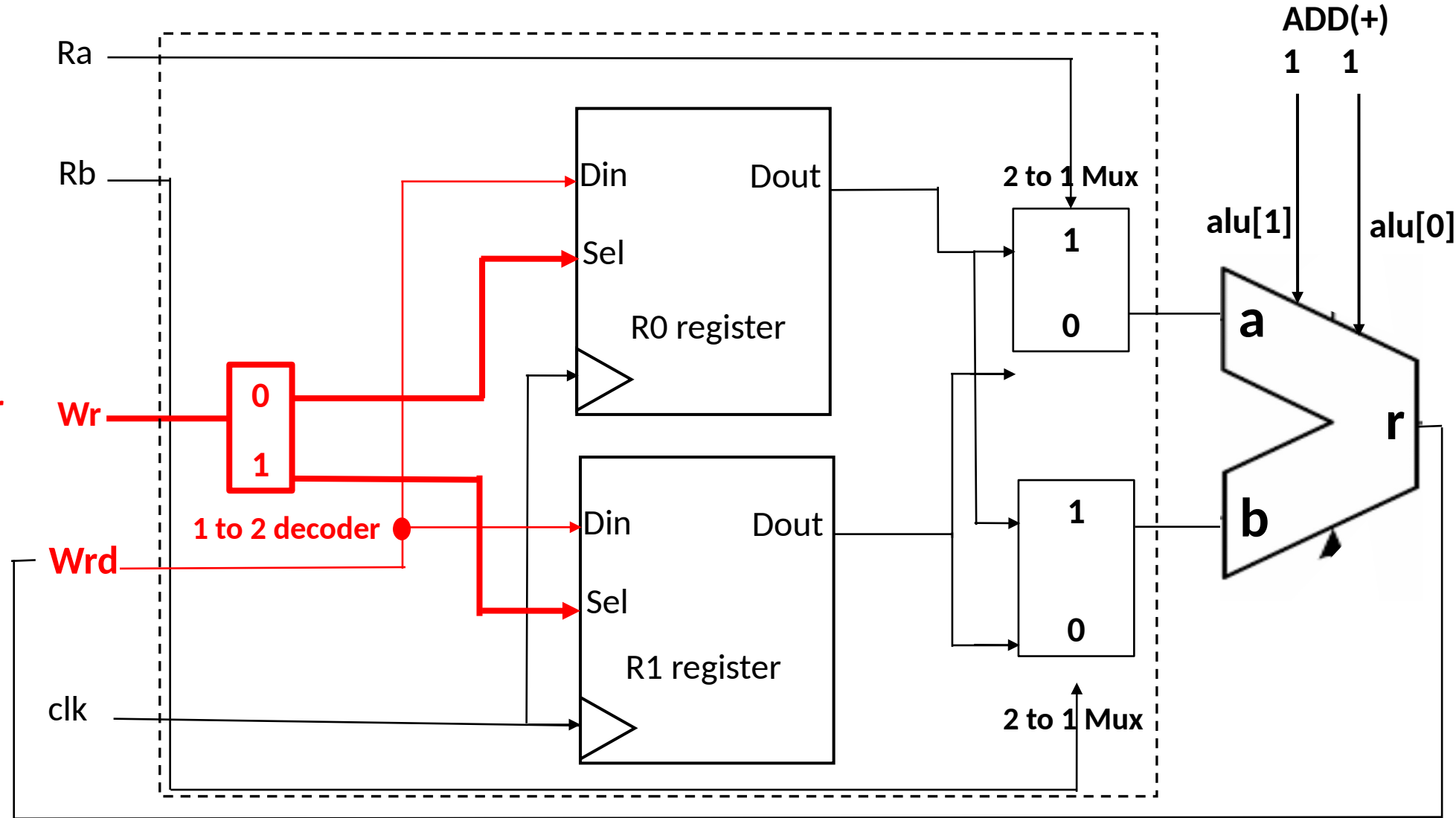
### 1bit Register Set with 2 1bit registers



# Register Set Design


## 1bit Register Set with 2 1bit registers

1 to 2 Decoder

 

S	A	B
0	1	0
1	0	1


Clock is on negative edge.

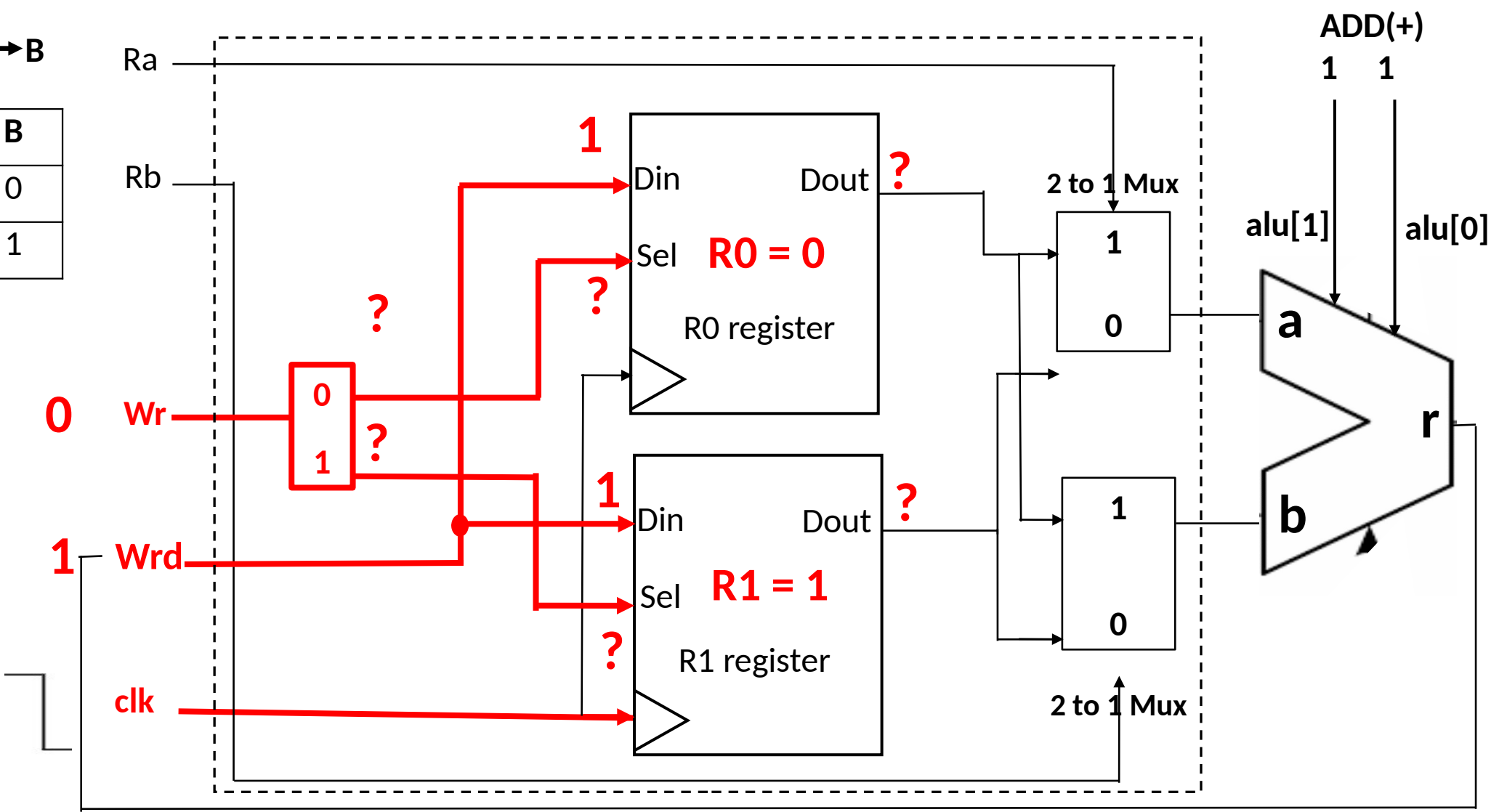


# Register Set Design

## 1bit Register Set with 2 1bit registers

1 to 2 Decoder

 

S	A	B
0	1	0
1	0	1

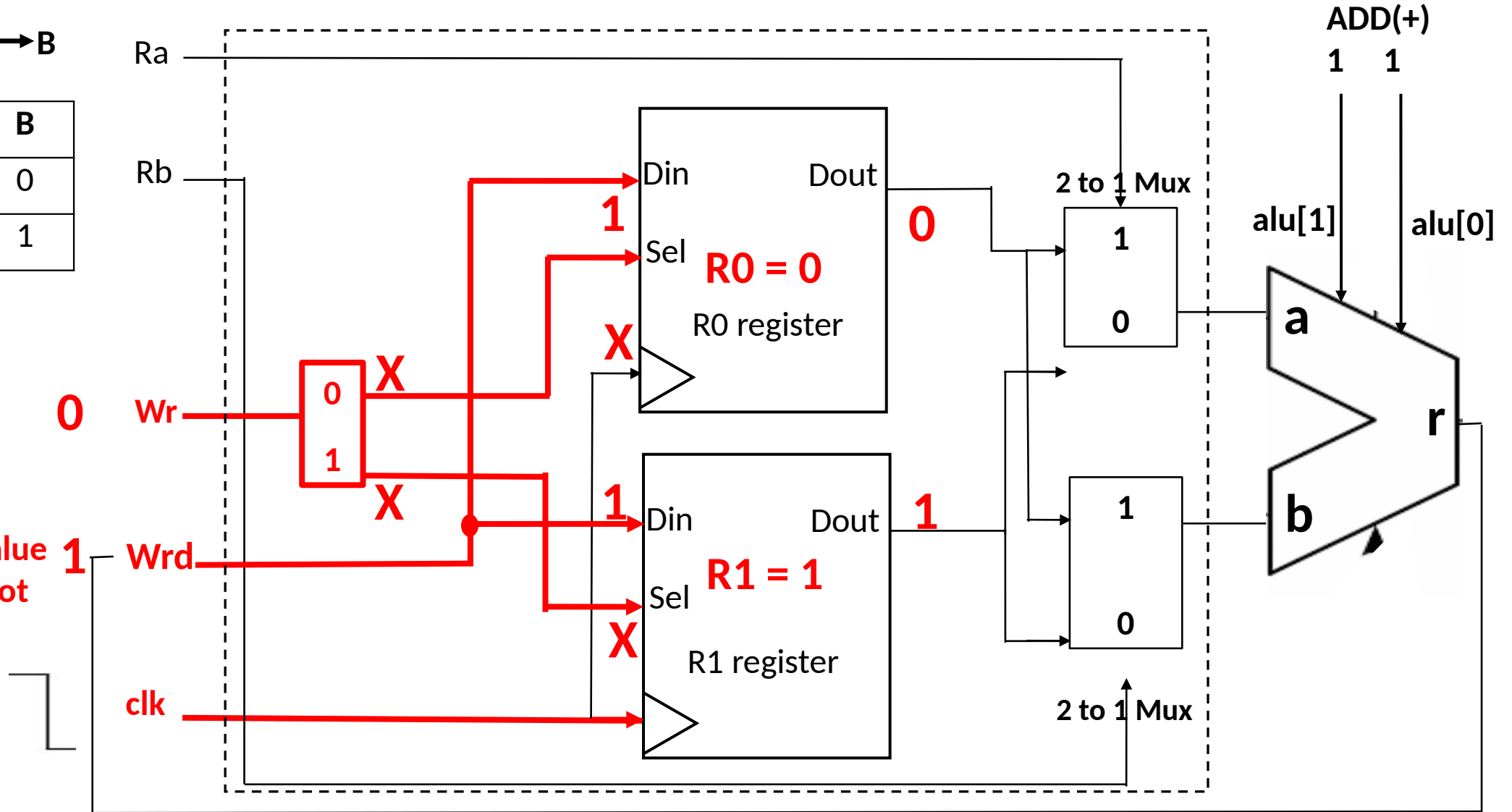





# Register Set Design

## 1bit Register Set with 2 1bit registers

1 to 2 Decoder

 

S	A	B
0	1	0
1	0	1

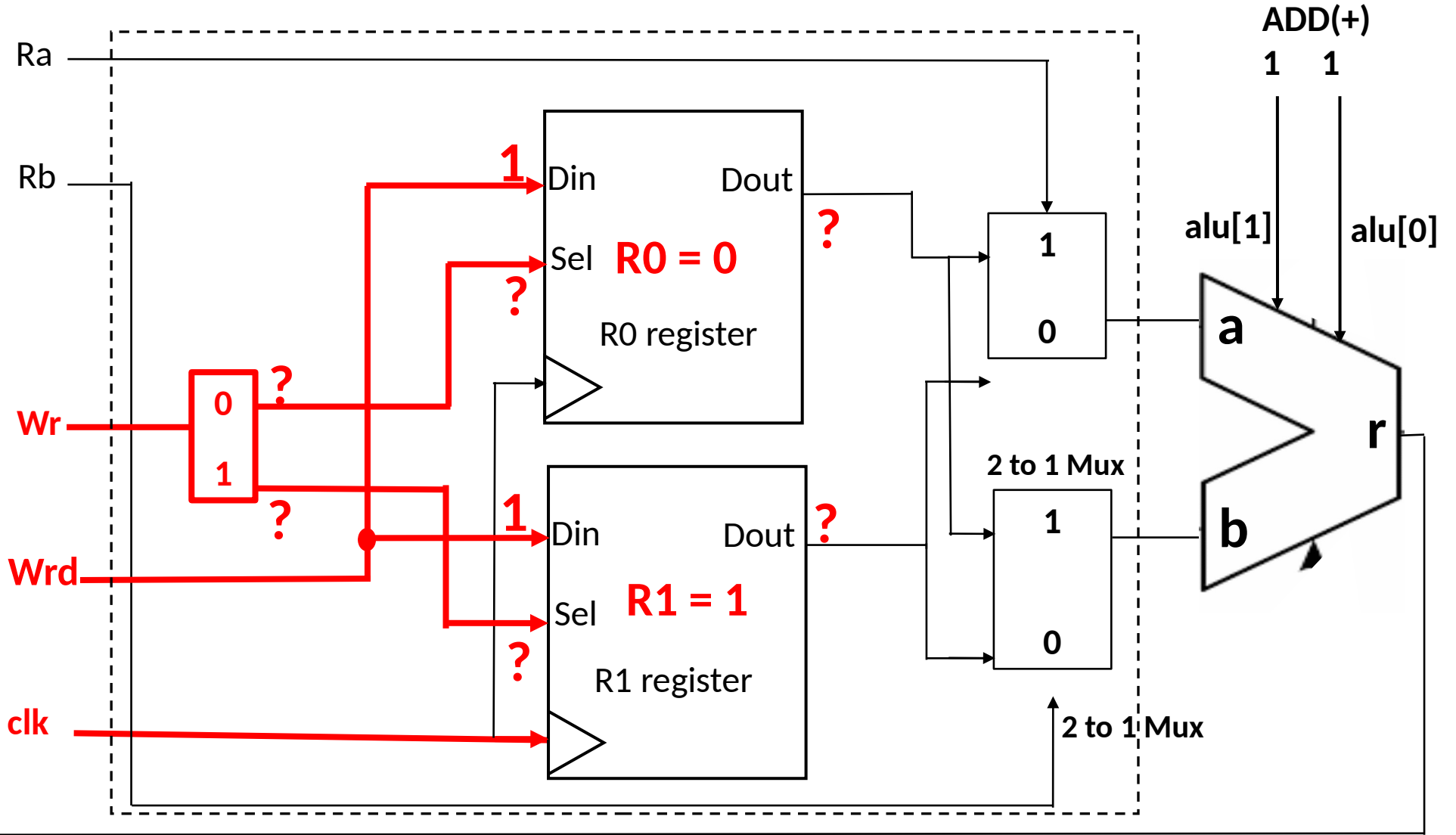


Clock is on positive edge.


## Register Set Design

### 1bit Register Set with 2 1bit registers

## 1 to 2 Decoder

 

S	A	B
0	1	0
1	0	1

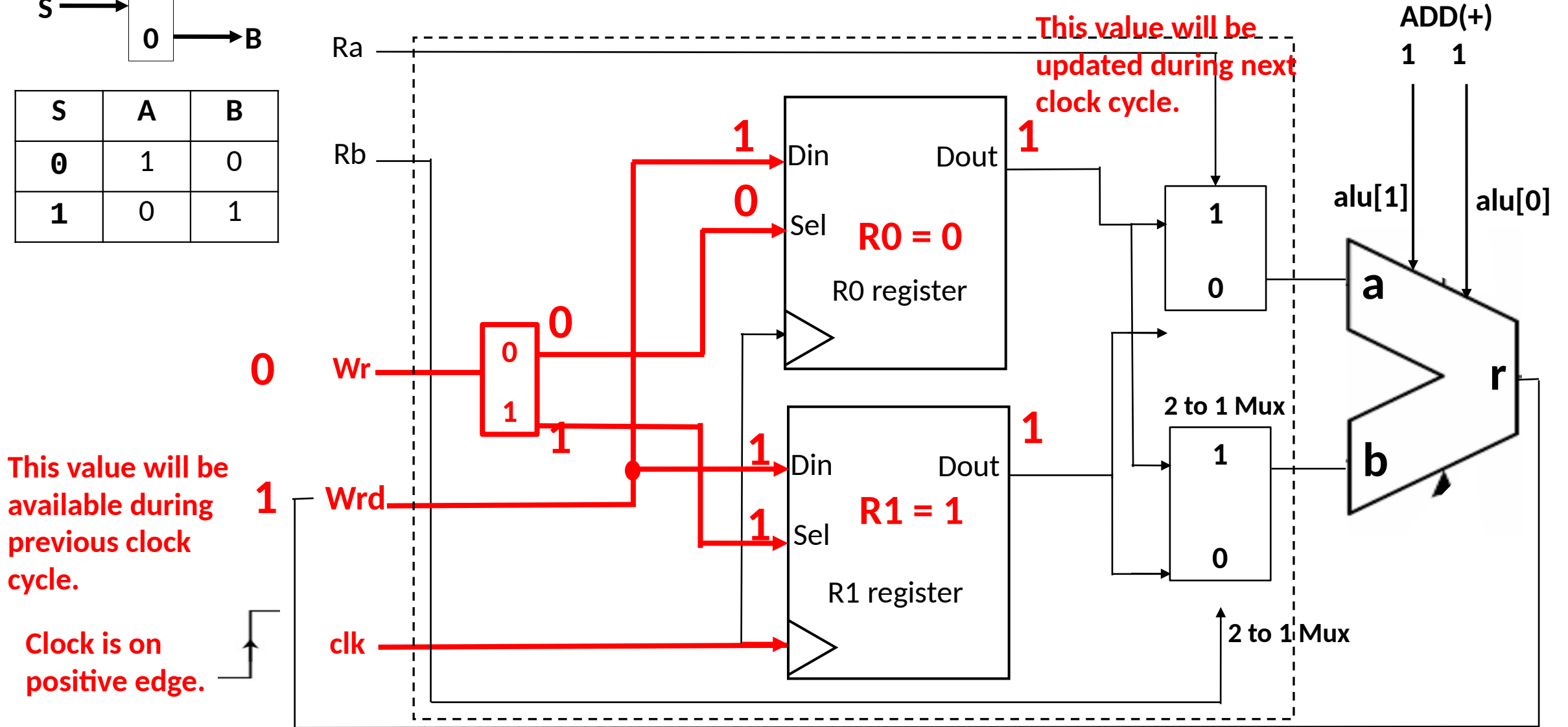

# Register Set Design

## 1bit Register Set with 2 1bit registers

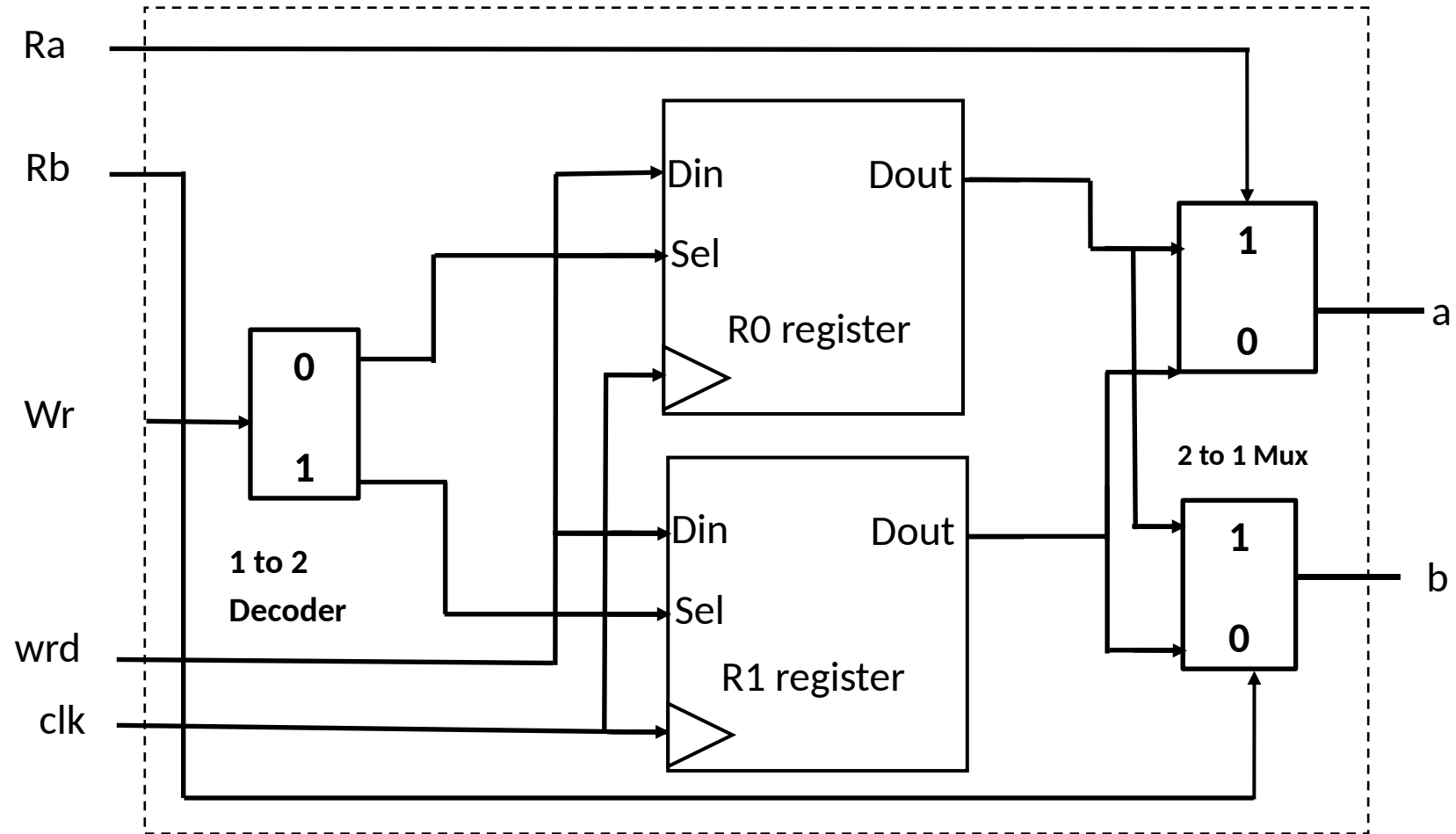


Figure: Register set with 2 1-bit registers (Final Design)

**Homework:**

**Similarly try to design 2bit/3bit/4bit  
Register Set with 1/2/3/4 register/registers**

**Next Day:  
Register Design II  
&  
SRAM**

Thank You ㄸ