

Adder, Shifter, MUX, Parity Generator

Mahit Kumar Paul

Assistant Professor, Dept. of CSE
RUET, Rajshahi-6204

mahit.cse@gmail.com

mahit@cse.ruet.ac.bd

Adder

- Adds two N-bit binary numbers
 - 2-bit adder: adds two 2-bit numbers
 - Can give output 3-bit result
 - e.g., $01 + 11 = 100$ ($1 + 3 = 4$)

Half Adder

- Adds **2** bits
- Generates sum and carry

Step 1: Capture the function

Inputs		Outputs	
a	b	co	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



Step 2: Convert to equations

$$co = ab$$

$$s = a'b + ab' \quad (\text{same as } s = a \text{ xor } b)$$

Half Adder...

Step 3: Create the circuit

  

Half Adder Using CMOS Logic

Try Yourself

Full Adder

- Adds **3** bits
- Generates sum and carry

Step 1: Capture the function

Inputs			Outputs	
a	b	ci	co	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder...

Step 2: Convert to equations

$$co = a'bc + ab'c + abc' + abc$$

$$co = a'bc + abc + ab'c + abc + abc' + abc$$

$$co = (a'+a)bc + (b'+b)ac + (c'+c)ab$$

$$co = bc + ac + ab$$

$$S = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A B C + A \overline{B} \overline{C}$$

$$S = \overline{A} (\overline{B} C + B \overline{C}) + A (BC + \overline{B} \overline{C})$$

$$S = \overline{A} (\overline{B} C + B \overline{C}) + A (\overline{\overline{B} C} + (\overline{B + C}))$$

$$S = \overline{A} (\overline{B} C + B \overline{C}) + A ((\overline{\overline{B} + C}) + (\overline{B + C}))$$

$$S = \overline{A} (\overline{B} C + B \overline{C}) + A (\overline{(\overline{B} + C)(B + C)})$$

$$S = \overline{A} (\overline{B} C + B \overline{C}) + A (\overline{\overline{B} B + \overline{B} C + C B + C C})$$


$$S = \overline{A} (\overline{B} C + B \overline{C}) + A (\overline{\overline{B} C + B \overline{C}})$$

$$S = \overline{A} (B \oplus C) + A (\overline{B \oplus C})$$

$$S = (A \oplus B) \oplus C$$

Full Adder...

Step 3: Create the circuit

 

Full Adder Using CMOS Logic...

Try Yourself

Shifter

- In Binary Operation, shifting is a bitwise operation that shifts the operand 1 to n-1 places to the right or left.

Original Data	1	0	1	1
---------------	---	---	---	---

After 2 bit shift	1	1	1	0
----------------------	---	---	---	---

Shifter...

- Left Shift
- Right Shift
- n-bit shift = original data

1	0	1	1
---	---	---	---

4-bit Input Data

1	1	0	1
---	---	---	---

3 bit left shift

1	0	1	1
---	---	---	---

4 bit left shift

Shifter...

- k -bit right shift = $n-k$ bit left shift

1	0	1	1
---	---	---	---

4-bit Input Data

1	1	0	1
---	---	---	---

1 bit right shift

1	1	0	1
---	---	---	---

3 bit left shift

4x4 Shifter

- Any general purpose n -bit shifter should be able to shift incoming data by up to $(n - 1)$ place in a right-shift or left-shift direction.
- Further specifying that all shifts should be on an end-around basis, so that any bit shifted out at one end of a data word will be shifted in at the other end of the word, then the problem of right shift or left shift is greatly eased.
- The shifter must have:
 - input from a four line parallel data bus
 - four output lines for the shifted data
 - means of transferring input data to output lines with any shift from 0 to 3 bits

Switch

 


Figure: A switch

4x4 Crossbar Switch



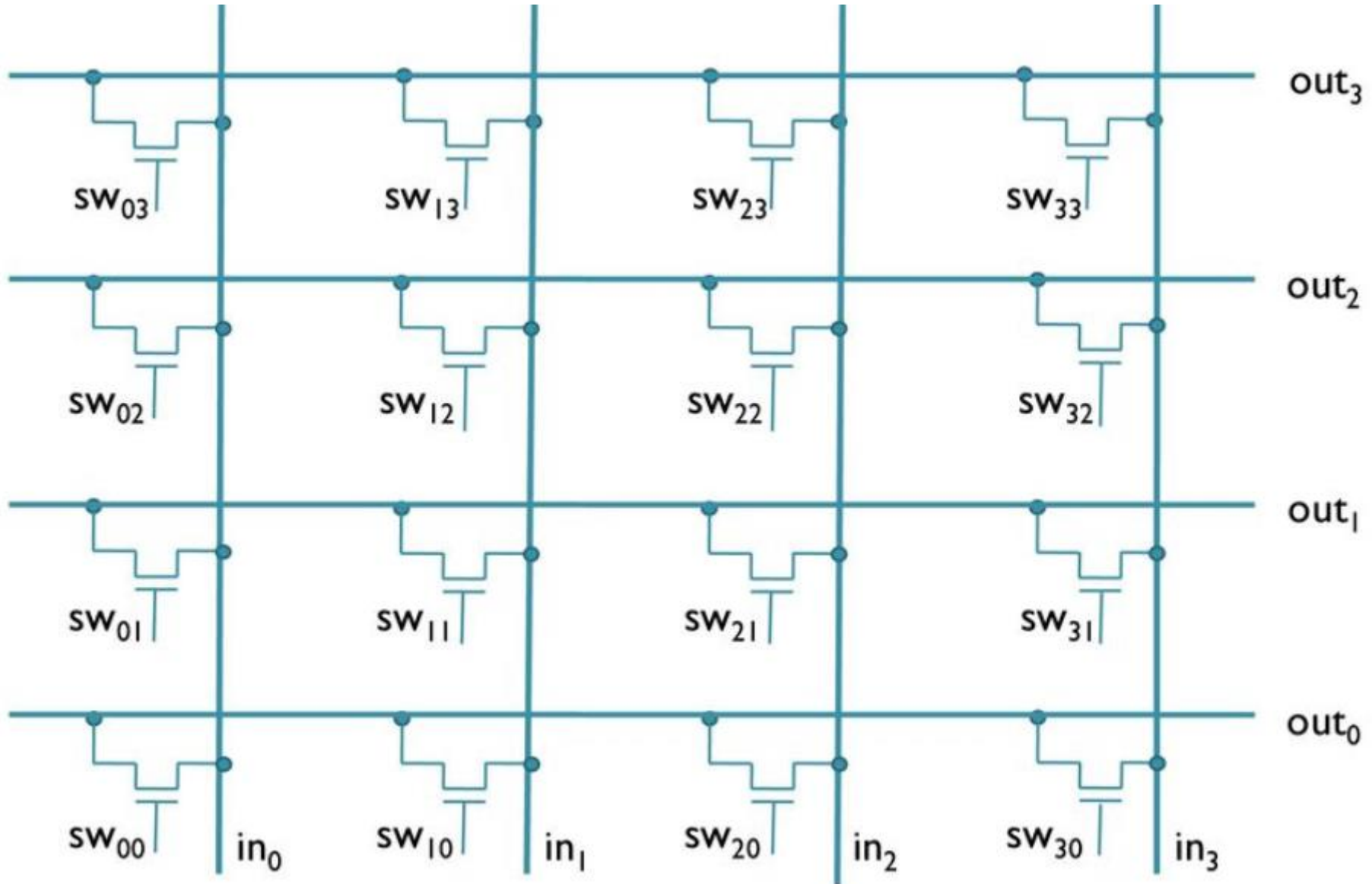


Fig.: 4x4 Crossbar Switch


4x4 Barrel Shifter...

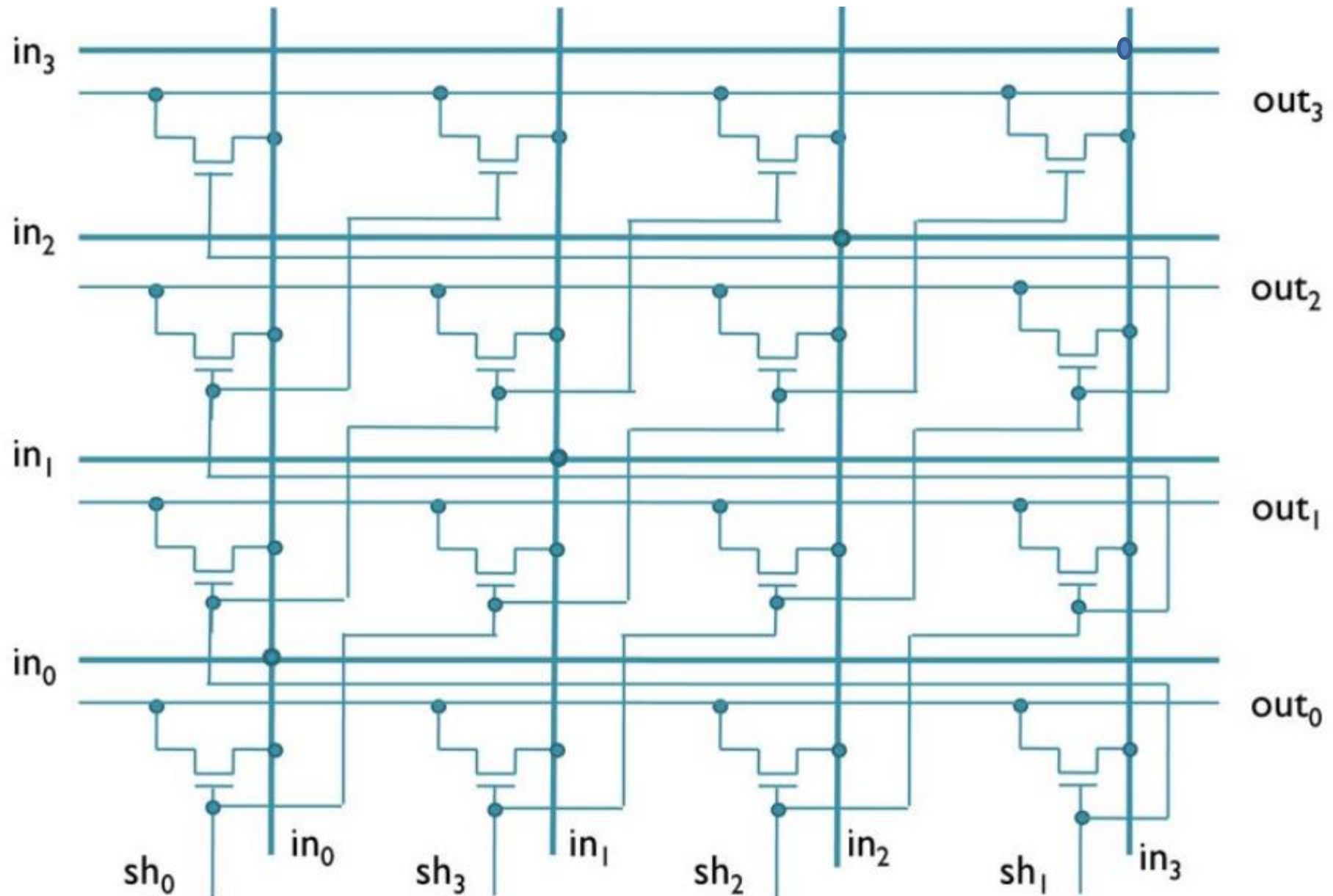


4x4 Barrel Shifter...

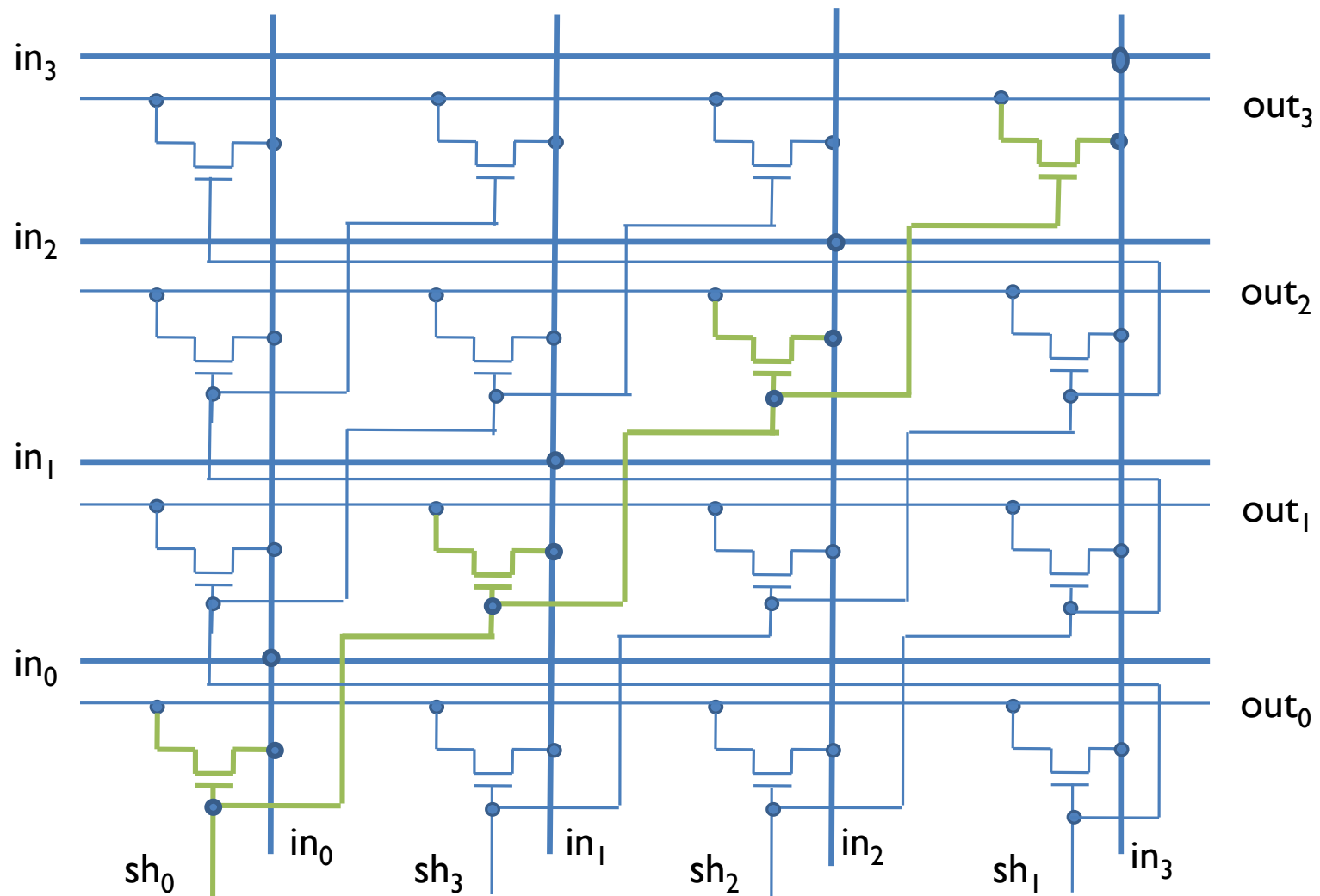


4x4 Barrel Shifter...

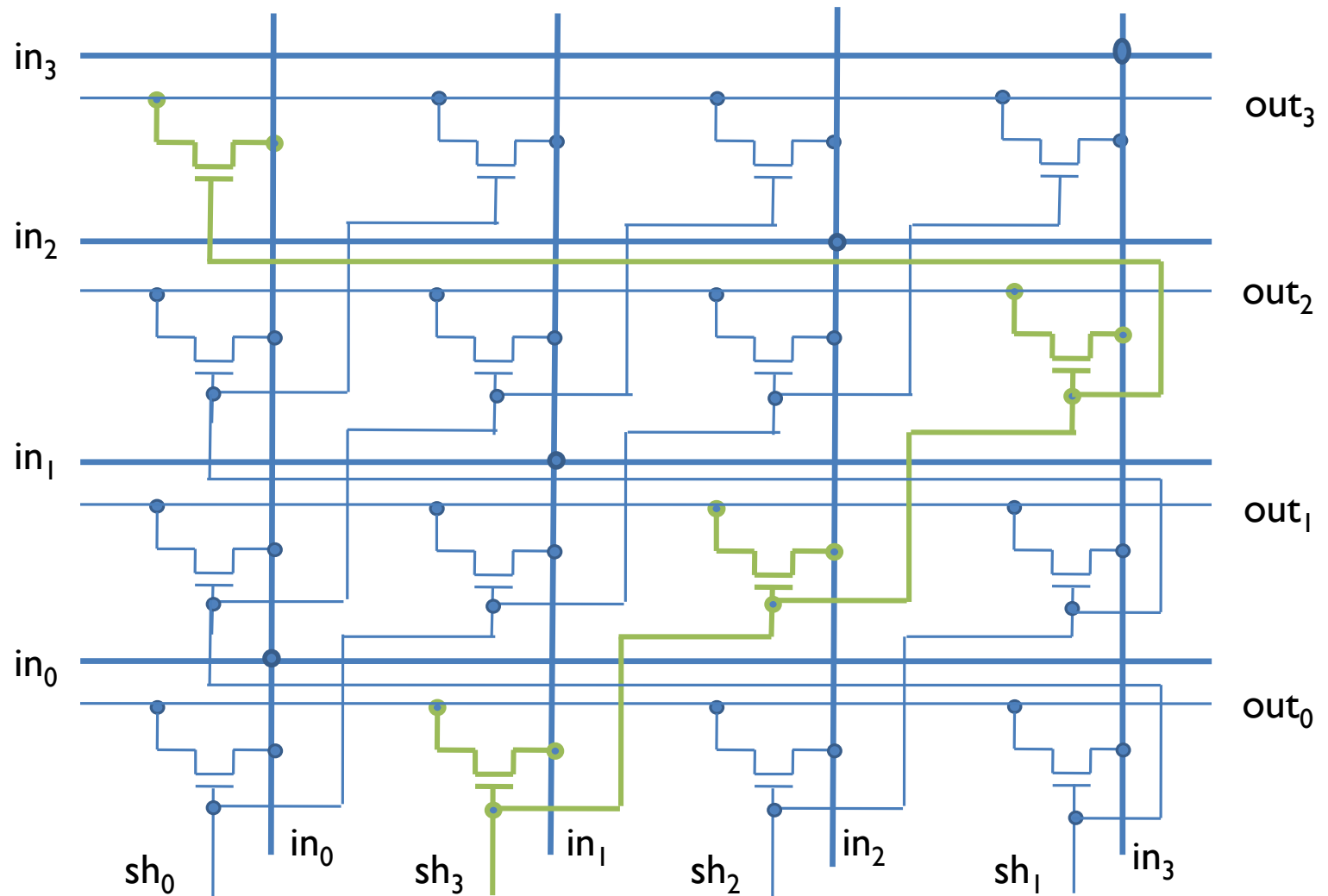


4x4 Barrel Shifter...

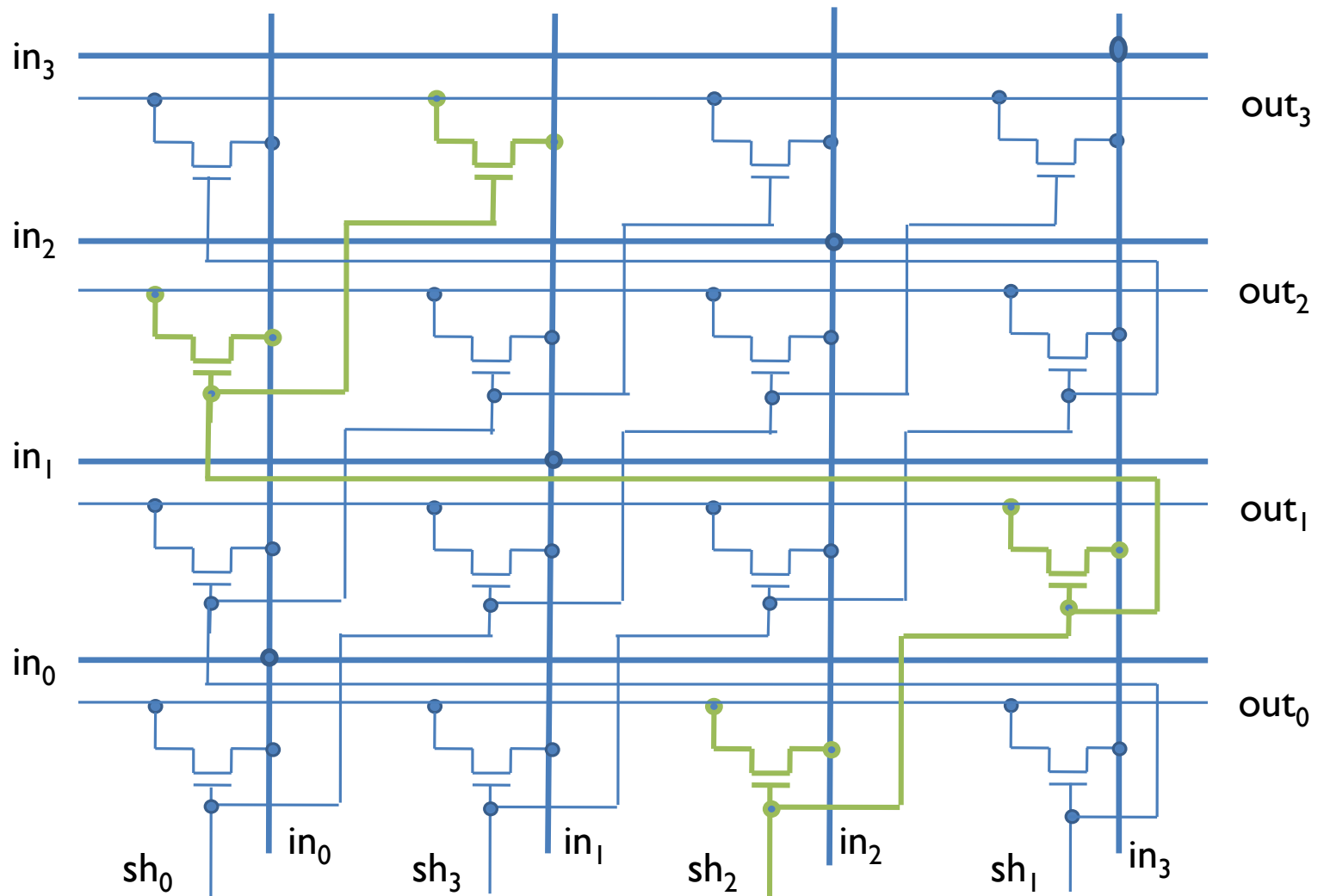

4x4 Barrel Shifter...

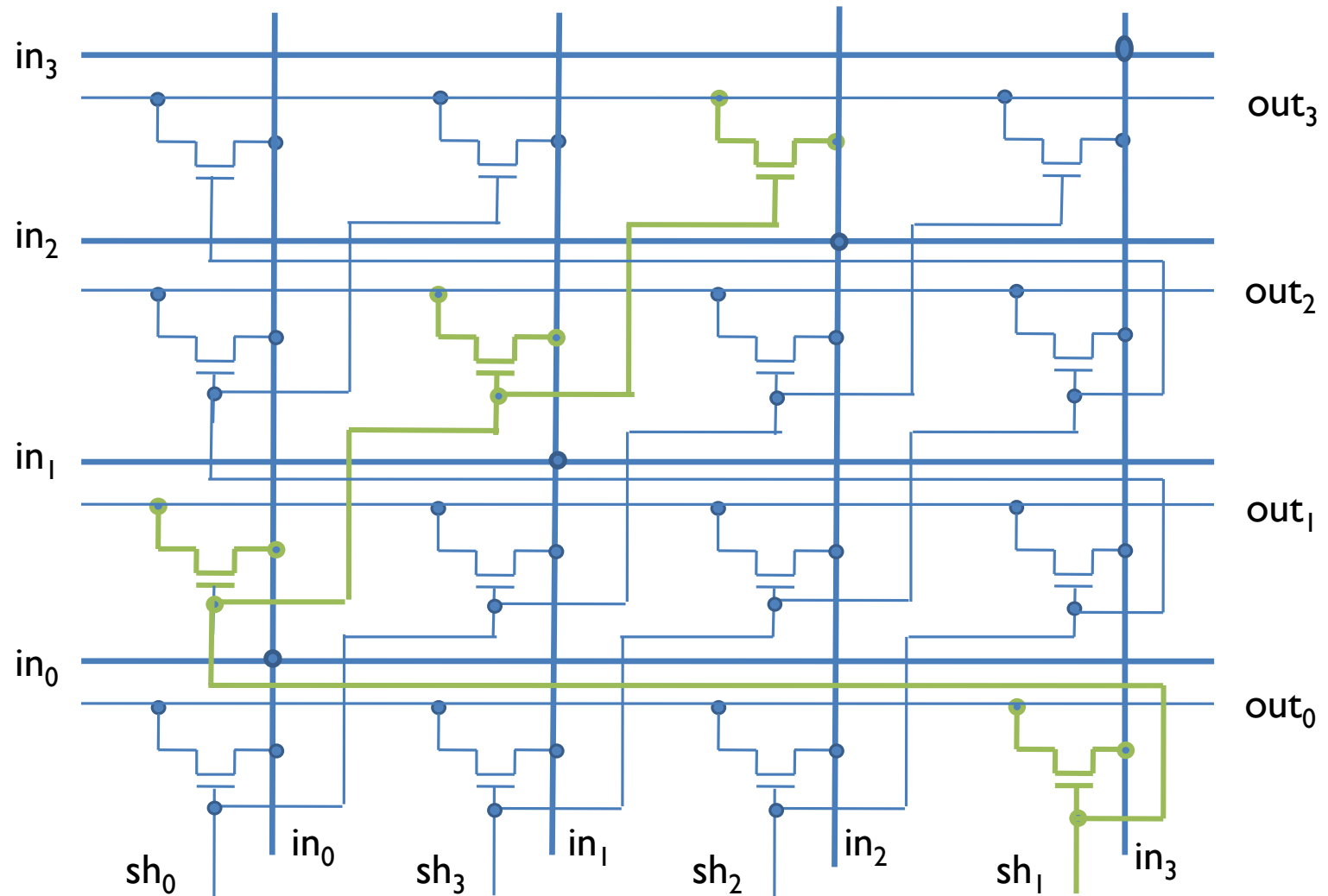


4x4 Barrel Shifter Stick Diagram

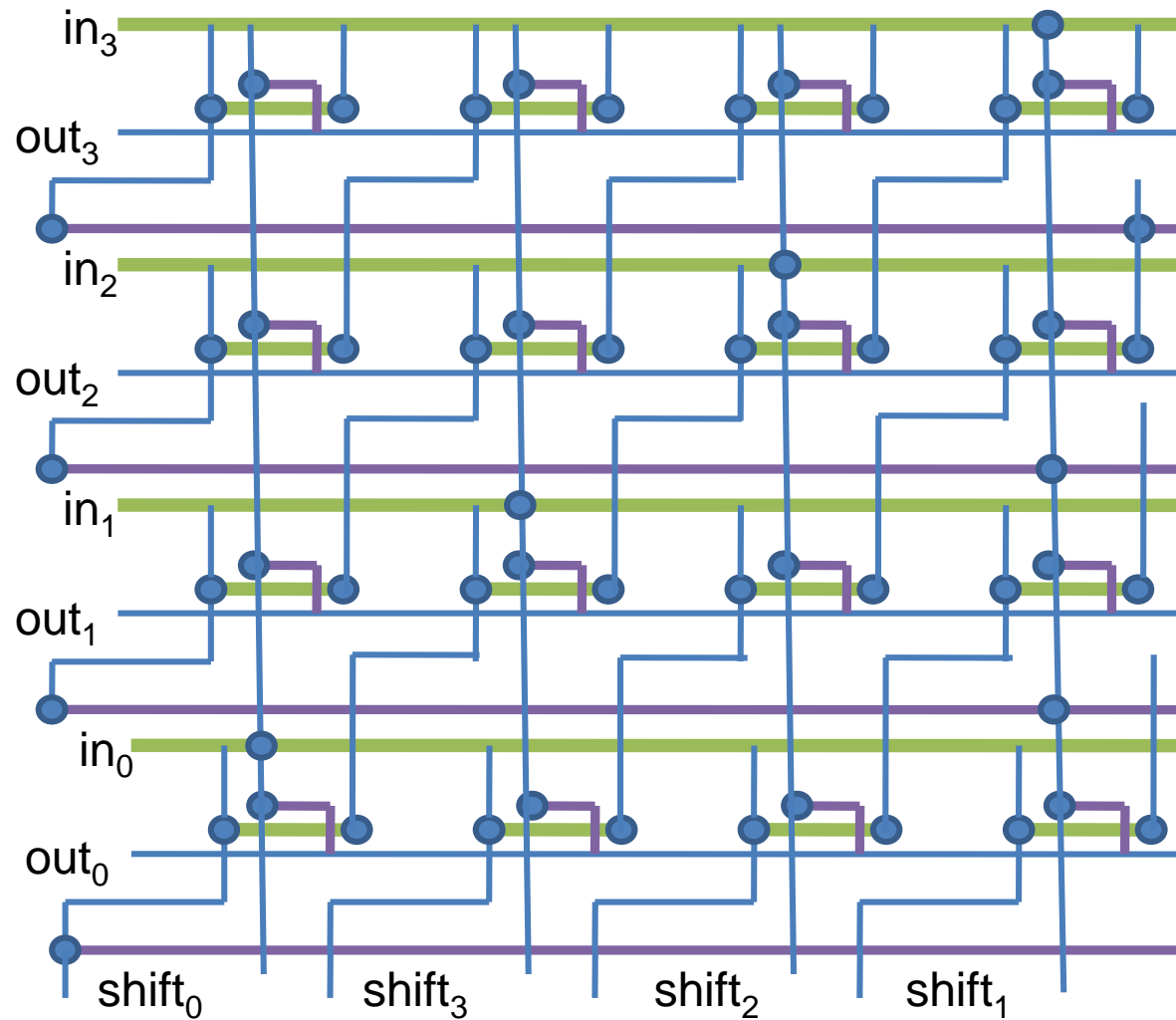

Applications

- Multiplication and Division
- Floating point arithmetic
- Alignment
- Microprocessor

Multiplexers (Data Selectors)

 

S_1	S_0	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$Z = I_0 \cdot \bar{S}_1 \cdot \bar{S}_0 + I_1 \cdot \bar{S}_1 \cdot S_0 + I_2 \cdot S_1 \cdot \bar{S}_0 + I_3 \cdot S_1 \cdot S_0$$

Fig: 4:1 MUX

Multiplexers...


 


Fig: 4:1 MUX using NMOS Pass Transistor

Multiplexers...

 

$$Z = I_0 \cdot \bar{S}_1 \cdot \bar{S}_0 + I_1 \cdot \bar{S}_1 \cdot S_0 + I_2 \cdot S_1 \cdot \bar{S}_0 + I_3 \cdot S_1 \cdot S_0$$

Fig: Stick diagram for 4:1 MUX using NMOS Pass Transistor

Multiplexers...

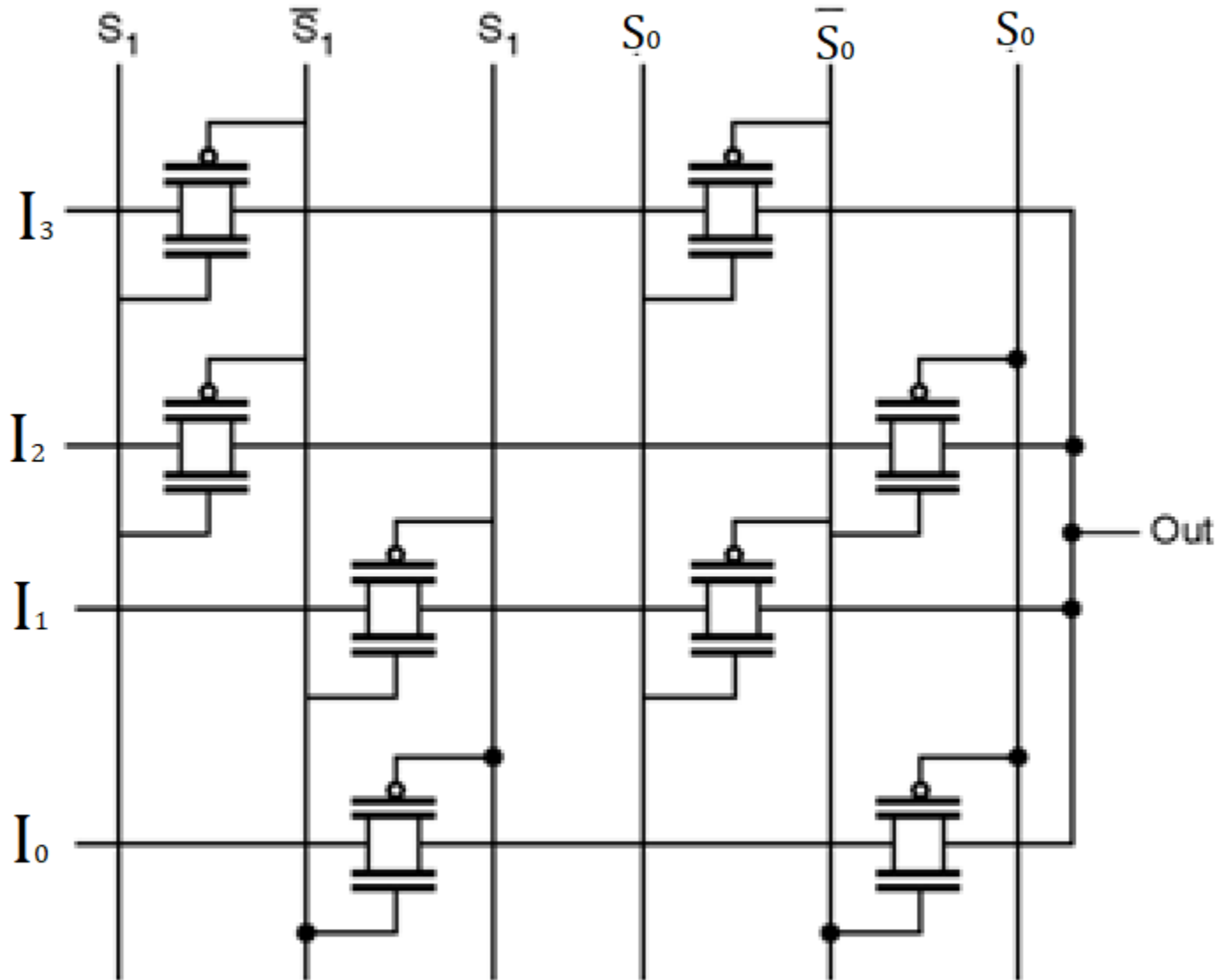


Fig: 4:1 MUX using CMOS Transmission/Pass Gate

Multiplexers...


 


Fig: Stick diagram for 4:1 MUX using CMOS Pass Gate

Parity Generator

 
- A circuit to be designed to indicate the **parity** of a binary number or word.



$$p = \begin{cases} 1 & \text{Even number of 1's at input} \\ 0 & \text{Odd number of 1's at input} \end{cases}$$

Fig: Parity Generator Basic Block Diagram

Parity Generator...

 

$A_i = 1$ parity is changed, $P_i = \bar{P}_{i-1}$
 $A_i = 0$ parity is unchanged, $P_i = P_{i-1}$

Fig: Parity Generator – Structured Design Approach

Parity Generator...

 


Fig: Parity Generator – Basic One Bit Cell

Parity Generator...

Truth Table of Parity Generator:


P_{i-1}	A	P_i
0	0	0
0	1	1
1	0	1
1	1	0

$$P_i = P'_{i-1} \cdot A_i + P_{i-1} \cdot A'_i$$

$$i.e. \quad P_i = P_{i-1} \oplus A$$

Parity Generator...

Parity Generator Circuit (CMOS):

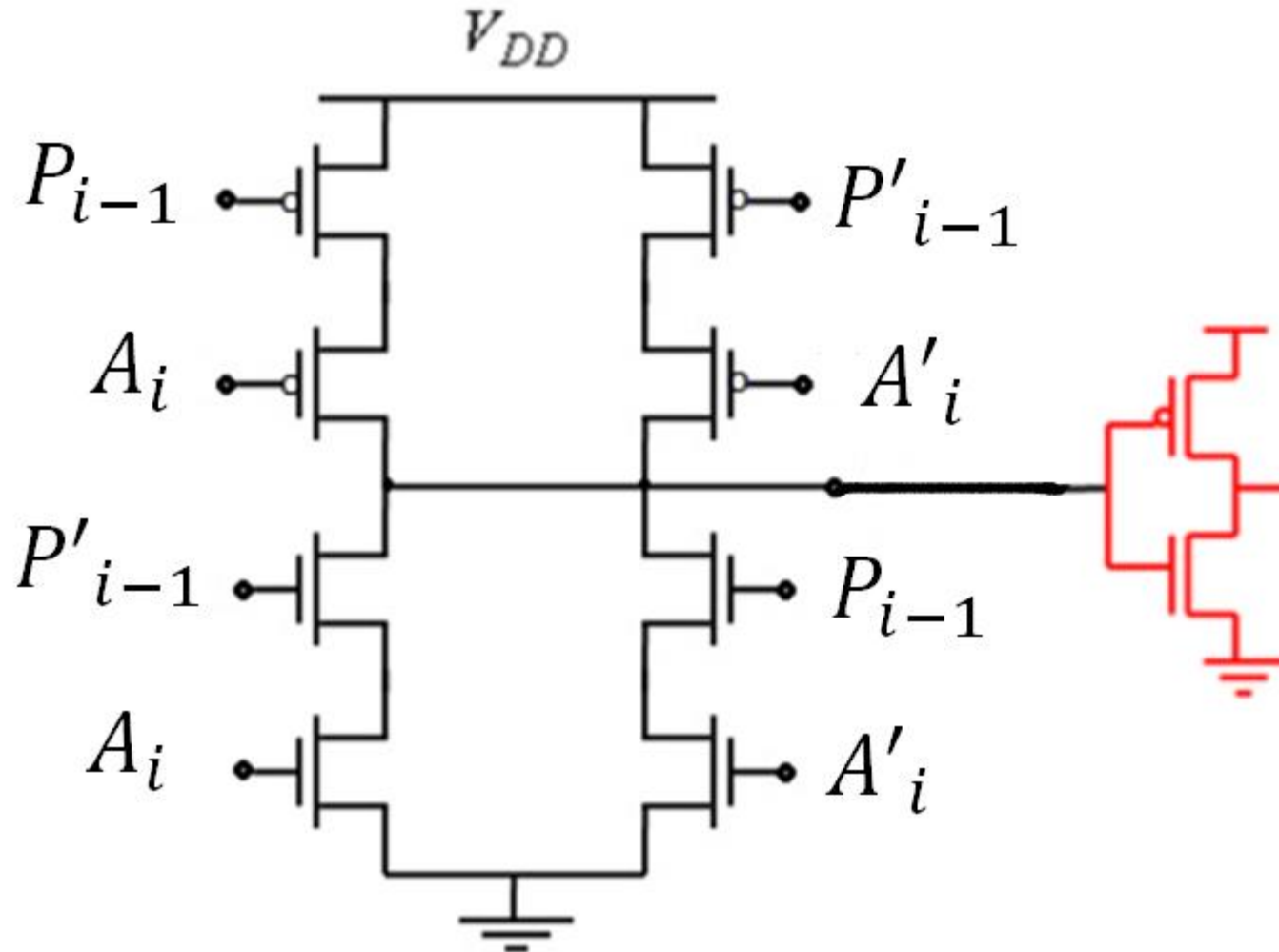

Parity Generator...

Parity Generator Stick Diagram (CMOS):

Try This Home

Acknowledgement

[1] http://bwrcs.eecs.berkeley.edu/Classes/ic541ca/ic541ca_f01/Notes/chapter6.pdf

[2] <https://slideplayer.com/slide/13382157/>

Thanks