

Electronic circuit - I

What is electronics ? what does it do?

Ans: Electronic circuit deals electronic devices.

& Electronic circuit deals with semiconductor devices.

→ It is the branch of Engineering that model the flow of electrons.

→ It is simply modeling the flow of electron and create conductivity in semiconductor devices in order to process signal.

→ The main object of electronics is to process signal.

→ Converter → from AC signal to D.C signal → Ex-changer.

→ Inverter → From D.C signal to AC signal.

→ Filtering → Signal processing job

→ Filtering converting signals.

How to process signals?

Signal \rightarrow A physical variables as a function of time.

Any physical variable when converted to time domain function is known as signal.

Signal \rightarrow i) Temperature signal

ii) Pressure signal \rightarrow cause \rightarrow airflow

iii) Voice signal

Electronic circuit process electrical signal.

$\xrightarrow{\text{Electronic device}}$

Transducer \rightarrow Voice signal \rightarrow electrical signal - এ পরিণত হয়ে,


Non-electrical signal \rightarrow electrical signal
পরিণত হবাত রক্ষে পুরো Transducer বলে।




Micro phone \rightarrow voice signal \rightarrow electrical signal - এ convert হয়ে,

Physical signal \rightarrow Transducer \rightarrow Electrical signal.

P.N junction diode

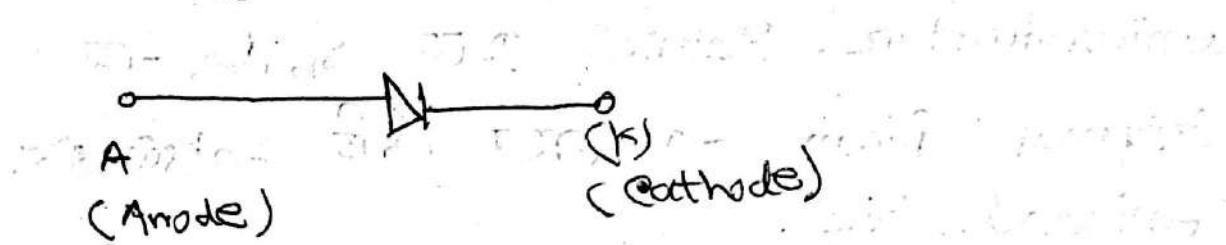

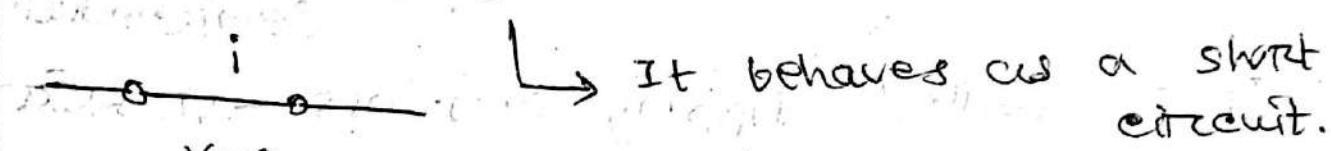When switch is on then we can assume it is a ideal diode.



When switch is off mode, $i=0$ But voltage $V \neq 0$,

so, it is open circuit.

Ideal diode or switch same form.

Semi-conductor \rightarrow Si, Ge, In, Ge

\hookrightarrow Valance electron \rightarrow 4 or 5


* perfect

\rightarrow Valance Electron \rightarrow Insulator.

\rightarrow Valance Electron \rightarrow 1 \rightarrow perfect conductor

Plenty of semi-conductors \rightarrow Si, Ge.

(iii) F.E.T → Field Effect Transistor

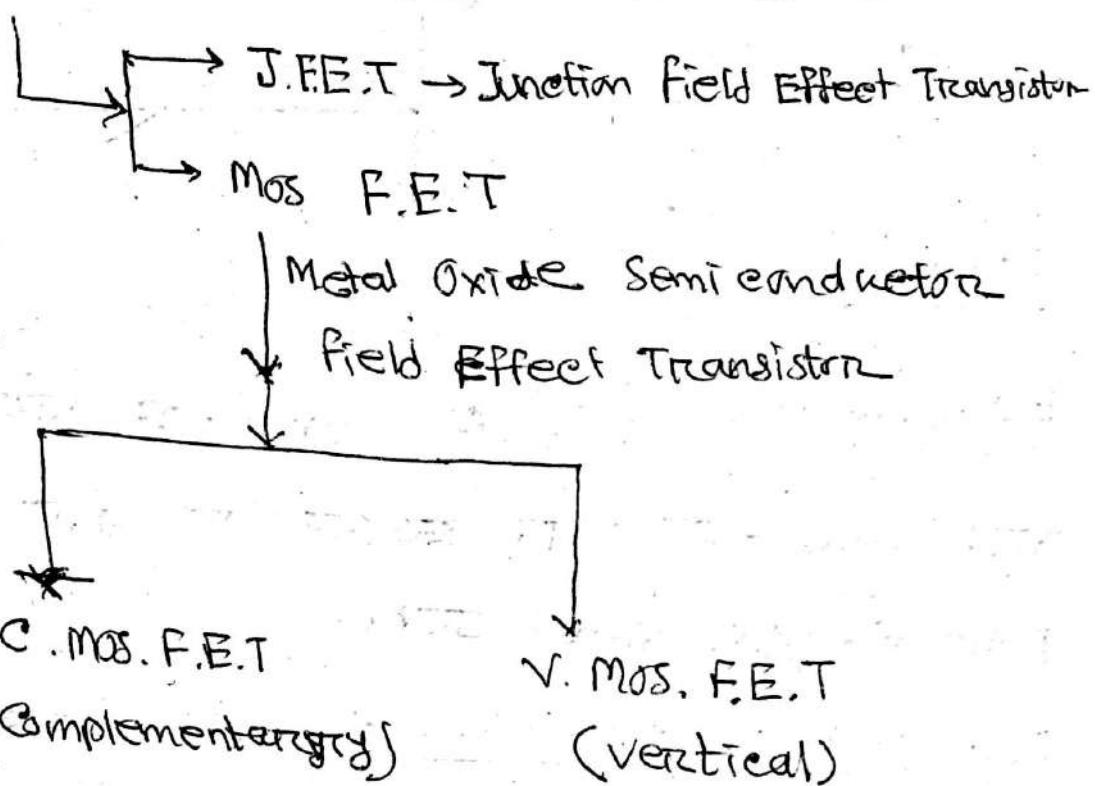



Diode: It is used as electronic switch.

Rectification (शक्तिप्रीकारक) क्षमता उपर नहीं।

* * Diode is a switching device.

→ It is a P.N junction.

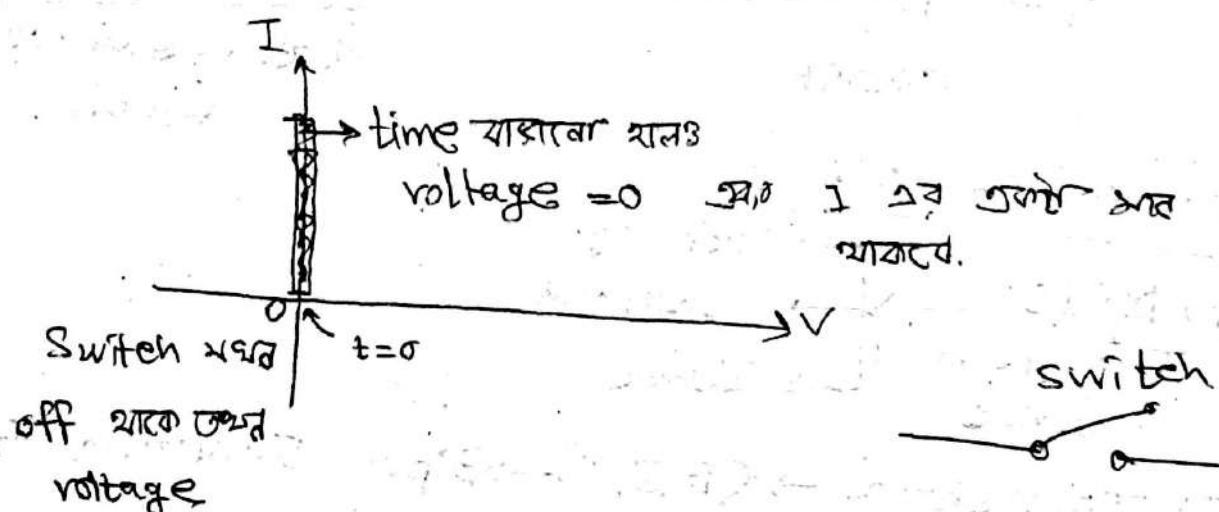

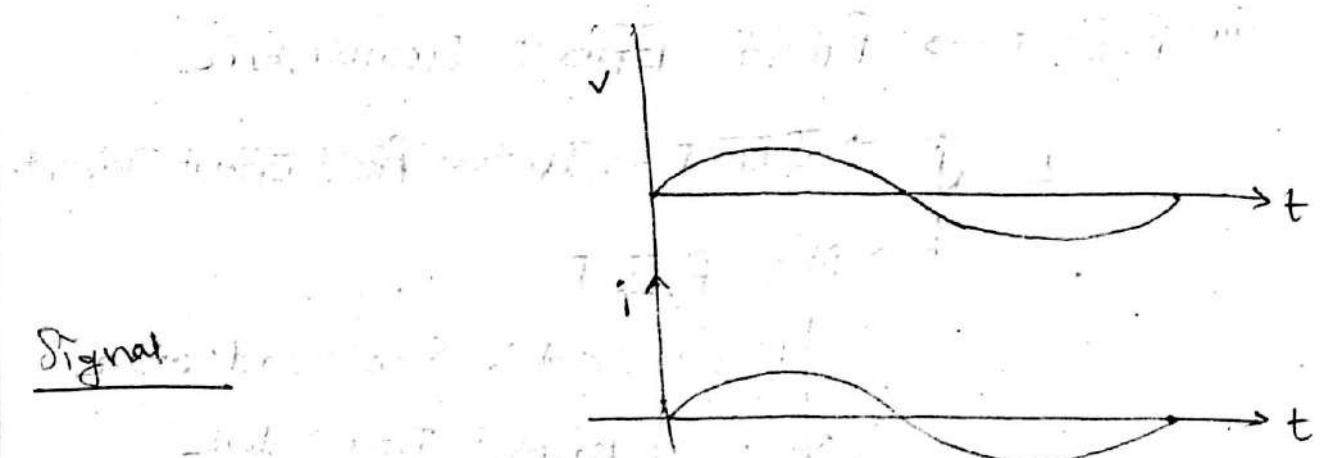


Deterministic signal ଅଧିକାରୀ ପାଇଁ


ମଧ୍ୟରେ wave - ତାଣେ ହୁଏ ରାଶି ଓ ଯେତା ମଧ୍ୟ ତାଣେ

Deterministic signal ତାଣେ

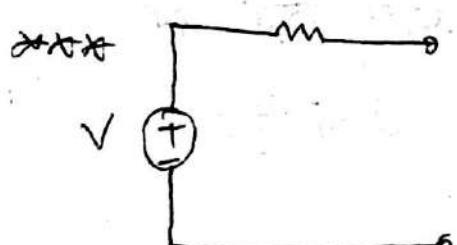Non-deterministic signal: → ମଧ୍ୟରେ wave ତାଣେ ହୁଏ ରାଶି ଓ ଯେତା ମଧ୍ୟ ତାଣେ ନାହିଁ non-deterministic signal



Thevenin-equivalent
circuit

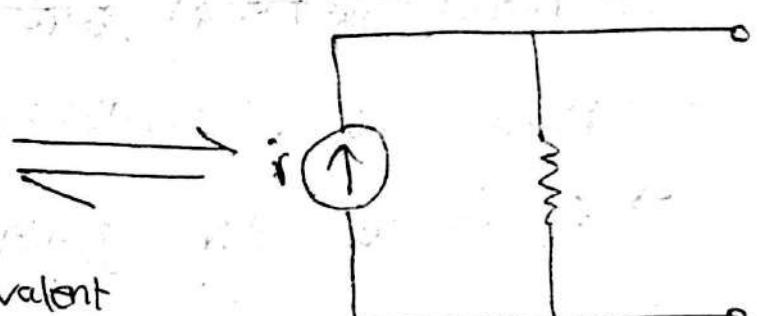

Norton-equivalent
circuit

Electronic devices:

(i) Diode → Ordinary
Two-terminal device
Schottky
Zener

(ii) Transistor → (B.J.T) → Bipolar Junction Transistor

Junction Transistor

Intrinsic Semiconductor: It is pure semiconductor. Nature (उत्तम सि, Ge - इन्ट्रिन्सिक) Original form - यहां पर्याप्त इन्ट्रिन्सिक Semiconductor.

Extrinsic Semiconductor:

Intrinsic (pure) + अत्यधिक (Vasuk) \rightarrow Extrinsic Semiconductor

It is called doping process - यहां मात्रा से अत्यधिक Semiconductor - यह conductivity बढ़ाव देता है।

17-04-2013 (A day \rightarrow 2nd) **Lecture - 2**

Extrinsic Semiconductor 2 types

(i) P type

Intrinsic + Trivalent atom

Si/Ge + Al \rightarrow space टॉप्पि करते
hole टॉप्पि करते

Minority carries
 \rightarrow electrons

majority carries \rightarrow holes.

Acceptor atom
Al \rightarrow acceptor (hole)

(ii) N type

Intrinsic + Pentavalent atom

Si/Ge + As
free electron - रोटि बाटे

Majority carries electrons

Minority carries holes,

Donor atom
As \rightarrow donor.


- Semiconductor → E_{F} conduction - σ electron and hole current পরিমাণ ক্ষয়,
- Conductor → E_{F} conduction - σ only electron current পরিমাণ ক্ষয়,
- Depletion region → Insulator
- Barrier potential → or junction or threshold potential.
- Reverse Bias → Source (-) এবং N
Source (+) এবং P
ডানে depletion region
হলে হাতে → current flow
করা।
- Forward bias → (-) এবং N এবং
(+) এবং P ডানে
depletion region কাম হাতে,
current flow হবে,
- Si $\rightarrow 1.1 \text{ V}$
Ge $\rightarrow 0.75 \text{ V}$ } for semiconductor :
- Transition process → electron থেকে valence
or conduction band - σ
কাম → exciting process

- Recombination → Electron ~~and~~ conduction
band out of valence Band
- P.N junctions diode 3 types of bias.

(i) No load \rightarrow no current flow,

(ii) Reverse bias \rightarrow Reverse saturation current (I_s)
ideally zero current $I = 0$,

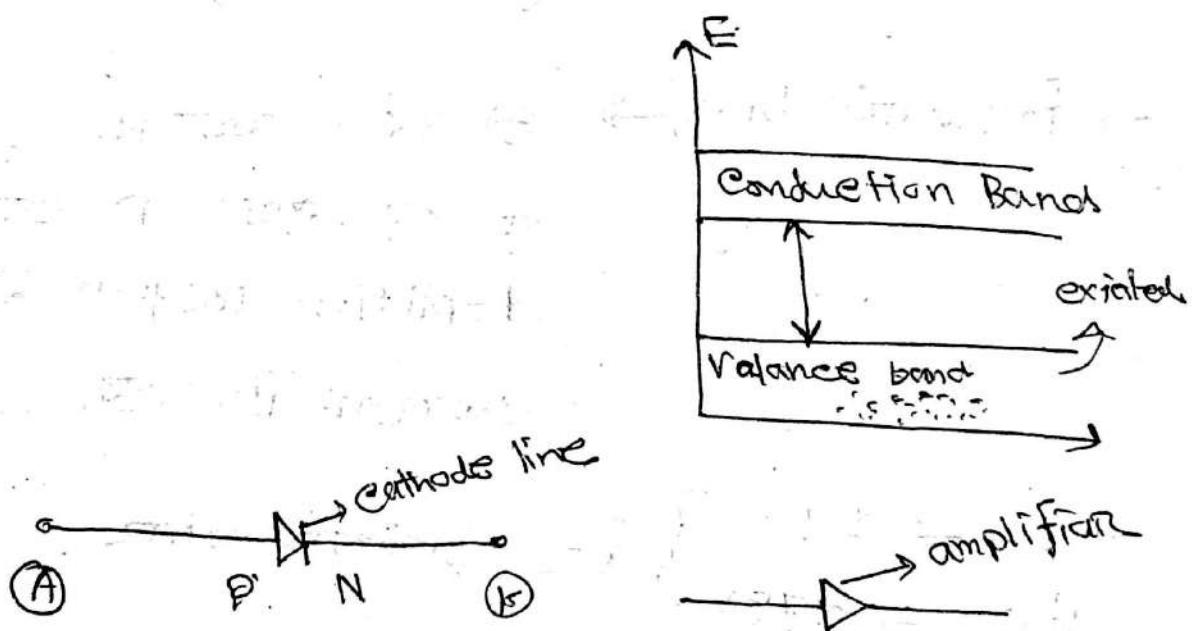(ii) Forward bias \rightarrow forward current
majority and minority current both enter.




ON 23rd condition $\rightarrow V_A > V_{IS}$ [Because forward bias]

$$\text{off } u \rightarrow v_A < v_F$$

$V_A = V_F$ & $\Delta \omega$ No bias.



Ge - diode:

Page 17

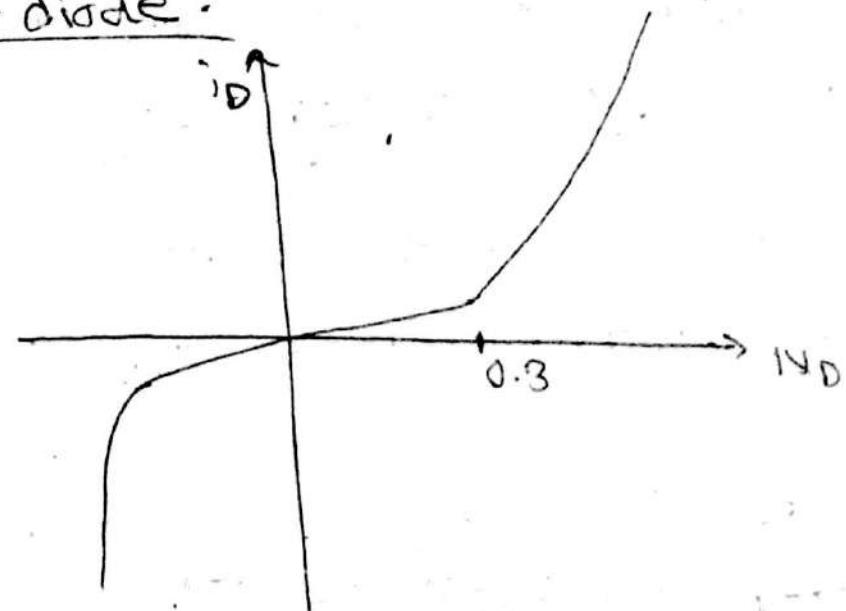

Si - diode:

18

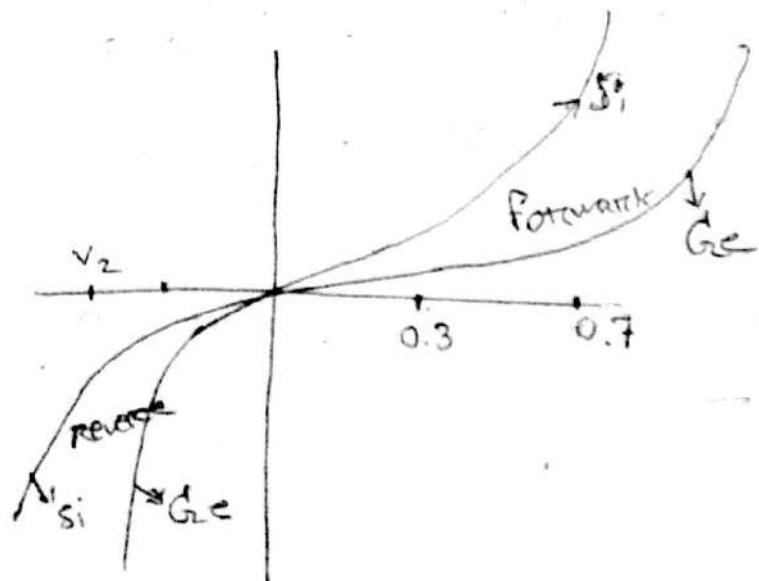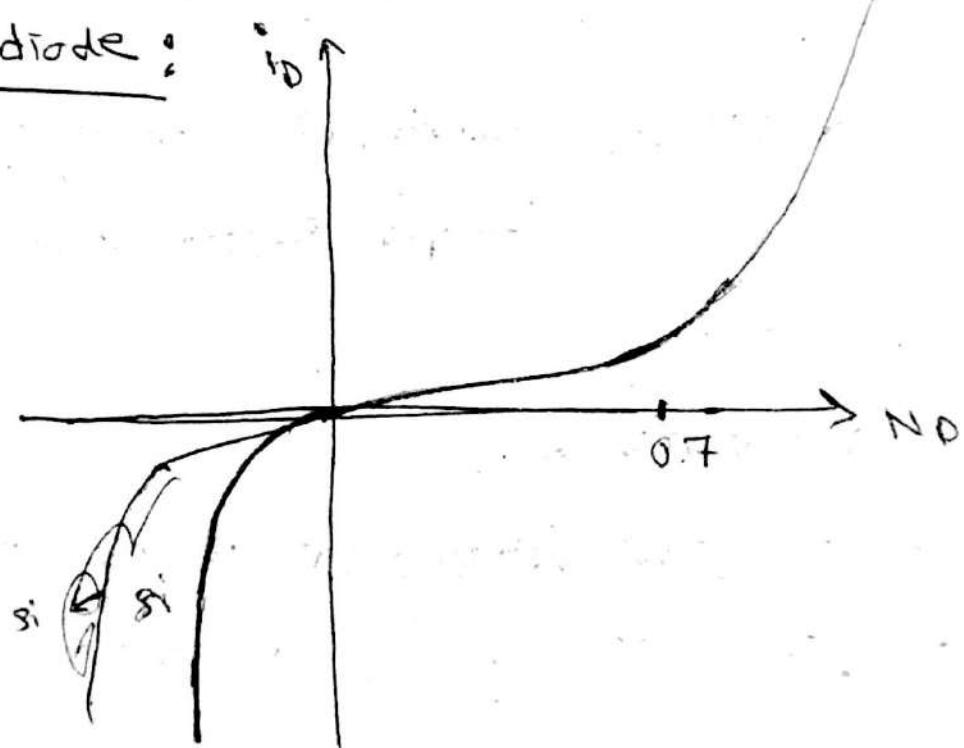

Today

→ Diode equation: $V_T \rightarrow$ thermal voltage.

$$I_D = I_S$$

↓

Diode current


$$(TR-1) I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

saturation current
reverse bias current

$k \rightarrow$ Boltzmann constant

$V_D \rightarrow$ Diode \rightarrow across \rightarrow voltage.

$T \rightarrow$ kelvin temperature.

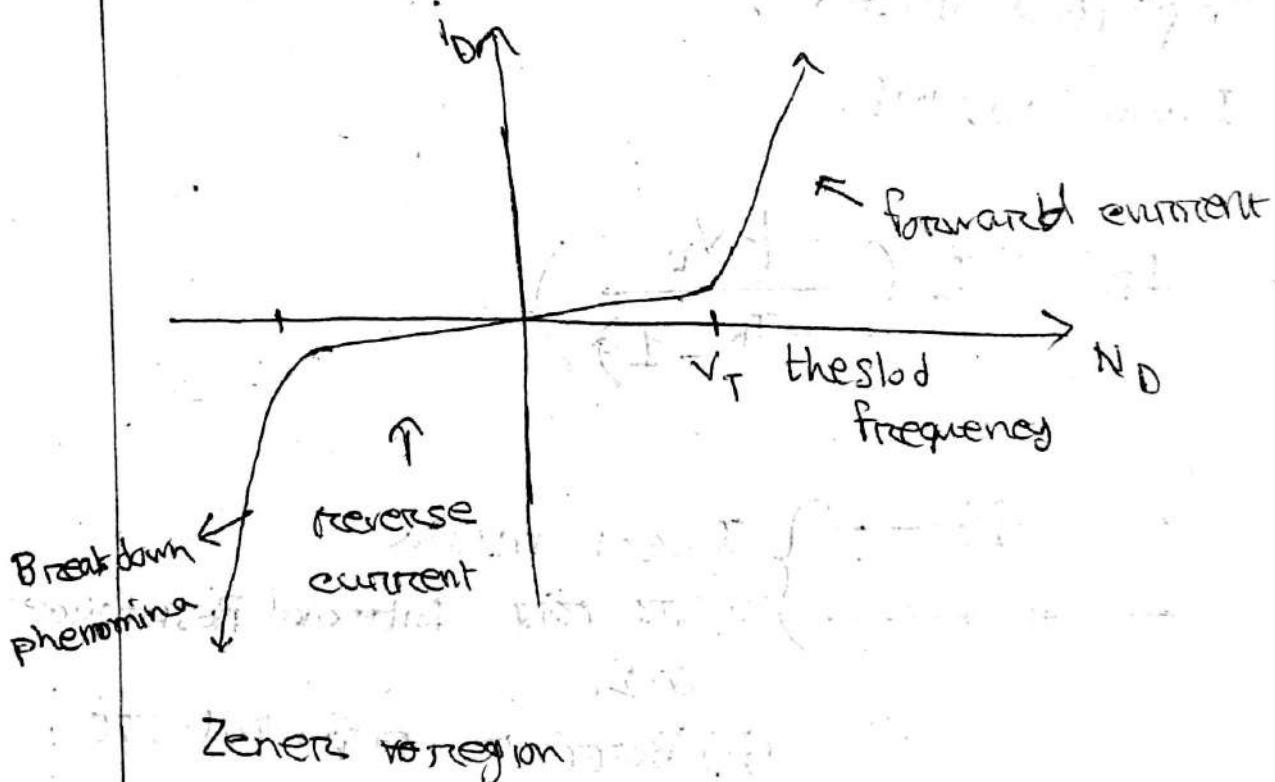

Diode \rightarrow Zinear characteristic

→ practical characteristic.

Ge diode at $V_T = 0.3$

and Si " " " $V_T = 0.7$

→ knee potential

3V

2V

3 > 2, current flow यहाँ

2V

3V


2 < 3, current flow यहाँ नहीं

Diode models:


- (1) Linear model
- (2) Simplified model
- (3) Ideal model.

$$\rightarrow I_D = I_s \left(\frac{kV_D}{e^{TR} - 1} \right)$$

(3)

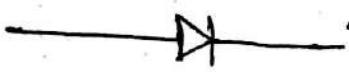

Ideal model

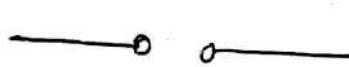

(i) प्राक्तिक Internal Resistance वाला

(ii) Barrier potential वाला


(1)



→ Simplified model.

→ barrier potential

(2) (3)

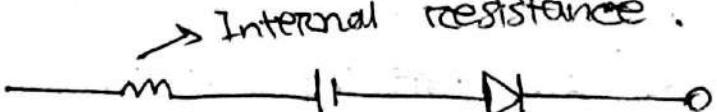

→ Internal resistance.

→ Practical diode

In ~~the~~ we
নামের প্রেরণা prefer to Si-diode in
comparison to Ge-diode. \rightarrow (CT and final)

\rightarrow নামের Si-diode -এর reverse current
নামের reverse voltage একটি হয়।

$$R_T = R_0 (1 - \alpha t)$$

Heat বায়নে conductivity ঘোড়ে।

Books: \rightarrow Micro electronic circuit

\rightarrow By Sedra and Smith.

Linear মানে মান্তব্য \rightarrow

input - এ কোন কোম �voltage or current দ্বারা

output - এ কোন কোম voltage or current দ্বারা,

মানে : মান

$$V = V_m \sin \omega t \quad \text{voltage supply curve}$$

মানে output এর voltage

Non-linear - এ input ও output আলাদা

মান

Power Supply Unit (PSU)


power converters → convert AC into DC
convert

IPS → Instant power supply

converter ↔ Inverter

Battery → capacitive field
Acid water plate.


Types of dry cell.

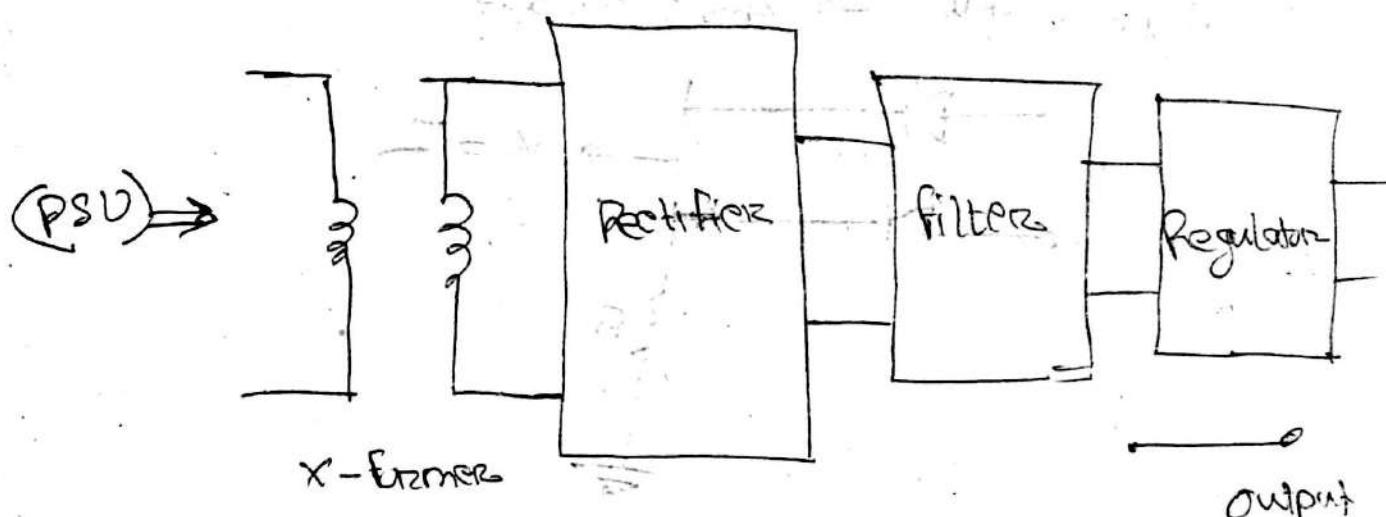

Transformer → 220 V AC step down করে।

Rectifier → Unit by direction করে।


Filter → Filter circuit-এর

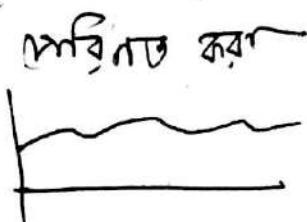

(ripple of AC)

220V প্রেক্ষ
220 volt - I
step down
transformer
যাতে প্রিমা নাম,

Regulator \rightarrow

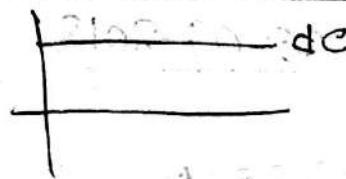

\rightarrow Output - \downarrow constant voltage ফর্ম,

PSU - পোর্টেবল \rightarrow Assignment.




OR - Gate

Input

(1) কান্দা output High গুলি output High হয়।

High input \rightarrow +ve voltage


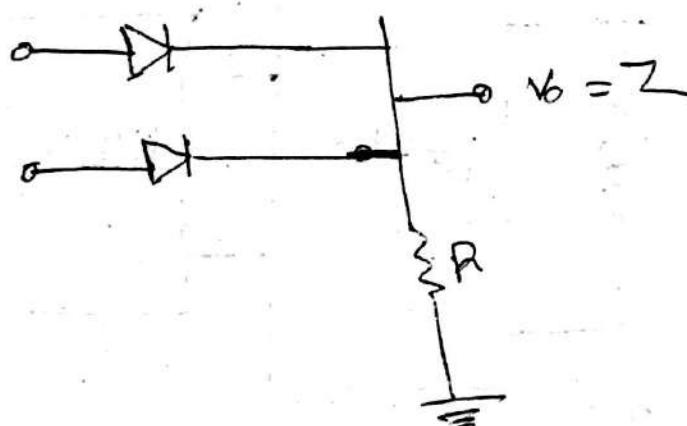


Logic \rightarrow 1 \rightarrow positive voltage (switch on)

0 \rightarrow switch off (open)

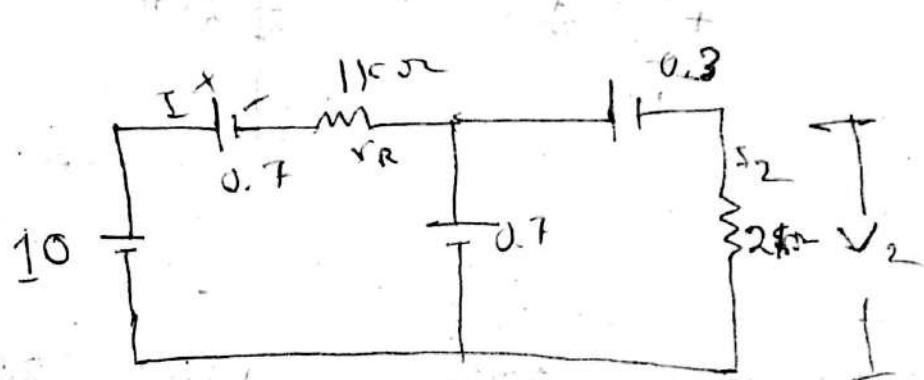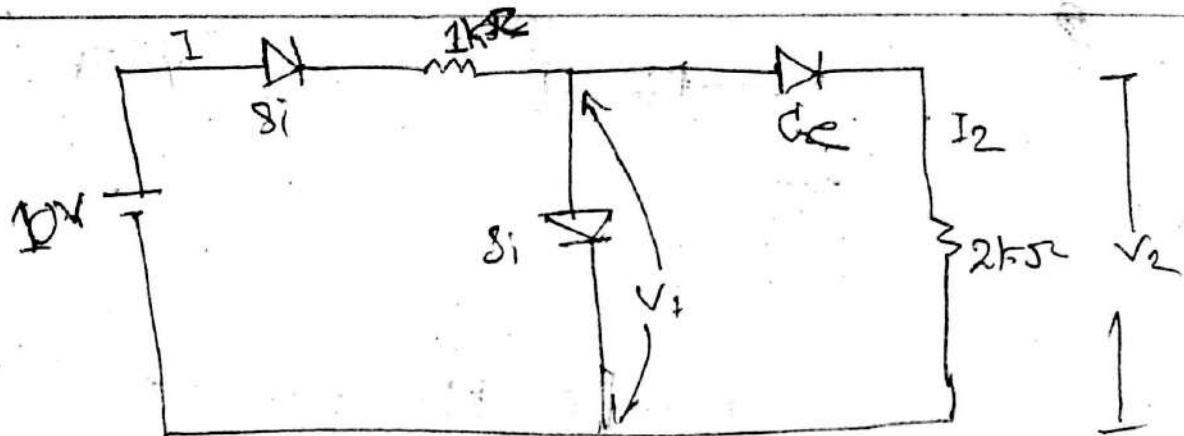parallel - circuit - \downarrow voltage
game





$$10 + 0.7 + V_R + 0.7 = 0$$


$$V_R = 9.3 - 0.7 = 8.6$$

$$I_1 = \frac{V_R}{1k\Omega} = 8.6 \text{ mA}$$


$$-0.7 + 0.3 + V_2 = 0$$

$$\Rightarrow V_2 = 0.9 \text{ V}$$
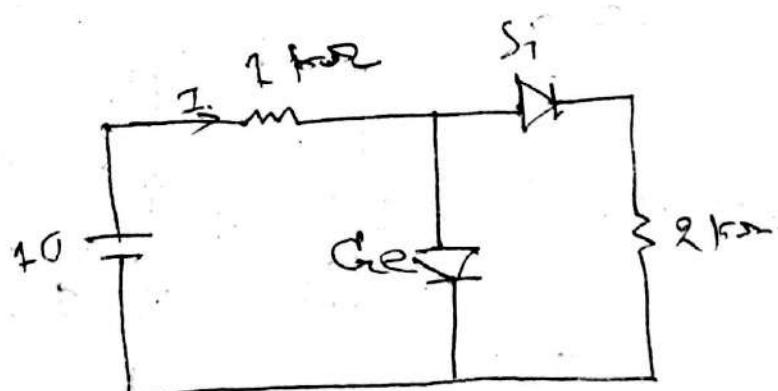
$$\Rightarrow I_2 = \frac{0.9 \text{ V}}{2k\Omega} = 0.2 \text{ mA}$$



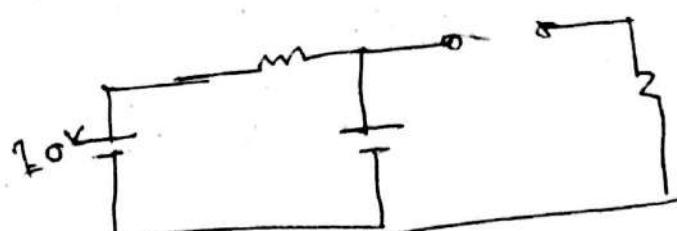Si - Ge
parallelled
at Ge
on Si
Ge threshold
potential
is 0.3V.



$$V = (10 - 0.3) = 9.7 \text{ V.}$$

$$I = \frac{9.7}{1k\Omega}$$

Not - Gate: single input & single output.

Input high & output low and vice - versa



$$X \rightarrow Z = \overline{X}$$

X	Z
0	1
1	0

Home work

Not - Gate

design করো ২৩৬

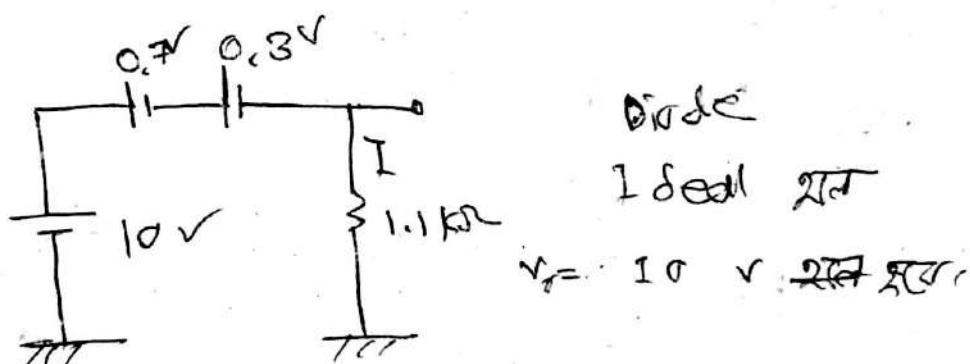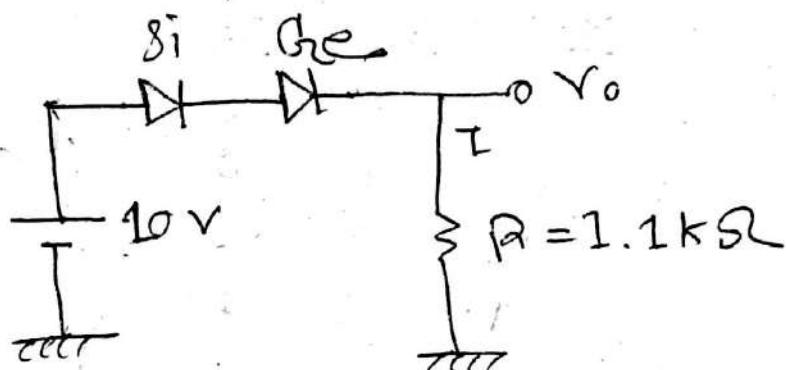


$$-10 + 0.7 + 0.3 + V_o = 0$$





$$\Rightarrow V_o = 9V$$

$$V_o = 9V$$
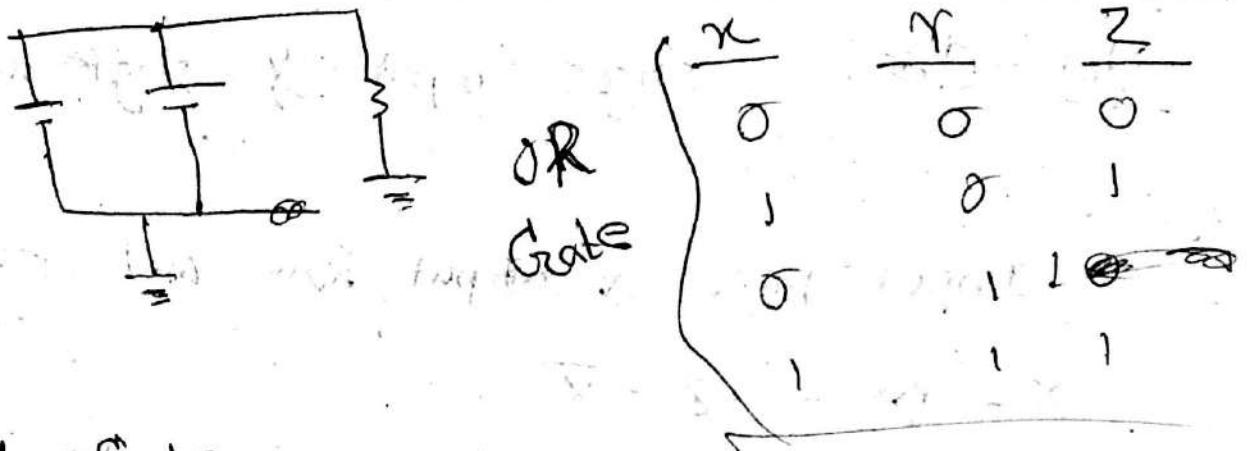
$$I = \frac{V}{R} = \frac{9V}{1.1k\Omega} = 8.182 \text{ mA}$$





And Gate

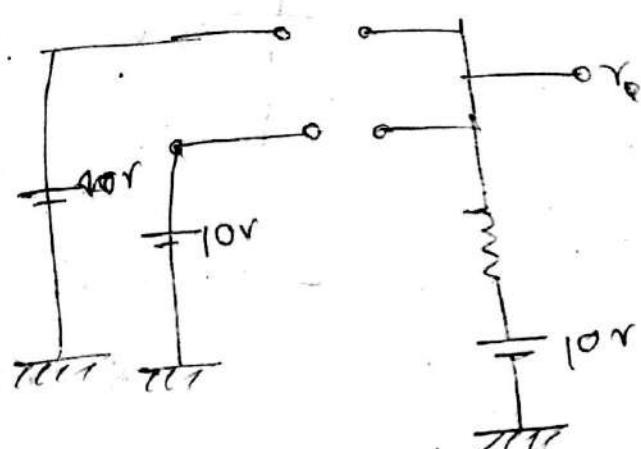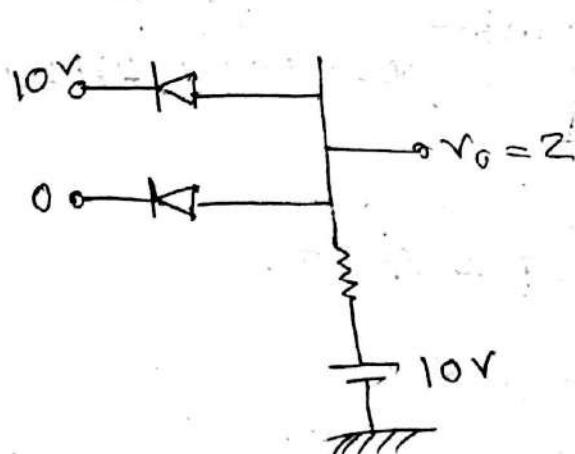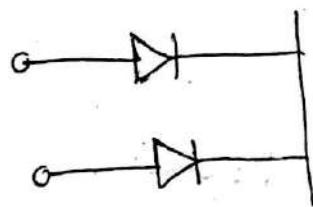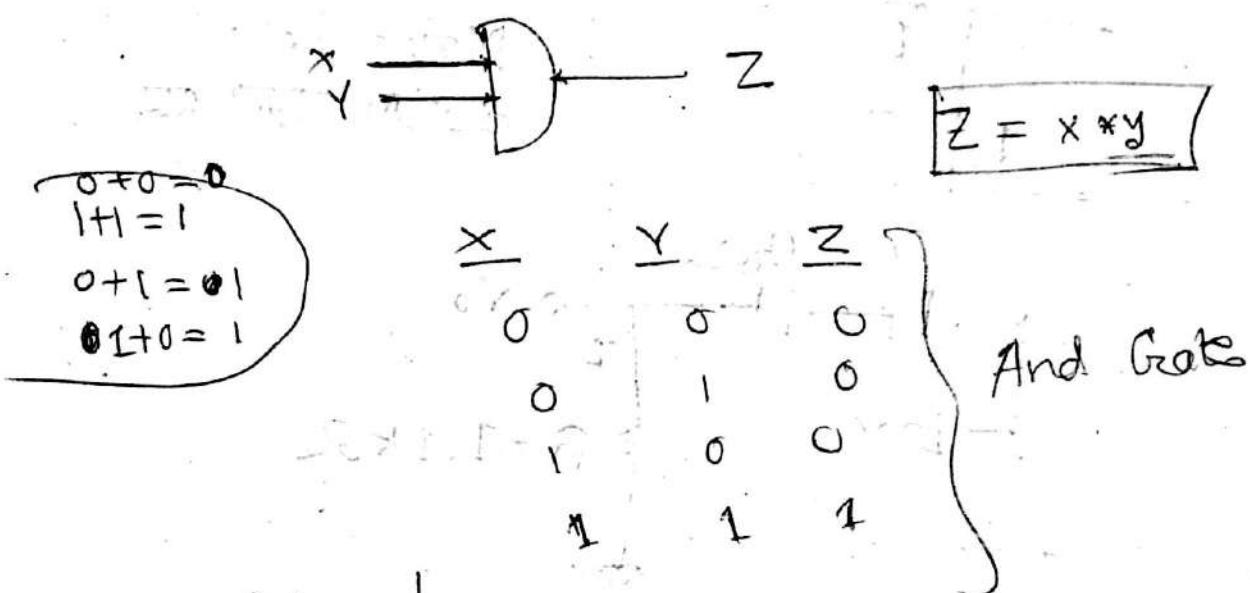

$$I = \frac{V}{R} = IR$$

$$V = IR$$

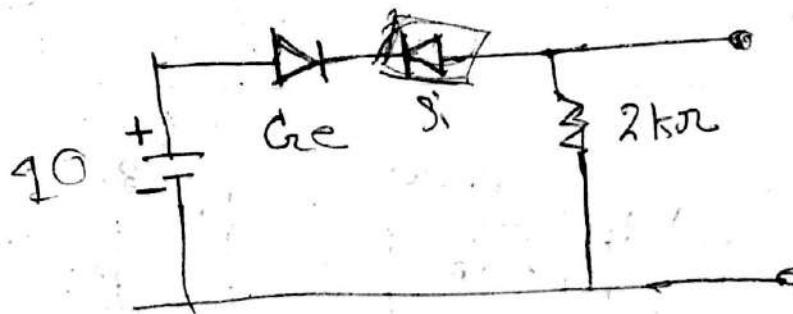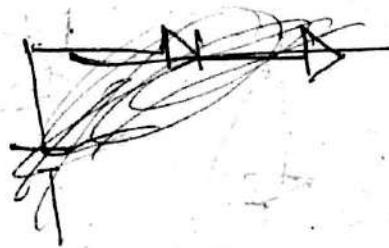


EEE-211 (SMR)

(3rd cycle A day)


30-09-2013

Lecture - 5

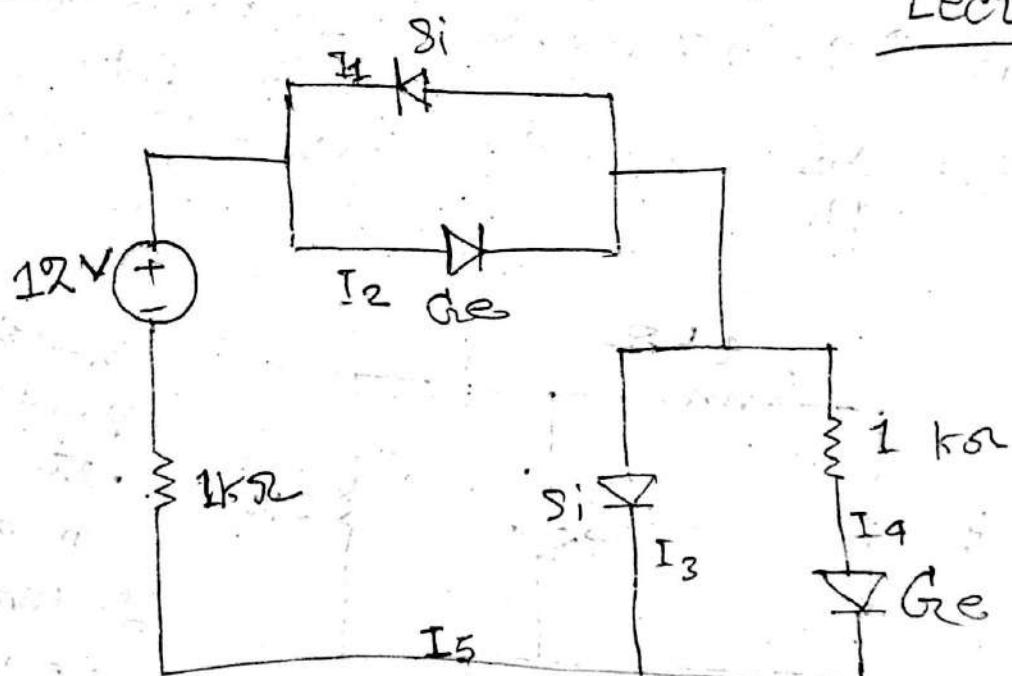

$$-0.7 + V_o + 10 = 0$$

$$\Rightarrow V_o = 9.3$$

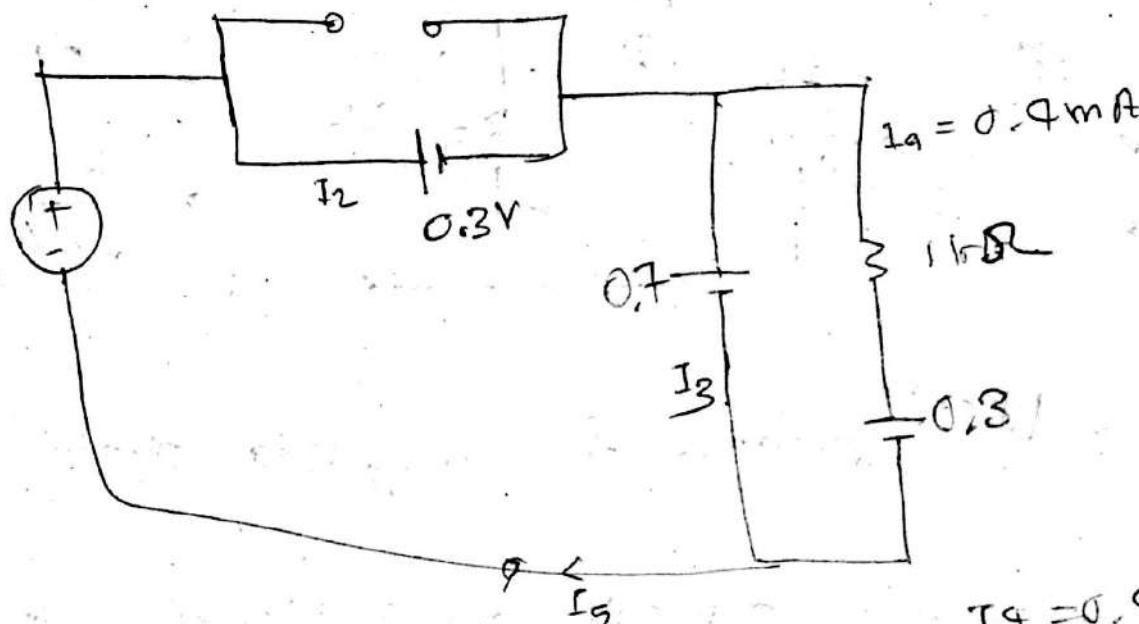

$$I_S = \frac{12 - 0.3}{1k\Omega} - 0.7$$

= 11 mA


$$I_3 = \frac{11 - 0.4}{1k\Omega}$$

= 10.6 mA


$$I_2 = 10.6 \text{ mA}$$

$$I_A = 11 \text{ mA}$$

Rectification:

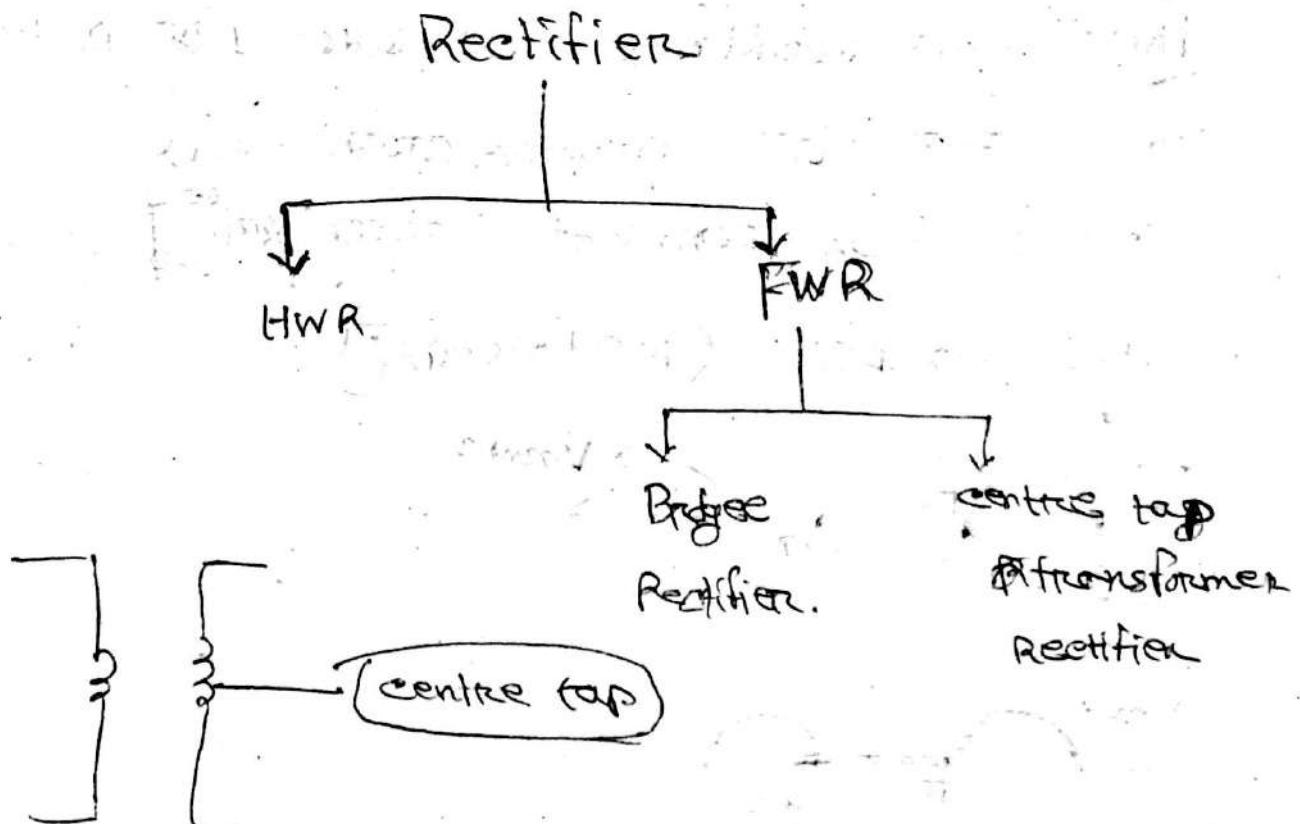


$$V_2 = V_m \sin \omega t$$

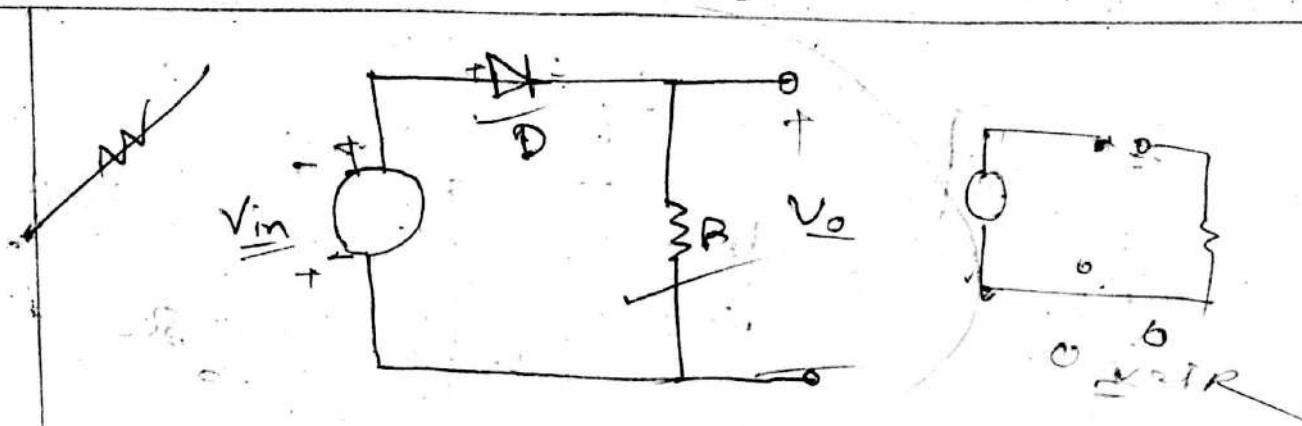


Rectification
process of ~~negative~~ cycle.

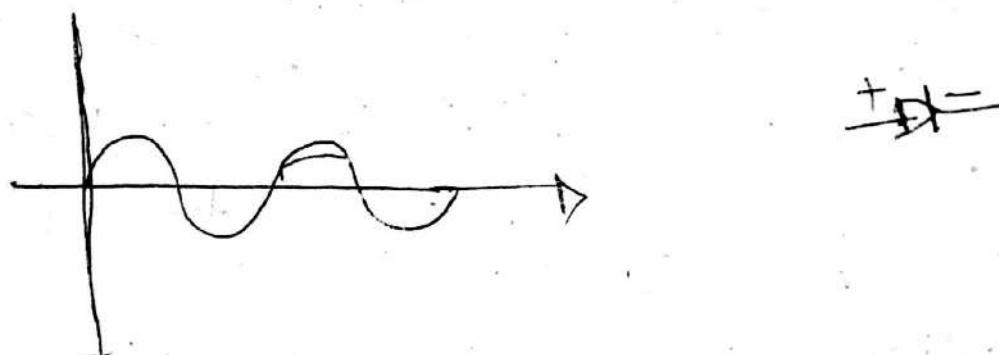Alternating current \rightarrow Unidirectional current.




Half wave rectifier - $\frac{1}{2}$ अंतर्वाले 1 Diode
3 फैफ और resistor लगाए, and
series - $\frac{1}{2}$ connect - दोबारा लगाए,

AC \rightarrow DC (rectification)

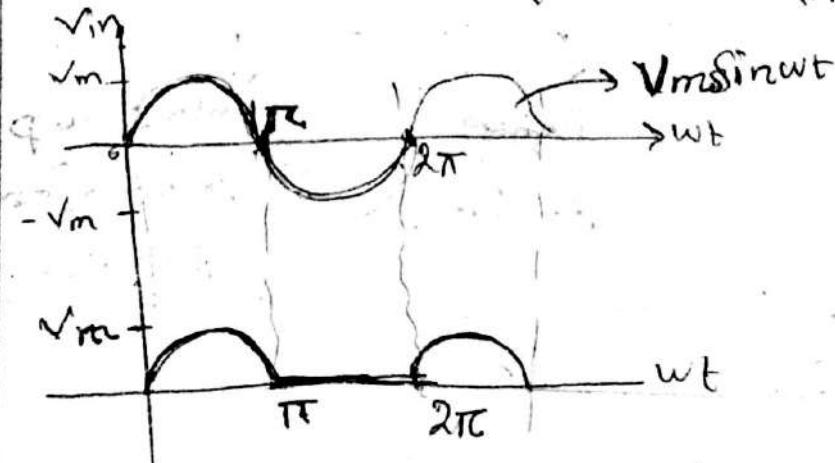

FWR

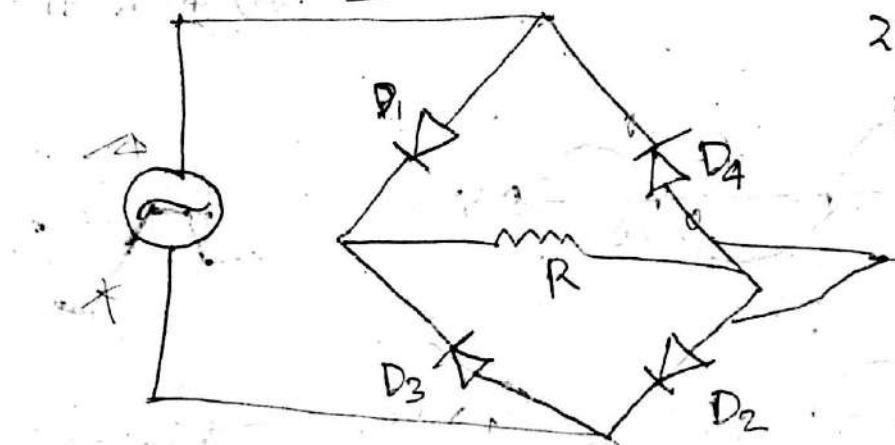




2nd फॉलोवर विस्तृत
Diode एवं इनके

anode एवं धूत
cathode एवं धृत





(3rd cycle c Day)

05-05-2013
Lecture - 6

full wave rectifier:

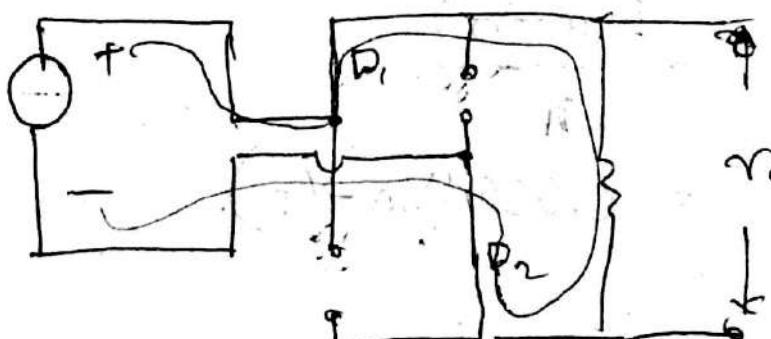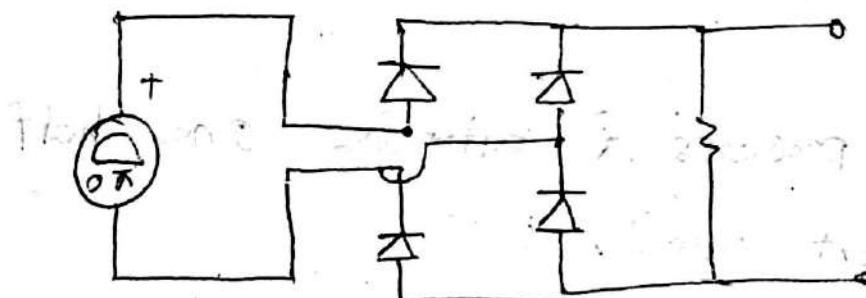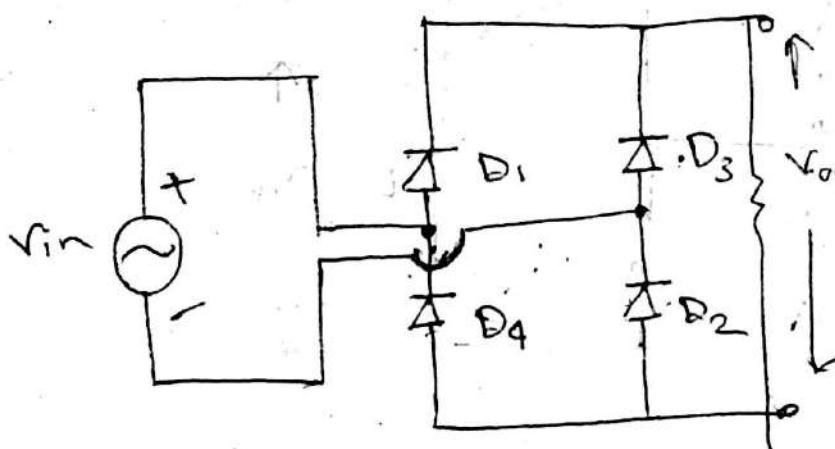

$$V_o = V_{in}$$

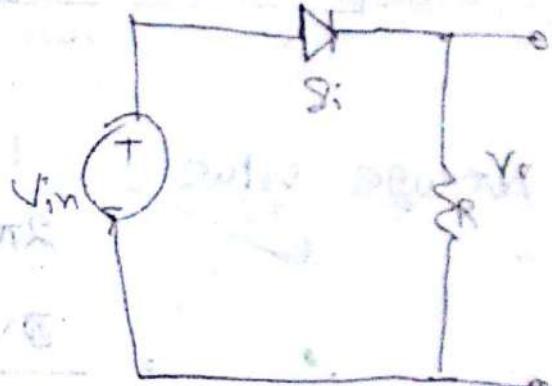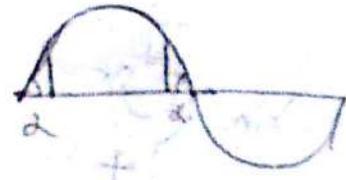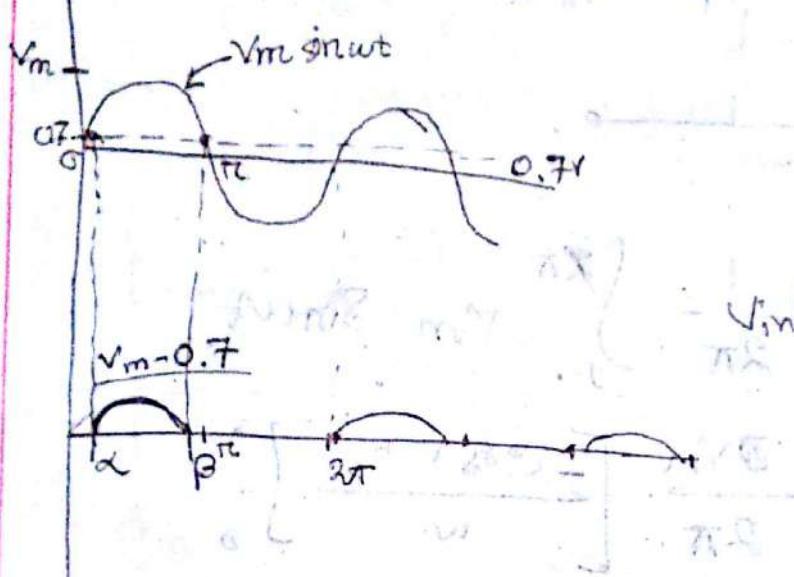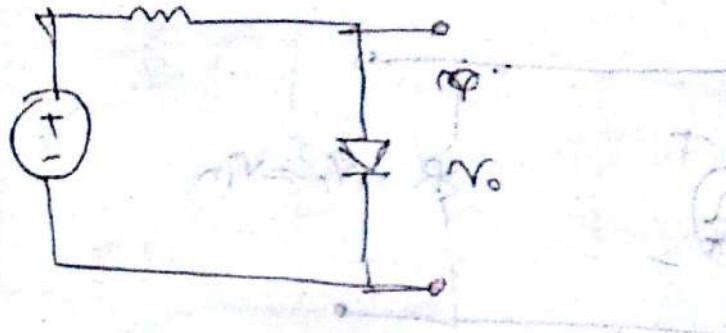

$$V_0 = V_m - V_T$$

$$\beta = \pi - \alpha$$

$$\alpha = \sin^{-1} \left(\frac{V_T}{V_m} \right)$$

$$V_m = V_m \sin \omega t$$

$$\Rightarrow V_T = V_m \sin \alpha$$



$$\Rightarrow \alpha = \sin^{-1} \left(\frac{V_T}{V_m} \right)$$

$$① V_m = V_m \sin \omega t$$

$$\Rightarrow V_T = V_m \sin \alpha$$

$$\Rightarrow \alpha = \sin^{-1} \left(\frac{V_T}{V_m} \right)$$

$$[\alpha = \omega t]$$

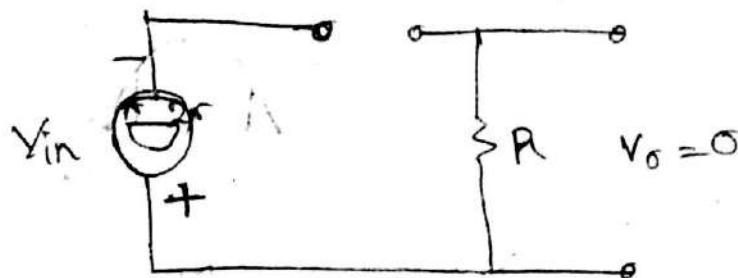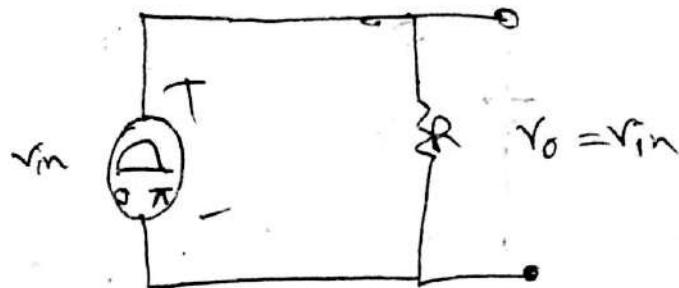


Average value $= \frac{1}{2\pi} \int_0^{\pi} V_m \sin wt dt$

$$= \frac{V_m}{2\pi} \left[\frac{-\cos wt}{w} \right]_0^\pi$$




$$\Rightarrow \frac{V_m}{2\pi} [+1 + 1]$$

$$= \frac{V_m}{\pi} = 0.318 V_m$$

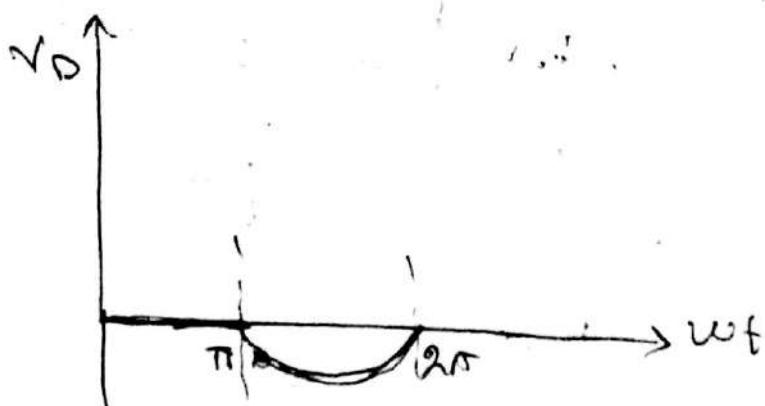

Supply voltage $\rightarrow V_i = V_o + V_D$

π

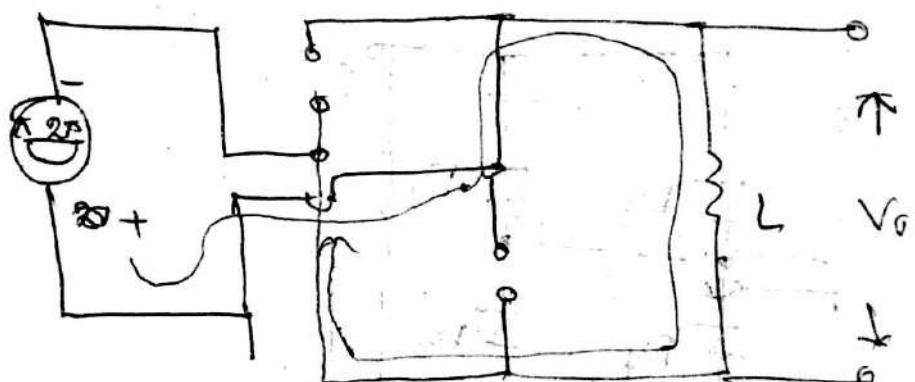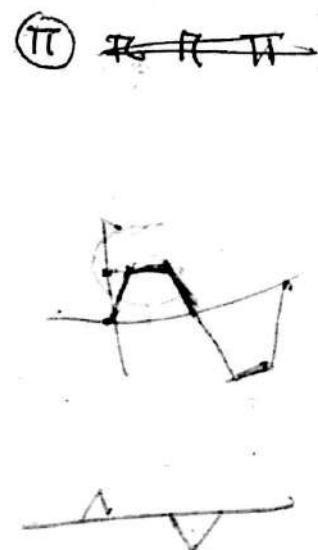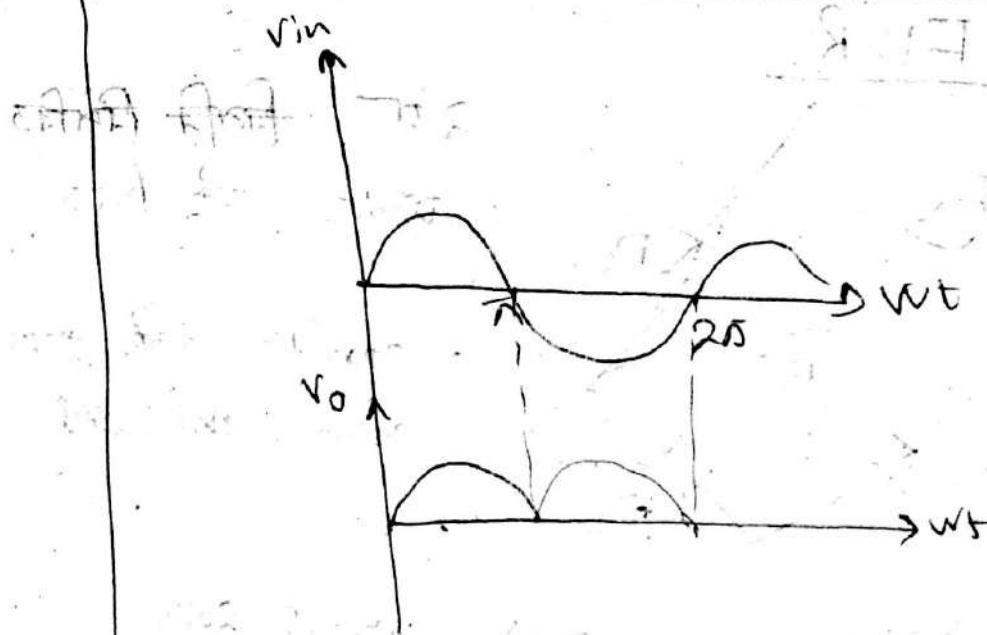

$$V_o = V_{in}$$

This is the process of altering one half of the input signal.

$$\begin{aligned} V_{dc} &= \frac{2V_m}{\pi} = \frac{2(V_m - V_T)}{\pi} \\ &= 0.636(V_m - V_T) \end{aligned}$$


$PIV \rightarrow P$ Inverse voltage

$PRV \rightarrow "$ Reverse " \rightarrow Reverse diode bias across - at maximum voltage

Half wave: $PIV \geq v_m$

Full wave: $PIV \geq v_m$

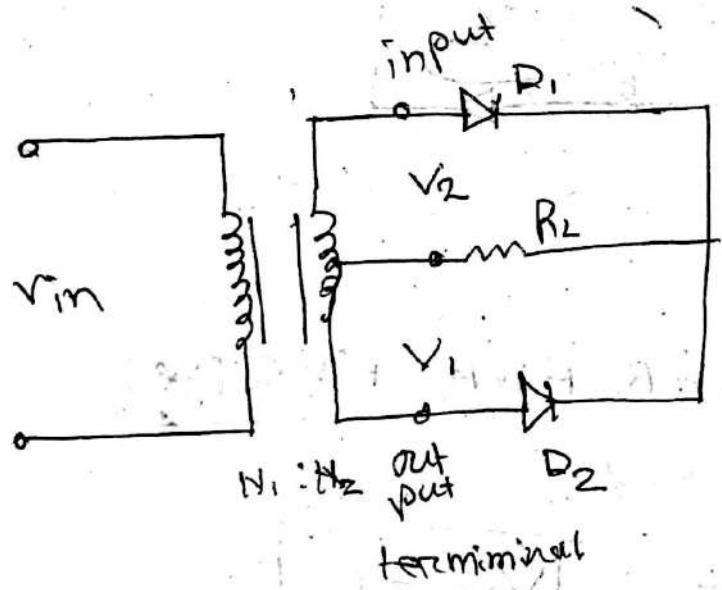
FWCTR \rightarrow Full wave centre tab rectifier:





centre Tab use
केंद्रीय ताब से
full wave -
पूर्ण वेव द्वारा
diode
प्राप्त होता.

input voltage $<$ output voltage. [step up] [1:2]

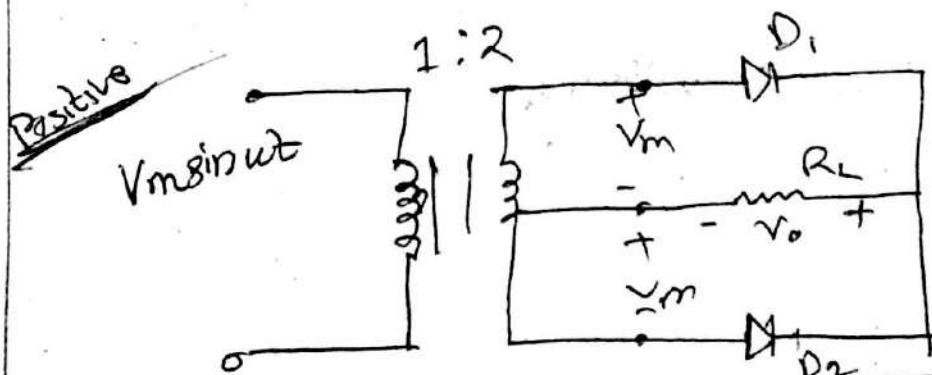input voltage $>$ output voltage [step down] [2:1]



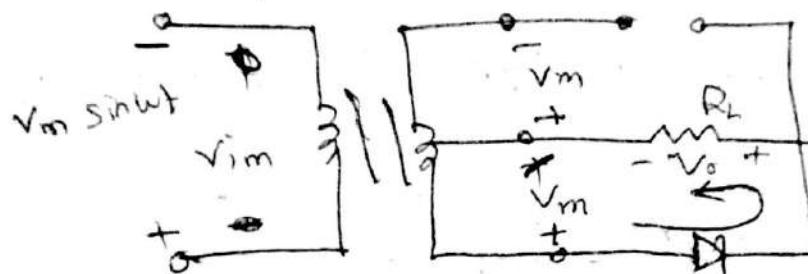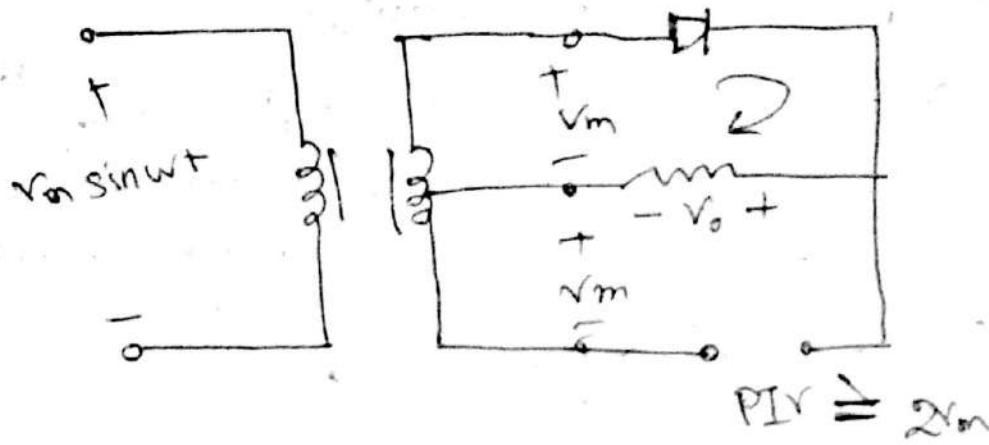

Compare

Formulas of HWR, FWR, FWCTR:

(i) Number of ~~dc~~ diode

(ii) Available ~~dc~~

$$V_{dc} = ?$$

(iii) Number of transformer




(iv) PIV rating.

PIV: Peak inverse voltage.

RC वर्ते रात चा. / session शृणु तरी मंजिल and cut
वाले charge / of charge . शृणु कर्म विषय लोक.


$$R_a C \ll R_L C$$

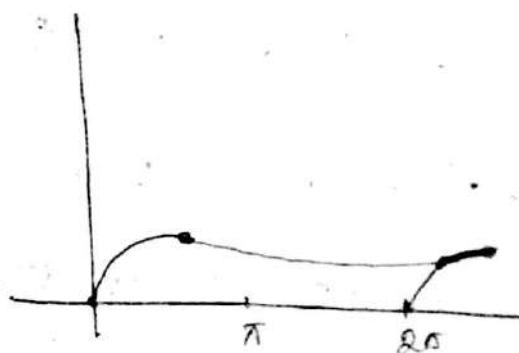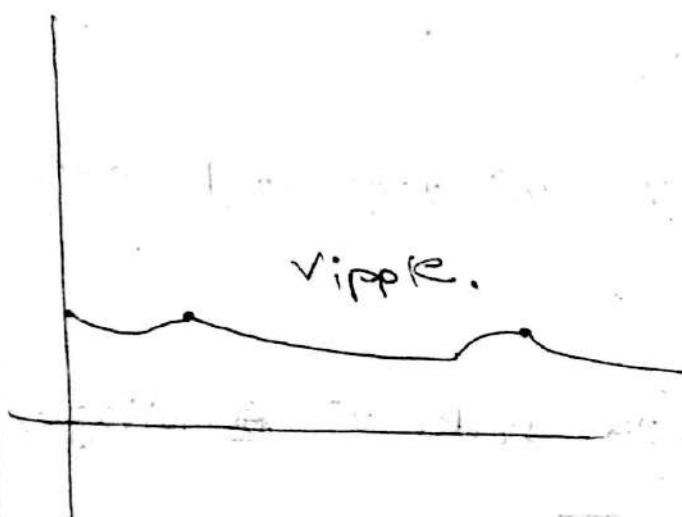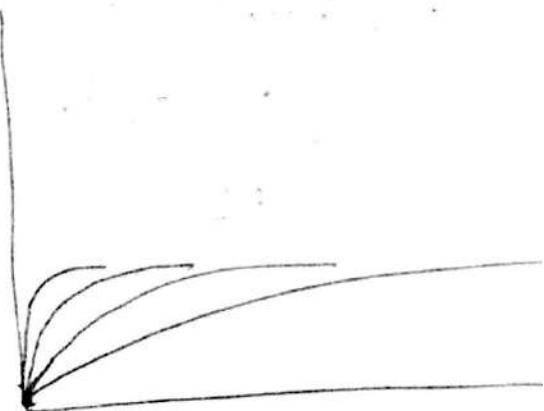$R_s = 5\Omega$ and $R_L = 10\Omega$ charge 200
and $R_L = 5\Omega$ discharge 200



- (i) Full wave ripple content as.

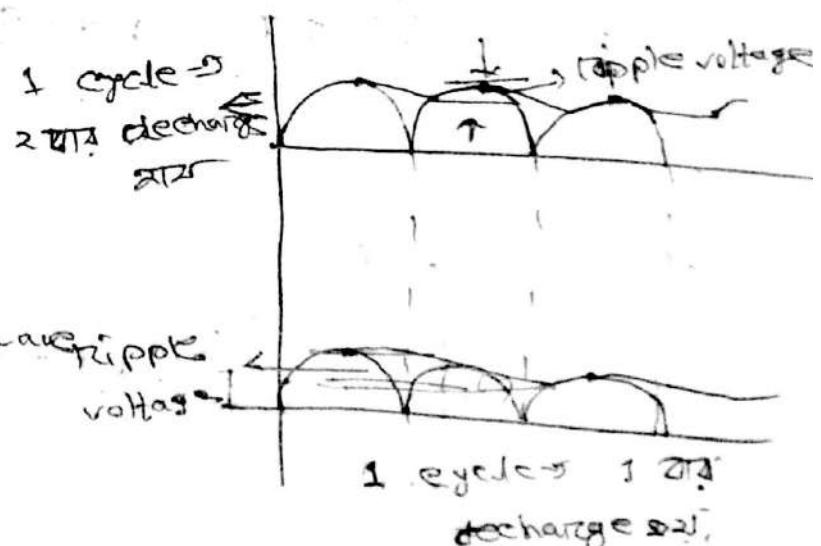
- (ii) Diode - as per half wave rectified voltage





Lectures-7

4th cycle A day

13-05-13

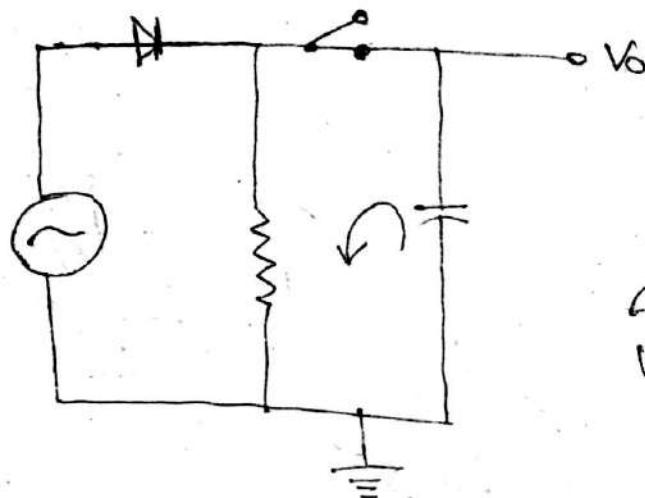


Unity directional
pulseating DC

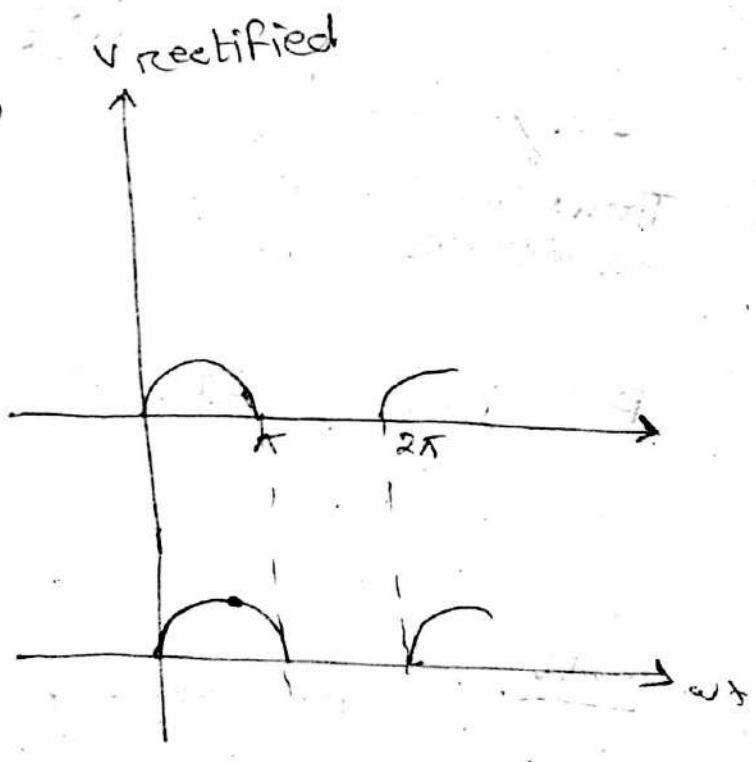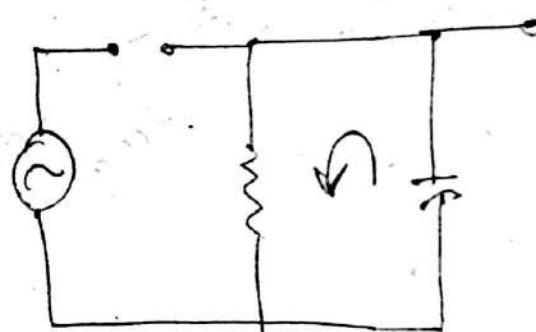

Charging

$$V_c(t) = E(1 - e^{-t/RC})$$

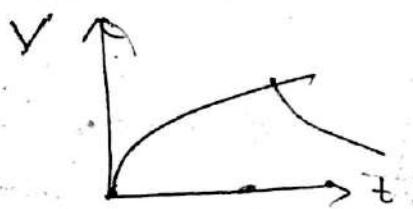


$RC \rightarrow$ time constant (T_{RC})

Recharging,


$$V_c(t) = E e^{-t/RC}$$

$RC = 5T$ 5 times ($5T_{RC}$)

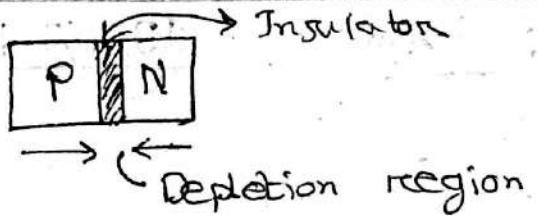$\Rightarrow 5T =$ Charge or
discharge $2T$,




~~Capacitor Capacitors~~

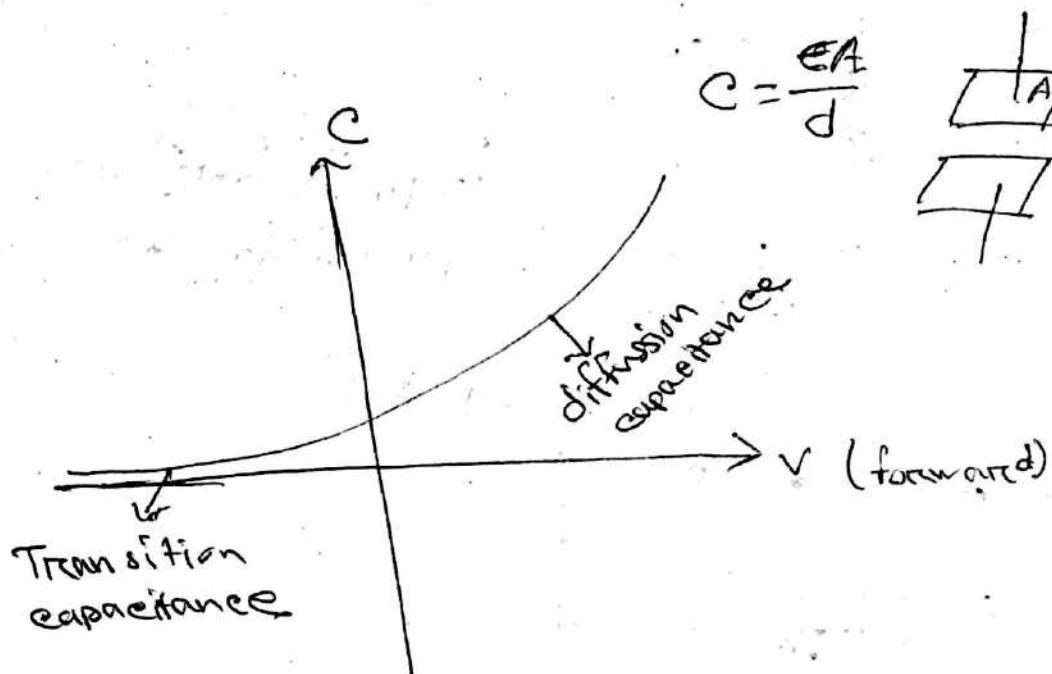

$$[C_t \quad C_d]$$

P-N junction - \square $C \sim T$

H.W.

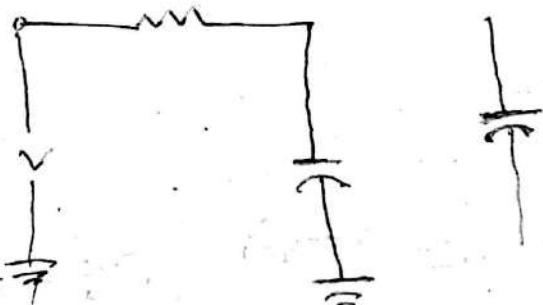

e across \square
voltage

Regulation




Ordinary Diode

(i) Zener diode



Zener
region

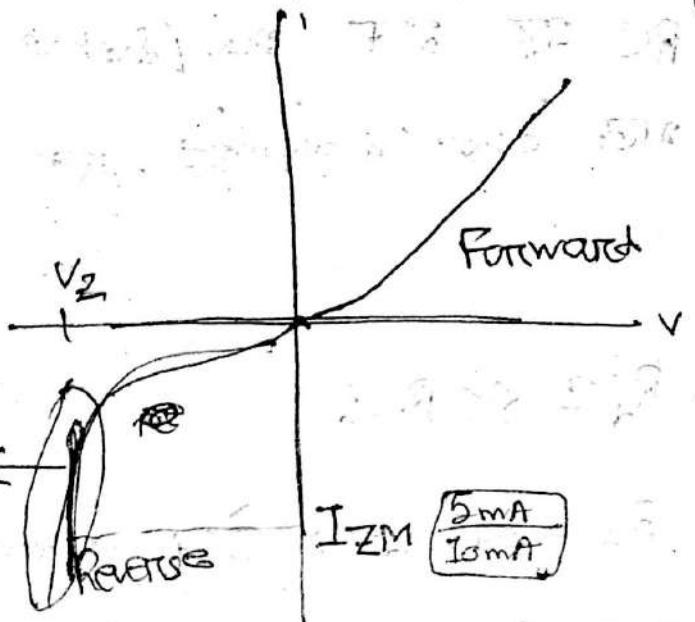

Ordinary diode - \rightarrow PIV V_Z - \rightarrow I_{ZM} \rightarrow 2mA
Diode damage \rightarrow 2mA

\Rightarrow Forward bias পরম্পরাগত ordinary and Zener
Diode same, এবং


\Rightarrow Reverse bias Zener diode - \rightarrow voltage

V_Z \rightarrow কম হলে open থাব.






$$V_Z = I_{ZM} \cdot R_{max}$$
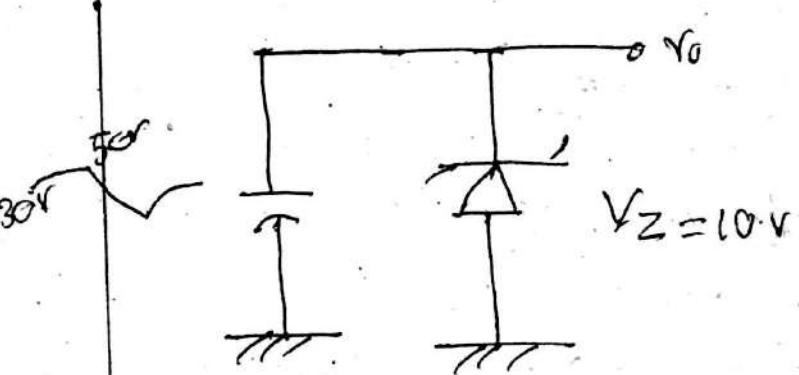
$$\begin{cases} V < V_Z \rightarrow \text{off} \\ V > V_Z \rightarrow \text{on} \end{cases}$$



Regulated output - 10V
G.D.


Zener diode:

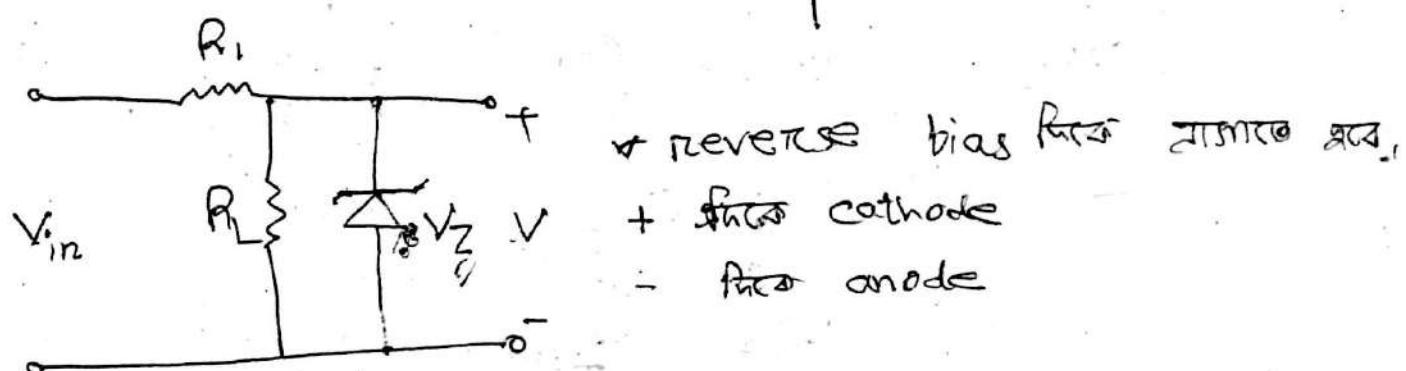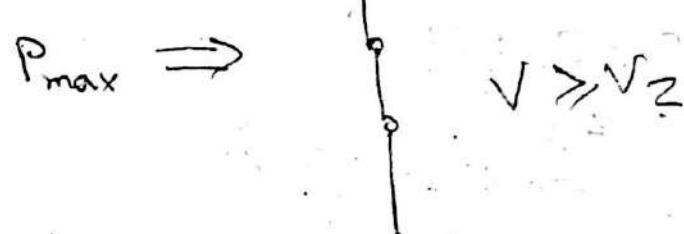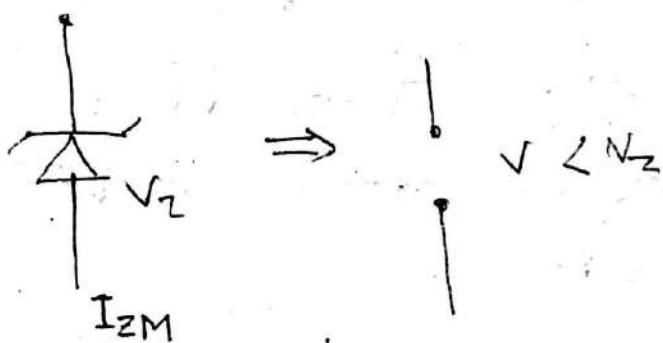

(i) Reverse

$$(ii) V \text{ (Zener off)} \quad V = \frac{R_L \times V}{R_1 + R_L}$$

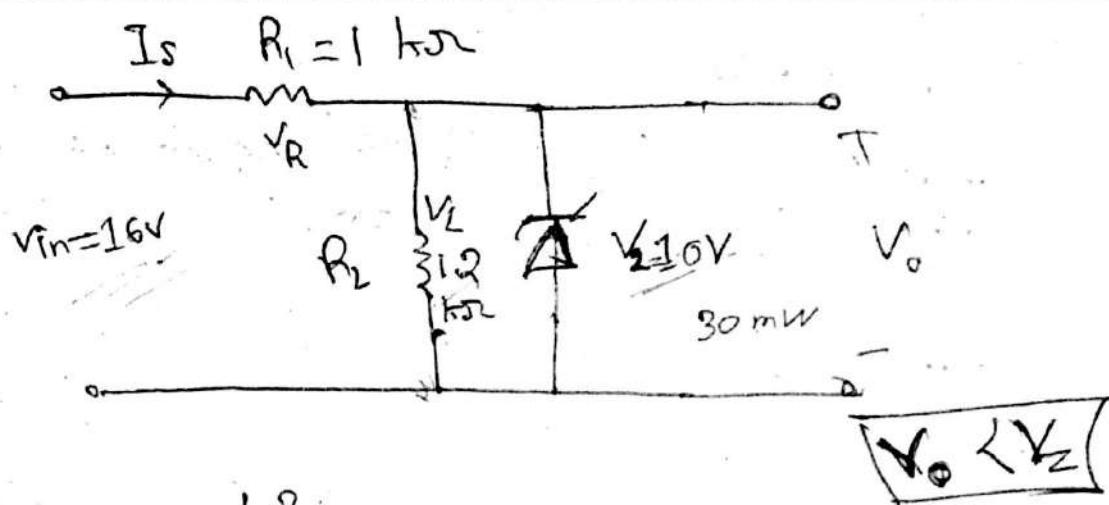(iii) Test कर ($V < V_Z$) तभि Zener off
($V > V_Z$ तभि Zener on)



$$V_o = \frac{1.2}{2.2} \times 16 = 8.727V$$

$V_o < V_z$ Zener off

Zener - off current $I_z = 0$


$$V_L = V$$

$$R_L = 3 \text{ k}\Omega$$

$$V_o = \frac{3}{4} \times 16 = 12V$$

$V_o > V_z$ ∴ Zener On
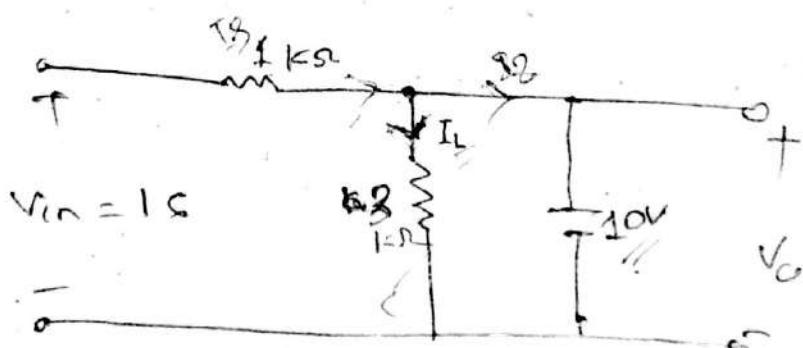
$$I_S = I_2 + I_z \\ \Rightarrow I_2 = I_S - I_z$$



$$V_o = V_L = 10V$$

$$I_L = \frac{10}{3} \frac{V_z}{R_L} = 10 \frac{10}{3} \text{ mA}$$


$$I_S = \frac{16 - 10}{1} = 6 \text{ mA}$$

Ripple voltage \rightarrow Appendix.

$$V_R = 1.21\%$$

$$= 98\%$$
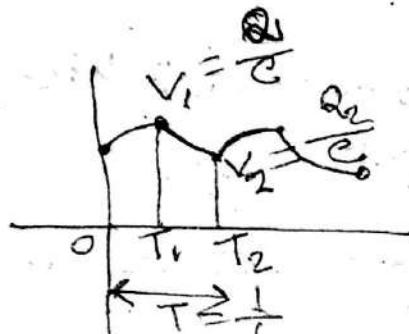
$$\sqrt{V_{\text{rms}}} = \sqrt{\frac{R}{2\pi}} \int_0^{2\pi} V_m^2 ds$$




Ripple \Rightarrow difference between V_1 and $V_2 = V_1 - V_2$

$$= \frac{Q_1 - Q_2}{C}$$

$$C = \frac{Q}{V}, \quad V = \frac{Q}{C}$$

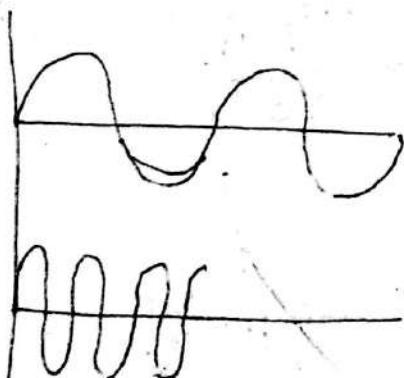Frequency - এর মধ্যে ripple voltage-এর relation:



Charging time period

চার্জিং

and discharging time period ডাই কার্বু.

$$T_1 - T_2 \gg T_1$$

$$T_2 - T_1 = T$$

$$\therefore \text{Ripple voltage} \Rightarrow \frac{V_1 - V_2}{T_2 - T_1} = \frac{Q_1 - Q_2}{C(T_2 - T_1)}$$


$$\Rightarrow \frac{V_1 - V_2}{T_2 - T} = \frac{Q_1 - Q_2}{CT}$$

Max current $I_{max} = 60\text{ mA}$




$$I_{L_{max}} = 20\text{ mA}$$

$$I_{Zm} = I_{max} - I_{L_{max}} = 90\text{ mA}$$


~~I_{Zm} off limit ताकि उत्तर नहीं हो~~

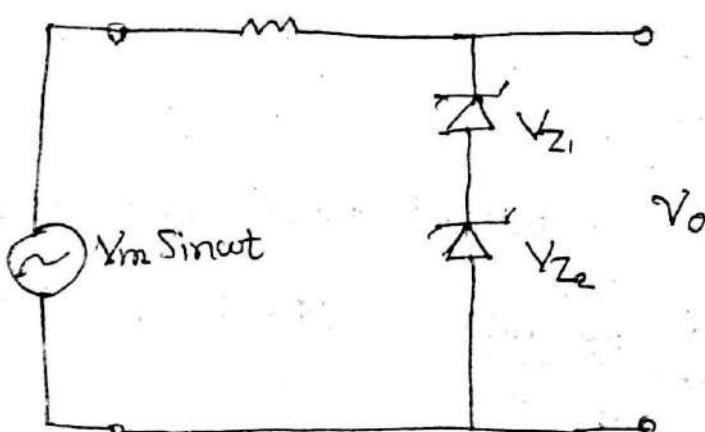

Voltage regulator
Rectifier
Filter

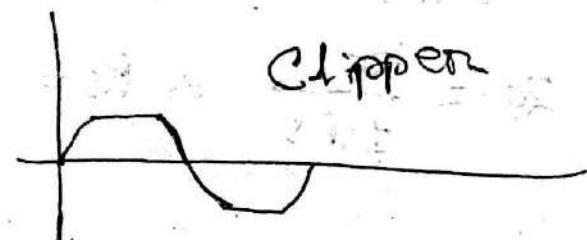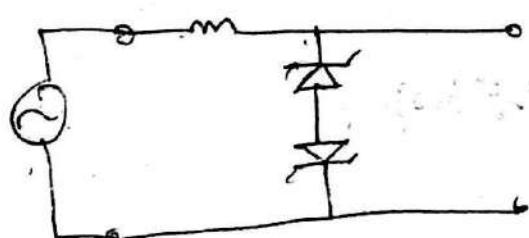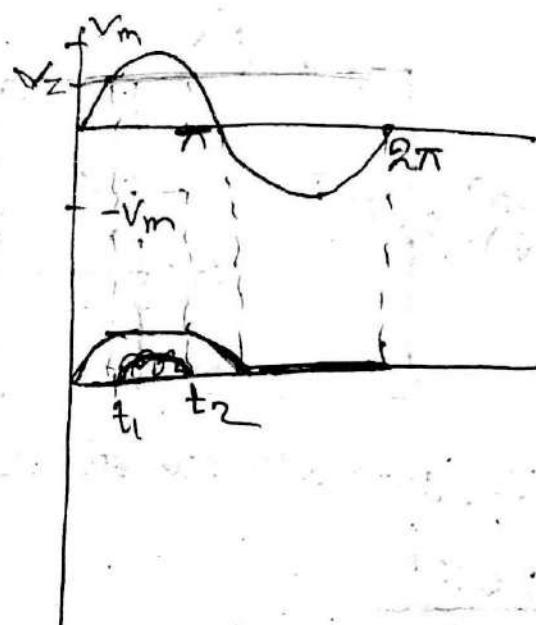


Clipper

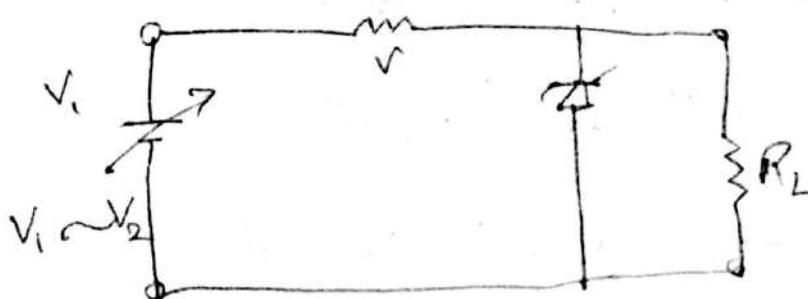

Law (10) - যদি জেনার ওন/অফ করে তবে লো ওন অল্টের জেনার ~~ওন~~ অফ করে।
হাইস্ট ওন হ্যাব ওন করে।

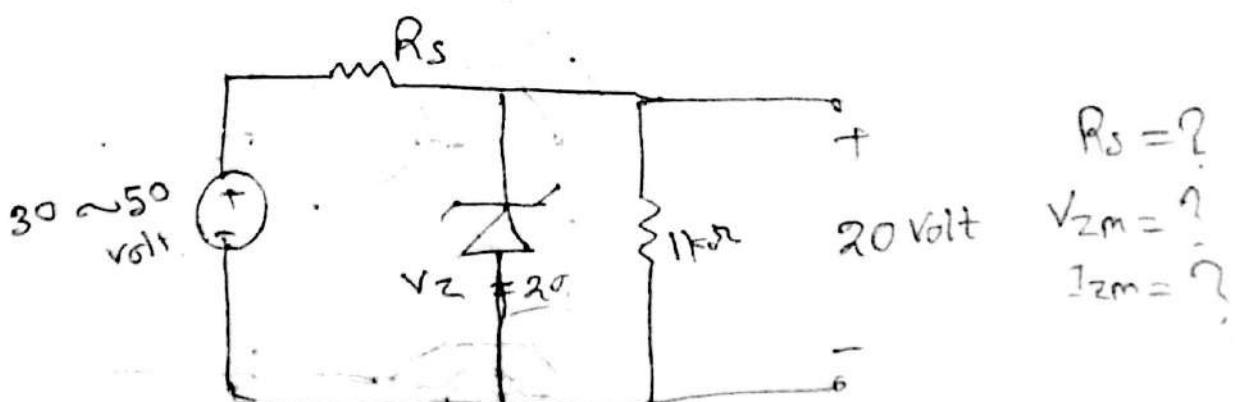Exercise

Design a voltage regulator that will maintain a output voltage of 20 volt across a $1\text{ k}\Omega$ with a input $\sim 30-50$ volt.



20 volt generate করা এবং 20 volt দিয়ে 20.


$$V = \frac{20 \times 1}{1 + R_s}$$

$$\rightarrow 20 = \frac{30}{1 + R_s} \Rightarrow R_s = 0.5 \text{ k}\Omega$$

$$1 = \frac{Q_1 + Q_2}{T}$$

$$\Rightarrow \frac{V_1 - V_2}{T} = \frac{1}{C} \left(\frac{Q_1 + Q_2}{T} \right) = \frac{I}{C}$$
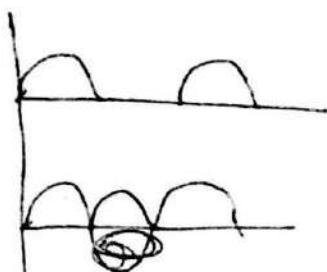
$$V_R = \frac{IT}{C} = \frac{I}{f_C} \cdot \frac{I}{f_C}$$



→ Half-wave of V_R
2 shot

→ Full wave of V_R .


Static DC resistance and dynamic resistance
AC resistance

$$h_{DC} = \frac{V_{DC}}{I_{DC}}$$

$$I_D = I_S \left(1 - e^{-\frac{kV_T}{V_D}} \right)$$

$$R_{DC, AC} = \frac{\Delta V_D}{\Delta I_D} = \frac{26 mV}{I_D}$$




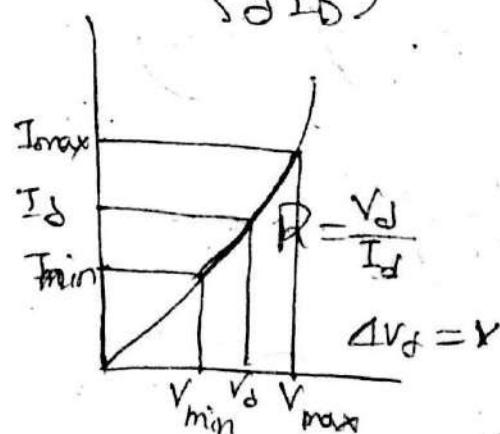
$$= \left(\frac{\partial V_D}{\partial I_D} \right)$$



1st chapter

28-05-2013

9th cycles E Day

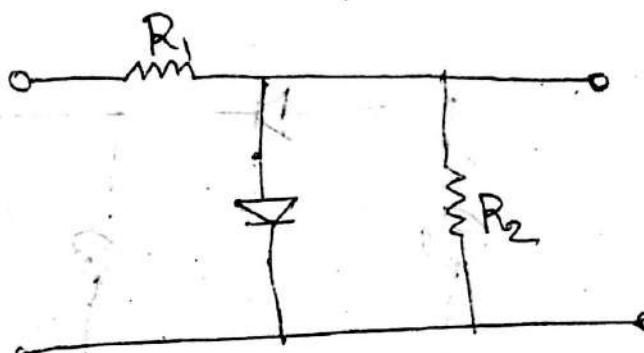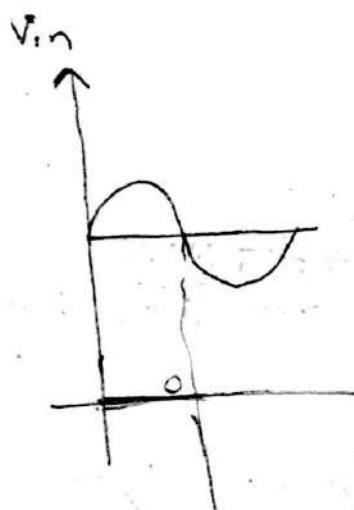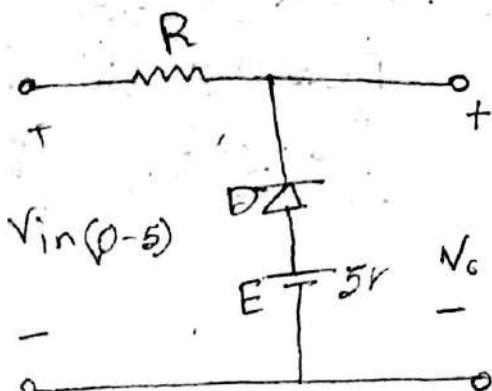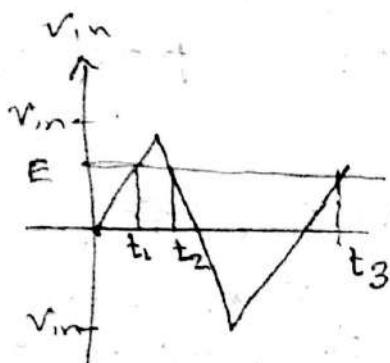

$$(0 - \pi) \rightarrow V_o = 0$$

$$(\pi - 2\pi) \rightarrow V_o = \frac{R_2 * V_{in}}{R_1 + R_2}$$

Reverse bias গ্রহণ \propto capacitance Transmission time
F.O.C D.C

Forward I_fI_o

Transmission exp


$$\text{Capacitance} = \frac{GA}{J}$$

Reverse Recovery \rightarrow air semiconductor - এর switching speed.



Reverse Recovery time $\propto \frac{1}{\text{switching speed.}}$

1st Diode forward or reverse OR
vice versa upto the time before the
Recovery time.

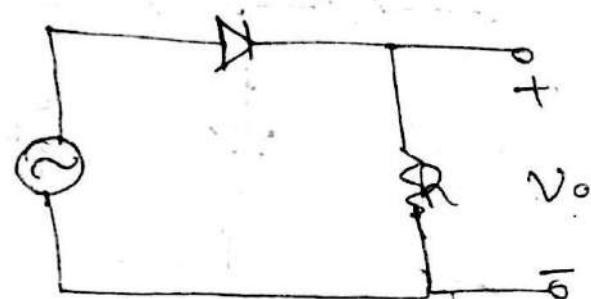Schottky Diode → consists P or n
junction OR
कठिन प्रति विद्युत विपरीत
P or n विकास



→ Half wave
rectifier circuit.

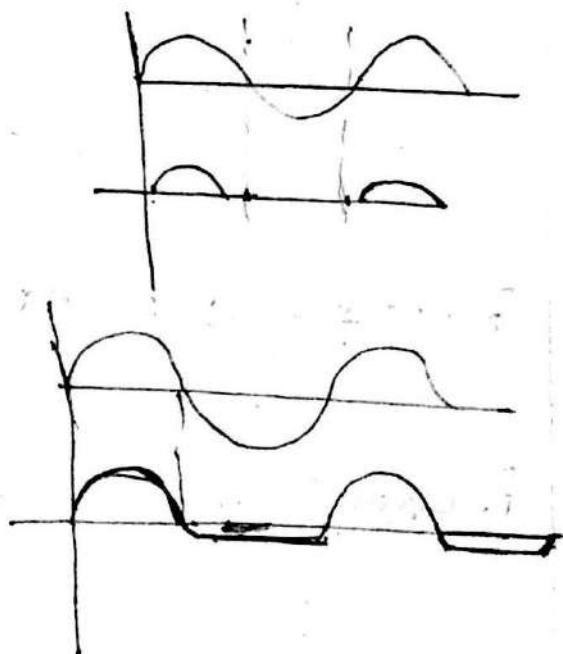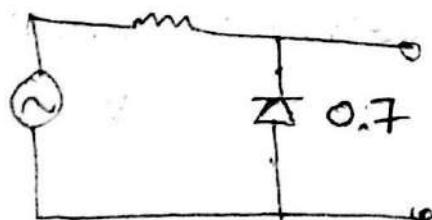

Bridge :- V_m

center tab: $\geq 2V_m$


[Bridge - 5 power bar]
[cathode]

Bridge → 2 1st Diode and
center tab → 1st "

B J T (abbreviation)
 Bipolar junction Transistor

(i) 3 Terminal Device.

semiconductor transistor

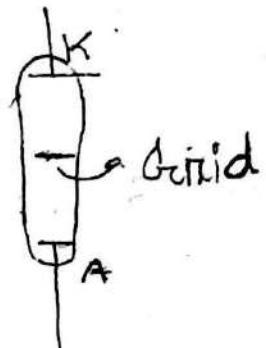


Diode \rightarrow 2 terminal device

\rightarrow switching - এর ক্ষেত্রে স্থানান্তর করা হয়,

Transistor \rightarrow 3 terminal device

\rightarrow switching and amplifier পদার্থে পরিবায় করা

হয়,

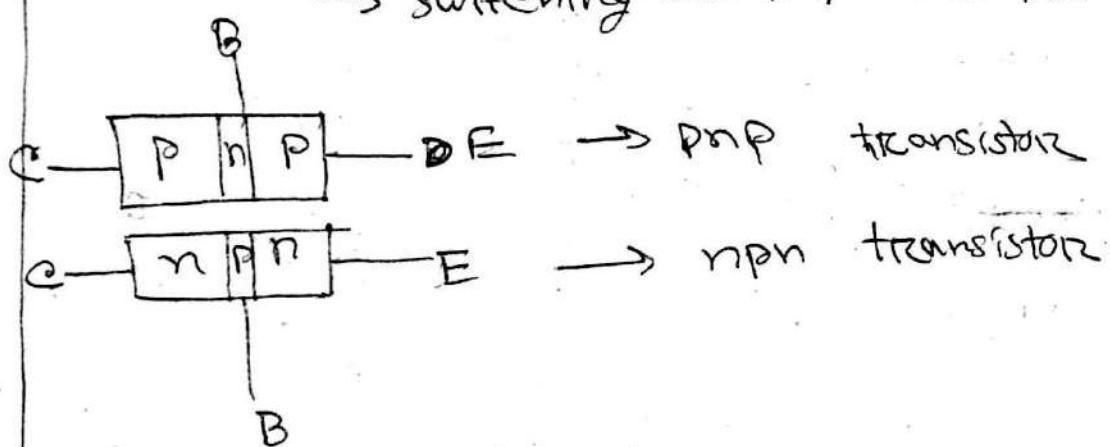

C \rightarrow collector \rightarrow collector or Emitter (কোটি),



B \rightarrow Base

E \rightarrow Emitter

এক ঘন্টা

Diode - এর মাল্টিমিটার - এর (+) এর প্লাট

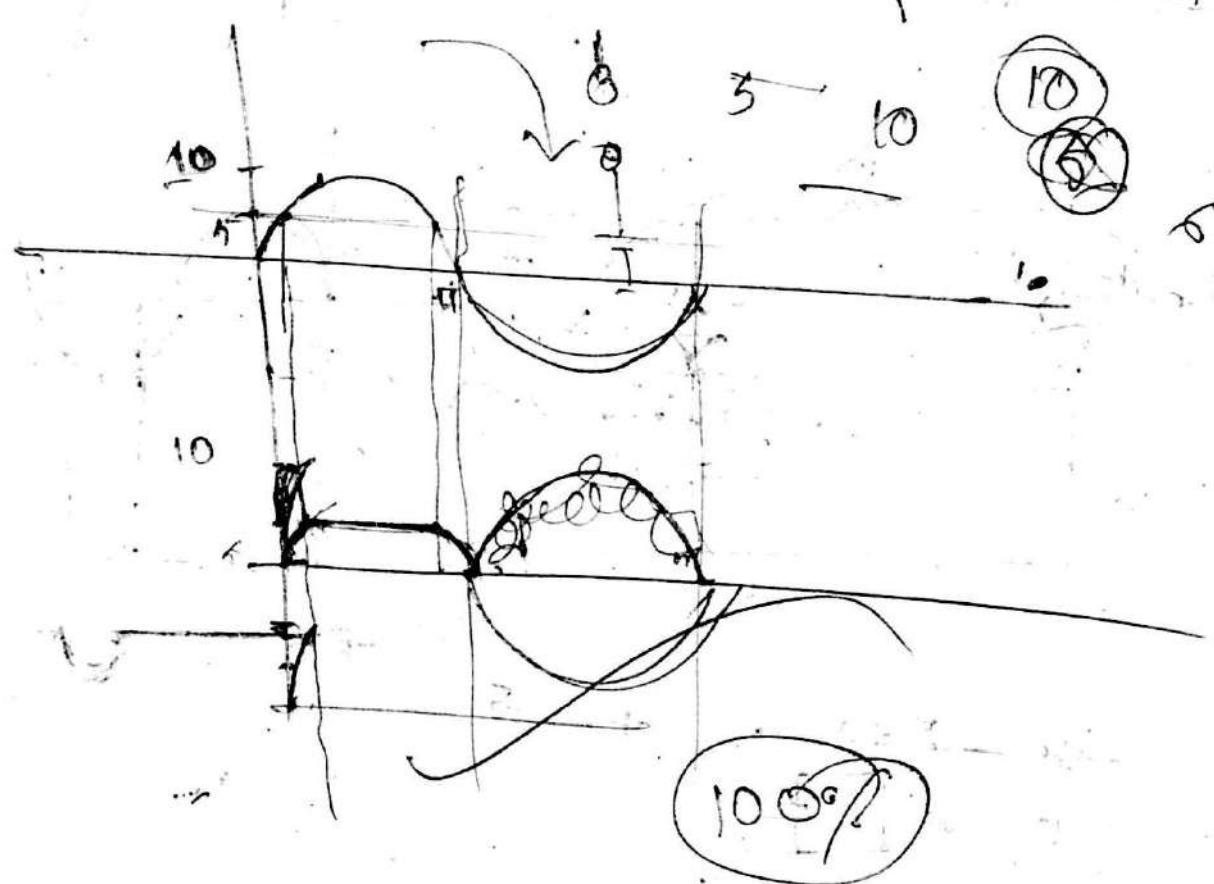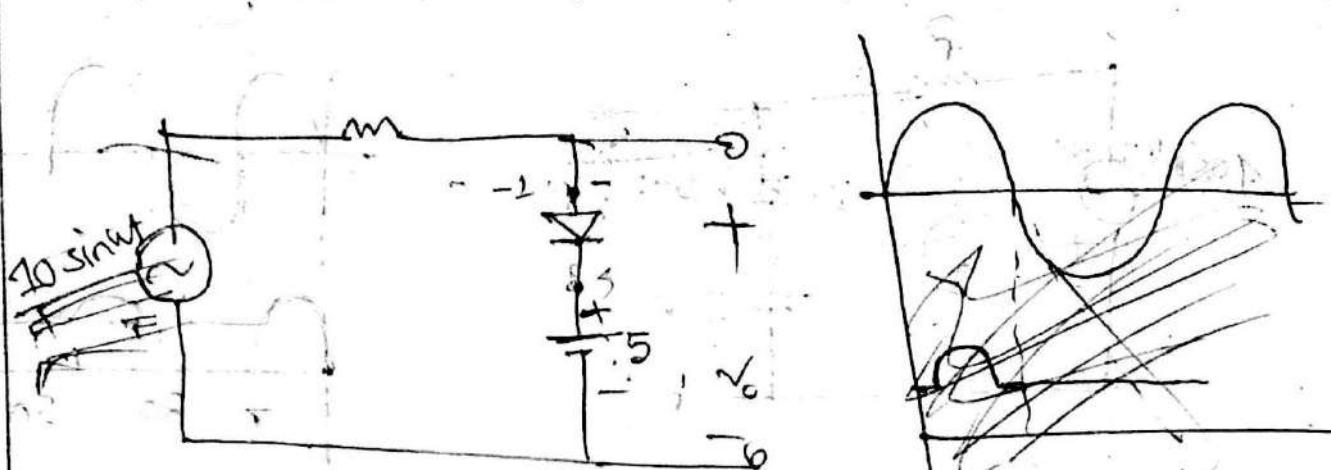Resistance \rightarrow অধিক দূরের ক্ষেত্রে ও অধিক দূরে
 cathode and ~~anode~~ \rightarrow 0 ohm on Anode.





10



-1, -10

$$\begin{aligned} V_1 - V_2 \\ 5 - 5 = -1 \\ -1 - 5 = -6 \end{aligned}$$

$$0 + v_0 + 5 = 0$$

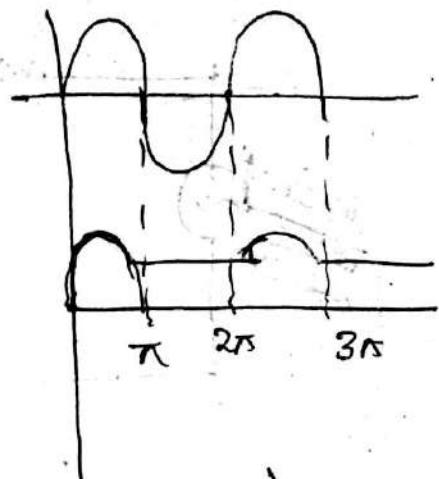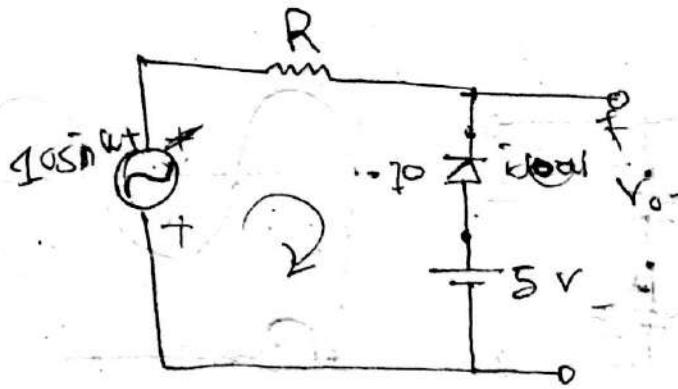

10

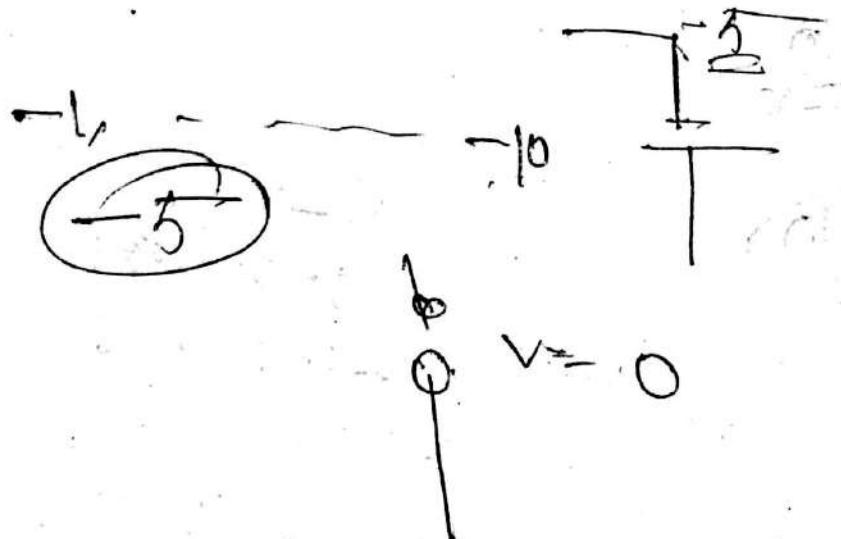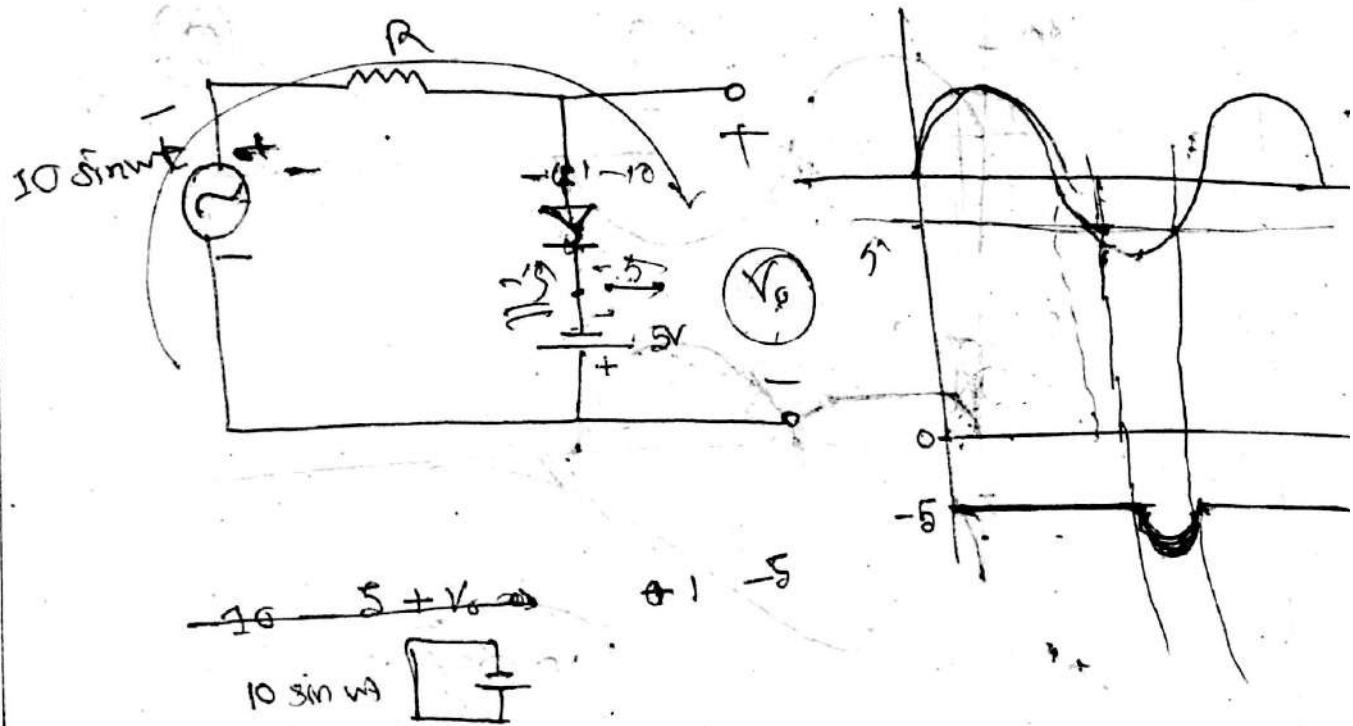



power transistor

$$\frac{220}{100\%} = \frac{1}{5}$$

Base \rightarrow କିମ୍ବା Doping level କିମ୍ବା କରୁଥିଲା
 \rightarrow Resistance କିମ୍ବା କରୁଥିଲା,

Base କେବେ 100-150 ମିଟର କିମ୍ବା Doping କରୁଥିଲା
 Collector and Emitter.

Emiter କିମ୍ବା Doping level କରୁଥିଲା,

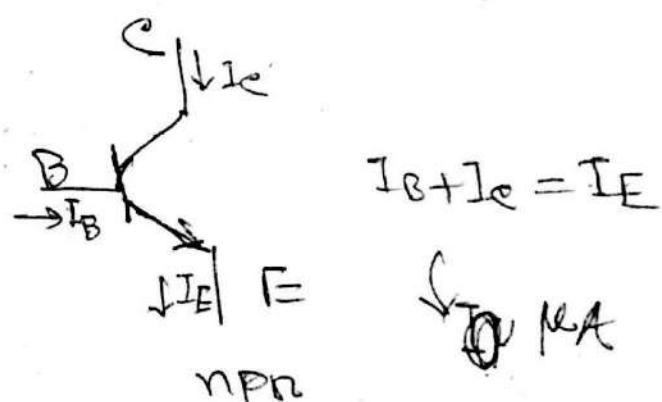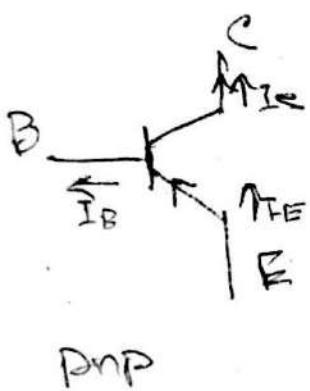

$$I_B + I_c = I_E$$

$\downarrow \mu A$

$$\alpha = \frac{I_c}{I_E} \quad \beta = \frac{I_c}{I_B}$$

$$\frac{I_B + I_c}{I_c}$$

$$\Rightarrow \frac{1}{\beta} + 1 = \frac{1}{\alpha}$$

$$\Rightarrow \frac{1+\beta}{\beta} = \frac{1}{\alpha}$$

$$\Rightarrow \boxed{\alpha = \frac{\beta}{1+\beta}}$$

$$\frac{1}{\beta} = \frac{1}{\alpha} - 1$$


$$\Rightarrow \frac{1}{\beta} = \frac{1-\alpha}{\alpha}$$

$$\Rightarrow \beta = \frac{\alpha}{1-\alpha}$$


$\alpha < 1$

$B > 1$

Configuration:

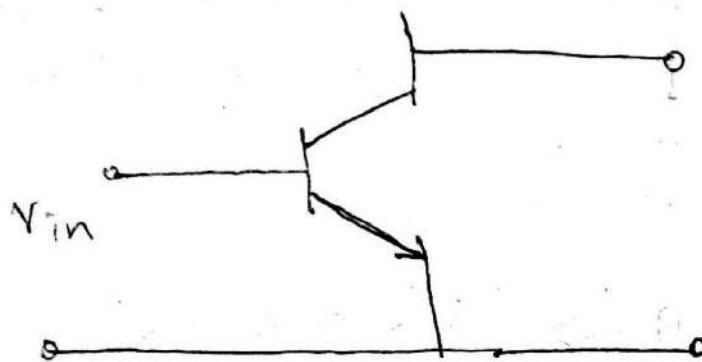


(1) Common Emitter configuration (CE)

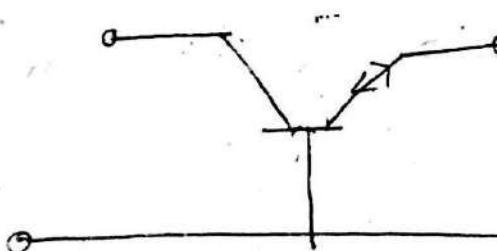

(2) Common Base configuration (CB)

(3) Common Collector configuration (CC)

CE \rightarrow Amplifier

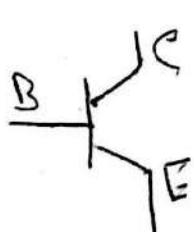


CB junction
 BE junction

Amplifier first use कर्ता - BE \rightarrow forward bias (F)

CB \rightarrow Reverse bias (RE)

ECE

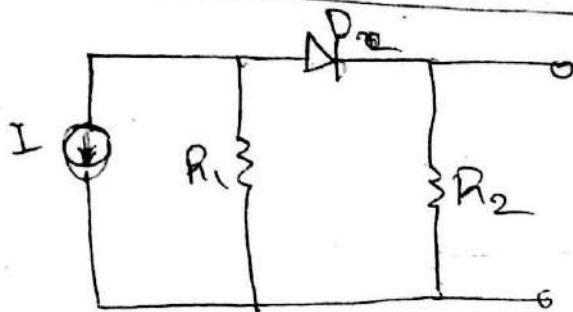Switch → ON → Reverse bias (2N junction)
 OFF → Forward bias (2N junction)



05-06-20

Si and Ge ~~diodes~~
 Parallel अवलंब
 Si on शुद्ध घास


Cutoff, Switch off } CB → Reverse bias

BE →

Saturation, Switch on


} CB → forward bias

BE →

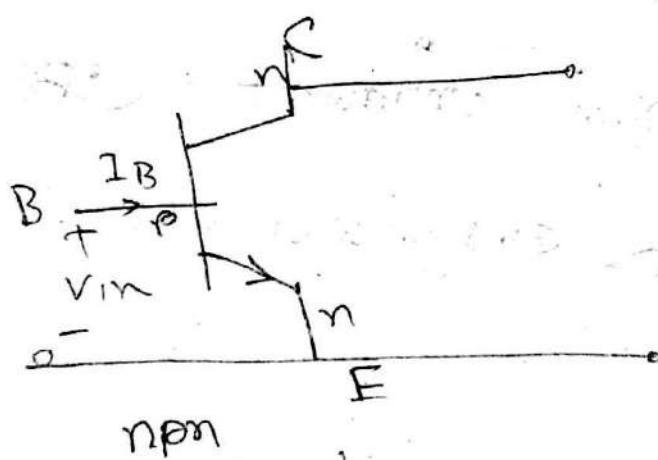

→ Amplifier बनाना
 use करा

common, Emitter,

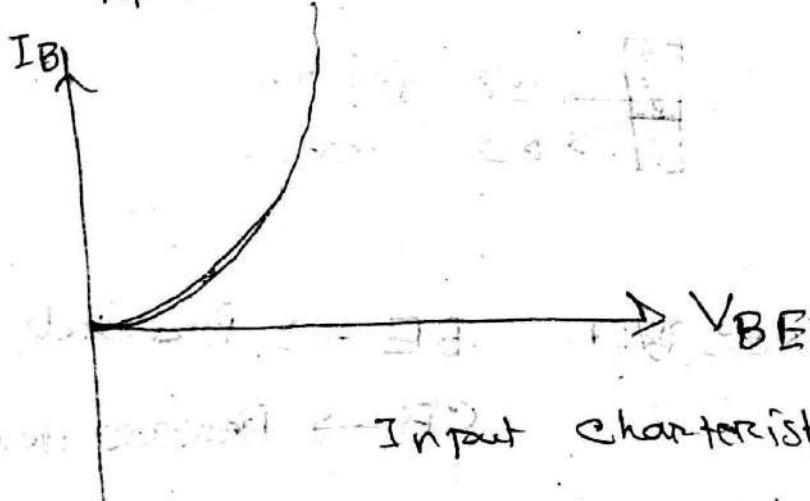


Input characteristic

10 - 06 - 2013

$$\frac{50 \text{ volt ac}}{50 \text{ volt rms value}} \rightarrow \text{peak value } \sqrt{2} \times 50$$

BJT biasing

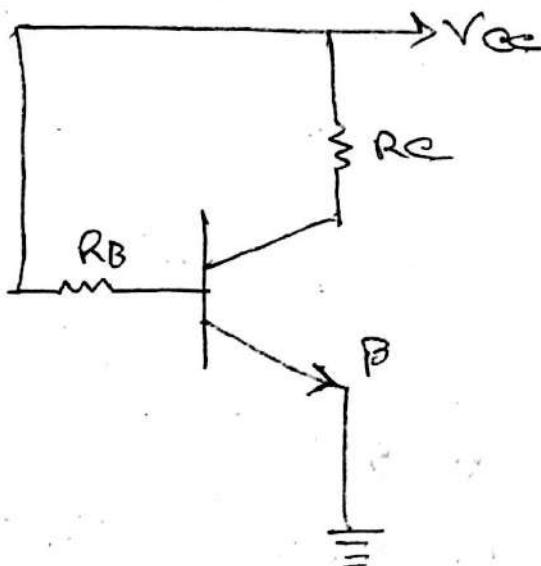- (1) Fixed bias
2. Emitter bias
- (3). Voltage divider bias.
4. Collector feedback.



$$V_{CE} = ?$$


$$I_C = ?$$

(1) Input loop - J KVL - apply করে I_C (current) করুন,

(2) Output loop - J KVL apply করে V_{CE} পতিত করুন,

Fixed bias

At first KVL law apply করাতে হবে input

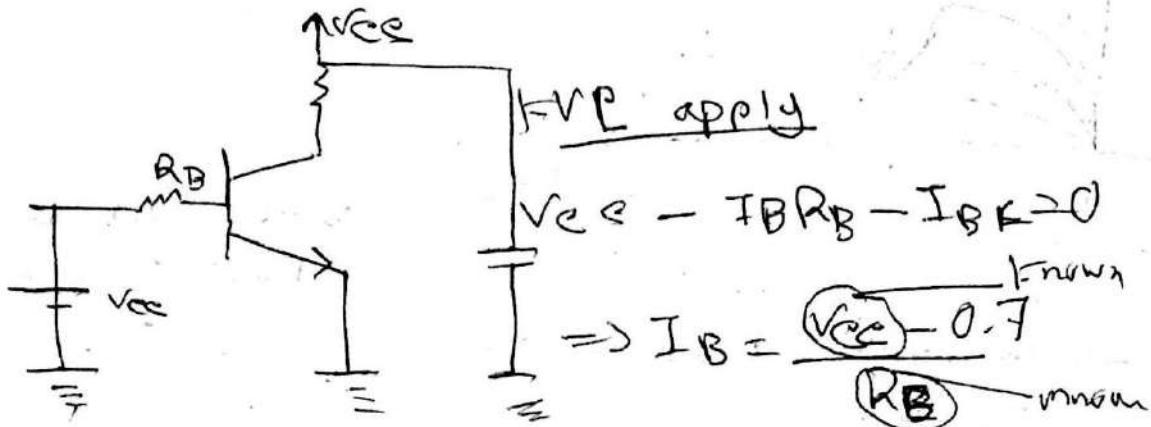

$$\Rightarrow I_B = \frac{I_C}{\beta}$$


$$\Rightarrow \beta = 1$$

$$\Rightarrow I_C = I_B \beta$$

V_{CE} - এর জন্য output - drop - ০ KVL apply করো ৱু.

$$V_{CE} - I_C R_C - V_{CE} = 0$$


$$\Rightarrow V_{CE} = I_C R_C$$

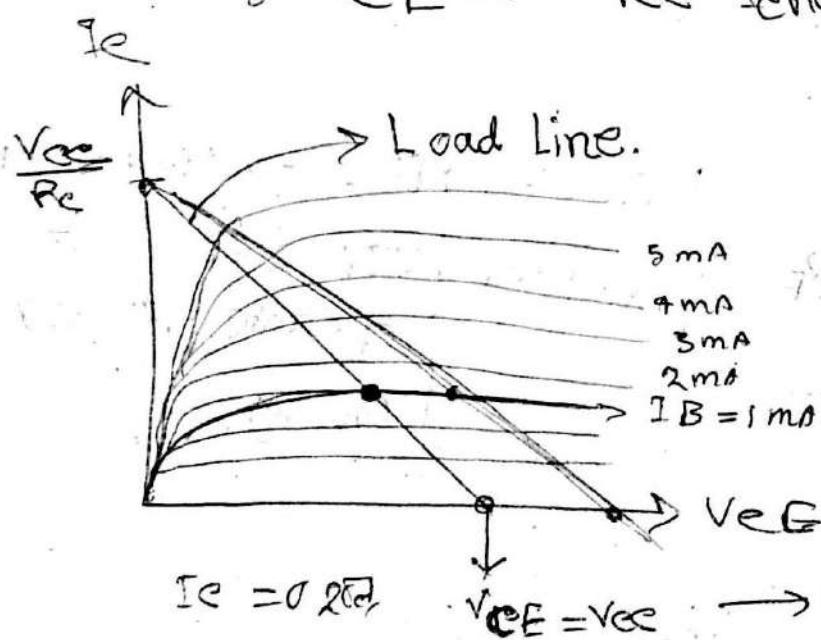

(i) β Level - এর V_{CE} use করিওৰ V_{CE} V_{CC} - এর
কোটা half β ।

কোটা কোটা

কোটা

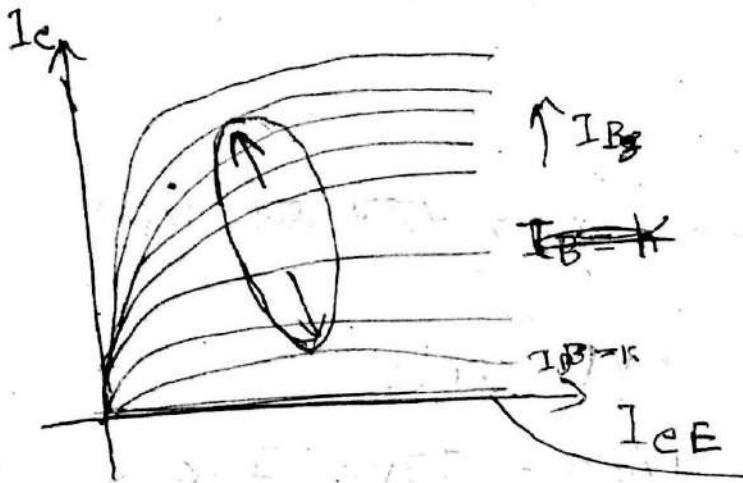

→ cut-off region
Base of current mirror

$\beta \rightarrow$ common limiting nutrient function.

$$\Rightarrow B = \frac{I_C}{I_D} \quad \xrightarrow{\text{2Dr bias}} \text{reverse bias.}$$

Cut-off region


Linear \sim \rightarrow cutoff and saturation -এর মধ্যে region.

saturation

$$I_B = \max_i V_{CE(i)} \approx 0.2V$$

2π bias \rightarrow towards


δ -pt \rightarrow Quiescent point

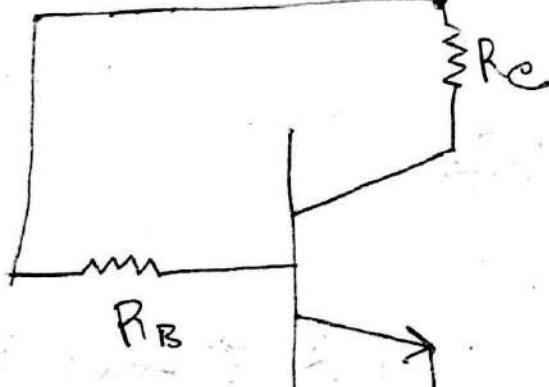

DC - voltage apply
কর্তৃপক্ষ Q-point or
operate কর্তৃপক্ষ জন্য, এবং
Biasing.

Fixed Bias

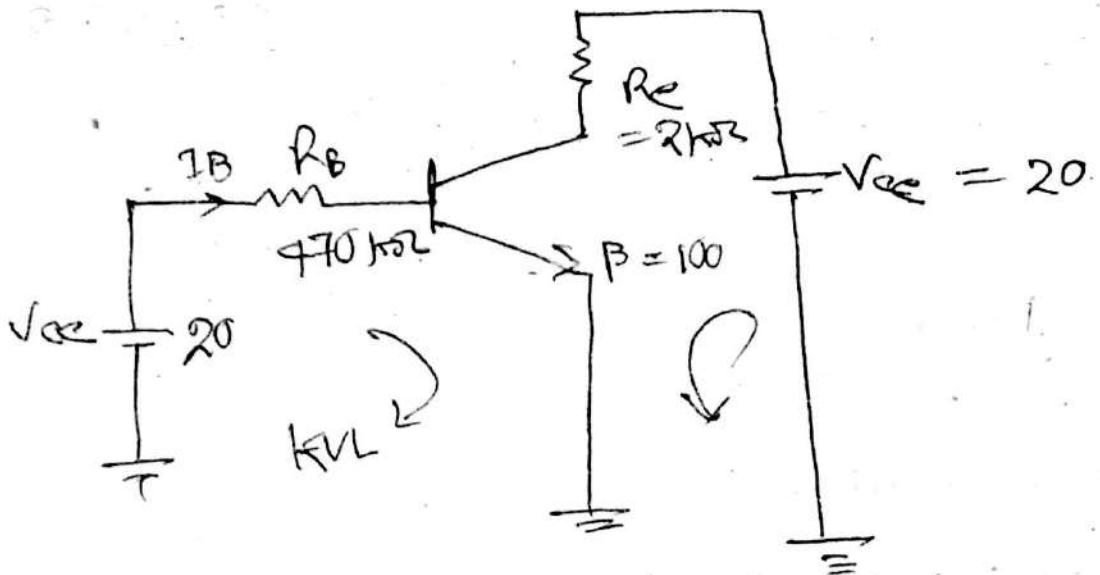switching-ଓঁ কে) cut-off / saturation-ওঁ ফি) গুরু



$$V_{CC} - I_B R_B - V_{BE} = 0$$

$\frac{0.7}{0.7}$

$$\Rightarrow I_B = \frac{20 - 0.7}{470 \text{ k}\Omega}$$

$$= 0.041 \text{ mA}$$

$$= 41 \mu\text{A}$$

BJT - 5

$$V_{BE} = 0.7 \text{ V}$$

always

$$I_C = \beta = \frac{I_E}{I_B}$$

$$\Rightarrow I_C = \beta I_B = 100 \times 0.041$$

$$= 4.1 \text{ mA}$$

Output loop:

$$V_{CC} - I_C R_E - V_{CE} = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C R_E$$

$$\Rightarrow V_{CE} = 11.78$$

Transistor amplifier - ये एक मात्र Q-point Linear - IC
का नहीं प्राप्ति करना चाहिए

$$V_B = ? \quad V_E = ? \quad V_C = ? \quad V_{EB} = ? \quad V_O <= 0$$

$$V_{BE} = 0.7 \Rightarrow V_B - V_E = 0.7 \Rightarrow V_B = 0.7$$

$$\text{If } V_{CE} = 11.78, \quad V_C - V_E = 11.78$$

$$\Rightarrow V_C = 11.78.$$


$$\text{If } V_{BE} = \frac{0.7 - 11.78}{11.08} \text{ V (reverse)}$$

$$V_{EB} = 11.08 \text{ (forward)}$$

ECE-211 ~~Emitter~~


12-June-2013

Emitter feedback bias.

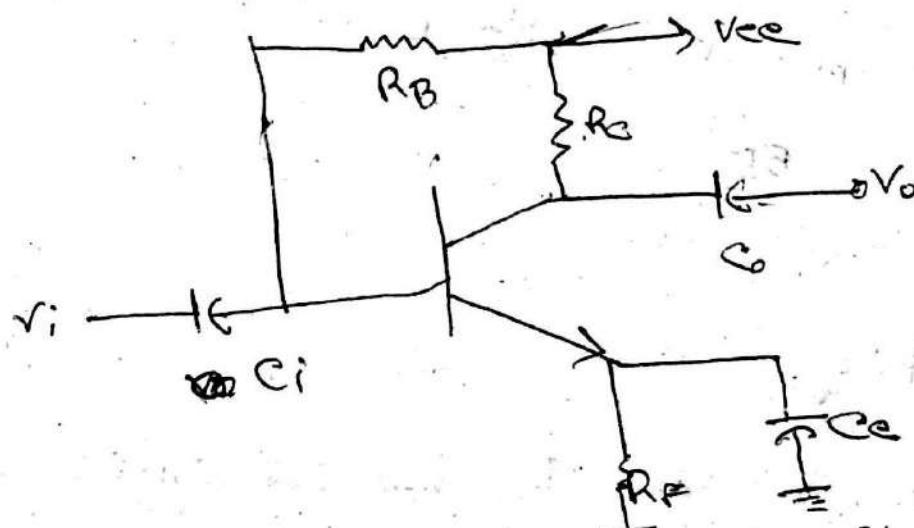

Complete amplifying circuit.

capacitor
AC - एस
लॉड मैट्री
आउट

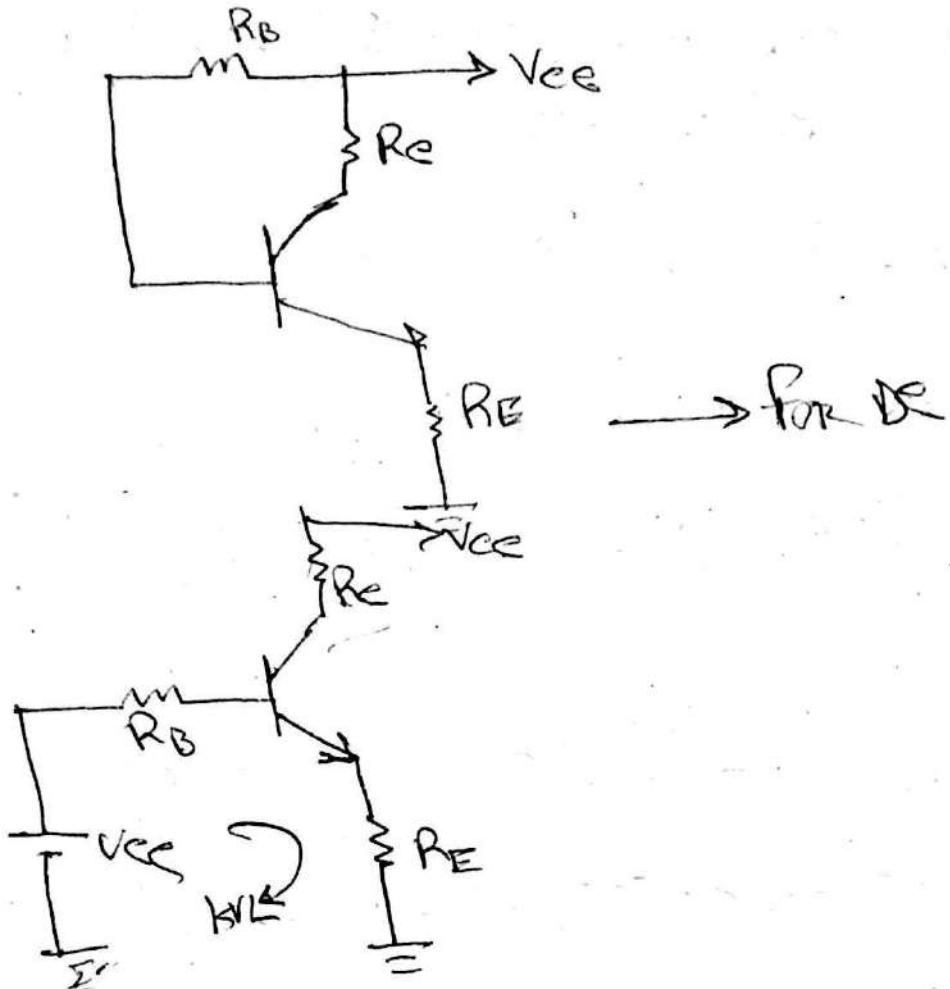

I_B - দেয় করা

$$\Rightarrow V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$\Rightarrow V_{CC} - I_B R_B - V_{BE} - (B+1) I_B R_E = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (B+1) R_E}$$

$$\therefore I_C = B I_B$$

Q-point দেয় করা হলো I_E V_{CE} দেয় করা হলো

Output Loop \rightarrow

$$V_{CE} - I_E R_E - V_E - I_E R_E = 0$$

$$\therefore V_{CE} - I_C R_E - V_E - I_E R_E = 0$$

$$\left. \begin{aligned} I_E &= \frac{I_C}{\alpha} \\ I_E &\approx I_C \end{aligned} \right\}$$

$$R_C = \frac{20}{8}$$

$$I_E = ?$$

$$I_B = ?$$

$I_{E\text{sat}} = 8 \text{ mA}$

$$I_E = \frac{V_{CE}}{R_C}$$

6-point

V_{CE}



Q_{AV}

EEE-211

7th A day

23-06-13

voltage divider bias:

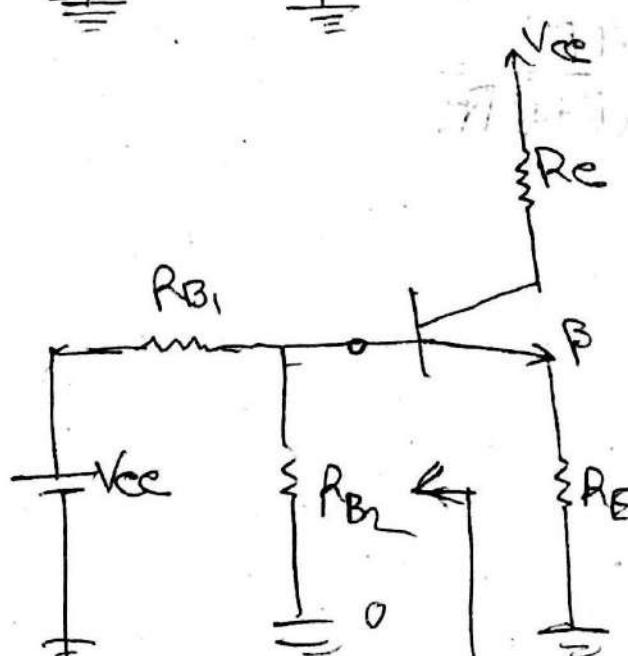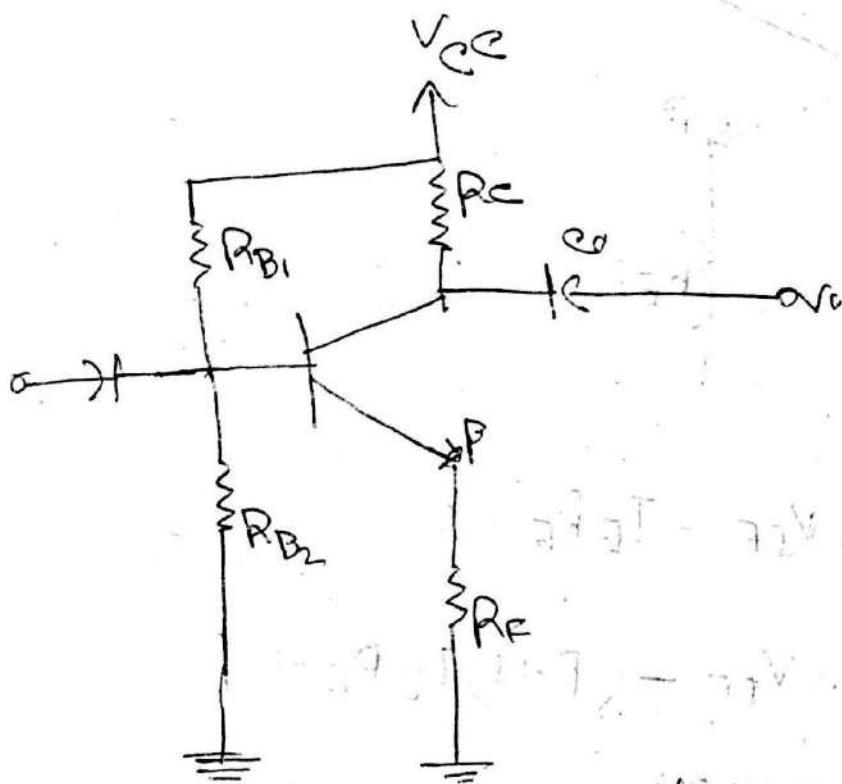


R_E , V_{CE} - ए का effect on Q-point:

R_E द्वारा Q-point

R_E Right - ए का पर्याप्त

R_E कमाते Q-point

left - ए कमाते.

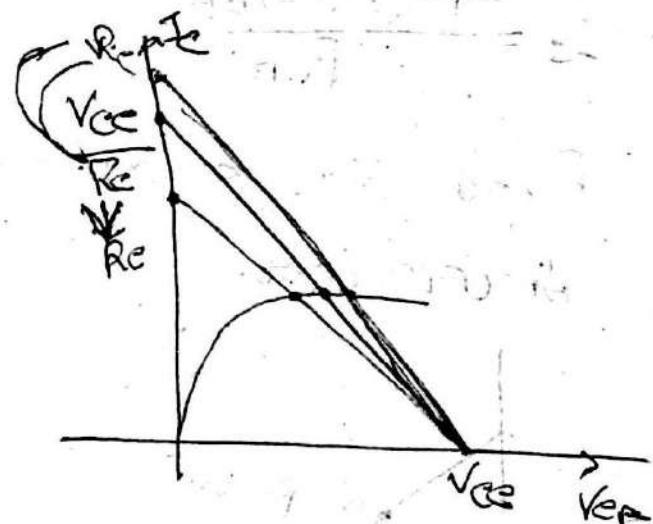


V_{CE} कमाते

Q-point Right ->

and V_{CE} बढ़ाते


Q-point left -> $\sqrt{V_A}$.

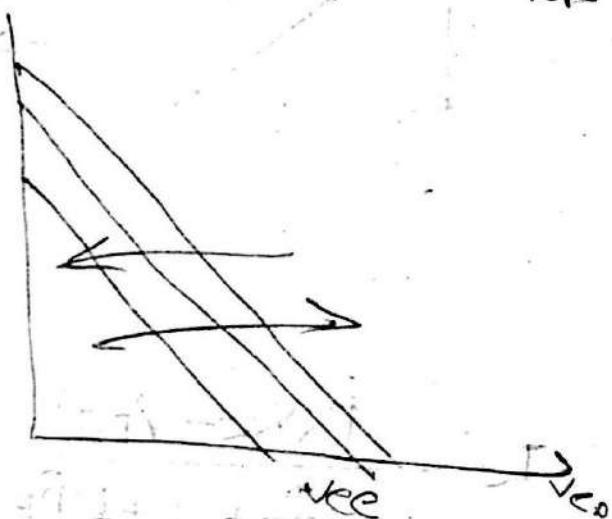

I_B change का प्रभाव

R_B कमाते I_B बढ़ाते

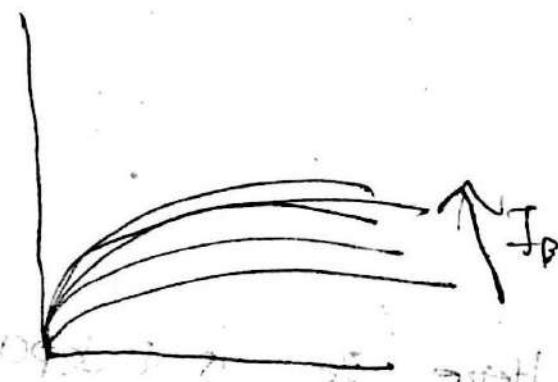I_B कमाते I_B का प्रभाव
saturation - एवं fixed $\sqrt{V_A}$.



I_B कमाते Q-point


Cut-off - एवं fixed $\sqrt{V_A}$.

Fixed bias and Ammeter bias - $\sqrt{V_A}$, Feedback
problem - कमाते.

$$V_{QE} = V_{CE} - I_C (R_E + R_E)$$

$$I_C = \frac{\beta (V_{CE} - V_{BE})}{R_B} \rightarrow \boxed{\text{Fixed bias}}$$

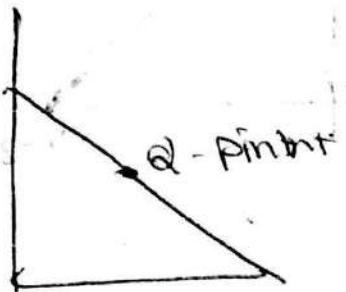fixed bias circuit - or collector current β dependent.



→ Q-point or variation temperature
or bias depend করে,

I_C করে রেজিস্টর হল) 2-point Change

$I_C \rightarrow \beta$ variation - এর জন্য চেঞ্চে
tem. variation নাম দেওয়া হল

$$I_C = \frac{\beta(V_{CE} - V_{BE})}{R_B + (\beta+1)R_E} \approx$$

$$\frac{\beta(V_{CE} - V_{BE})}{R_B + \beta R_E}$$

$$\text{If } \beta R_E \gg R_B$$


$$\approx \frac{\beta(V_{CE} - V_{BE})}{\beta R_E}$$

Here, I_C is independent on β .

A meter feedback bias circuit is more stability
than fixed bias circuit.

$$V_{Th} = \frac{R_{B2} V_{BE}}{R_{B1} + R_{B2}}$$

$$R_{Th} = R_{B1} || R_{B2} = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}}$$

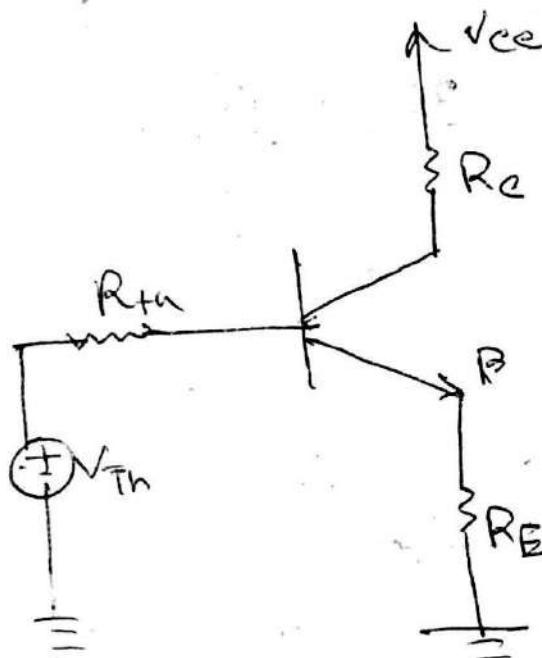

$$V_{Th} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{Th} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$\Rightarrow I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}$$

$V_{CC} = 16V$, $R_E = 3.6 k\Omega$, $R_E = 1.2 k\Omega$, $R_{B1} = 91 k\Omega$

$$R_{B2} = \frac{80 k\Omega}{18100} \quad \beta = 100,$$

$I_B, I_C, I_E, V_B, V_{CE}, V_{BE} = ?$

$$V_{TH} = \frac{R_{B2} \times V_{CC}}{R_{B1} + R_{B2}} = \frac{7.98}{91 + 80} V = 2.69$$

$$R_{TH} = \frac{R_{B1} \times R_{B2}}{R_{B1} + R_{B2}} = \frac{91 \times 80}{91 + 80} = \frac{72.57}{171} = 15.03 k\Omega$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E} = \frac{7.98 - 0.7}{92.57 + 101 \times 1.2} = 0.09 mA = 0.0192 mA$$

$$I_C = \beta I_B$$

$$= 9 mA = 1.42 mA$$

$$\textcircled{1} \quad I_E = (\beta + 1) I_B$$

$$I_E = 101 I_B$$

$$= 101 \times 0.09 mA$$

$$= 9.09 mA$$

$$V_{CE} = I_C R_C - V_{CF} - I_E R_E =$$

$$\Rightarrow V_{CF} = V_{CE} - I_C R_C - I_E R_E$$

$$= V_{CE} - I_C R_C - I_E R_E (\beta + 1) I_B R_E$$

$$= -3.278 V$$


$$V_B = 0.7 + V_E$$

$$V_C = E - V_{CE} - I_C R_C$$

$$V_{CE} = E - V_E = 9.16 \text{ V}$$

$$V_{BC} - V_B - V_E = -8.47 \text{ V}$$
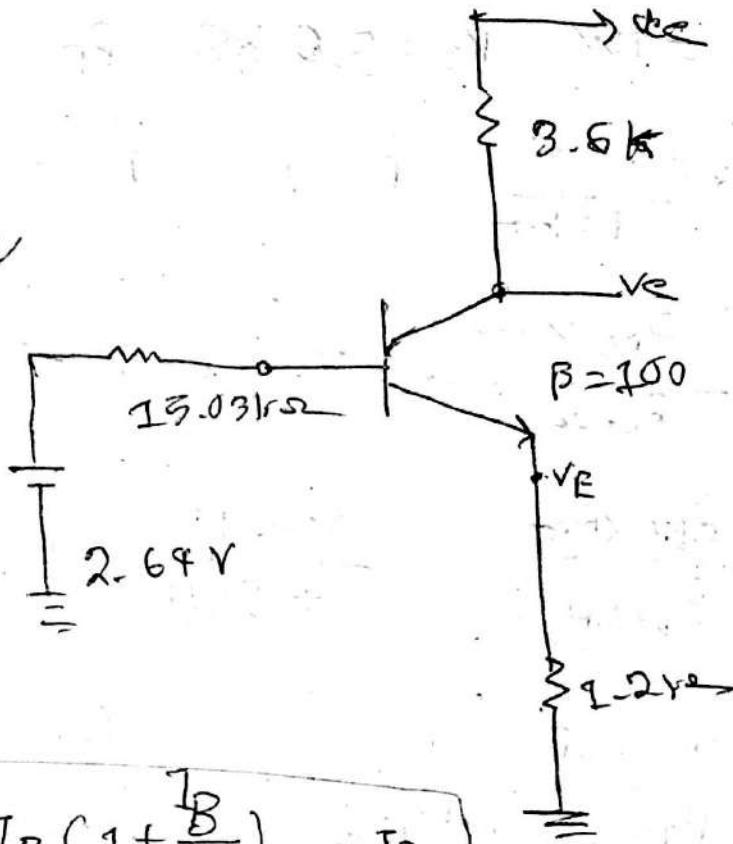
$$I_F = \frac{I_B}{I_c} \times I_B + I_B$$




$$I_F = I_B + \beta I_B = I_B \left(1 + \frac{\beta}{I_c} \right) = I_B$$

2nd CT

যদি V_{CE} ও R_E -র স্টেন্ডার্ড মান এবং ফিল্ড
ডিজাইন করতে হবে,

Exam - ১ একটি Design problem দিতে।

Emitter feedback stage

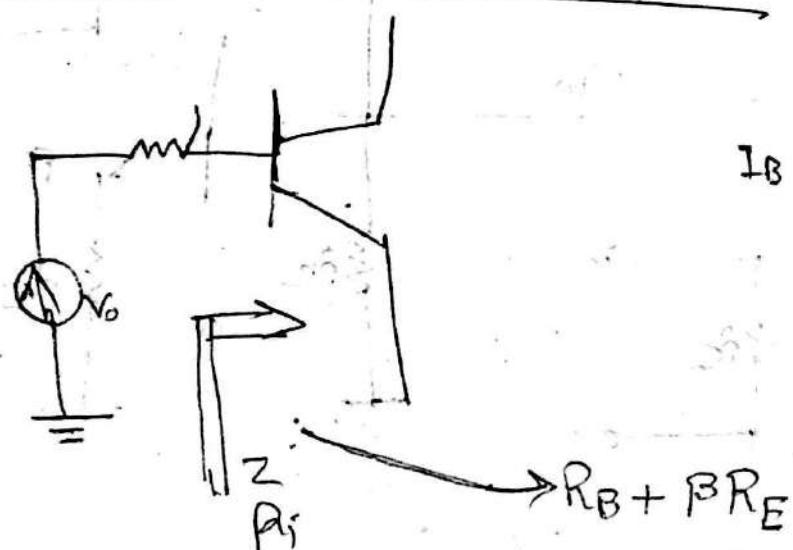



$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

Input resistance at Emitter or r_e resistance
ওসে প্রায় β times উচ্চ হবে।

$$V_{CE} - I_B R_B - V_{BE} = 0$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

(If $I_B = 90\text{mA}$)

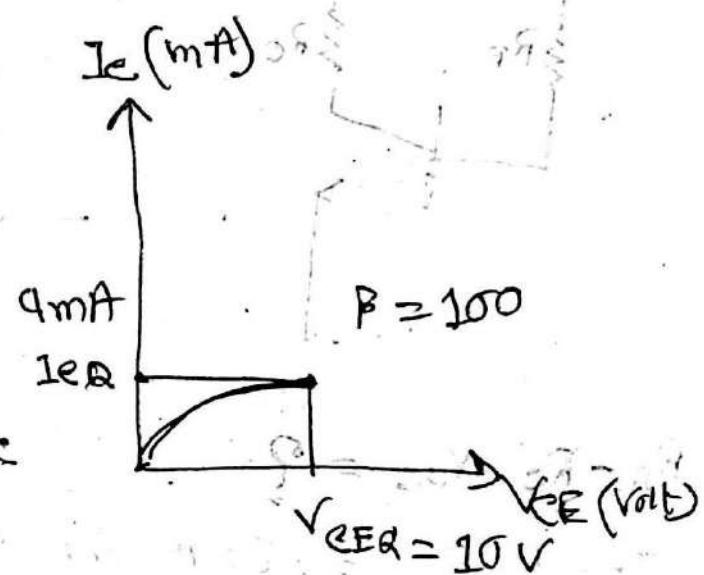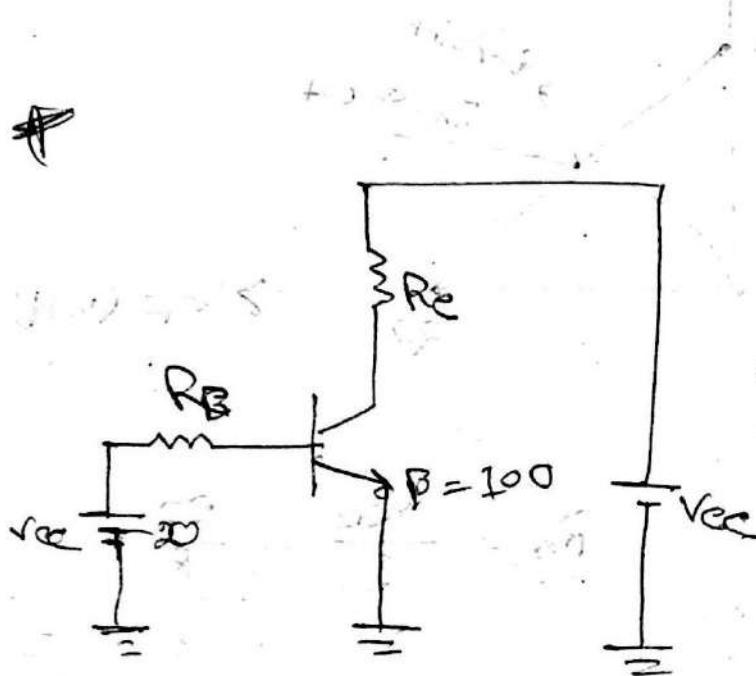

$$\beta = \frac{I_C}{I_B}$$

$$\Rightarrow I_B = 100 \times 9 = 900 \text{ mA}$$

$$V_{CC} - I_B R_B - V_{BE} =$$

$$\Rightarrow R_B = \frac{(20 - 0.7)\text{V}}{900 \text{ mA}}$$

$$= 21.875 \Omega$$

$$V_{CC} - I_C R_E - V_{CE} = 0$$

$$\Rightarrow R_E = \frac{V_{CC} - V_{CE}}{I_C}$$

V_{CE} & R_E unknown

Fairly Amplifier

- \approx V_{CC}


$V_{CE} - \text{or double}$

$$\boxed{V_{CC} = 2 V_{CE}}$$

EEE-211

7th cycle of day

26-06-2013

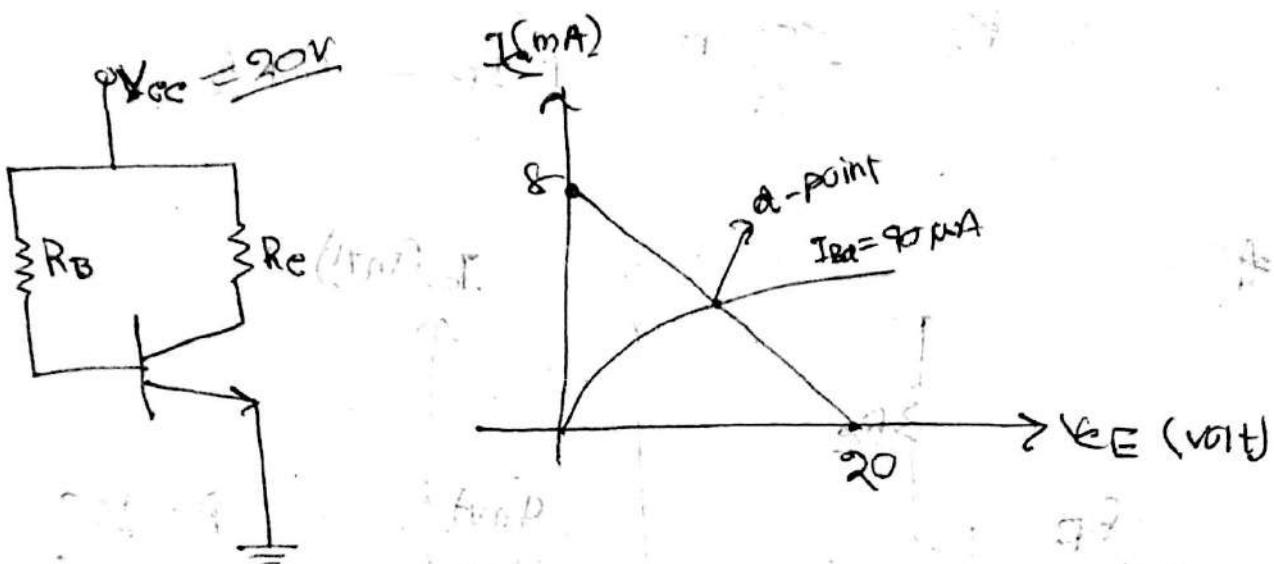

$$R_B = R_C, V_{CC} = ?$$

$$I_B = 40 \mu A, I_c = 8 mA, V_{CE} = 20$$

$$R_C = \frac{V_{CC}}{I_c} = \frac{20}{8} = 2.5 k\Omega$$

~~$$R_B = \frac{V_{BE}}{I_B} = \frac{0.7}{40mA}$$~~

$$R_B = \frac{V_{BE}}{I_B} =$$

$$V_{CC} - I_c R_C - V_{CE} = 0$$


$$\Rightarrow V_{CC} = V_{CE} \quad (I_c = 0)$$

when, $V_{CE} = 0$,

$$V_{CC} - I_c R_C = 0$$

$$\Rightarrow I_c = \frac{V_{CC}}{R_C} = 8 \times 10^{-3}$$
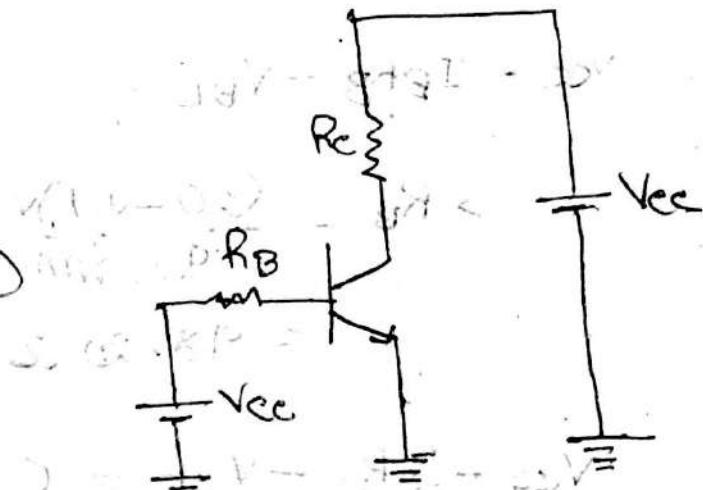
$$R_C = \frac{V_{CC}}{I_c} = \frac{20}{8}$$





Approximate Analysis:

$$I_B = \frac{V_{CE} - V_{BE}}{R_B + (\beta + 1)R_E}$$

$r_{th} = \frac{R_2 \parallel R_C}{R_1 + R_2}$

$R_1 \parallel R_2$

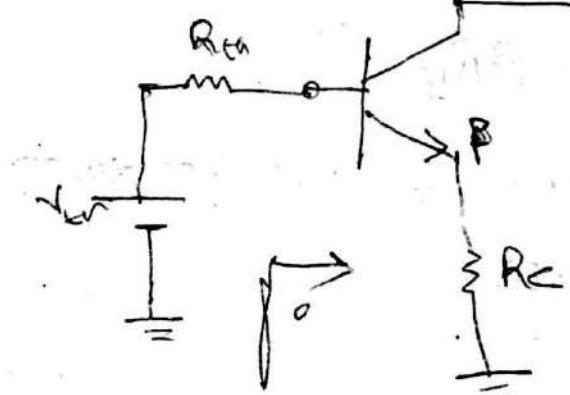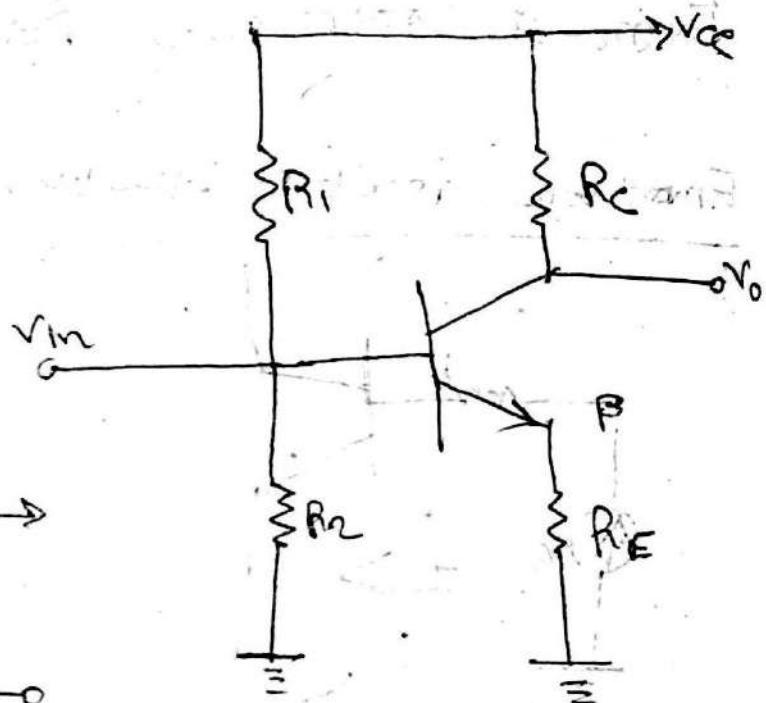

Base current approximately $I_B \approx 0$

$$\boxed{\beta R_E \gg R_2}$$

$I_B \approx 0$

$$V_B = \frac{V_{CE} R_2}{R_1 + R_{th}}$$

$$V_B = V_{BE} + I_E R_E$$

$$I_E \approx I_C \quad (I_B \text{ almost } 0)$$

$$I_E = \beta I_B$$

* I_E independent of P .

2-point - \approx variation minimizes V_{CE} when $10R_2 \leq R_E$

Exact:

$$I_B = \frac{V_{EE} - V_{BE}}{R_D + (\beta + 1)R_E}$$

$$\approx 2.07$$

$$\approx \frac{2.07}{3.545 + 241 \times 1.5}$$

$$\approx 3.56 \mu A$$

$$R_{th} = R_D || R_E$$


$$= \frac{39 \times 3.9}{39 + 3.9}$$

$$\approx 3.545$$

$$V_{th} = \frac{V_{EE} \times R_2}{R_1 + R_2}$$

$$= \frac{22 \times 3.9}{42.9}$$

$$\approx 2$$

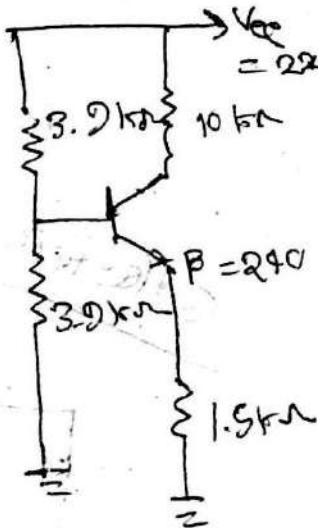

$$I_E = I_C = \beta I_B$$

$$= 240 \times 3.56 \text{ mA}$$

$$= 0.854 \text{ mA}$$

$$I_E = I_B + I_C = 0.8582 \text{ mA}$$

$$V_{CE} - I_C R_C - V_{EE} - (I_B + I_C) R_B = 0$$

$$\Rightarrow V_{CE} = 12.21 \text{ V}$$



Approximate:

$$V_{CC} - I_C R_E - V_{BE} - \beta I_C R_C < 0$$

$$\Rightarrow V_{BE} = V_{CC} - I_C (R_E + R_C)$$

$$= 12.285 \checkmark$$


Opamp for feedback

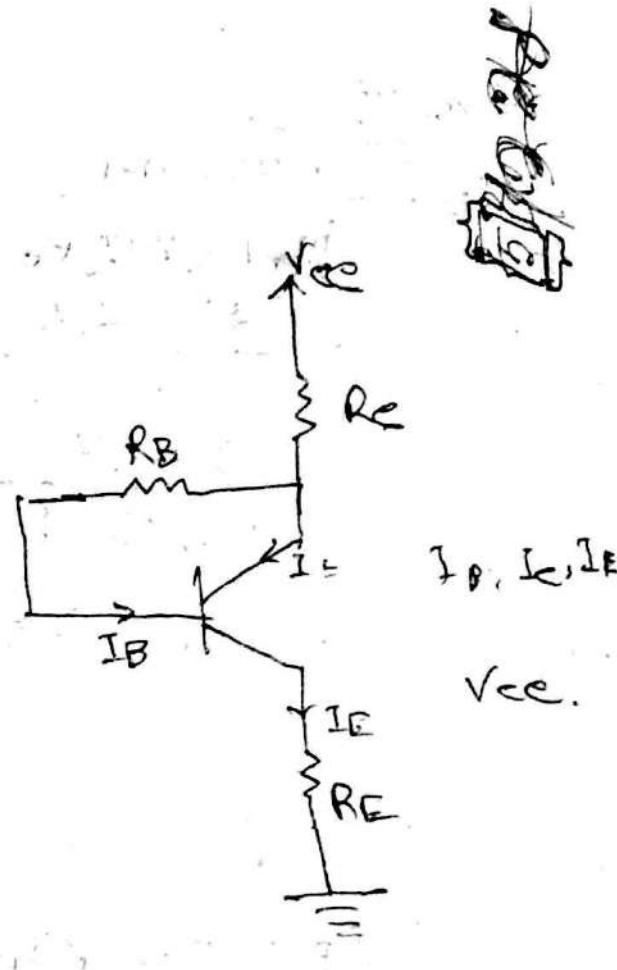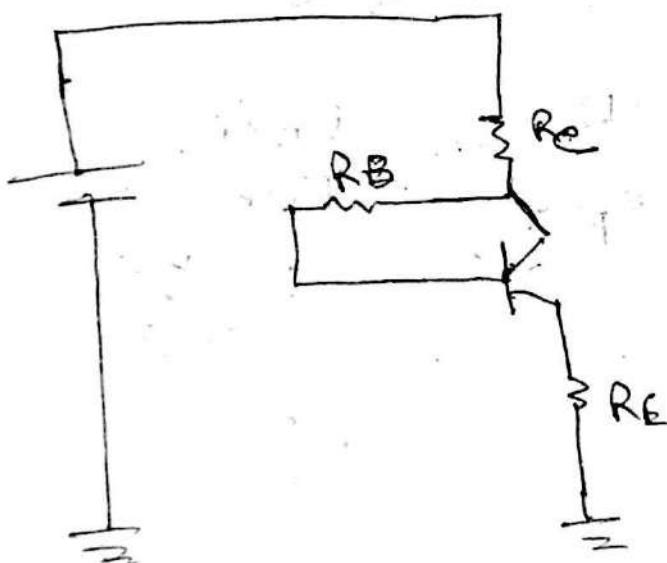

$$V_{CC} - I_E R_E - (I_B + I_C) R_C - I_B R_B - V_{BE} = 0$$

$$\Rightarrow V_{CC} - I_B R_B - (I_B + \beta I_B) R_C - V_{BE} - (\beta + 1) R_E I_E = 0$$
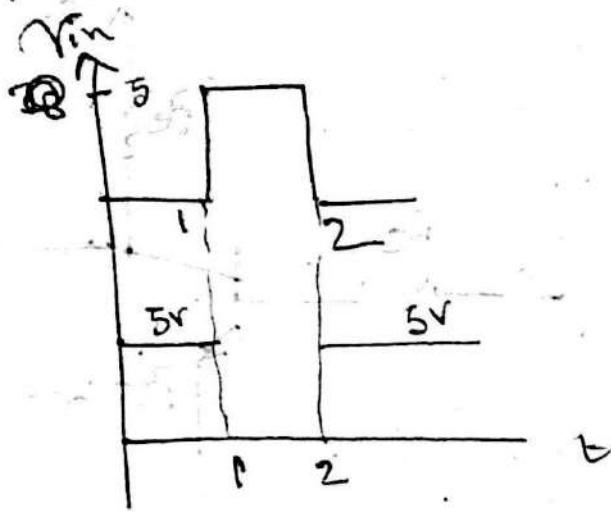
$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)(\beta R_C + R_E)}$$



Input low \rightarrow output high

Input high \rightarrow output low

not gate



X

1

0

X
0

1

Digital circuit \rightarrow high volt
 $5V \rightarrow$ logic 1

Digit " \rightarrow low volt
 either 0 or $-5V$.

logic 0.

$$I_B = \frac{V_0 - 0.7}{R_B} = I_C = \beta I_B$$

Ideal switch \rightarrow output volt 0.

$I_C > I_{C\text{sat}}$

$I_C = I_{C\text{sat}} \rightarrow$ soft saturation.

Or saturation হলি transistor আৰু নিৰে গুৱাত পাৰে এই
 মেঘ আৰু নিৰে গুৱাত এই অবস্থা Hard saturation.

Switch-এই কোন Hard saturation -এ হৈত দুবে আৰে P
 vary-এই কোন se change এই $I_C > I_{C\text{sat}}$.

EEE-211


8th cycle 1st day

06 July 2013

BJT as a switch



Switch OFF \rightarrow cut off

on \rightarrow saturation.

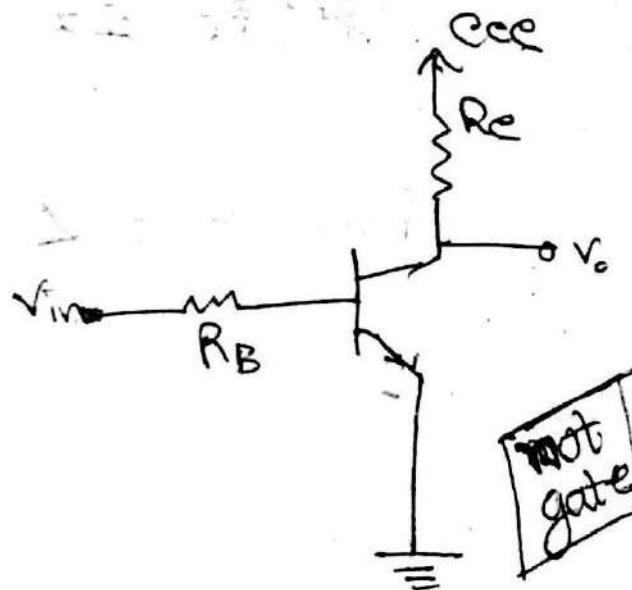

Input voltage $< 0.7 \text{ V}$. ২৮

circuit cut off অবস্থা,

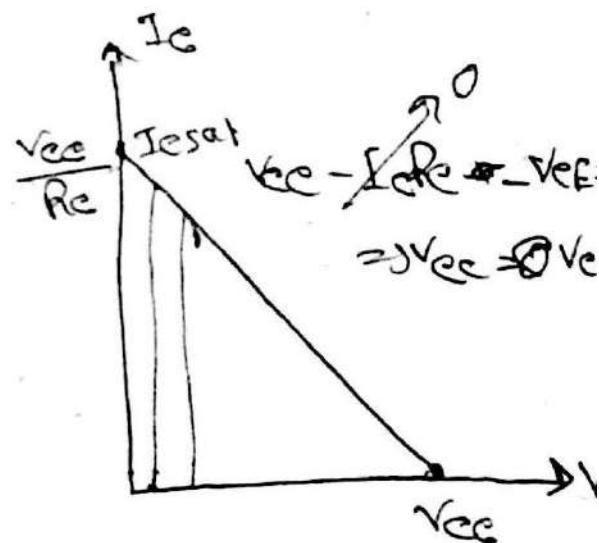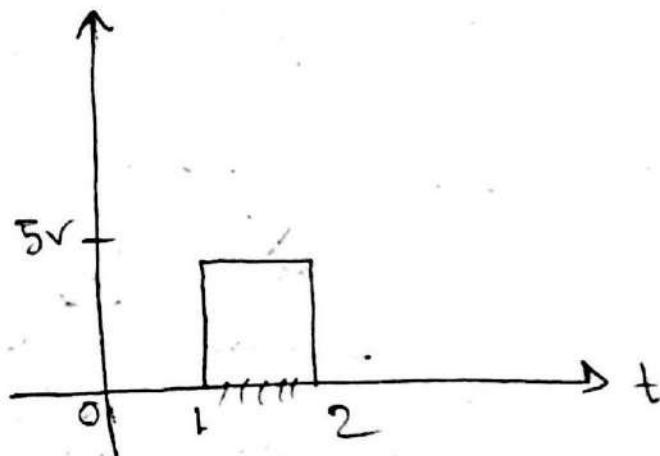

Input $V_{in} = 0$, $I_B = 0$, $I_C = 0$, $V_{ce} = 5\text{V}$

Collector resistance ও এর প্রযুক্তি ও সুবিধা


$$(P+1)R_E \xrightarrow{\text{হচ্ছে}} (P+1)(R_C + R_E) \text{ এর হচ্ছে } P > 1$$



Fixed bias < Emitter feedback bias < collector
voltage-divider bias
feedback & bias
-এর stability.

npn - এর use সুবিধা.

pnp - এর use limited.

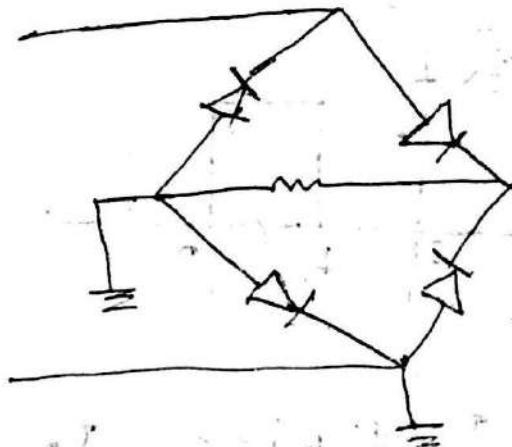AC volt. এল r-ve dc voltage দেওয়া
difficult.



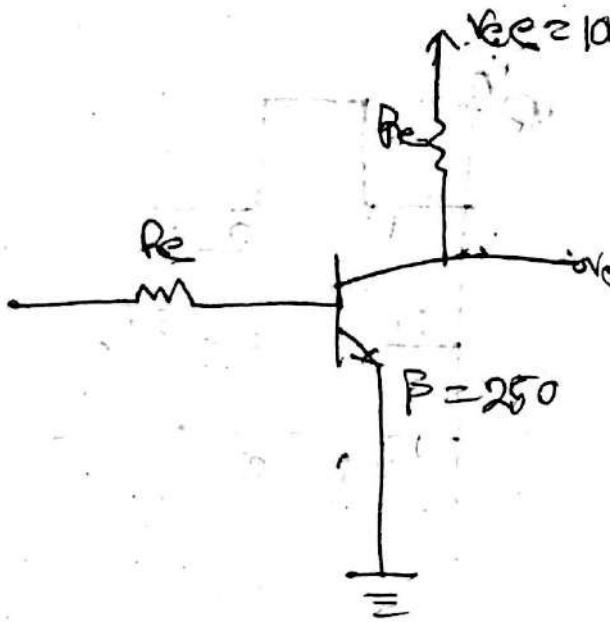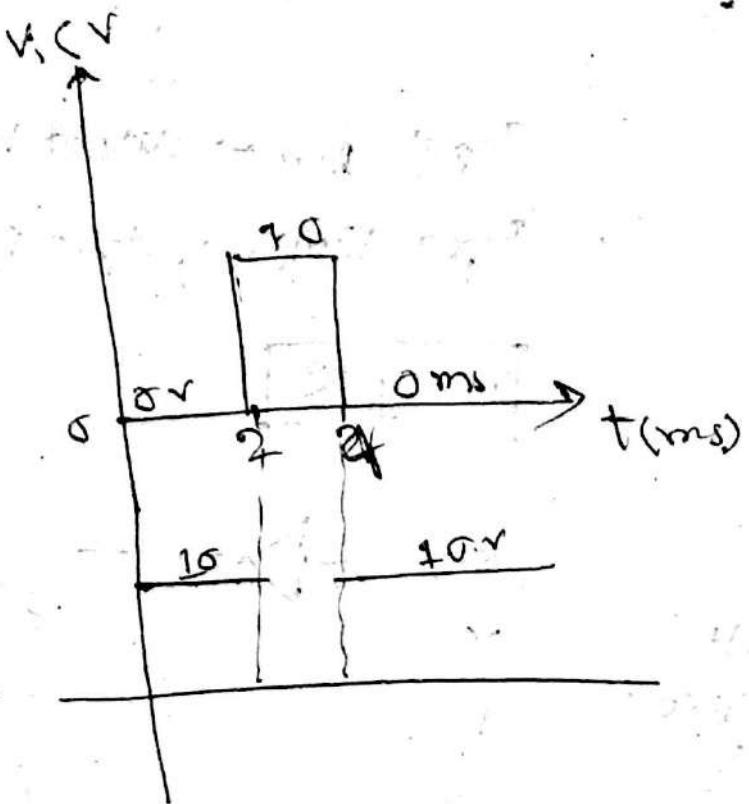

$$I_{C\text{sat}} = 10 \text{ mA}$$

$t = 0 - 2$ and $4 >$ Base-E current ≥ 2

output $+10$

$$I_{B\text{sat}} = \frac{V_{CE}}{R_E} = 10 \text{ mA}$$

$$\Rightarrow R_E = 1k\Omega$$

$$\text{Saturation-E current, } I_{BS\text{sat}} = \frac{I_{C\text{sat}}}{\beta} = \frac{10 \text{ mA}}{250} \\ = 40 \mu\text{A}$$

$I_{B>\text{sat}}$ OR after saturation-E from one cut

hard saturation-E $\geq 10\mu\text{A}$,



$I_{B\text{sat}}$ must be $> 40 \mu\text{A}$.

Let, $I_B = 50\mu A$. এখন R_B কত হবে?

$$I_B = \frac{V_i - V_{BE}}{R_B}$$

$$\Rightarrow R_B = \frac{10 - 0.7}{50}$$

(এখন নির্ণয় করো স্বিচ ভিত্তি দ্রুতি কত)

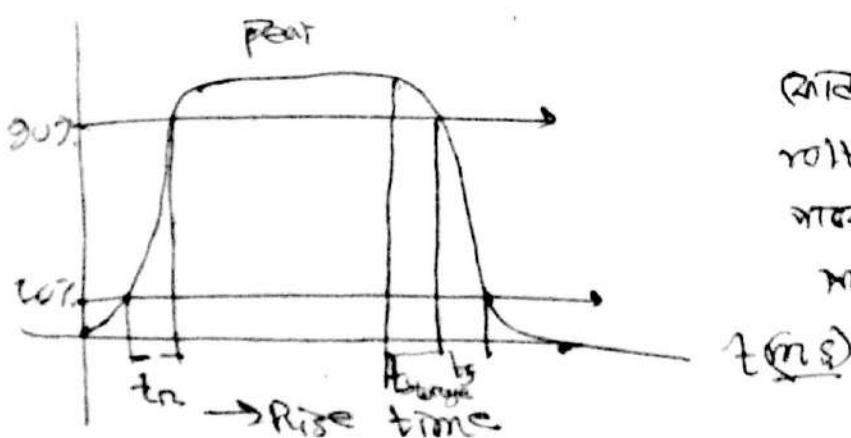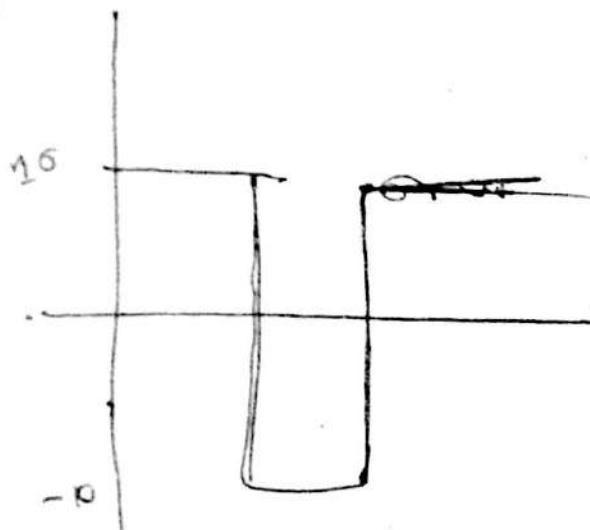

দিয়ে দেবে $t=0$ থেকে
বলে আর / স্বিচ হও
মানে কি?

$V_{BE} = 5$ মভ. $5 - 0.7 = 10 - 90\%$ হও আর কথা

অরু R_{on} time

$0 - 10\%$ মভ. delay time

delay time + rise time = On time ($0 - 90\%$)

Fall - or errors after storage time

90% - 10% = 10% fall time

Storage time + fall time \rightarrow off time

10% - 10%

Off time = 10% + 10% = 20%

out of storage time

10% + 10% = 20%

Out of storage time

Storage

10%

fall time 10%

10% + 10% = 20% off time

Storage time 10%

fall time 10%

10% + 10% = 20% off time