 


Final Register Set Design

Nahin Ul Sadad
Lecturer
CSE, RUET

Register Set Review

4-bit Register Set (Reading)



Suppose, Register set has eight 4-bit registers.

Since Register Set has 8 registers, it will need $\log_2 8 = 3$ address lines.

Since registers are 4-bit registers, so it will store 4-bit value.


Reading in
Register Set

Ra will take address of register and show value stored in that register in **a (4-bit value)**.

and

Rb will take address of register and show value stored in that register in **b (4-bit value)**.

4-bit Register Set (Reading)

 

**R2 register
has 0011
(3) value
stored.**

**R7 register
has 0010
(2) value
stored.**

**Reading in
Register Set**


Address	Register	Value stored
000	R0	0111 (7)
001	R1	0100 (4)
010	R2	0011 (3)
011	R3	0111 (7)
100	R4	1000 (8)
101	R5	0001 (1)
110	R6	1000 (8)
111	R7	0010 (2)

Ra will take address of register and show value stored in that register in a (4-bit value).

and

Rb will take address of register and show value stored in that register in b (4-bit value).

4-bit Register Set (Writing)

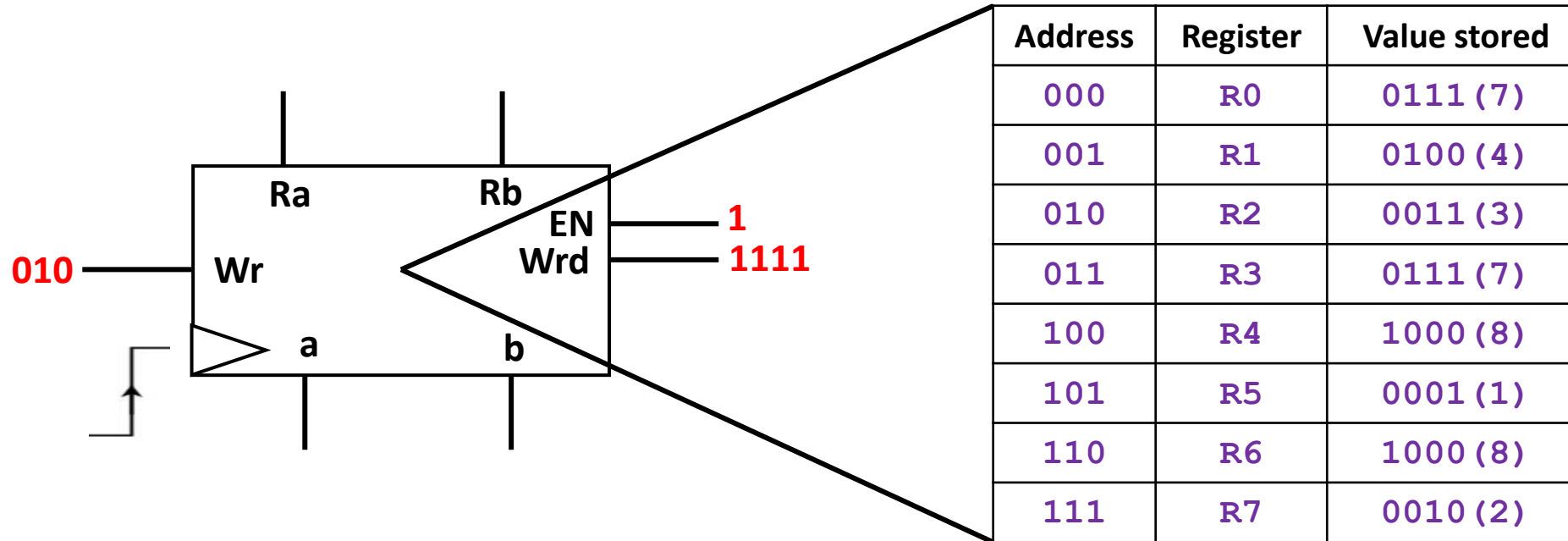

What will happen?

Writing in
Register Set

EN will enable/disable writing operation in register set.
(1-Enable/0-Disable)


and

Wr will take address of register to be written.

and

Wrd will take (4-bit value) value to be written in **Wr** register.

4-bit Register Set (Writing)

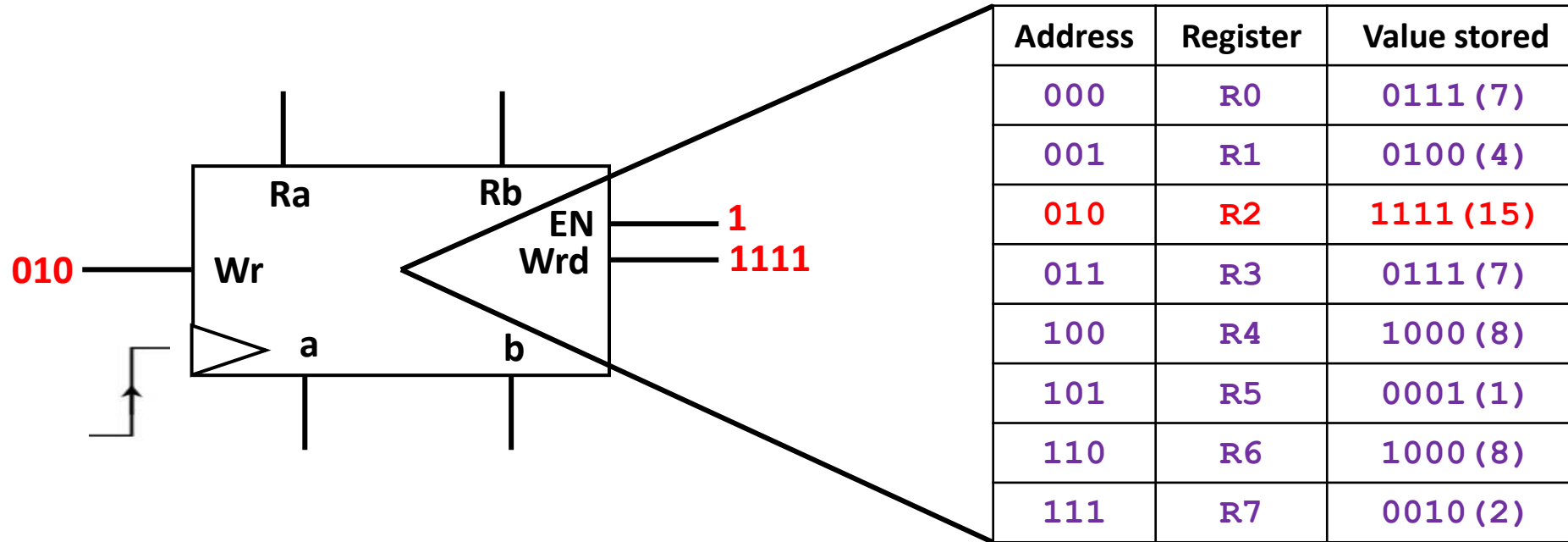

What will happen?

Writing in
Register Set

EN will enable/disable writing operation in register set.
(1-Enable/0-Disable)

and

Wr will take address of register to be written.

and

Wrd will take (4-bit value) value to be written in **Wr** register.

Final Register Set Design

Register Set

Register Set chip is shown below:

 


Figure: 4-bit Register Set with 8 Registers Chip

Here,

Ra = Register A

Rb = Register B

A = Data of Register A

B = Data of Register B

Wr = Register to be written

Wrd = Data to be written in Wr

REG_EN = Write in Register Enable


InRData = Data to be written in Input Register

InR_EN = Write Enable in Input Register

OutRD = Data in Output Register

1-bit Register Cell

1-bit Register

 

1-bit Register


 
 


Figure: 1-bit Register Chip

4-bit Register Cell

4-bit Register

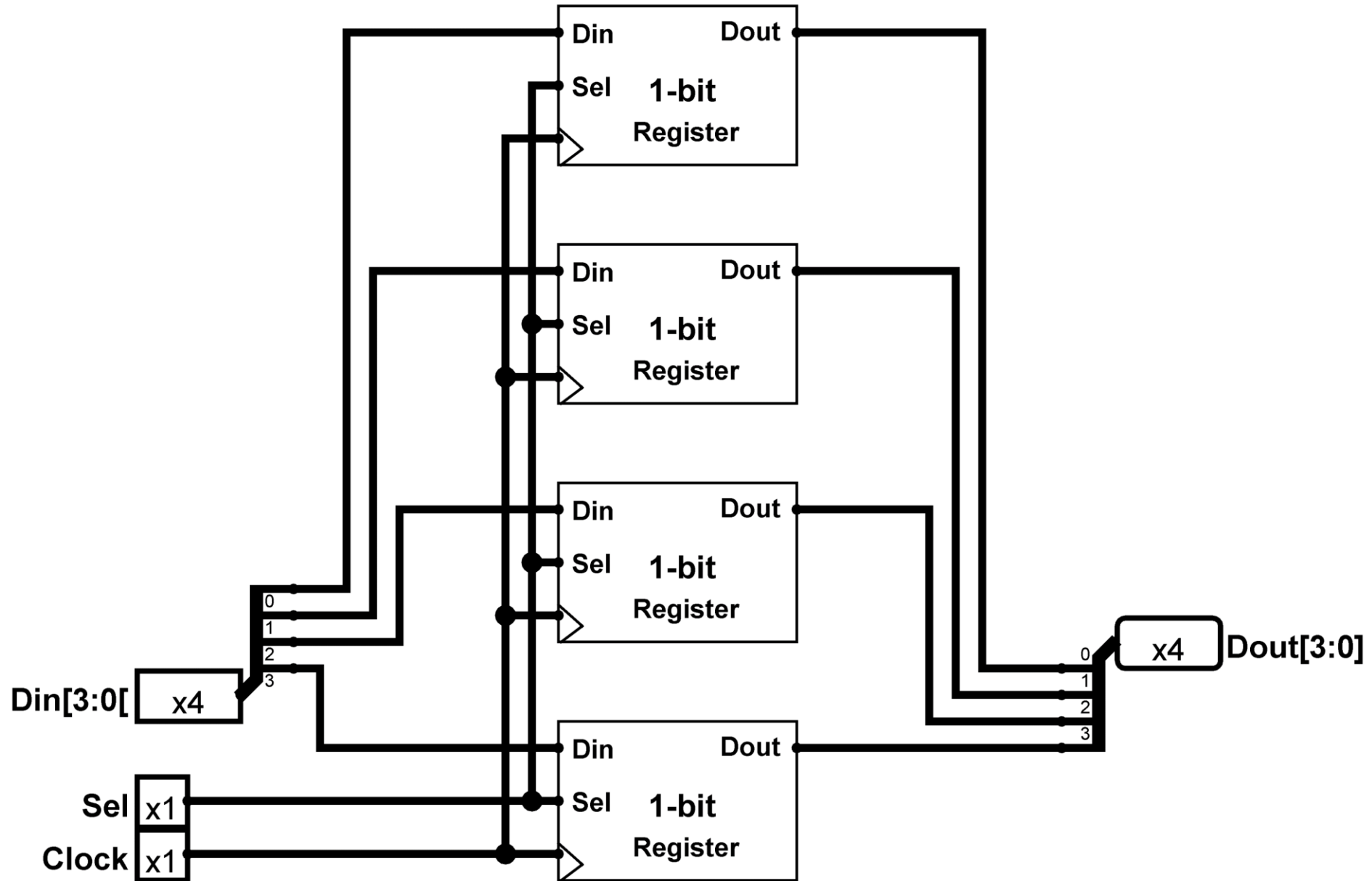

4-bit Register


 
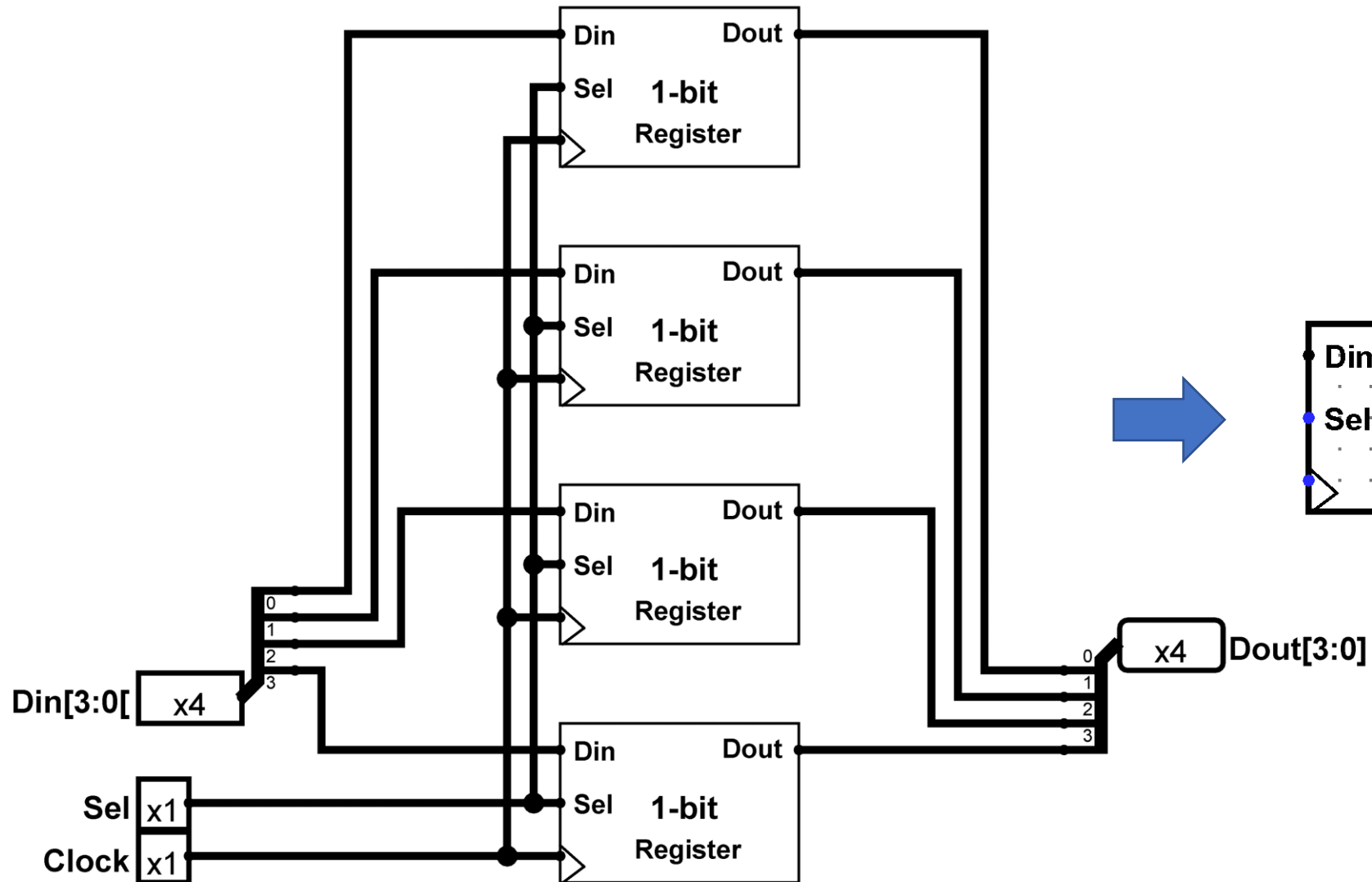


Figure: 4-bit Register Chip

4-bit Register Set with 8 Registers

4-bit Register Set with 8 Registers

 

4-bit Register Set with 8 Registers


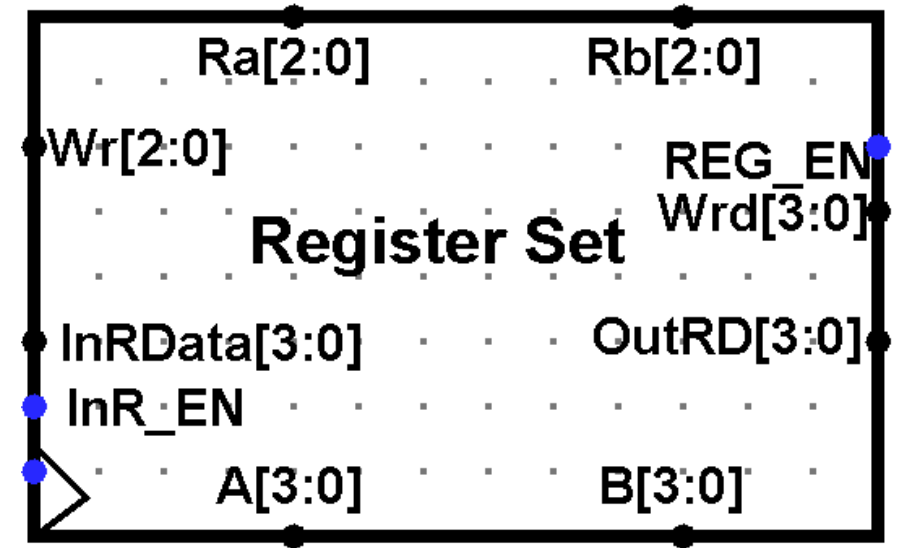
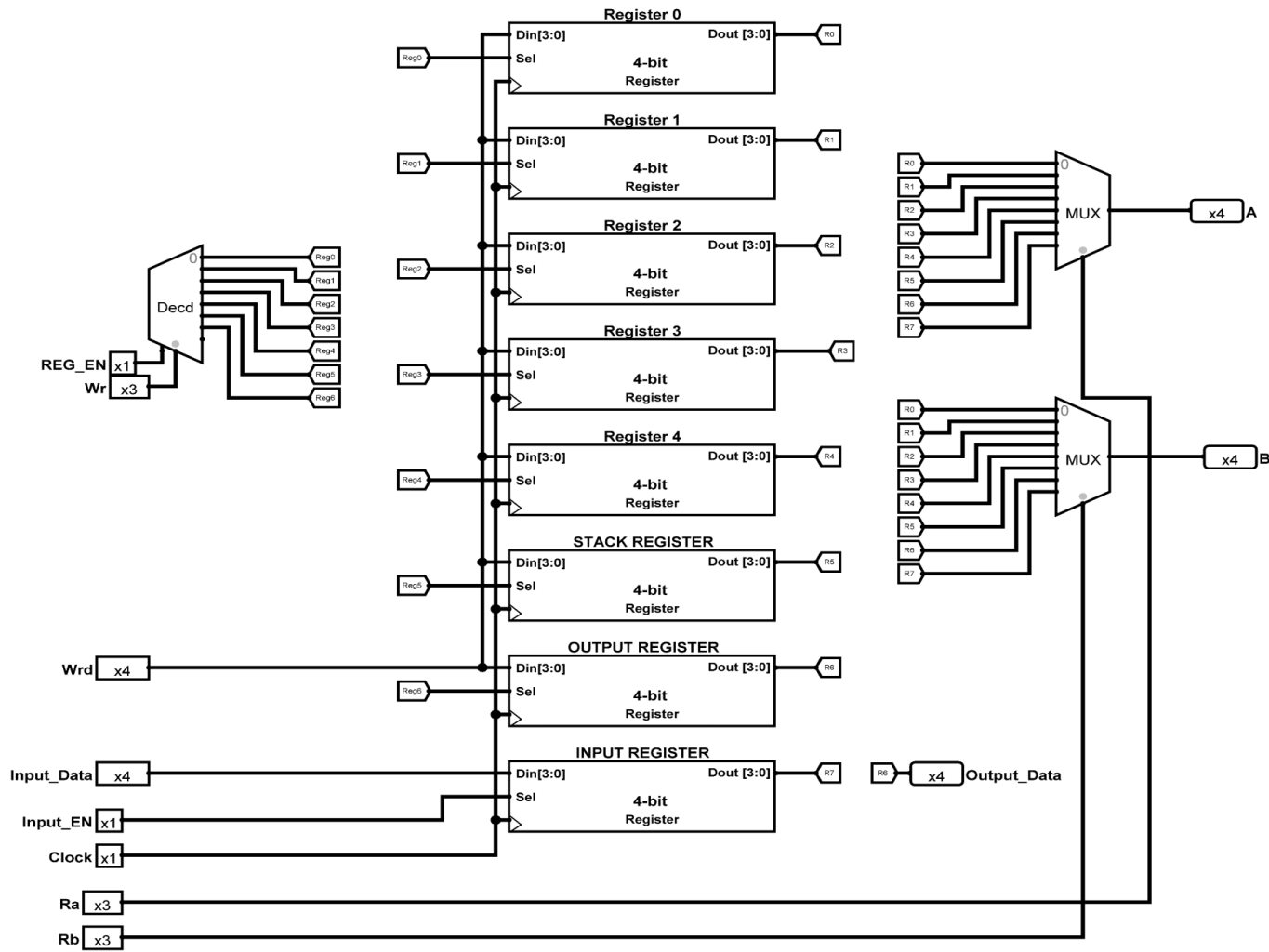


Figure: 4-bit Register Set with 8 Registers Chip

4-bit FLAG Register

4-bit FLAG Register

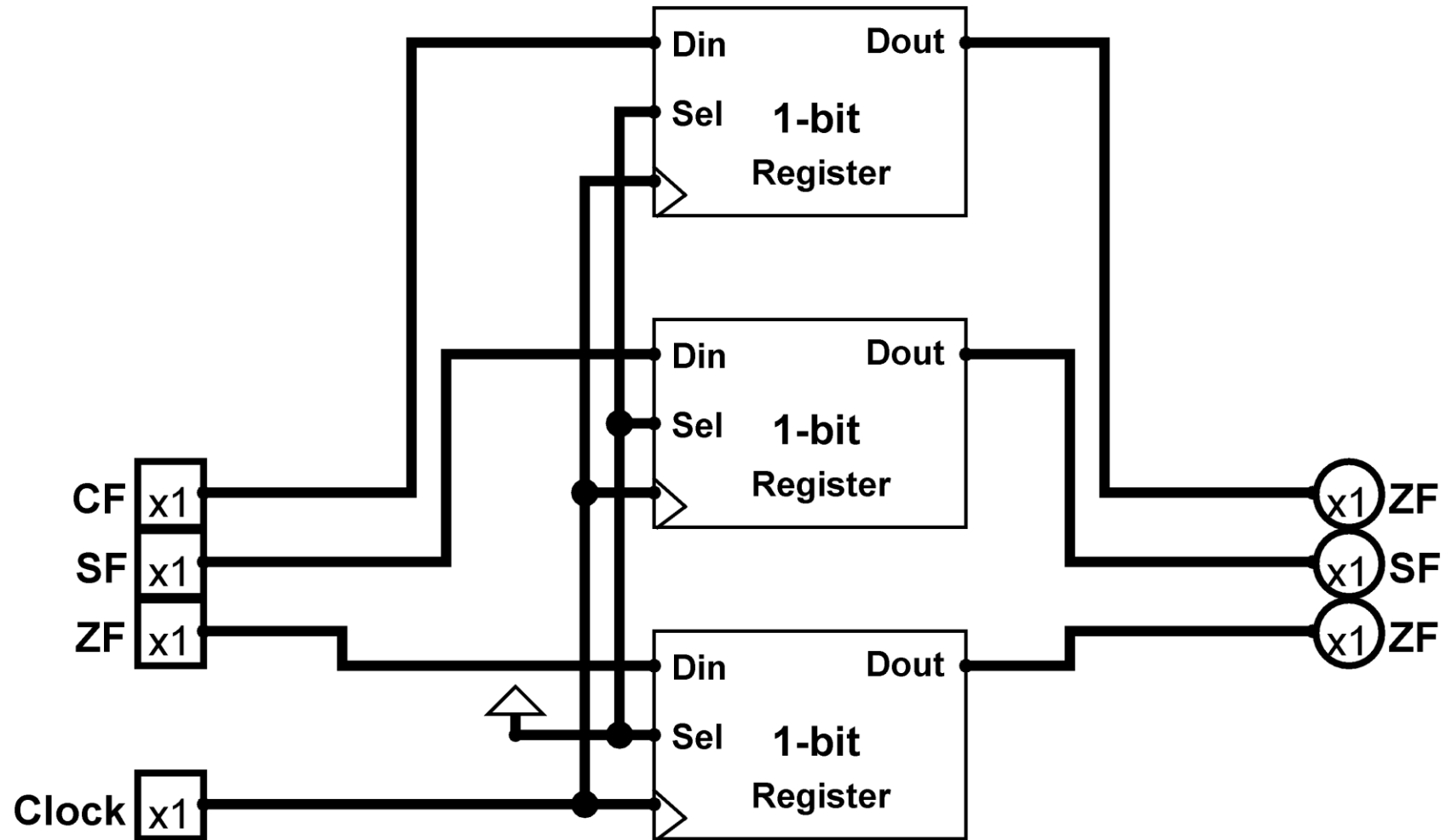

4-bit Register Set with 8 Registers

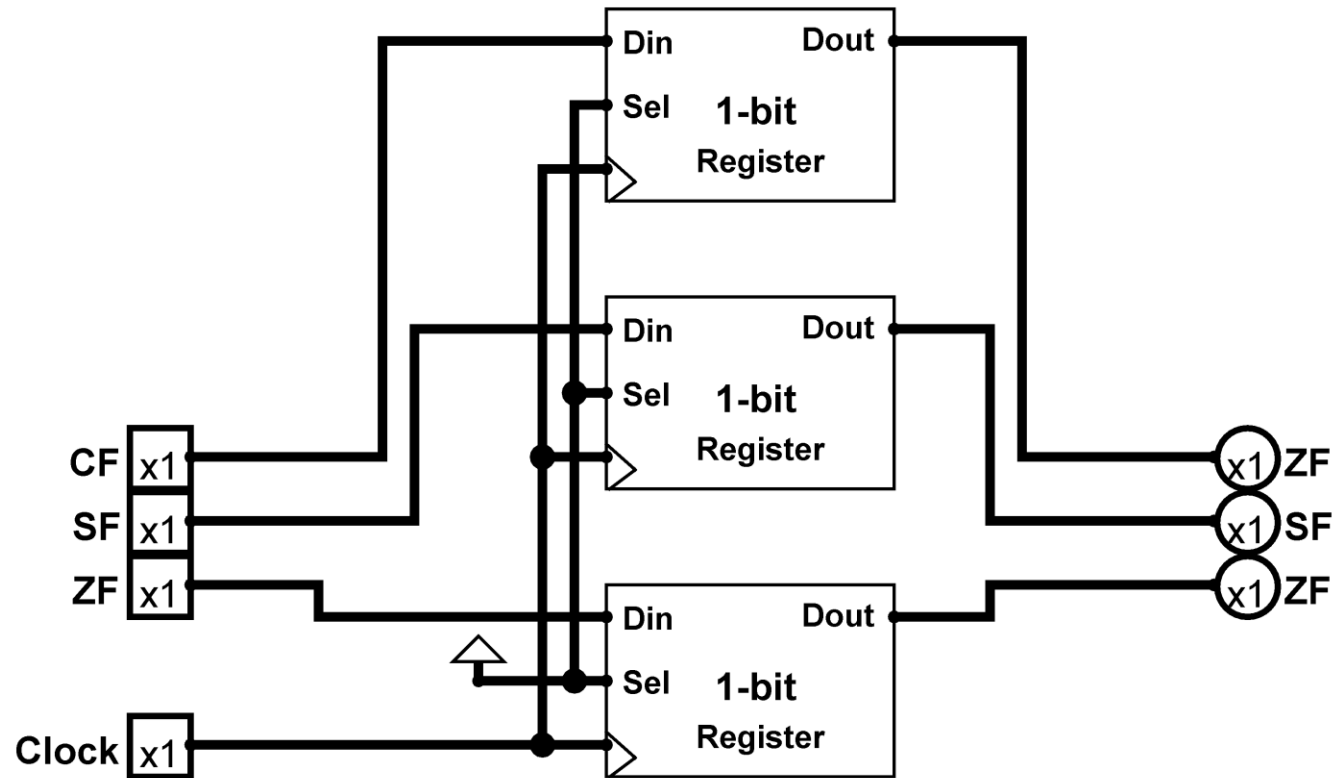


Figure: FLAG Register

Thank You 😊