

Example K-map simplification

- Let's consider simplifying $f(x,y,z) = xy + y'z + xz$.
- First, you should convert the expression into a sum of minterms form, if it's not already.
 - The easiest way to do this is to make a truth table for the function, and then read off the minterms.
 - You can either write out the literals or use the minterm shorthand.
- Here is the truth table and sum of minterms for our example:

x	y	z	$f(x,y,z)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned}f(x,y,z) &= x'y'z + xy'z + xyz' + xyz \\ &= m_1 + m_5 + m_6 + m_7\end{aligned}$$

Unsimplifying expressions

- You can also convert the expression to a sum of minterms with Boolean algebra.
 - Apply the distributive law in reverse to add in missing variables.
 - Very few people actually do this, but it's occasionally useful.

$$\begin{aligned}xy + y'z + xz &= (xy \cdot 1) + (y'z \cdot 1) + (xz \cdot 1) \\&= (xy \cdot (z' + z)) + (y'z \cdot (x' + x)) + (xz \cdot (y' + y)) \\&= (xyz' + xyz) + (x'y'z + xy'z) + (xy'z + xyz) \\&= xyz' + xyz + x'y'z + xy'z\end{aligned}$$

- In both cases, we're actually "unsimplifying" our example expression.
 - The resulting expression is larger than the original one!
 - But having all the individual minterms makes it easy to combine them together with the K-map.

Making the example K-map

- Next up is drawing and filling in the K-map.
 - Put 1s in the map for each minterm, and 0s in the other squares.
 - You can use either the minterm products or the shorthand to show you where the 1s and 0s belong.
- In our example, we can write $f(x,y,z)$ in two equivalent ways.

$$f(x,y,z) = x'y'z + xy'z + xyz' + xyz$$

		y			
		$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
X		$xy'z'$	$xy'z$	xyz	xyz'

$$f(x,y,z) = m_1 + m_5 + m_6 + m_7$$


		y			
		m_0	m_1	m_3	m_2
X		m_4	m_5	m_7	m_6

- In either case, the resulting K-map is shown below.

		y			
		0	1	0	0
X		0	1	1	1

K-maps from truth tables

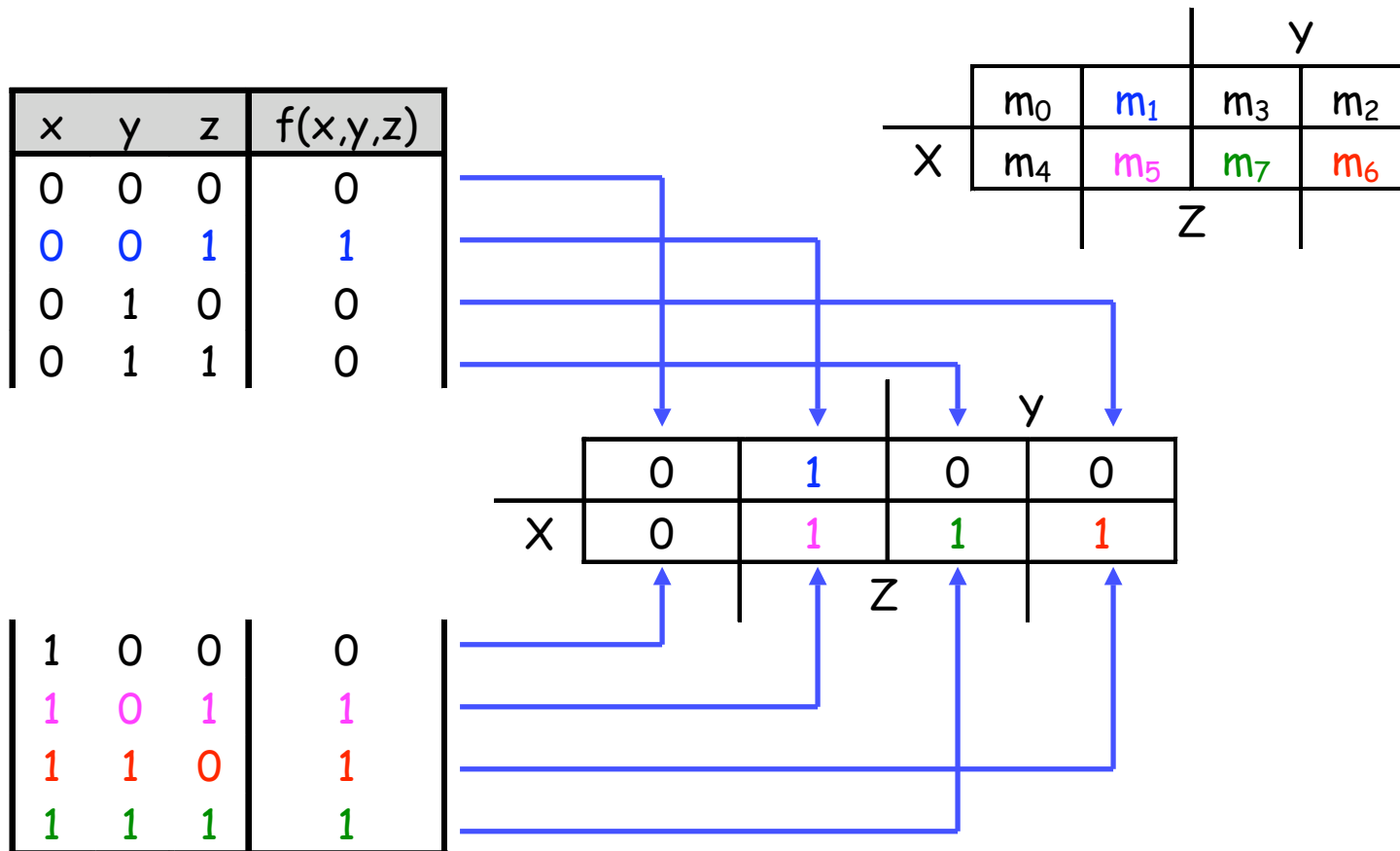- You can also fill in the K-map directly from a truth table.
 - The output in row i of the table goes into square m_i of the K-map.
 - Remember that the rightmost columns of the K-map are "switched."



Grouping the minterms together

- The most difficult step is grouping together all the 1s in the K-map.
 - Make **rectangles** around groups of one, two, four or eight 1s.
 - All of the 1s in the map should be included in at least one rectangle.
 - Do *not* include any of the 0s.

			y	
	0	1	0	0
x	0	1	1	1
		z		

- Each group corresponds to one product term. For the simplest result:
 - Make as few rectangles as possible, to minimize the number of products in the final expression.
 - Make each rectangle as large as possible, to minimize the number of literals in each term.
 - It's all right for rectangles to overlap, if that makes them larger.

Reading the MSP from the K-map

- Finally, you can find the MSP.
 - Each rectangle corresponds to one product term.
 - The product is determined by finding the common literals in that rectangle.

			y	
	0	1	0	0
x	0	1	1	1
		z		

			y	
	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
x	$xy'z'$	$xy'z$	xyz	xyz'

- For our example, we find that $xy + y'z \neq xz = y'z + xy$. (This is one of the additional algebraic laws from last time.)

Practice K-map 1

- Simplify the sum of minterms $m_1 + m_3 + m_5 + m_6$.

			y
X			
		Z	

			y	
	m ₀	m ₁	m ₃	m ₂
x	m ₄	m ₅	m ₇	m ₆
		Z		

Solutions for practice K-map 1

- Here is the filled in K-map, with all groups shown.
 - The magenta and green groups overlap, which makes each of them as large as possible.
 - Minterm m_6 is in a group all by its lonesome.

				y
	0	1	1	0
x	0	1	0	1
			z	

- The final MSP here is $x'z + y'z + xyz'$.

Four-variable K-maps

- We can do four-variable expressions too!
 - The minterms in the third and fourth columns, *and* in the third and fourth rows, are switched around.
 - Again, this ensures that adjacent squares have common literals.

		y		
		w'x'y'z'	w'x'y'z	X
		w'x'yz'	w'x'yz	
W	wxy'z'	wxy'z	wxyz	
	wx'y'z'	wx'y'z	wx'yz	
		Z		

		y		
		m ₀	m ₁	X
		m ₄	m ₅	
W	m ₁₂	m ₁₃	m ₁₅	
	m ₈	m ₉	m ₁₁	
		Z		

- Grouping minterms is similar to the three-variable case, but:
 - You can have rectangular groups of 1, 2, 4, 8 or 16 minterms.
 - You can wrap around *all four* sides.

Example: Simplify $m_0 + m_2 + m_5 + m_8 + m_{10} + m_{13}$

- The expression is already a sum of minterms, so here's the K-map:

		y				
		1	0	0	1	
		0	1	0	0	
w	0	1	0	0		x
	1	0	0	1		
		z				

		y				
		m_0	m_1	m_3	m_2	
		m_4	m_5	m_7	m_6	
W	m_{12}	m_{13}	m_{15}	m_{14}		X
	m_8	m_9	m_{11}	m_{10}		
		Z				


- We can make the following groups, resulting in the MSP $x'z' + xy'z$.

		y				
		1	0	0	1	
		0	1	0	0	
w	0	1	0	0		x
	0	1	0	0		
		z				
		1	0	0	1	

				y		
		$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$	
		$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$	
W	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$		X
	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$		
		Z				

K-maps can be tricky!

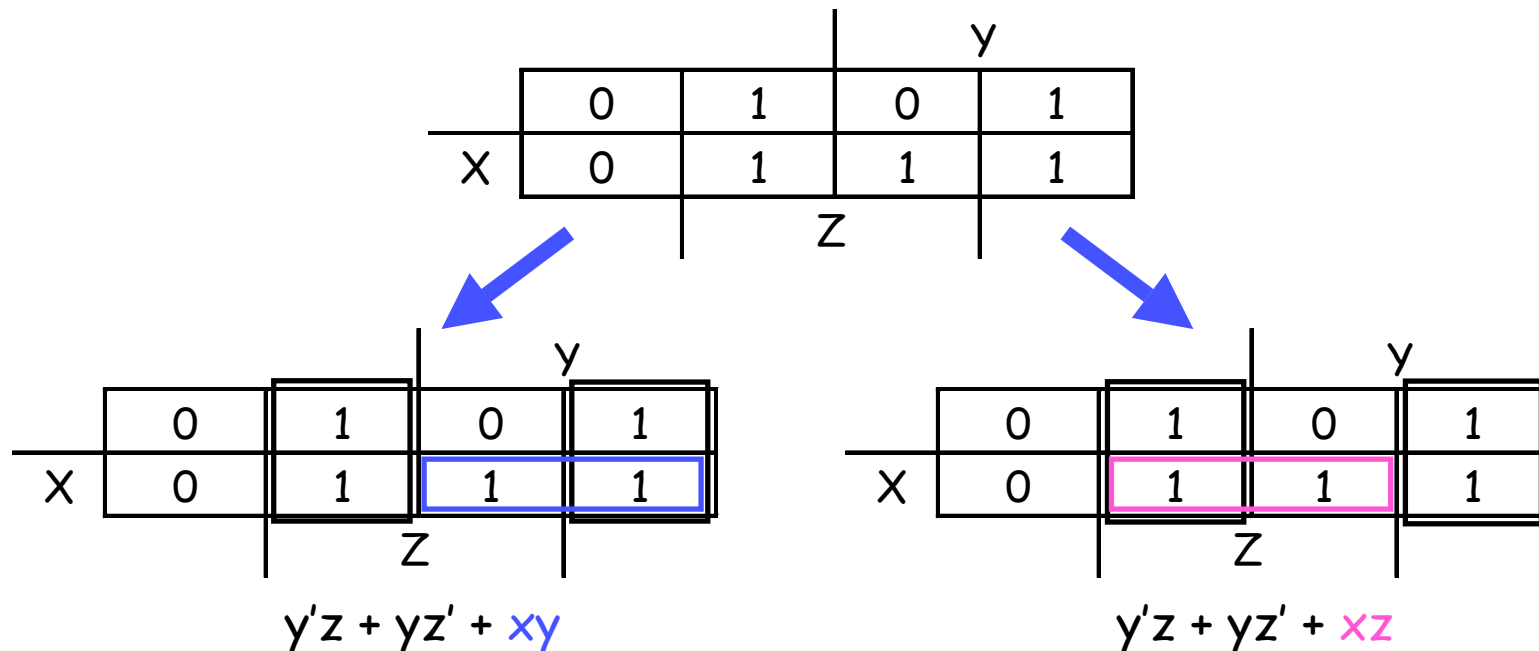
- There may not necessarily be a *unique* MSP. The K-map below yields two valid and equivalent MSPs, because there are two possible ways to include minterm m_7 .



- Remember that overlapping groups is possible, as shown above.

Prime implicants

- The challenge in using K-maps is selecting the right groups. If you don't minimize the number of groups and maximize the size of each group:
 - Your resulting expression will still be equivalent to the original one.
 - But it won't be a *minimal* sum of products.
- What's a good approach to finding an actual MSP?
- First find all of the largest possible groupings of 1s.
 - These are called the **prime implicants**.
 - The final MSP will contain a subset of these prime implicants.
- Here is an example Karnaugh map with prime implicants marked:

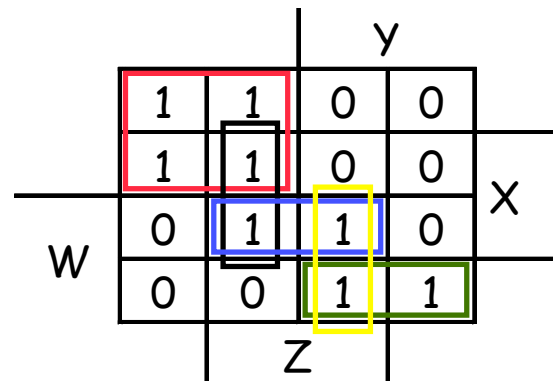

A 4x4 grid representing a 2D spatial domain with axes X, Y, Z, and W. The grid contains binary values (0 or 1). A red box highlights a 2x2 region of 1s in the top-left. A black box highlights a 2x2 region of 1s in the top-right. A blue box highlights a 2x2 region of 1s in the bottom-left. A yellow box highlights a 2x2 region of 1s in the bottom-right. A green box highlights a 2x2 region of 1s in the bottom-right. The axes are labeled X, Y, Z, and W.

- 13

A 4x4 grid representing a 2D array with dimensions $W=4$ and $H=4$. The grid contains values 0 and 1. A red box highlights a 2x2 region of 1s at (0,0) to (1,1). A blue box highlights a 2x2 region of 1s at (1,1) to (2,2). A yellow box highlights a 2x2 region of 1s at (2,2) to (3,3). A green box highlights a 2x2 region of 1s at (3,2) to (4,3). The axes are labeled W , H , and Z .

- Finally pick as few other prime implicants as necessary to ensure that all the minterms are covered.
- After choosing the red and green rectangles in our example, there are just two minterms left to be covered, m_{13} and m_{15} .
 - These are both included in the blue prime implicant, wxz .
 - The resulting MSP is $w'y' + wxz + wx'y$.
- The black and yellow groups are not needed, since all the minterms are covered by the other three groups.

Practice K-map 2

- Simplify for the following K-map:

		y			
		0	0	1	0
		1	0	1	1
w		1	1	1	1
		0	0	1	0
		z			

Solutions for practice K-map 2

- Simplify for the following K-map:

			y	
	0	0	1	0
	1	0	1	1
w	1	1	1	1
	0	0	1	0
			z	

All prime implicants are circled.

Essential prime implicants are xz' , wx and yz .

The MSP is $xz' + wx + yz$.
(Including the group xy would be redundant.)

I don't care!

- You don't always need all 2^n input combinations in an n -variable function.
 - If you can guarantee that certain input combinations never occur.
 - If some outputs aren't used in the rest of the circuit.
- We mark don't-care outputs in truth tables and K-maps with Xs.

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	1
0	1	0	X
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	X
1	1	1	1

- Within a K-map, each X can be considered as either 0 or 1. You should pick the interpretation that allows for the most simplification.

Example: Seven Segment Display

Input: digit encoded as 4 bits: ABCD

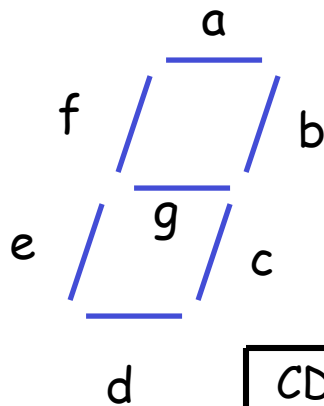


Table for e

Assumption: Input represents a legal digit (0-9)

CD \ AB	00	01	11	10
00	1	0	0	1
01	0	0	0	1
11	X	X	X	X
10	1	0	X	X

$$CD' + B'D'$$

	A	B	C	D	e
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
X					X
X					X
X					X
X					X
X					X
X					X
X					X

Example: Seven Segment Display

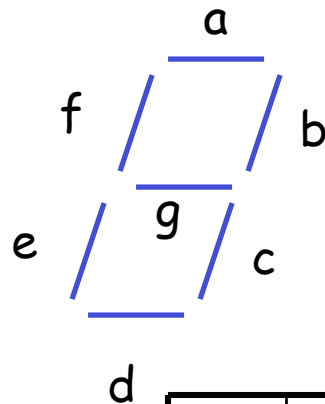


Table for a

CD \ AB	00	01	11	10
00	1		1	1
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$$A + C + BD + B'D'$$

	A	B	C	D	a
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
X					X
X					X
X					X
X					X
X					X
X					X

Practice K-map 3

- Find a MSP for

$$f(w,x,y,z) = \sum m(0,2,4,5,8,14,15), d(w,x,y,z) = \sum m(7,10,13)$$

This notation means that input combinations $wxyz = 0111, 1010$ and 1101 (corresponding to minterms m_7, m_{10} and m_{13}) are unused.

		y		
		1	0	
w	1	0	0	1
	1	1	x	0
	0	x	1	1
	1	0	0	x
		z		

Solutions for practice K-map 3

- Find a MSP for:

$$f(w,x,y,z) = \sum m(0,2,4,5,8,14,15), d(w,x,y,z) = \sum m(7,10,13)$$

				y	
		1	0	0	1
		1	1	x	0
W		0	x	1	1
		1	0	0	x
					z

All prime implicants are circled. We can treat X's as 1s if we want, so the red group includes two X's, and the light blue group includes one X.

The *only* essential prime implicant is $x'z'$. The red group is not essential because the minterms in it also appear in other groups.

The MSP is $x'z' + wxy + w'xy'$. It turns out the red group is redundant; we can cover all of the minterms in the map without it.

Summary

- K-maps are an alternative to algebra for simplifying expressions.
 - The result is a *minimal sum of products*, which leads to a minimal two-level circuit.
 - It's easy to handle don't-care conditions.
 - K-maps are really only good for manual simplification of small expressions... but that's good enough for CS231!
- Things to keep in mind:
 - Remember the correct order of minterms on the K-map.
 - When grouping, you can wrap around all sides of the K-map, and your groups can overlap.
 - Make as few rectangles as possible, but make each of them as large as possible. This leads to fewer, but simpler, product terms.
 - There may be more than one valid solution.