

Figure: Wave-shape for
Input signal in case of
inverting amplifier

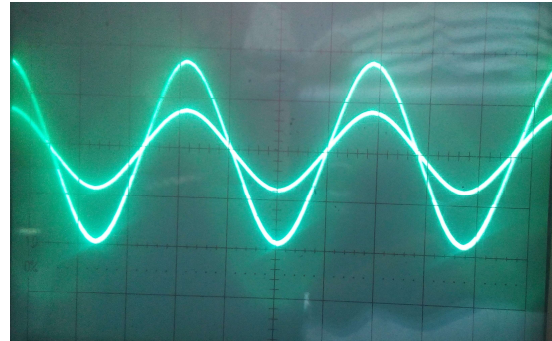


Figure: Wave-shape for
Input and Output signal in
case of non-inverting
amplifier

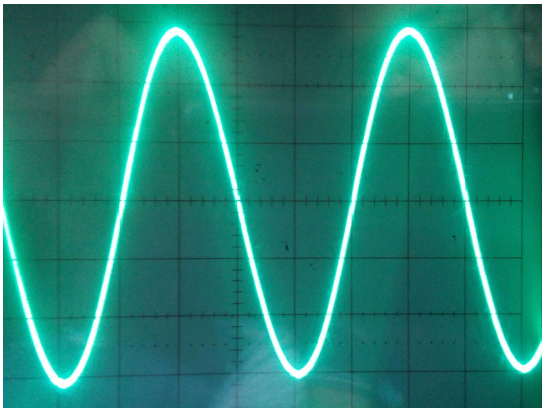


Figure: Wave-shape for
output signal in case of
inverting amplifier