

Most Important Instructions: -2 will be awarded to those who will submit blank answer scripts.

1. Design an 2-bit ALU that supports the following 2 operations: ADD and SUB.
Provide detailed implementation of each chip used in the design (at least Boolean equation).

2. Suppose you have been given the following chip with internal schematics:

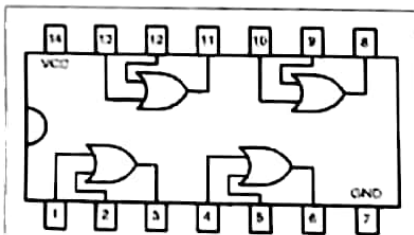


Figure: Quad 2-Input OR gate

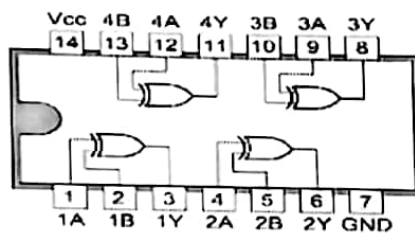


Figure: Quad 2-Input XOR gate (7486)

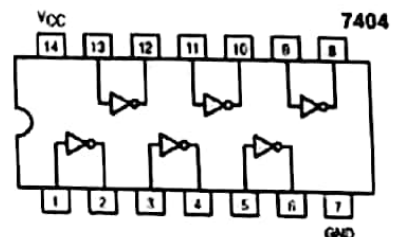


Figure: Hex NOT gate (7404)

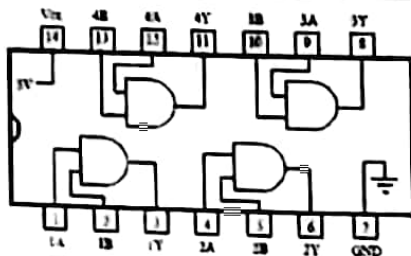


Figure: Quad 2-Input AND gate



Figure: 7805 IC (Voltage Regulator)

You have a 9V power supply.
You can use the above chips any number of times.

Draw schematics of a 2-bit ALU that supports ADD and SUB operations using all chips mentioned above.

15

5