

Sequential circuit


S.M. Shovan

Contents


- Concept of Sequential circuits
- Types of sequential circuits
- Latch
 - S-R latch (NOR, NAND, with enable)
 - Latch timing problem
- Flipflop
 - S-R flipflop
 - D flipflop
 - J-K flipflop
 - T flipflop

Concept of sequential circuits

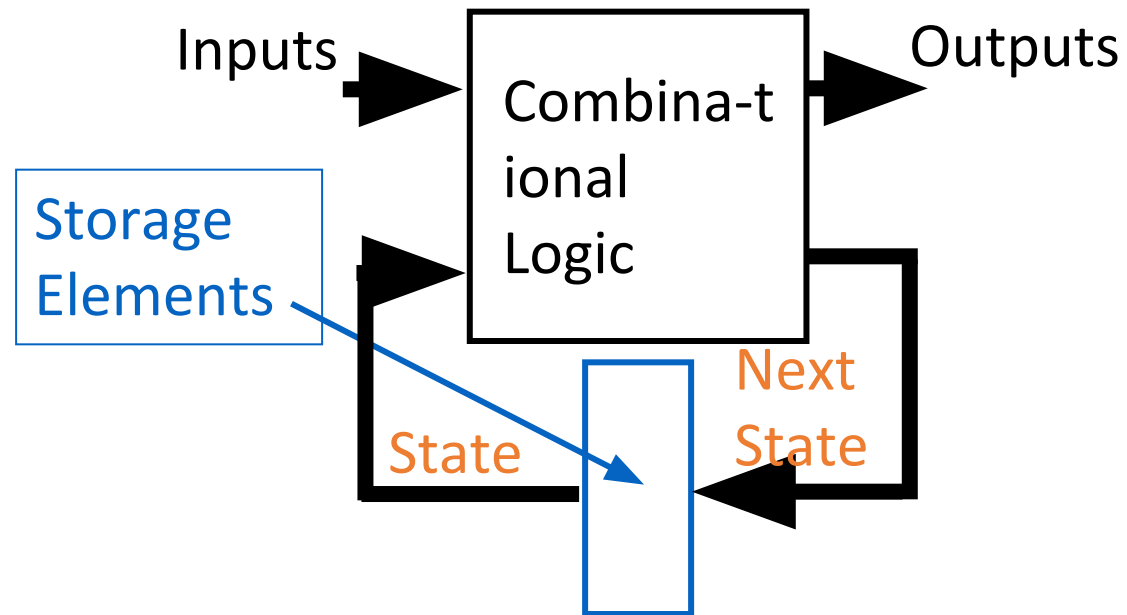- Next state depends on current state
- Stores current state in a memory (Latch / Flipflop)




Types of sequential circuits

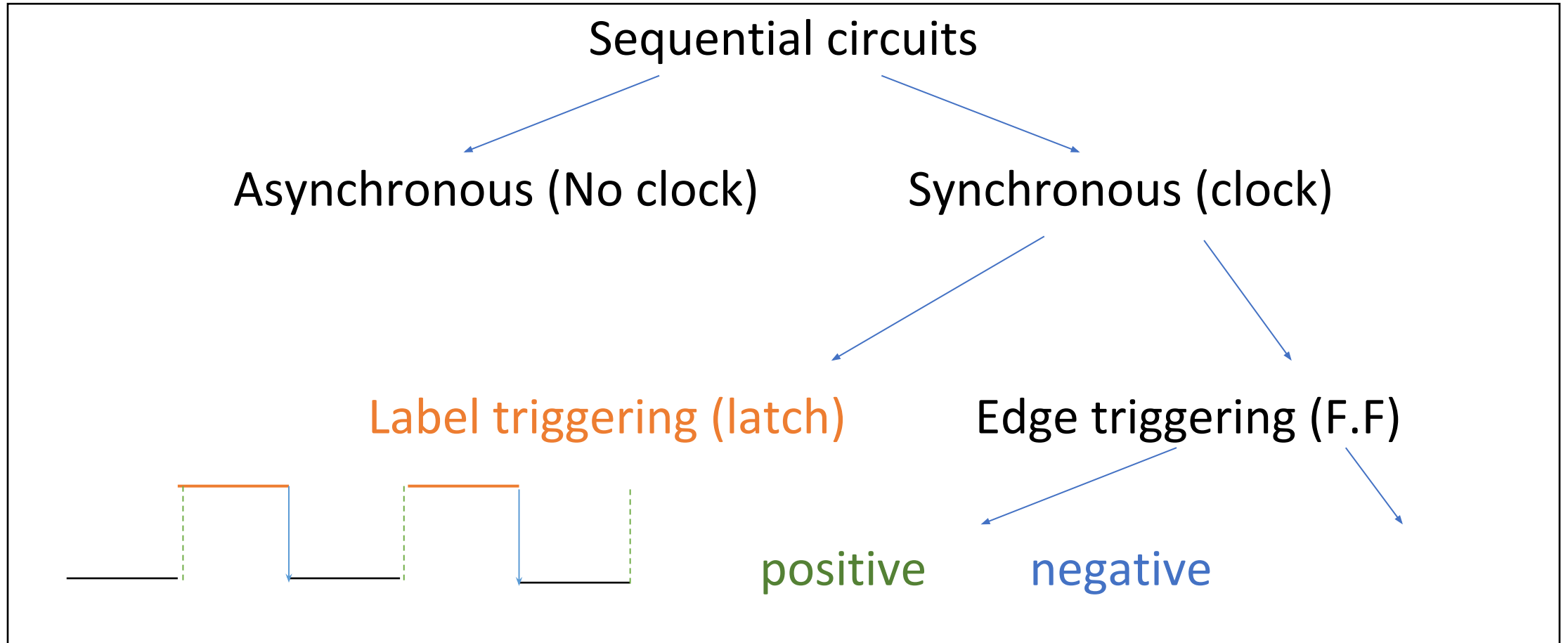

Basic (NOR) S-R Latch

 - When $S=0$ and $R=0$, the SR-Latch is in *Memory state*
- When $S=1$ and $R=0$, the SR-Latch is in the *Set state*
- When $S=0$ and $R=1$, the SR-Latch is in the *Reset state*
- $S=1$ and $R=1$ generates illogical results



(a) Logic diagram

| S | R | Q | \bar{Q} | |
|---|---|---|-----------|-----------------------|
| 1 | 0 | 1 | 0 | Set state Memory |
| 0 | 0 | 1 | 0 | |
| 0 | 1 | 0 | 1 | Reset state Memory |
| 0 | 0 | 0 | 1 | |
| 1 | 1 | 0 | 0 | Undefined |

(b) Function table

| S | R | Q | \bar{Q} | |
|---|---|---|-----------|-------------|
| 1 | 0 | 1 | 0 | Set state |
| 0 | 0 | 1 | 0 | |
| 0 | 1 | 0 | 1 | Reset state |
| 0 | 0 | 0 | 1 | |
| 1 | 1 | 0 | 0 | Undefined |

(b) Function table


Time



| R | S | Q | \bar{Q} | Comment |
|---|---|---|-----------|----------------------|
| 0 | 0 | ? | ? | Stored state unknown |
| 0 | 1 | 1 | 0 | "Set" Q to 1 |
| 0 | 0 | 1 | 0 | Now Q "remembers" 1 |
| 1 | 0 | 0 | 1 | "Reset" Q to 0 |
| 0 | 0 | 0 | 1 | Now Q "remembers" 0 |
| 1 | 1 | 0 | 0 | Both go low |
| 0 | 0 | ? | ? | Unstable! |

Basic (NAND) S-R Latch / $\overline{S} \overline{R}$ Latch

 - When $S=1$ and $R=1$, the SR-Latch is in *Memory state*
- When $S=0$ and $R=1$, the SR-Latch is in the *Set state*
- When $S=1$ and $R=0$, the SR-Latch is in the *Reset state*
- $S=0$ and $R=0$ generates illogical results




(a) Logic diagram

| S | R | Q | \overline{Q} | |
|---|---|---|----------------|-----------------------|
| 0 | 1 | 1 | 0 | Set state Memory |
| 1 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 1 | Reset state Memory |
| 1 | 1 | 0 | 1 | |
| 0 | 0 | 1 | 1 | Undefined |


(b) Function table

S-R latch with control (Enable)

 


| Enable | S | R | Q | \bar{Q} |
|--------|---|---|----------|-----------|
| 0 | 0 | 0 | Memory | |
| 0 | 0 | 1 | Memory | |
| 0 | 1 | 0 | Memory | |
| 0 | 1 | 1 | Memory | |
| 1 | 0 | 0 | Memory | |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | Not Used | |

Latch timing problem

 


- Solution:
 - Flipflop (Edge triggered)

S-R flipflop with clock

 

| CLK | S | R | Q | \bar{Q} |
|-----|---|---|----------|-----------|
| 0 | 0 | 0 | Memory | |
| 0 | 0 | 1 | Memory | |
| 0 | 1 | 0 | Memory | |
| 0 | 1 | 1 | Memory | |
| 1 | 0 | 0 | Memory | |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | Not Used | |

Truth table of S-R flipflop

 

TRUTH TABLE

| S | R | Q_N | Q_{N+1} |
|---|---|-------|-----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | - |
| 1 | 1 | 1 | - |

D-flipflop

 


Table of truth:

| clk | D | Q | \bar{Q} |
|-----|---|---|-----------|
| 0 | 0 | Q | \bar{Q} |
| 0 | 1 | Q | \bar{Q} |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |


Memory

Memory

Reset


Set

Truth table of D flipflop

 

| Q | D | Q(t+1) |
|---|---|--------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

J-K flipflop with truth table

 


A JK flip-flop has the characteristic table below:

| J | K | Q(t+1) |
|---|---|--------|
| 0 | 0 | Q(t) |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q(t)' |

TRUTH TABLE

| J | K | Q _N | Q _{N+1} |
|---|---|----------------|------------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

T flipflop with truth table

 

| T | Q_n | Q_{n+1} |
|-----|-------|-----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |