 


Adder & Subtractor


Nahin Ul Sadad
Lecturer
CSE, RUET

Adder Overview

Half Adder



X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


$$S = X \cdot \overline{Y} + \overline{X} \cdot Y = X \oplus Y$$

$$C = X \cdot Y$$

Adder Overview

Full Adder

 

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \overline{X} \overline{Y} Z + \overline{X} Y \overline{Z} + \overline{X} Y Z + X \overline{Y} \overline{Z}$$
$$C = X Y + X Z + Y Z$$

Adder Overview

Adder circuit simplification

		Y			
X \ YZ		00	01	11	10
	0		1		1
	1	1		1	
		Z			


$$\begin{aligned}
 S &= \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ \\
 &= X \oplus Y \oplus Z
 \end{aligned}$$

		Y			
X \ YZ		00	01	11	10
	0			1	
	1		1	1	1
		Z			

$$\begin{aligned}
 C &= XY + XZ + YZ \\
 &= XY + Z(X\bar{Y} + \bar{X}Y) \\
 &= XY + Z(X \oplus Y)
 \end{aligned}$$

Adder Overview

Adder circuit simplification

 


$$S = X \oplus Y \oplus Z$$


$$C = X Y + (X \oplus Y) Z$$

Adder Overview

Full Adder

 

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$S = \overline{X}\overline{Y}Z + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z} + XYZ$$
$$C = XY + XZ + YZ$$

$$S = X \oplus Y \oplus Z$$

$$C = XY + (X \oplus Y)Z$$

Adder Overview

Full Adder

 


Remember this is only 1-bit Adder!

Q: How can we build 2-bit/4-bit/...32-bit adder?

A: n-bit parallel adder!

Adder Overview

4-bit Parallel Adder

 

4-bit Parallel Adder!


Unsigned Subtraction

Q: How can we build 2-bit/4-bit/...32-bit subtractor (unsigned)?


A: First, we have to build

1. Half-subtractor and
2. Full-subtractor

Half-subtractor

 


A	B	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

 

$$D = A \cdot \overline{B} + \overline{A} \cdot B = A \oplus B$$
$$C = \overline{A} \cdot B$$

Full Subtractor

 

A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = \overline{A} \overline{B} \text{Bin} + \overline{A} B \overline{\text{Bin}} + A \overline{B} \overline{\text{Bin}} + A B \text{Bin}$$


$$\text{Bout} = \overline{A} \overline{B} \text{Bin} + \overline{A} B \overline{\text{Bin}} + \overline{A} B \text{Bin} + A B \text{Bin}$$

Full Subtractor


$$\begin{aligned}\mathbf{D} &= A'B'Bin + A'BBin' + AB'Bin' + ABBin \\ &= Bin(A'B' + AB) + Bin'(AB' + A'B) \\ &= Bin(A \text{ XNOR } B) + Bin'(A \text{ XOR } B) \\ &= Bin(A \text{ XOR } B)' + Bin'(A \text{ XOR } B) \\ &= Bin \text{ XOR } (A \text{ XOR } B) \\ &= (A \text{ XOR } B) \text{ XOR } Bin\end{aligned}$$

$$\begin{aligned}\mathbf{Bout} &= A'B'Bin + A'BBin' + A'BBin + ABBin \\ &= Bin(AB + A'B') + A'B(Bin + Bin') \\ &= Bin(A \text{ XNOR } B) + A'B \\ &= Bin(A \text{ XOR } B)' + A'B\end{aligned}$$

Full Subtractor

 

A	B	Bin	D	Bou
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 

$$D = \overline{A} \overline{B} \text{Bin} + \overline{A} B \overline{\text{Bin}} + A \overline{B} \overline{\text{Bin}} + A B \text{Bin}$$


$$\text{Bout} = \overline{A} \overline{B} \text{Bin} + \overline{A} B \overline{\text{Bin}} + \overline{A} B \text{Bin} + A B \text{Bin}$$

$$D = A \oplus B \oplus \text{Bin}$$

$$\text{Bout} = \text{Bin} (\overline{A \oplus B}) + \overline{A} B$$

Q: How can we build 2-bit/4-bit/...32-bit unsigned subtractor?

A:

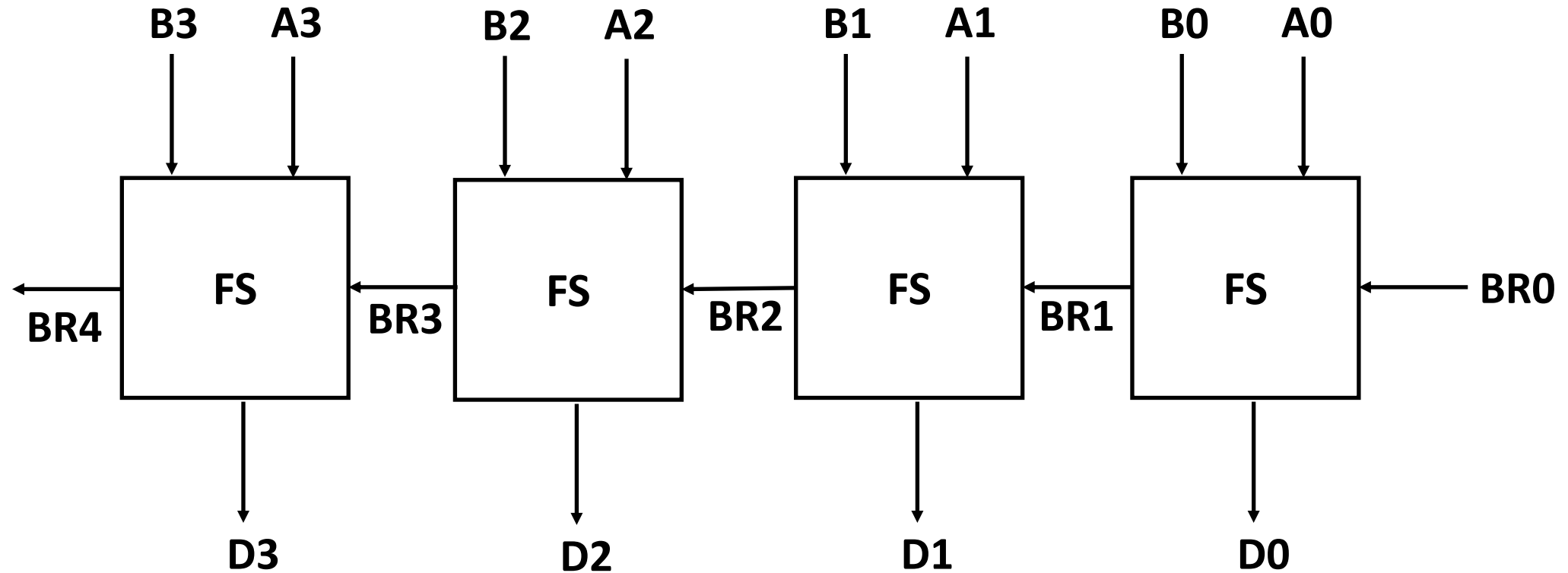

Signed Subtraction

Q: What are the limitations of Unsigned subtractor (built using half-subtractor and full-subtractor)?

A:

1. It cannot calculate signed subtraction like $-4-2$ etc. (For adders, there is no difference between signed and unsigned adders.)
2. It requires a separate circuit to perform this operations. It is possible to perform subtraction using Adder circuit.

Q: How can we perform signed subtraction?

A: It can be done using 2's complement!

Signed 2's compl (n=4)	decimal value
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	$7 = 2^{n-1} - 1$
1000	$-8 = -2^{n-1}$
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

When MSB = 0,

No of positive values = 2^{n-1}

Range of positive values = 2^{n-1} to 0

When MSB = 1,

No of negative values = 2^{n-1}

Range of negative values = -2^{n-1} to -1

Total number of values represented by n bits is $2^{n-1} + 2^{n-1} = 2^n$.

Q: How can to calculate negative number (For example : -4) using 2's complement?

A:

1. Calculate binary representation of its positive number:

$$(4)_{10} = (0100)_2$$

2. Calculate 1's complement: It means flipping/inverting its bits

$$0100 \rightarrow 1011 \text{ (Flipping its bits)}$$

3. Calculate 2's complement: It means adding 1 to its 1's complement result

$$\begin{array}{r} 1011 \\ +1 \\ \hline 1100 \end{array}$$

Q: How can to calculate equivalent decimal value (For example : 1100) using 2's complement?

A: Just Perform 2's complement operation!

1. Calculate 1's complement: It means flipping/inverting its bits

1100 \rightarrow 0011 (Flipping its bits)

2. Calculate 2's complement: It means adding 1 to its 1's complement result

$$\begin{array}{r} 0011 \\ +1 \\ \hline 0100 \end{array}$$

3. Calculate its equivalent decimal:

$$(0100)_2 = (4)_{10}$$

Q: Calculate +4-3

A:

1. Binary representation of +4 is 0100

Binary representation of -3 is 1101

2.

$$\begin{array}{r} 0100 \\ 1101 \\ \hline 0001 \\ \text{Carry} = 1 \text{ (Ignore It)} \end{array}$$

3. Calculate its equivalent decimal:

$$(0001)_2 = (1)_{10}$$

Q: Calculate $-4+3$

A:

1. Binary representation of -4 is 1100
Binary representation of $+3$ is 0011

2.

$$\begin{array}{r} 1100 \\ 0011 \\ \hline 1111 \end{array}$$

3. Calculate its equivalent decimal:

$$(1111)_2 = (-1)_{10}$$

Q: Calculate -4-5

A:

1. Binary representation of -4 is 1100

Binary representation of -5 is 1011

2.

$$\begin{array}{r} 1100 \\ 1011 \\ \hline 0111 \\ \text{Carry} = 1 \end{array}$$

3. Calculate its equivalent decimal:

$$(0111)_2 = (7)_{10}$$

But answer is Positive and it is 7 instead of -9!

This is called **Signed Overflow problem**.

Q: Calculate +4+5

A:

1. Binary representation of +4 is 0100

Binary representation of +5 is 0101

2.

$$\begin{array}{r} 0100 \\ 0101 \\ \hline 1001 \\ \text{Carry} = 1 \end{array}$$

3. Calculate its equivalent decimal:

$$(1001)_2 = (-7)_{10}$$

But answer is Negative and it is -7 instead of +9!

This is called **Signed Overflow problem**.

Signed Overflow occurs when

Same signed numbers are added but result is opposite sign.

For example: $+4+5 = -7$
 $-4-5 = +7$

We can design a Flag Register to flag signed overflow problem!

Q: How can we perform subtraction using Adder circuit for 1-bit numbers (For example: 0-1)?

A:

Remember this is 1-bit Adder.

It means it can only add not subtraction!

We can write,

$$\begin{aligned} 0 - 1 &= 0 + (-1) = 0 + 2\text{'s complement of } 1! \\ &= 0 + 1\text{'s complement of } 1 + 1 \\ &= 0 + \text{Inverting/Flipping of } 1 + 1 \\ &= 0 + \sim 1 + 1 \\ &= 0 + 0 + 1 \end{aligned}$$

Binary representation of 0 is 0
Binary representation of 1 is 1

Inverting means using NOT gate!

Signed Subtraction using Full Adder

$$A - B = A + \sim B + 1 = A + NOT(B) + 1(C1)$$


 


Figure: 1-bit Subtractor (Signed Subtraction)

Q: How can we build 2-bit/4-bit/...32-bit (signed) subtractor?

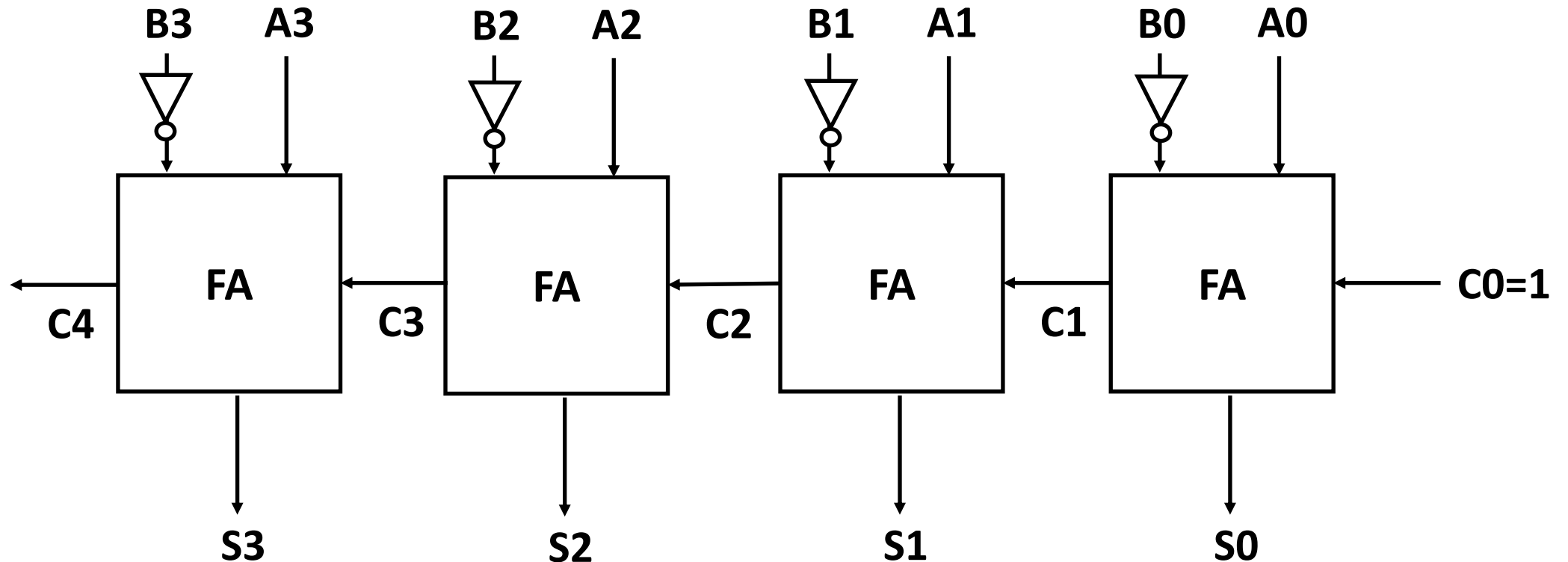A: 4-bit Parallel Subtractor (Using Adder circuit)



Q: How can we combine addition and subtraction in same Adder circuit?


A: Using XOR gate!

XOR is also called Programmable Inverter!

If $A = 0$, $Z = B$


If $A = 1$, $Z = \sim B$

XOR (exclusive OR)

 


A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

4-bit Parallel Adder/Subtractor

 


4-bit Parallel Adder/Subtractor

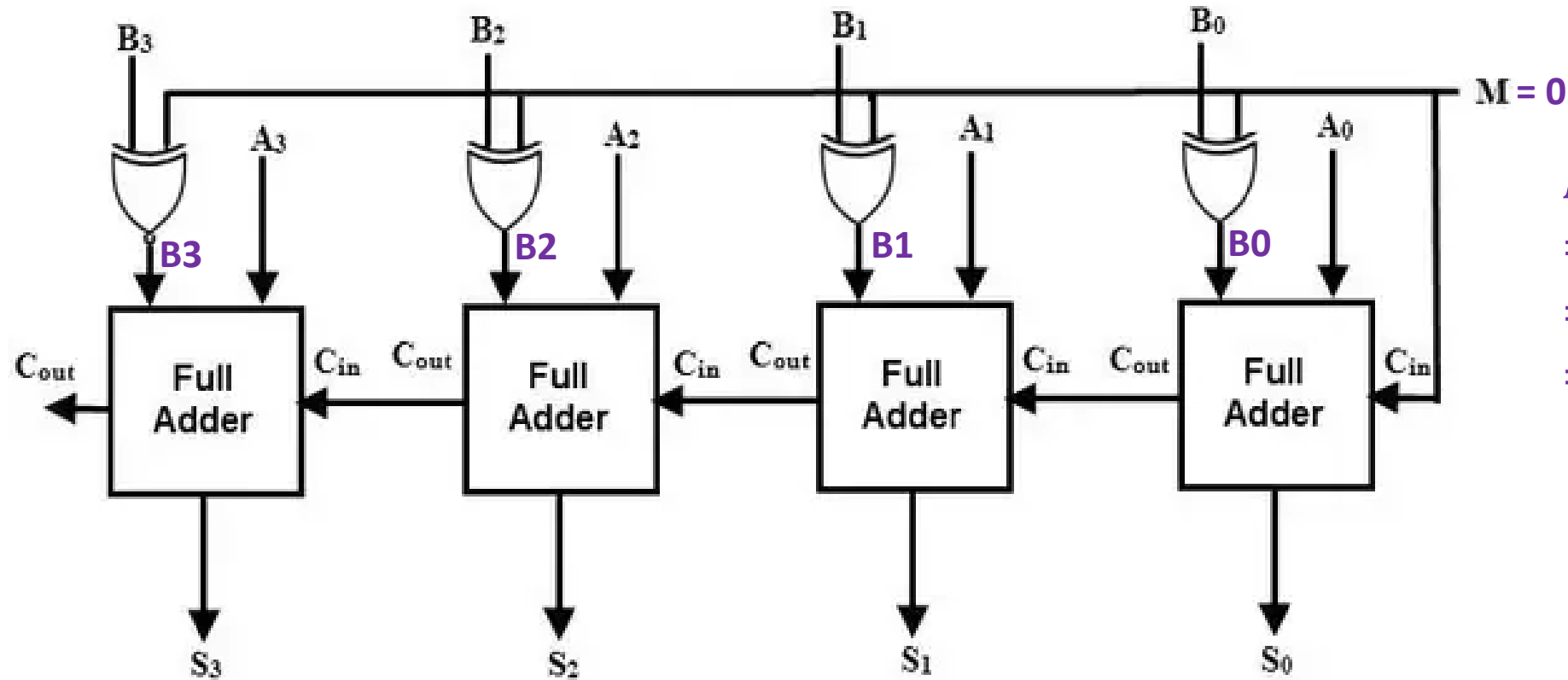

$$\begin{aligned} M \oplus B_n &= M \cdot \overline{B_n} + \overline{M} \cdot B_n \\ &= 0 \cdot \overline{B_n} + \overline{0} B_n \\ &= B_n \end{aligned}$$


4-bit Parallel Adder/Subtractor

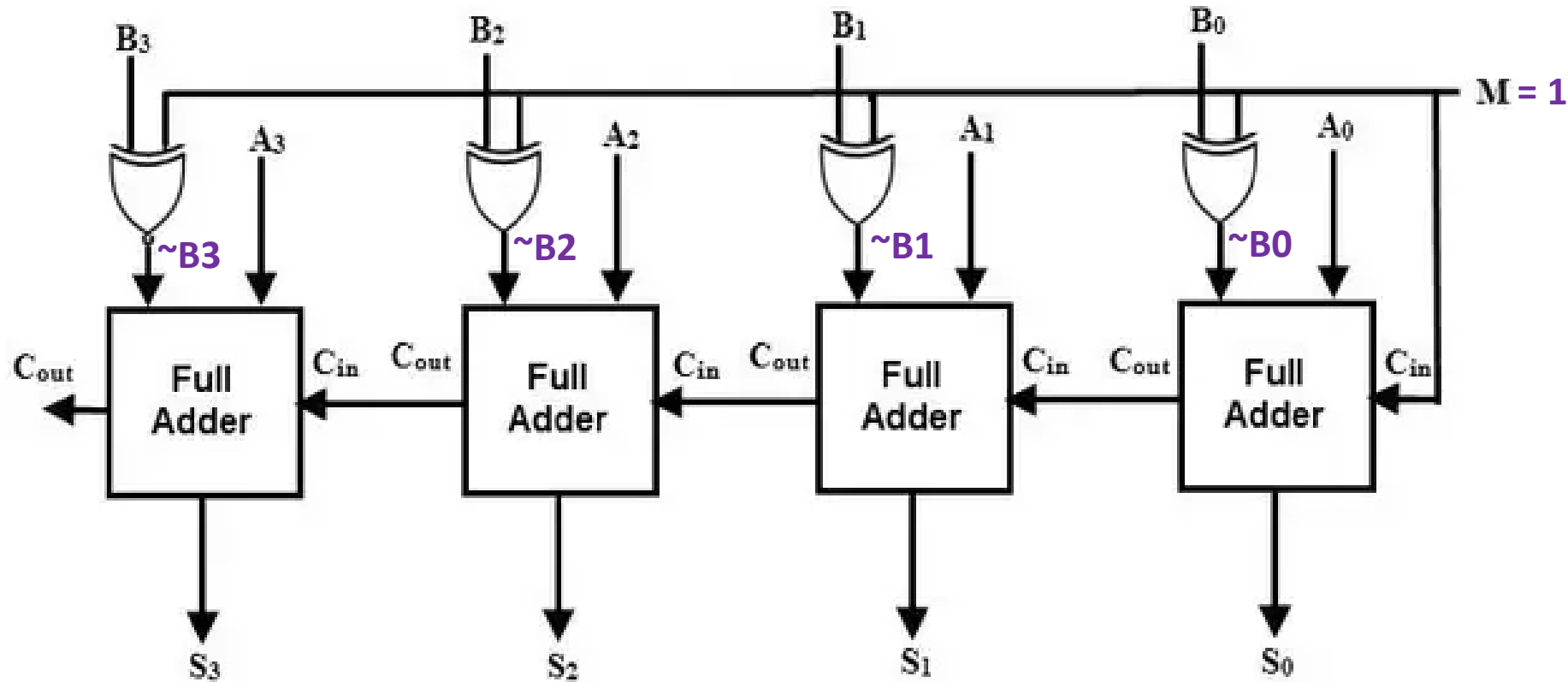

$$\begin{aligned} M \oplus B_n &= M \cdot \overline{B_n} + \overline{M} \cdot B_n \\ &= 1 \cdot \overline{B_n} + \overline{1} B_n \\ &= \overline{B_n} \end{aligned}$$

Q: What are the limitations of parallel adder/subtractor?

 A: Parallel adder/subtractor is very slow. Because:



4th FA has to wait for
3rd FA to get value of C₃
Which is waiting for
2nd FA to get value of C₂
Which is waiting for
3rd FA to get value of C₁

3rd FA has to wait for
2nd FA to get value of C₂
Which is waiting for
1st FA to get value of C₁


2nd FA has to wait for
1st FA to get value of C₁

So, Parallel Adder/Subtractor is slower!

Q: How can we solve this problem?


A: We can use another variant of Parallel adder which is called Carry Look Ahead Adder!

 A: First consider simple 2-bit Parallel Adder



Because waiting for carry is bottleneck of this design.
What we can do is calculate carry as early as possible!

 A: First consider simple 2-bit Parallel Adder



$$S = A_n \oplus B_n \oplus C_{n-1}$$

$$C_n = A_n B_n + (A_n \oplus B_n) C_{n-1}$$

Let,


$$G_n = A_n B_n$$

$$P_n = A_n \oplus B_n$$


$$C_n = G_n + P_n C_{n-1}$$

This design is faster than that design.

A: simple 2-bit Parallel Adder

 

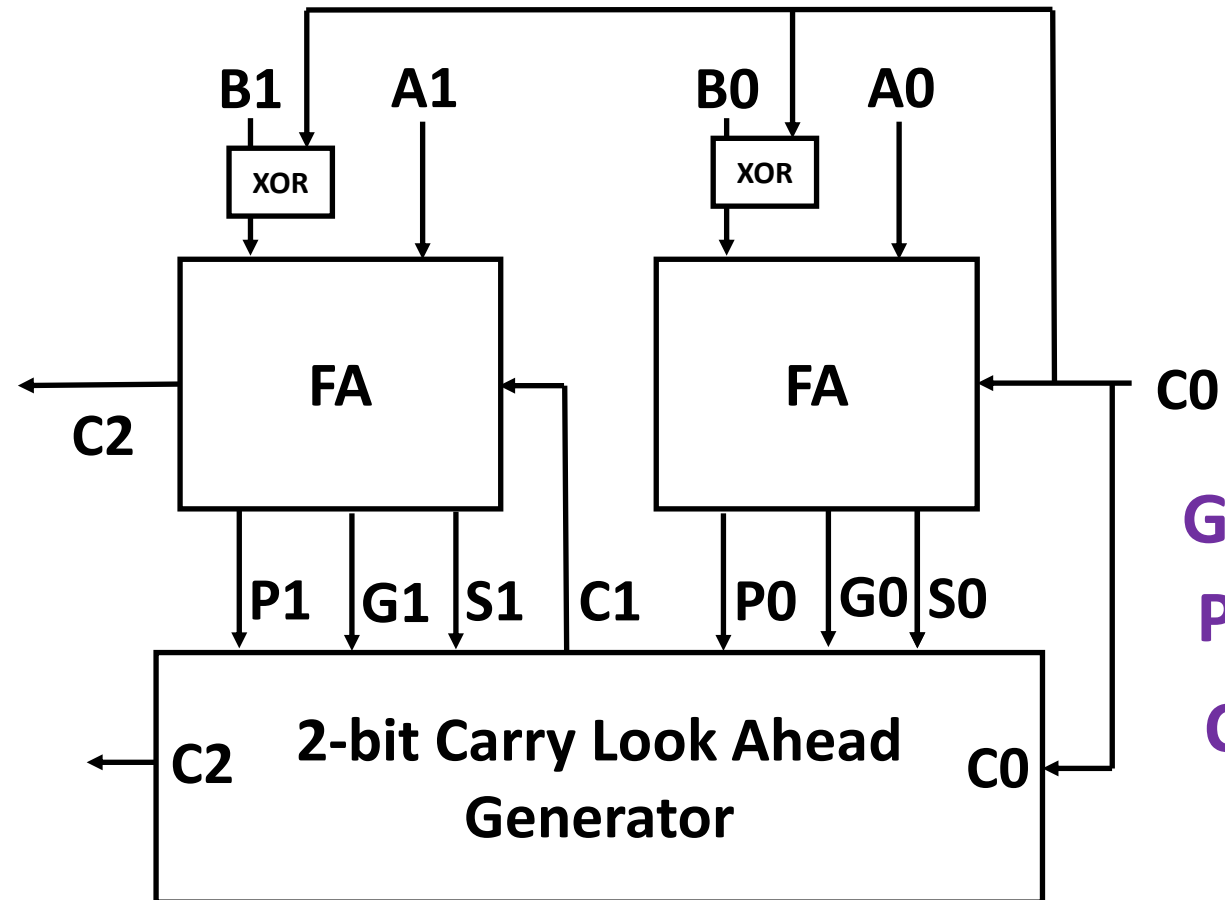A: Similarly 2-bit Parallel Adder/Subtractor



**Similarly, Create 4-bit Carry Look Ahead
Adder/Subtractor!**

Example: Adder

Question: Design a 4 bit signed adder (normal) and show output of each circuit in when $X = 1001$ and $Y = 1111$.

Answer:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Figure: 1-bit Full Adder Circuit

 


Figure: 1-bit Full Adder Chip

$$S = \overline{X}\overline{Y}Z + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z} + XYZ$$

$$C = XY + XZ + YZ$$

$$S = X \oplus Y \oplus Z$$

$$C = XY + (X \oplus Y)Z$$

Example: Adder

 


Figure: 4-bit Full Adder Circuit with output when $X=1001$ and $Y=1111$

Exercises

1. Consider

$X = 11011/1111/110/11$ (5-bit/4-bit/3-bit/2-bit)

$Y = 11011/1111/110/11$ (5-bit/4-bit/3-bit/2-bit)

i. Calculate $X+Y$ (Unsigned/Signed)

ii. Calculate $X-Y$ (Unsigned/Signed)

2. Calculate $1010-0100/1010+0100$ (Signed/Unsigned) and design a circuit which can calculate this.

3. How does your computer do subtract in program statement,

$Z = X - Y$ or $Z = 1010 - 0100$ (both are Unsigned).

Design a circuit and show how it calculates the result in each component.

4. Design a 2/3/4 bit unsigned/signed adder (normal/carry look ahead) and show output of each circuit in when $X = 10$ or 111 or 1001 and $Y=11$ or 100 or 1111 .

Thank You 😊