

Unsigned Binary Divider

Nahin Ul Sadad
Lecturer,
CSE, RUET

Unsigned Division Example

Example: $1111 \div 0111$

Here, Dividend, A = 1111 (15)

Divisor, B = 0111 (7)

0111) 1111 (0010

- 0

11

- 00

111

- 111

0001

- 0000

0001

Here, Subtraction is unsigned subtraction.

Quotient = 0010 (2)

Remainder = 0001 (1)

Unsigned Division Example

Example: $1111 \div 0111$

Here, Dividend, A = 1111 (15)

Divisor, B = 0111 (7)

If we slightly change its way of calculation, then

0111) 0001111 (0010

- 0000

0011

- 0000

0111

- 0111

0001

- 0000

0001

Quotient = 0010 (2)

Remainder = 0001 (1)

Unsigned Division Example

Table: Example of Unsigned Division

A = 1111 (4-bit) and **B** = 0111 (4-bit)

So, **Q** = 0010 (4-bit) and **R** = 0001(4-bit)

Extend A = 0001011 (7-bit)

Step	A	PA (Partial A)	B	PA-B	Borrow Out	Q	Operation	New PA
1	0001111	<u>0001</u> 111 <u>0001</u> 111	0111	1010	1	0	PA = PA Right Shift PA	<u>0001</u> 111
2	0001111	<u>0001</u> 111 <u>0001</u> 111	0111	1100	1	0	PA = PA Right Shift PA	000 <u>111</u> 1
3	0001111	<u>0001</u> 111 000 <u>0001</u>	0111	0000	0	1	PA = PA-B Right Shift PA	000 <u>0001</u>
4	0001111	000 <u>0001</u>	0111	1010	1	0	PA = PA	000 <u>0001</u> Remainder

Unsigned Divider Building Block (Cell D)

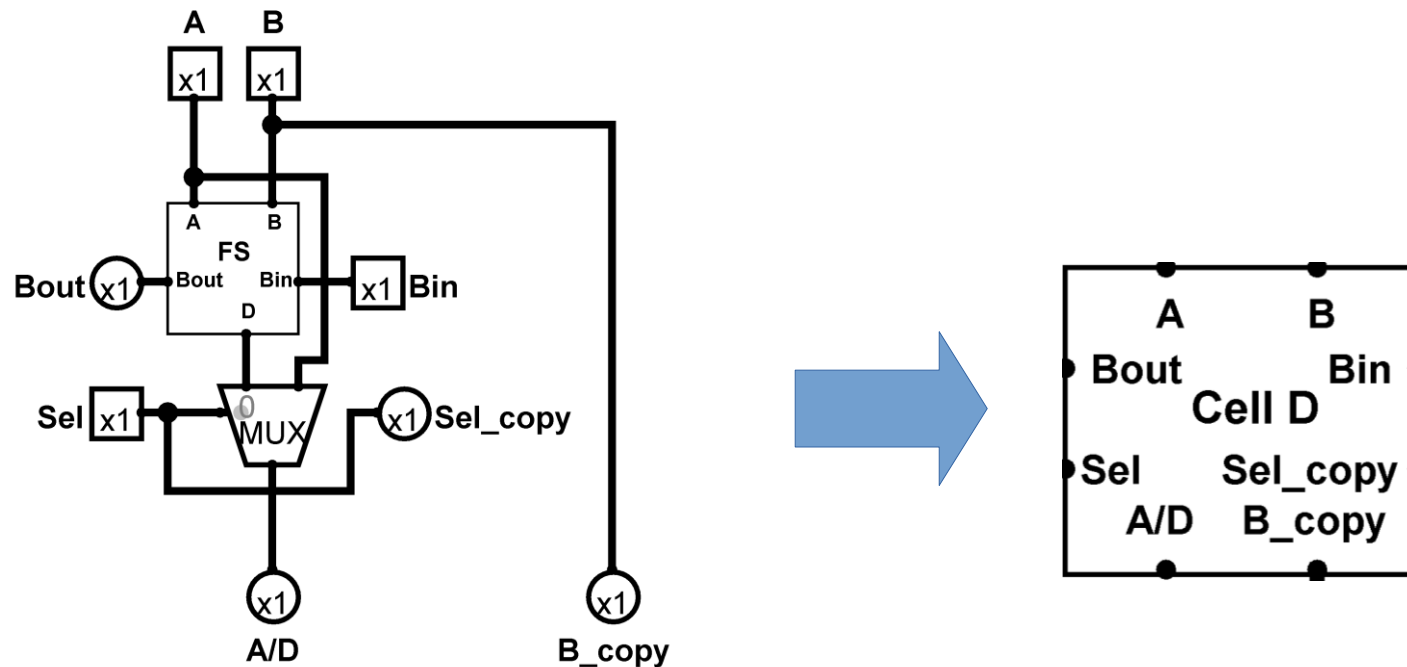


Figure: Cell D (Building Block)

Here,

1. FS is the Full Subtractor.
2. MUX is 1bit 2 to 1 Multiplexer which will select between A and D.
3. Value of B and Sel will propagate to next Block which means they are also outputs.

We are going to use a building block (Cell D) to create Unsigned Divider₅

Unsigned Divider Building Block (FS)

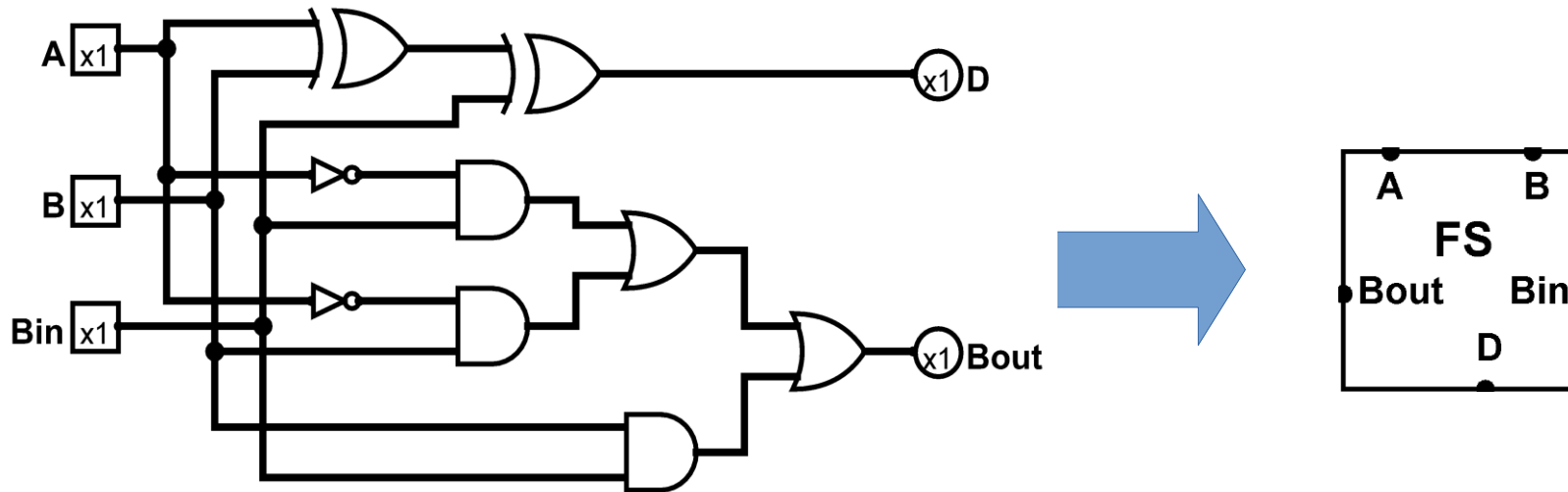


Figure: FS (Full Subtractor)

$$D = A \text{ XOR } B \text{ XOR } Bin$$

$$B_{out} = (\sim A \text{ AND } B) \text{ OR } (\sim A \text{ AND } Bin) \text{ OR } (B \text{ AND } Bin)$$

Here, a, b and Bin (Borrow in) are inputs.
Bout (Borrow out) and D (Difference) are outputs

2-bit Unsigned Divider


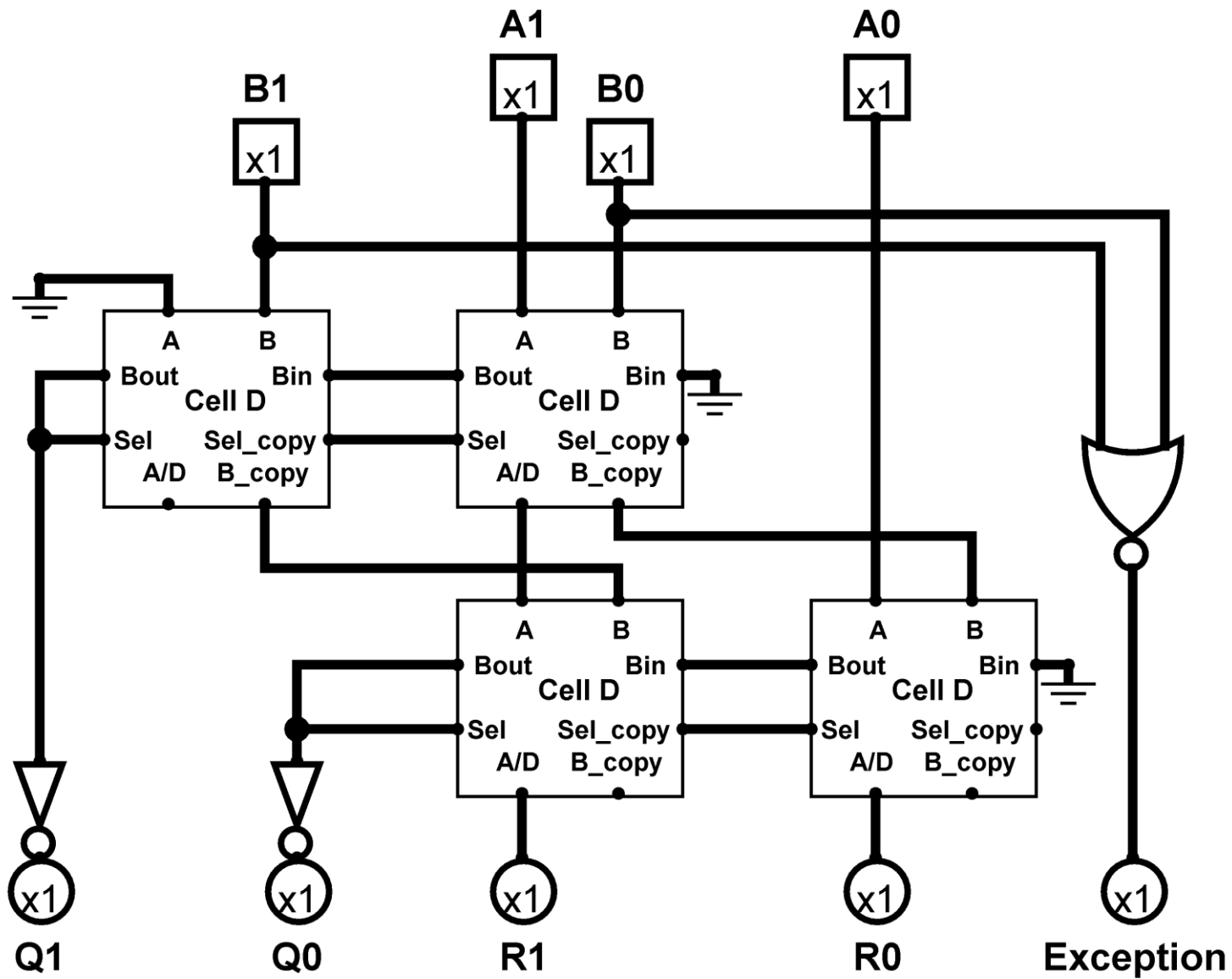


Figure: 2-bit Unsigned Divider

2-bit Unsigned Divider Simulation

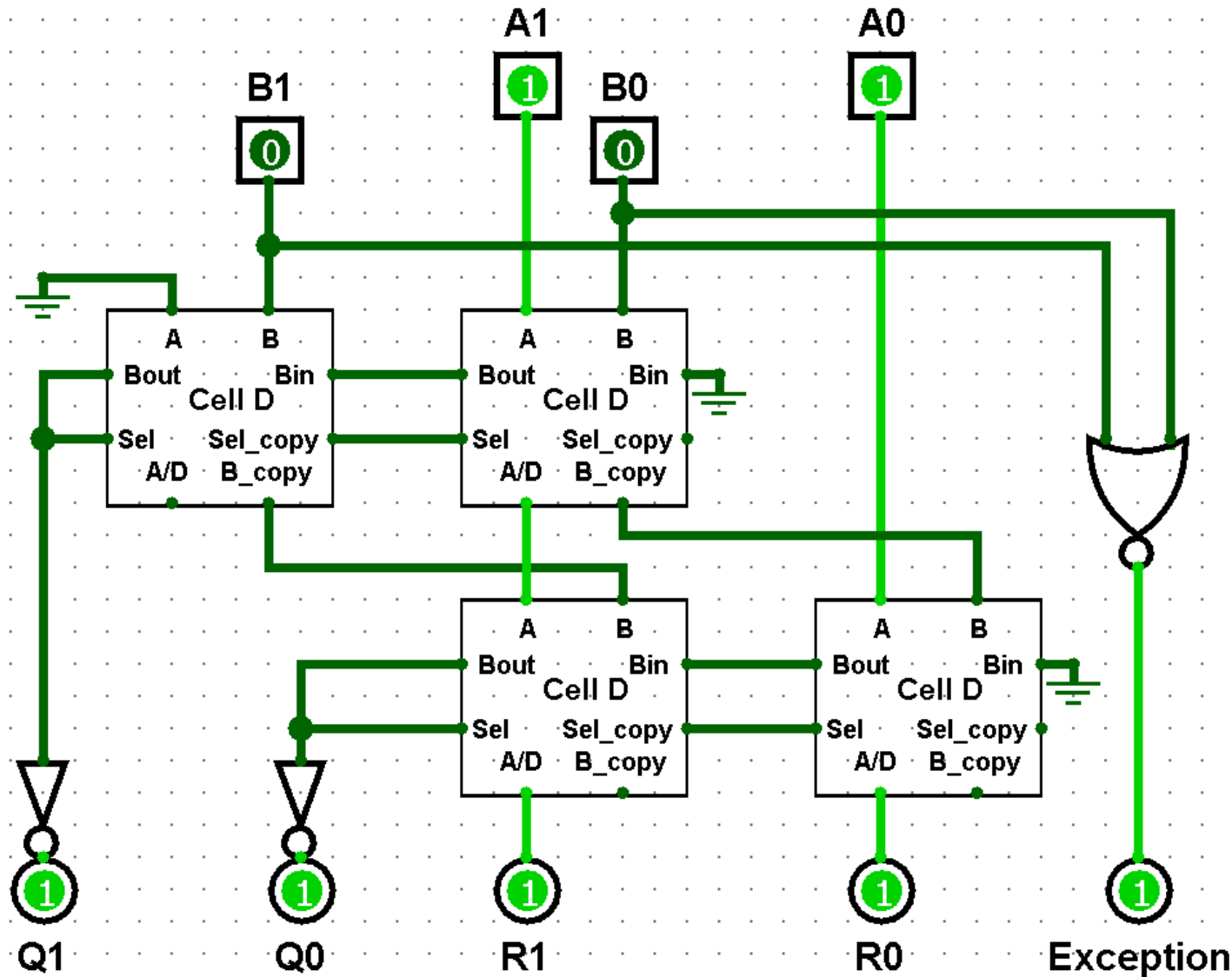

**Figure: 2-bit Unsigned Divider Simulation for input A = 11 (3) and B = 00 (0).
Output Q = XX, R = XX and Exception = 1.
Because B = 0 and Division by 0 is not allowed.**

2-bit Unsigned Divider Simulation

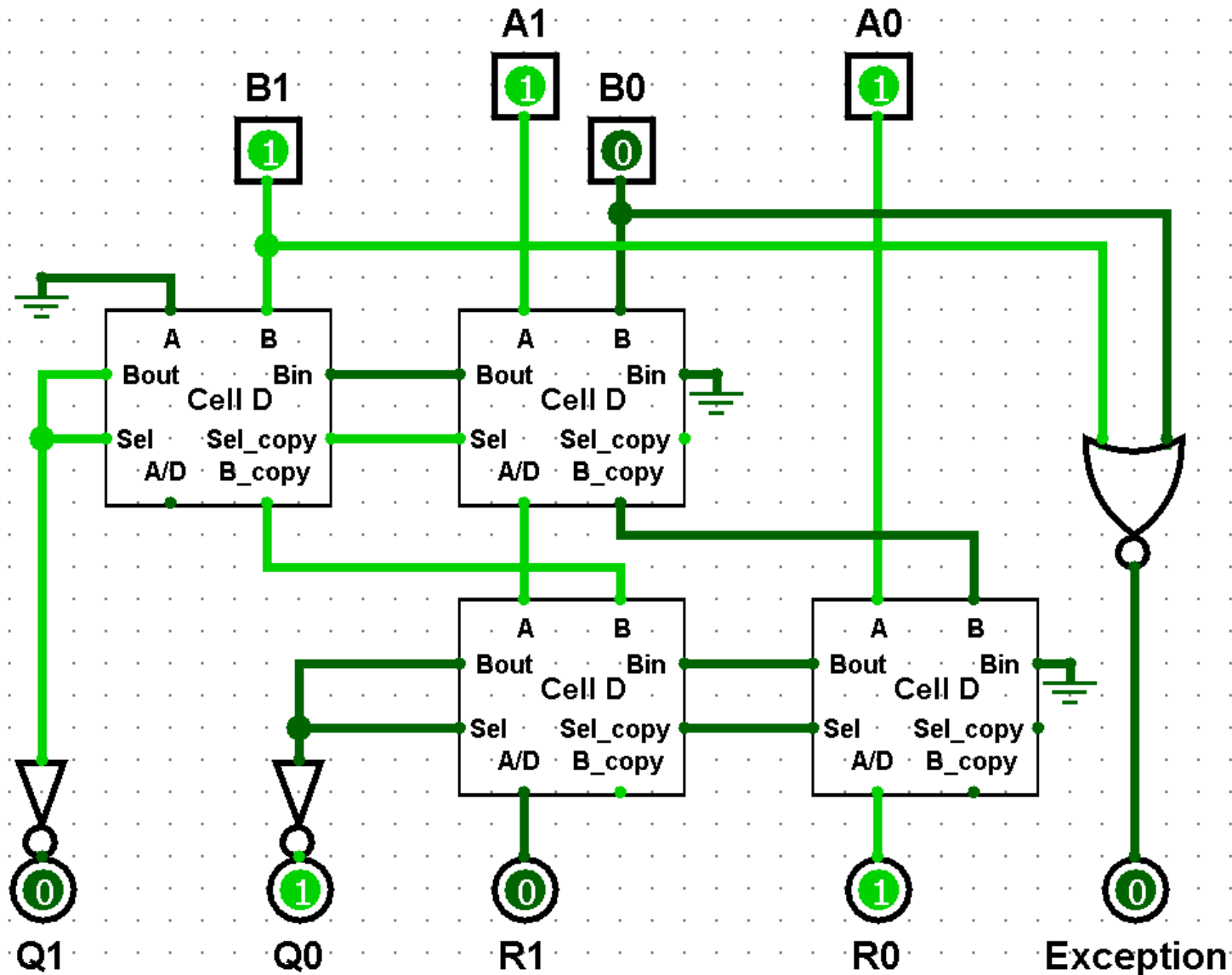


Figure: 2-bit Unsigned Divider Simulation for input A = 11 (3) and B = 10 (2).
Output Q = 01 (1), R = 01 (1) and Exception = 1

4-bit Unsigned Divider


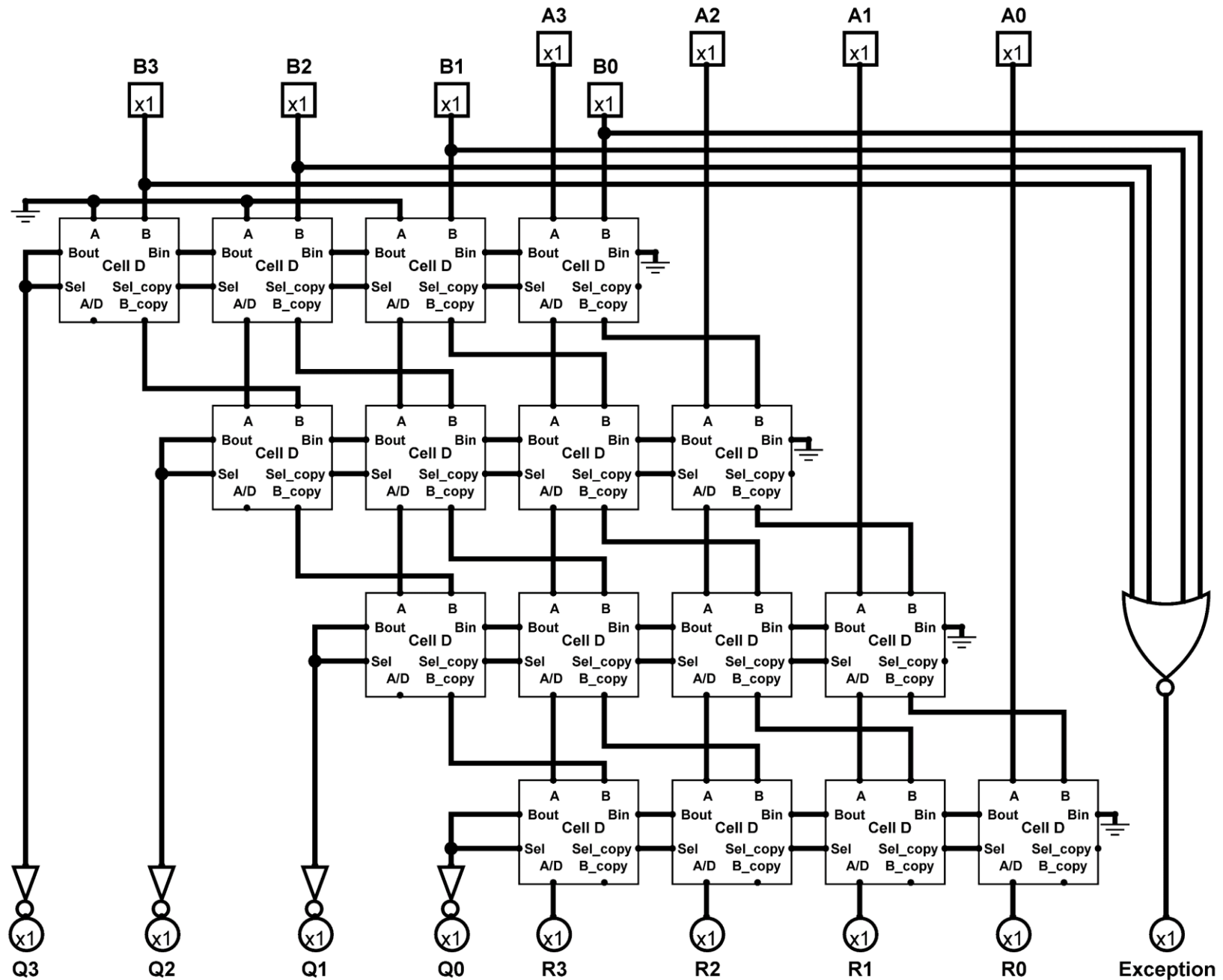


Figure: 4-bit Unsigned Divider

4-bit Unsigned Divider Simulation

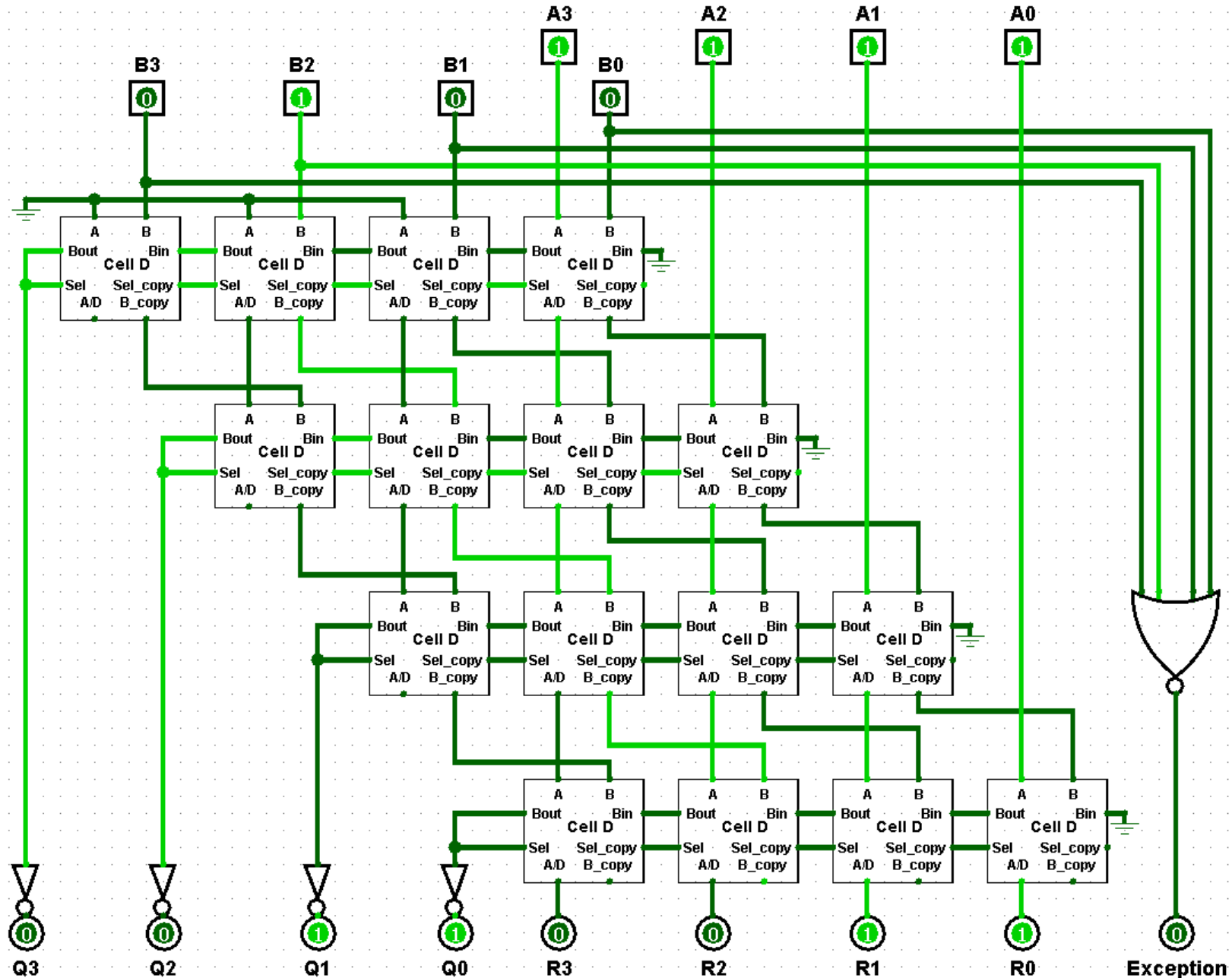

**Figure: 4-bit Unsigned Divider Simulation for input A = 1111 (15) and B = 0100 (4).
Output Q = 0011 (3), R = 0011 (3) and Exception = 0**

**Figure: 4-bit Unsigned Divider Simulation for input A = 1111 (15) and B = 0111 (7).
Output Q = 0010 (2), R = 0001 (1) and Exception = 0**

Exercises

1. Divide 1010/0100 and design a circuit which can calculate this.
2. How does your computer do divide in program statement,
 $Z = X / Y$ or $Z = 1010 / 0100$ (both are unsigned).
Design a circuit and show how it calculates the result in each component.
3. Design a 2/3/4 bit unsigned divider and
show output of each circuit in when $X = 10$ or 111 or 1001 and $Y=11$ or 100 or 1111 .