 


# Final 4-bit ALU Design for 4-bit CPU

Nahin Ul Sadad  
Lecturer  
CSE, RUET

# ALU

ALU chip is shown below:



**Figure:** 4-bit ALU where it performs operations on A and B based on OP value.

Here,

**A** = Data1 of ALU

**B** = Data2 of ALU

**OP** = Opcode of ALU

**R** = Result of ALU

**CF** = Carry Flag

**SF** = Sign Flag

**ZF** = Zero Flag

**DIVE** = DIV Exception

**MULE** = MUL Exception

# **Logic Circuits**








**AND Gate**

**OR Gate**

**XOR Gate**

**NOT Gate**

# 4-bit AND gate

       

# 4-bit AND Gate Simulation


 
 
 
 


Figure: 4-bit AND Gate Simulation for input A = 1111 and B = 1011.  
Output is O = 1011

## 4-bit OR gate

 

# 4-bit OR Gate Simulation



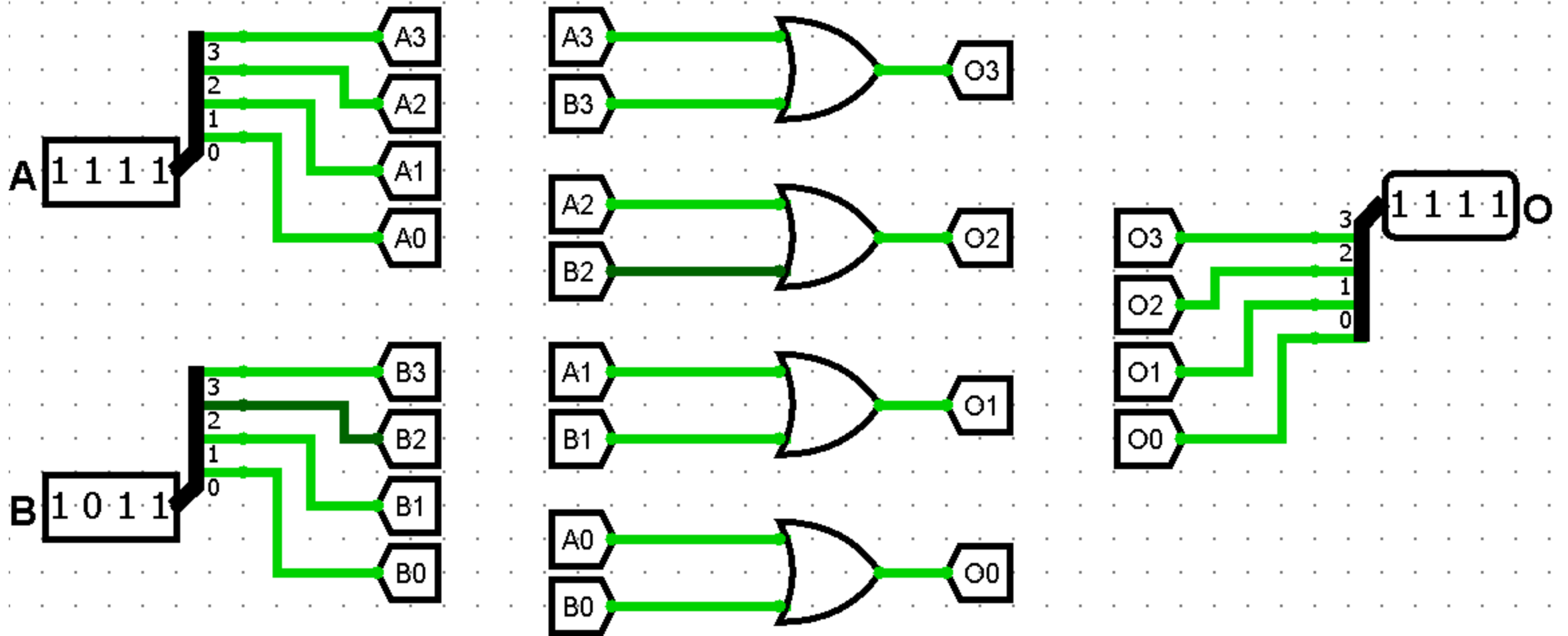
 
 
 
 
 


Figure: 4-bit OR Gate Simulation for input A = 1111 and B = 1011.  
Output is O = 1111

## 4-bit XOR gate

 

 

# 4-bit XOR Gate Simulation


 
 
 


Figure: 4-bit XOR Gate Simulation for input A = 1111 and B = 1011.  
Output is O = 0100

# 4-bit NOT Gate

 

# 4-bit NOT Gate Simulation


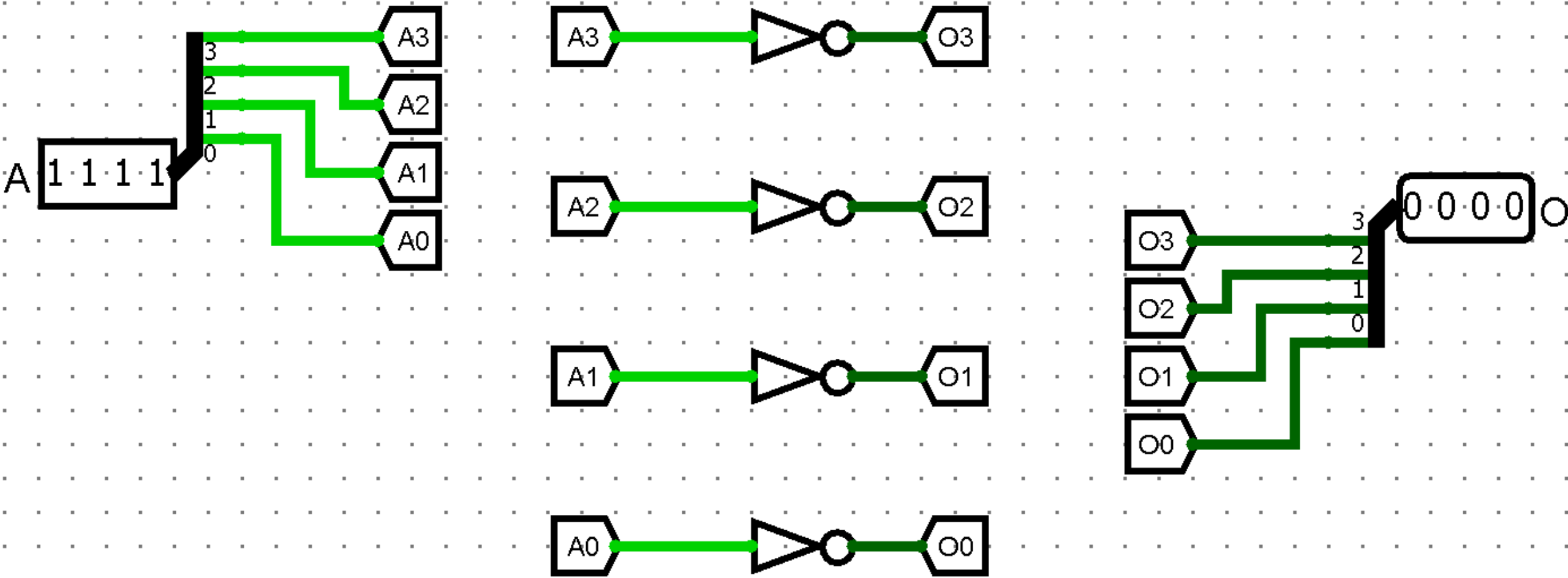
 
 
 


Figure: 4-bit NOT Gate Simulation for input A = 1111. Output is O = 0000

# Logic Circuits

 

# **Arithmetic Circuits**



**Adder**

**Subtractor**




**Multiplier**

**Divider**

# 4-bit Adder/Subtractor

  

# 4-bit Adder/Subtractor

   

# 4-bit Adder/Subtractor Simulation

 


Figure: 4-bit Adder/Subtractor Simulation for input A = 1111, B = 1011, Sel = 0 (ADD).  
Output O = 1010 and Carry = 1



# 4-bit Adder/Subtractor Simulation


 


Figure: 4-bit Adder/Subtractor Simulation for input A = 1111, B = 1011, Sel = 0 (SUB).  
Output O = 0100 and Carry = 1

## 4-bit Multiplier (Unsigned)

 

# 4-bit Multiplier (Unsigned) Simulation


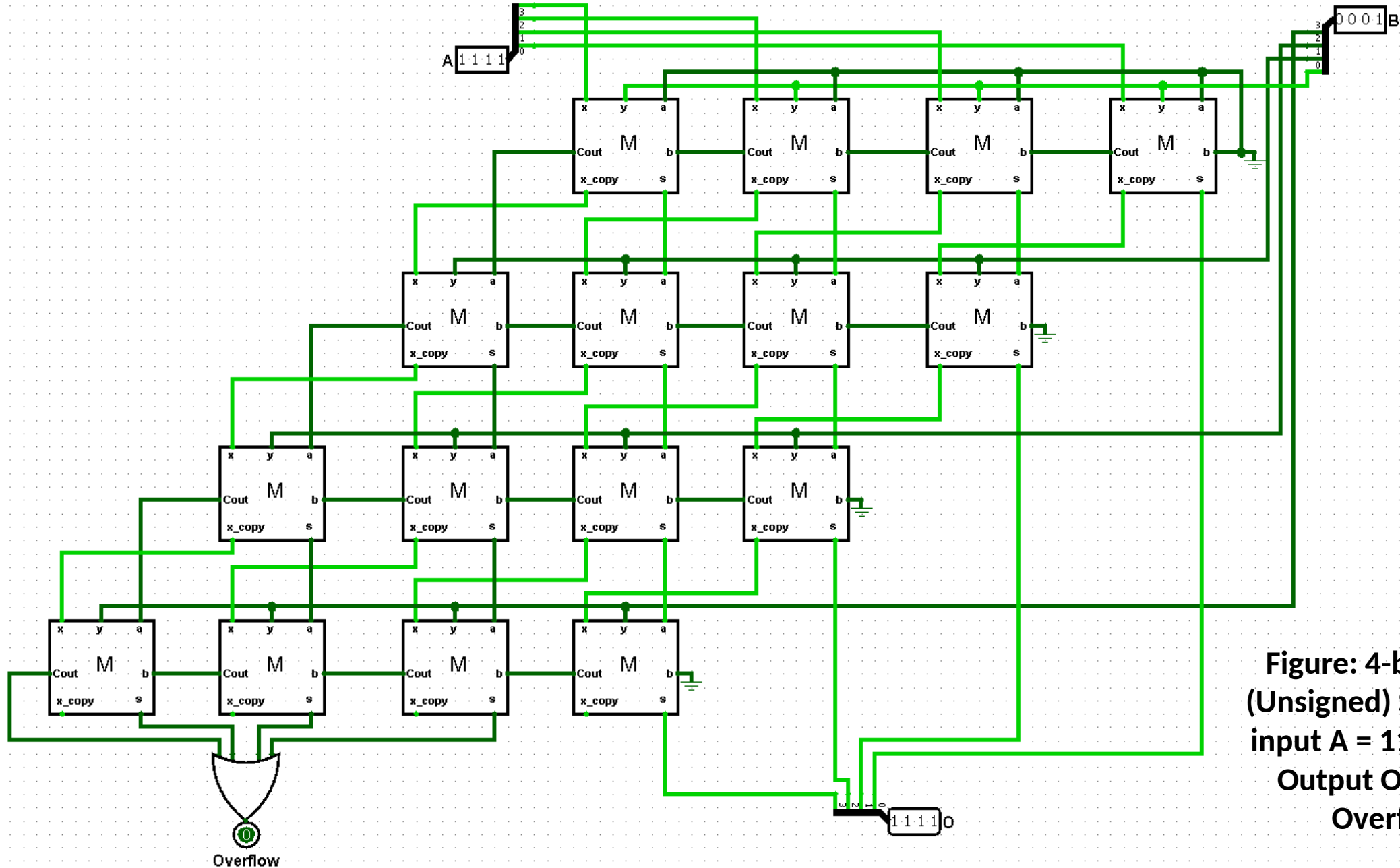


Figure: 4-bit Multiplier (Unsigned) Simulation for input A = 1111, B = 0001. Output O = 1111 and Overflow = 0

## 4-bit Divider (Unsigned)

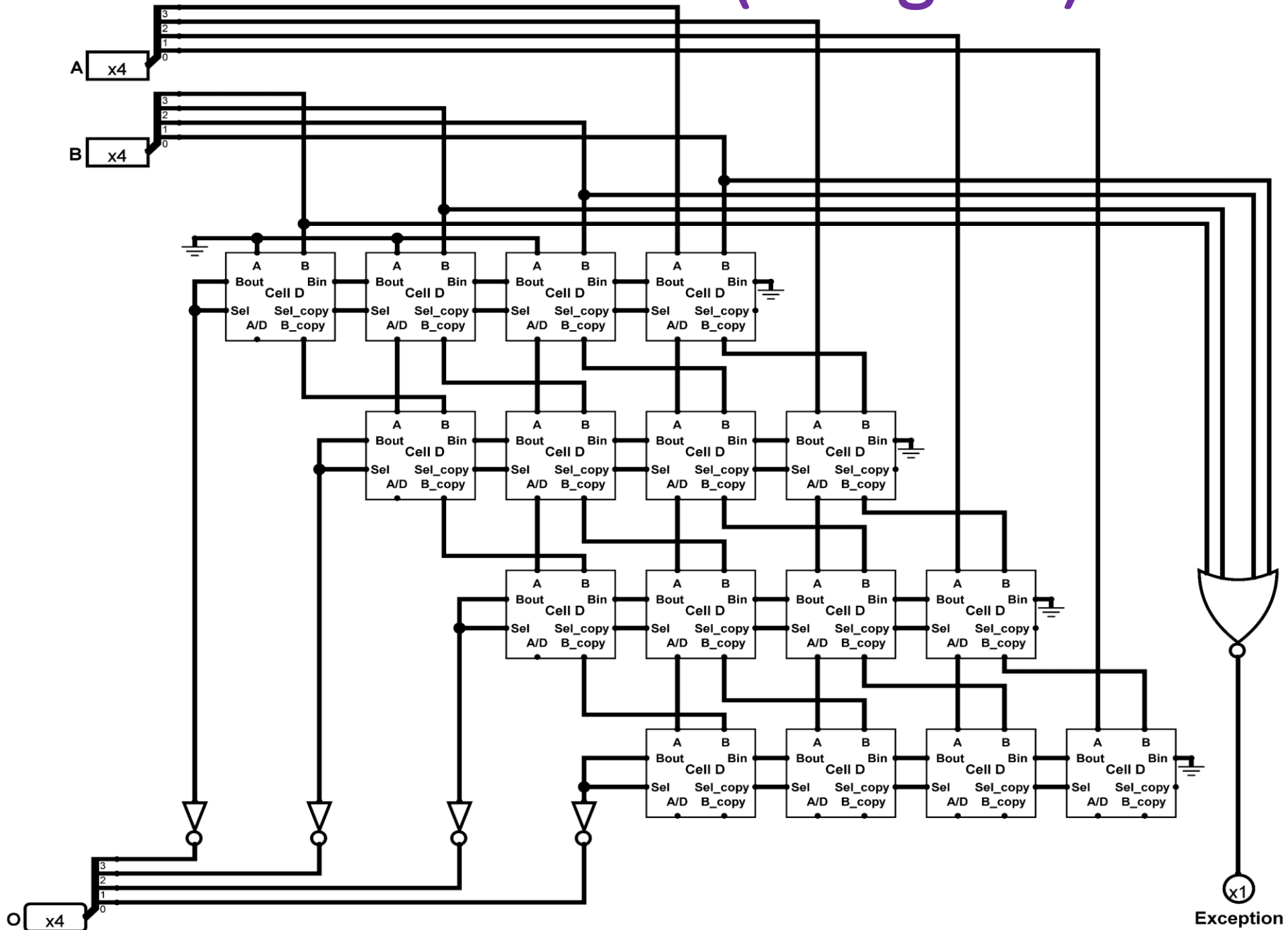

# 4-bit Divider (Unsigned) Simulation


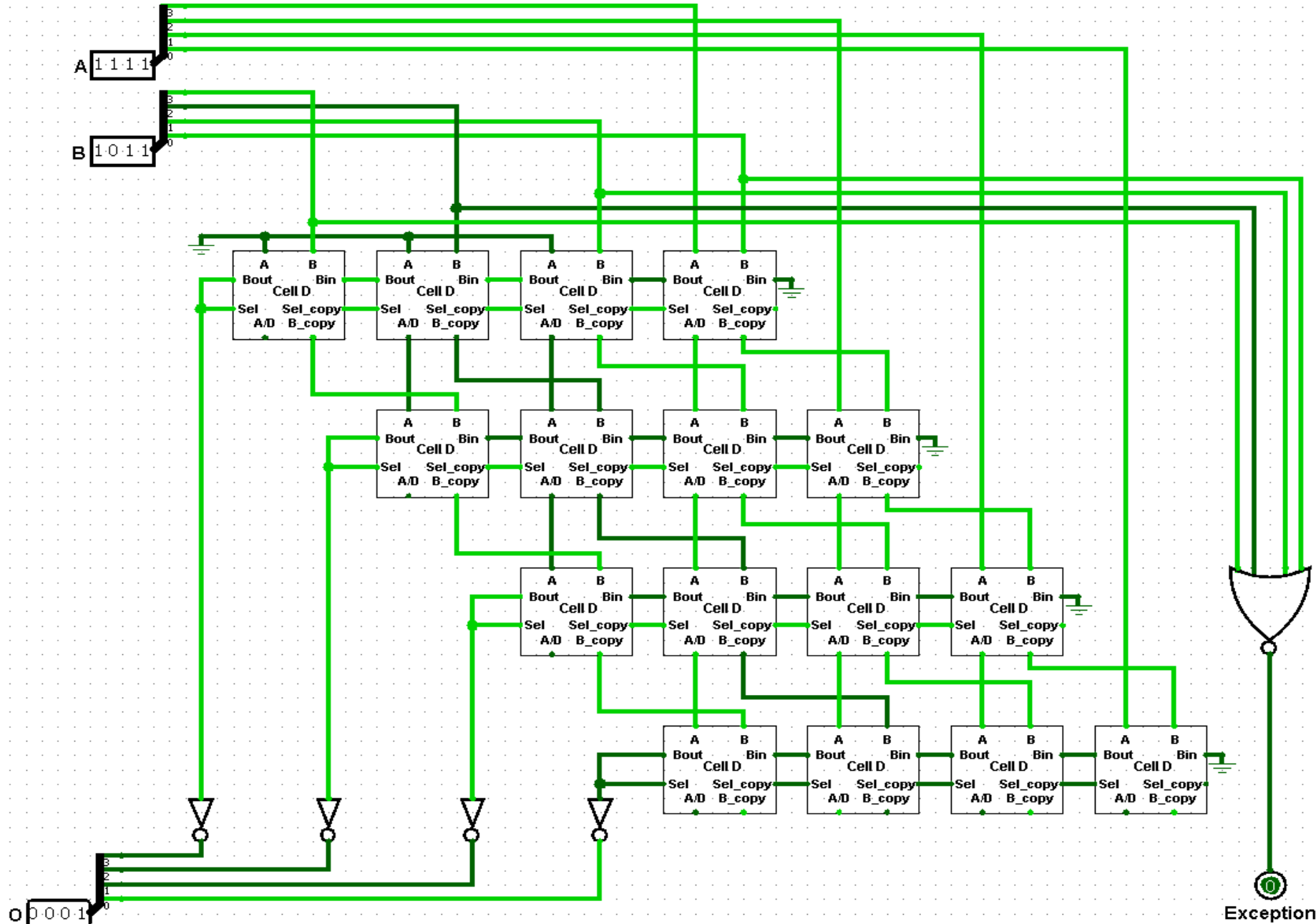


Figure: 4-bit Divider  
(Unsigned) Simulation for  
input A = 1111, B = 1011.  
Output O = 0001 and  
Exception = 0
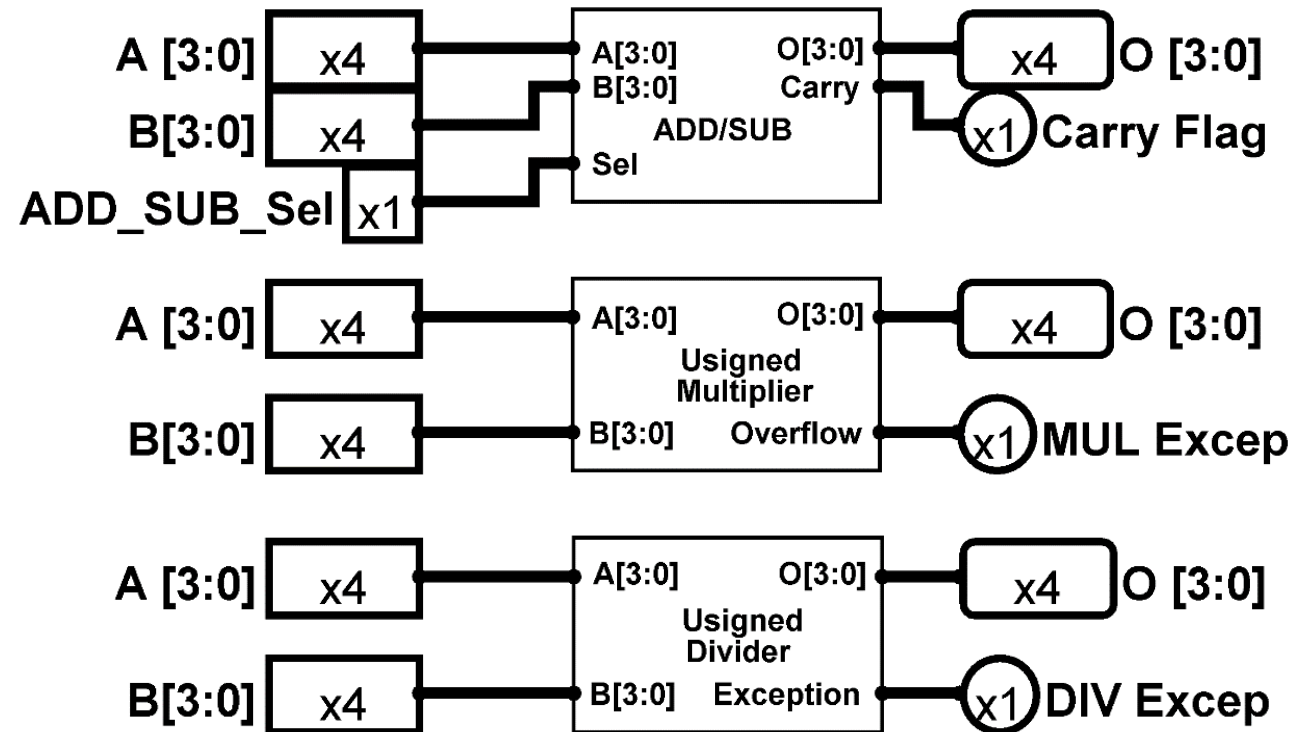
# Arithmetic Circuits Block

If **ADD\_SUB\_Sel** = 0, **O** = **ADD**  
If **ADD\_SUB\_Sel** = 1, **O** = **SUB**




# **Shifter and Rotate Circuits**

## **Shifter**


## **Rotate (Barrel Shifter)**

# 4-bit Left Shifter

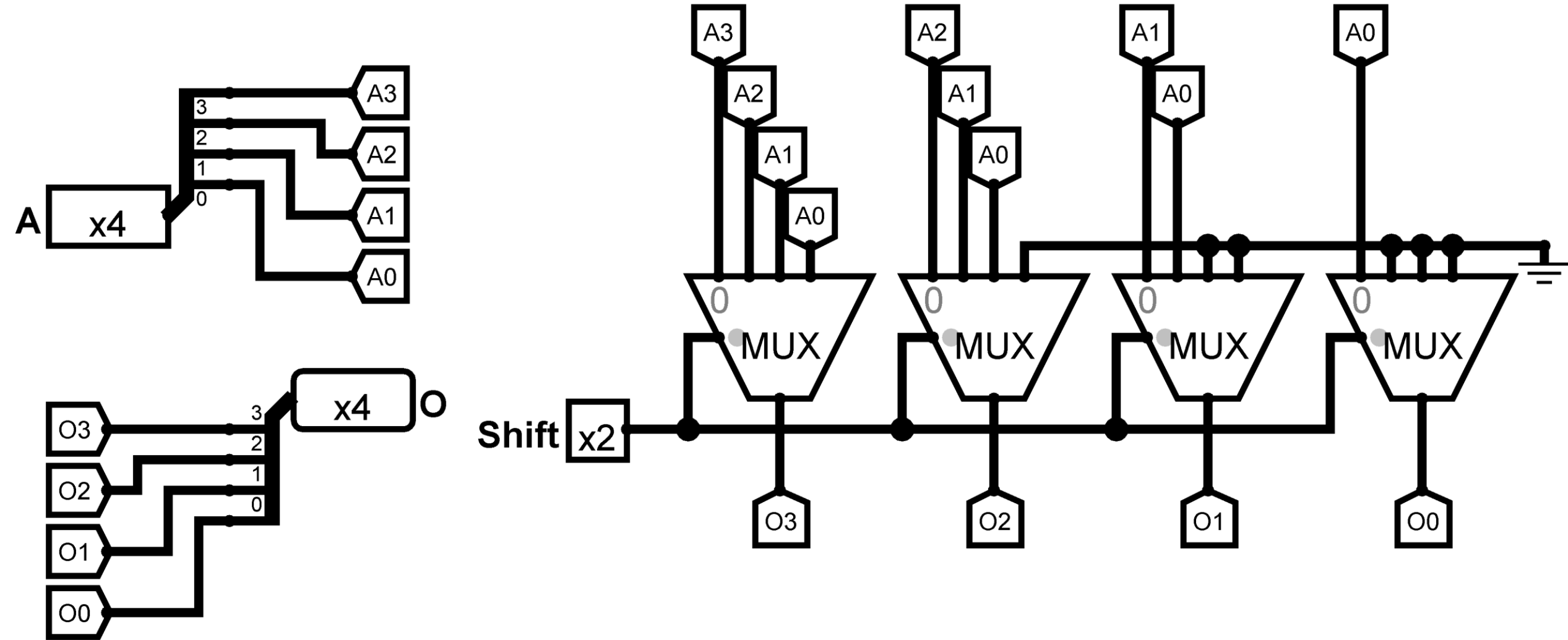



# 4-bit Left Shifter

 

Shift[1]	Shift[0]	Output	Operation
0	0	A[3]A[2]A[1]A[0]	No Shift
0	1	A[2]A[1]A[0]0	1 bit Left Shift
1	0	A[1]A[0]00	2 bit Left Shift
1	1	A[0]000	3 bit Left Shift

# 4-bit Left Shifter Simulation



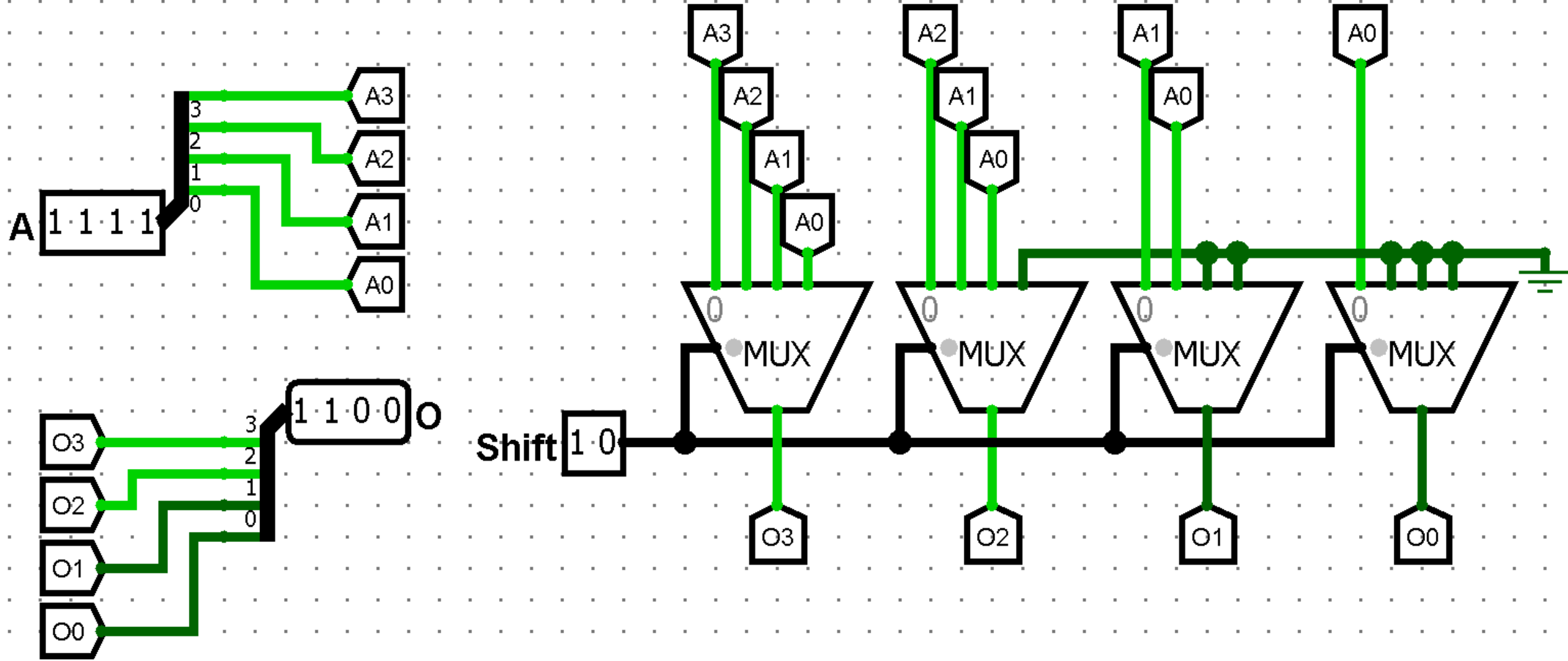


Figure: 4-bit Left Shifter Simulation for input **A** = 1111, Shift = 10 (2-bit Left Shift).  
Output **O** = 1100

# 4-bit Right Shifter

 

# 4-bit Right Shifter

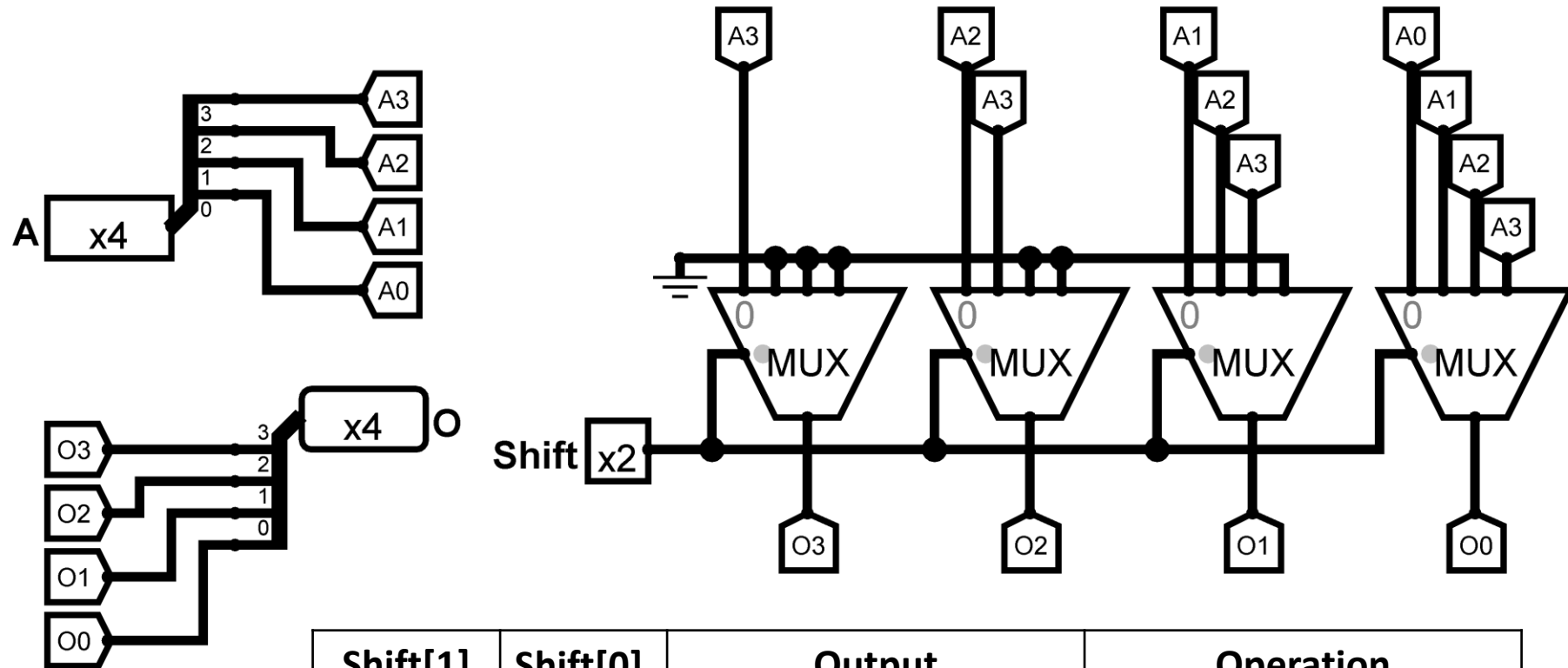

Shift[1]	Shift[0]	Output	Operation
0	0	A[3]A[2]A[1]A[0]	No Shift
0	1	0A[3]A[2]A[1]	1 bit Right Shift
1	0	00A[3]A[2]	2 bit Right Shift
1	1	000A[3]	3 bit Right Shift

# 4-bit Right Shifter Simulation



 


Figure: 4-bit Right Shifter Simulation for input **A = 1111**, Shift = **01** (1-bit Right Shift).  
Output **O = 0111**

# 4-bit Left Rotate

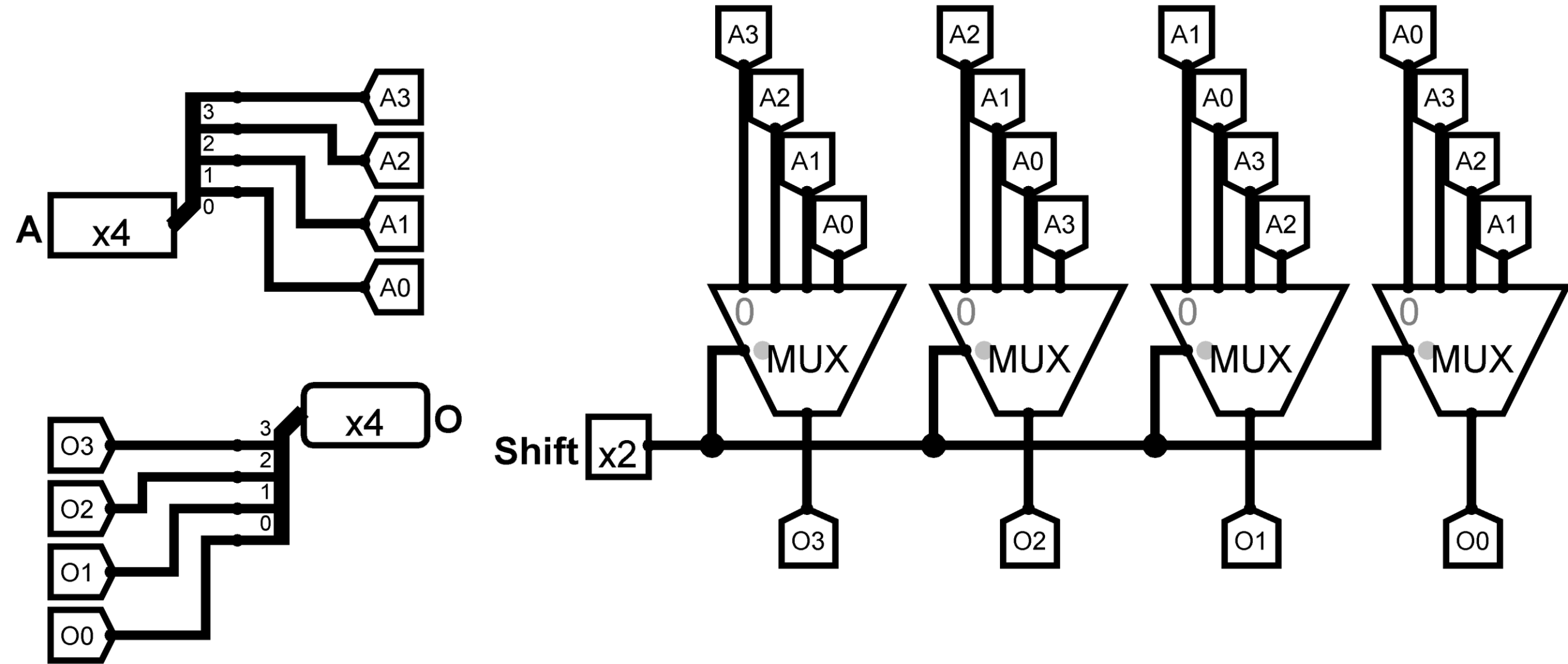

# 4-bit Left Rotate

 

Shift[1]	Shift[0]	Output	Operation
0	0	A[3]A[2]A[1]A[0]	No Rotate
0	1	A[2]A[1]A[0]A[3]	1 bit Left Rotate
1	0	A[1]A[0]A[3]A[2]	2 bit Left Rotate
1	1	A[0]A[3]A[2]A[1]	3 bit Left Rotate

# 4-bit Left Rotate Simulation



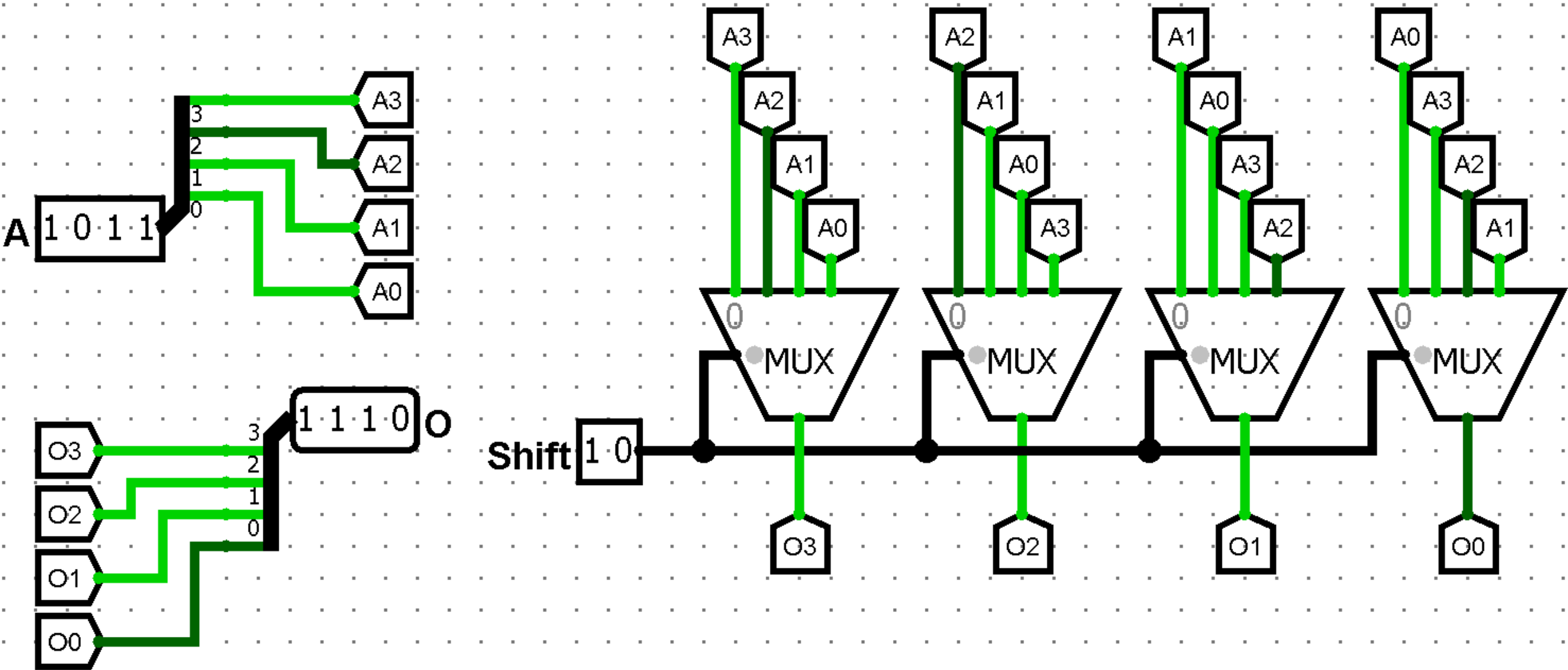



Figure: 4-bit Left Rotate Simulation for input A = 1111, Shift = 10 (1-bit Left Rotate).  
Output O = 1110

 

# 4-bit Right Rotate

 

# 4-bit Right Rotate

 

Shift[1]	Shift[0]	Output	Operation
0	0	A[3]A[2]A[1]A[0]	No Rotate
0	1	A[0]A[3]A[2]A[1]	1 bit Right Rotate
1	0	A[1]A[0]A[3]A[2]	2 bit Right Rotate
1	1	A[2]A[1]A[0]A[3]	3 bit Right Rotate

# 4-bit Right Rotate Simulation



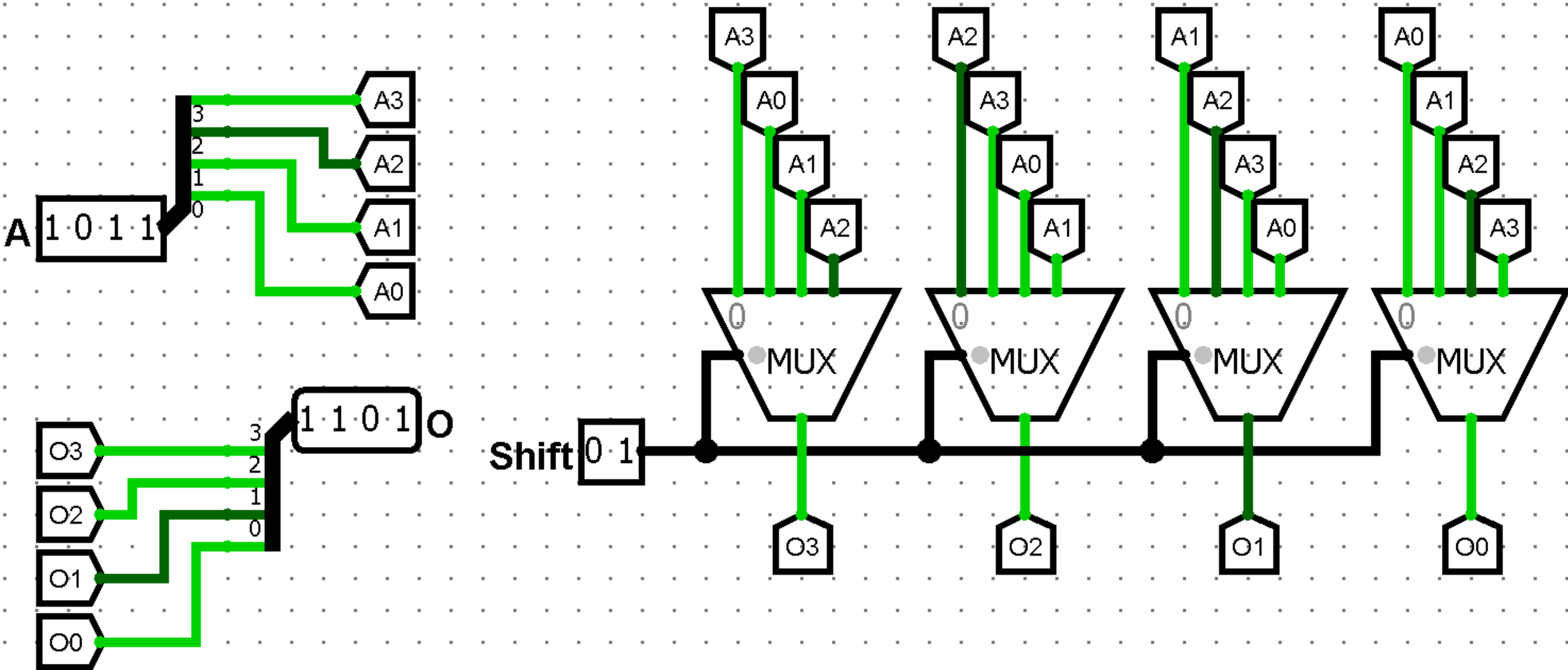
 
 
 


Figure: 4-bit Right Rotate Simulation for input **A** = 1111, Shift = 10 (1-bit Right Rotate).  
Output **O** = 1110


# Shift and Rotate Circuits Block

 

# 4-bit ALU Circuit (Final)

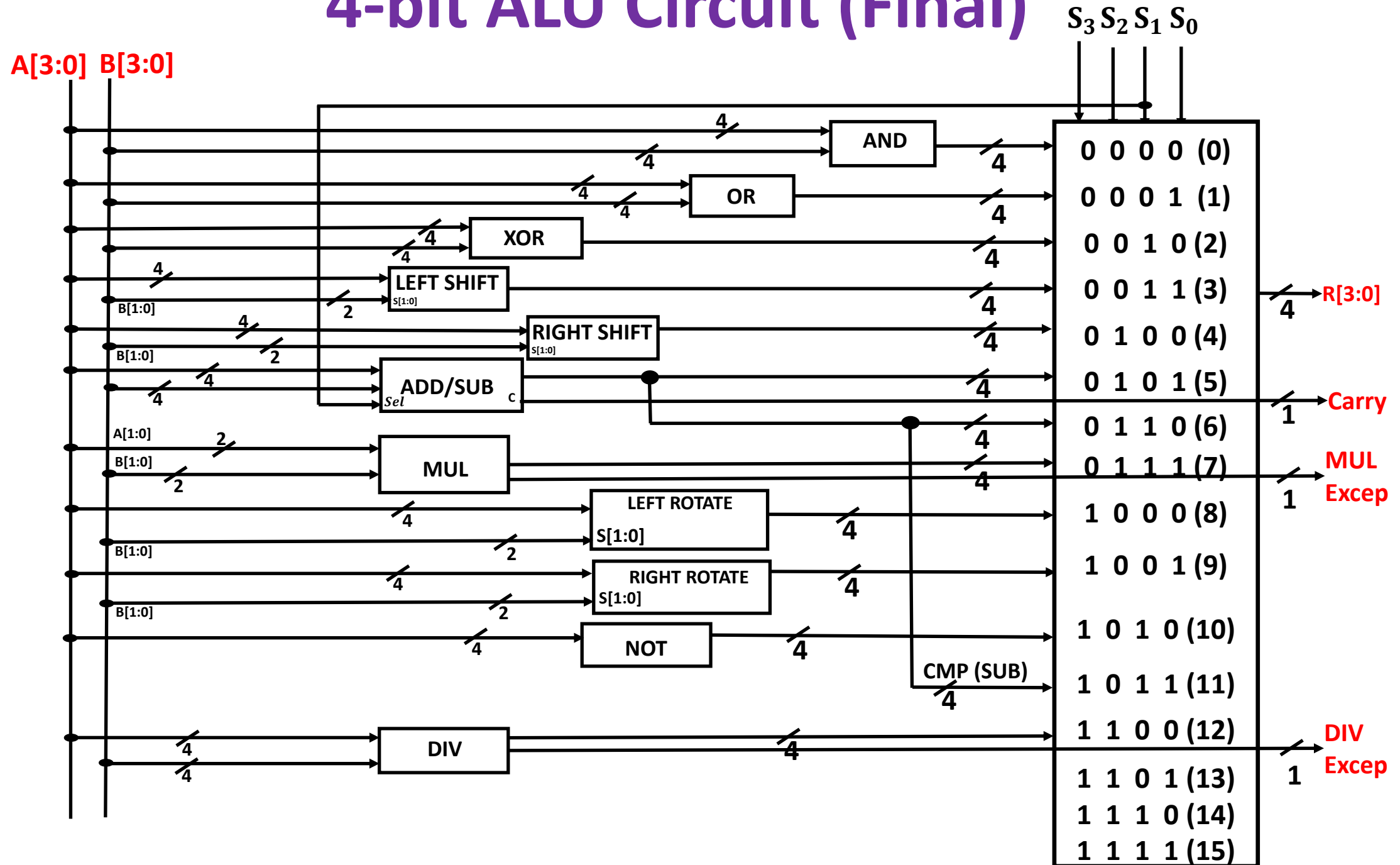

# 4-bit ALU Circuit

 


Operation	Selection lines			
	$S_3$	$S_2$	$S_1$	$S_0$
AND	0	0	0	0
OR	0	0	0	1
XOR	0	0	1	0
NOT	1	0	1	0
ADD	0	1	0	1
SUB	0	1	1	0
MUL	0	1	1	1
DIV	1	1	0	0
SHL	0	0	1	1
SHR	0	1	0	0
ROL	1	0	0	0
ROR	1	0	0	1
CMP	1	0	1	1


Here,  
 $A[3:0]$  is data to be shifted or rotated.  
And  $B[1:0]$  is number of shift/rotate (Max 3).

Here, CMP is same as SUB but it doesn't update register value.

# 4-bit ALU Design (Final)

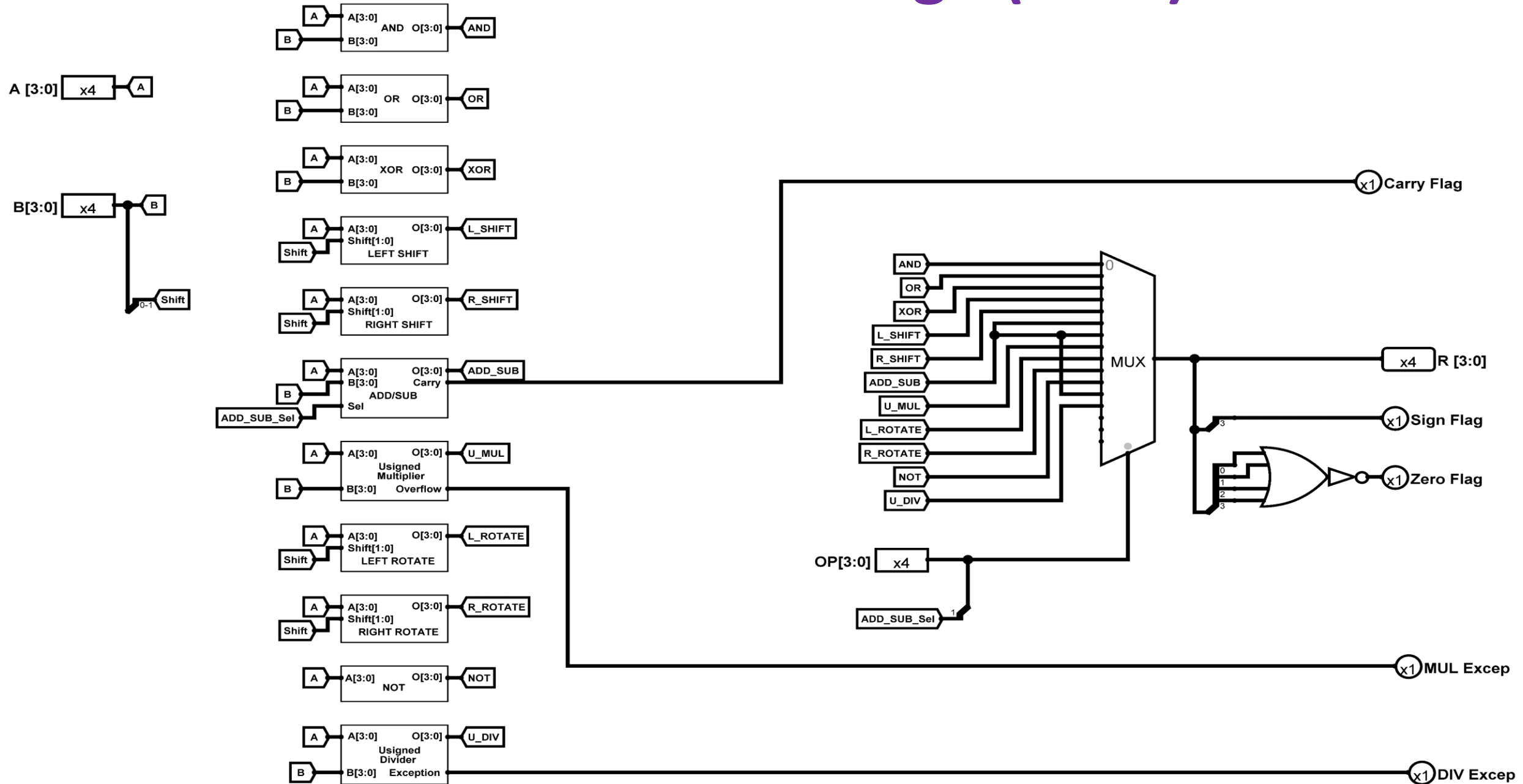

# 4-bit ALU Simulation

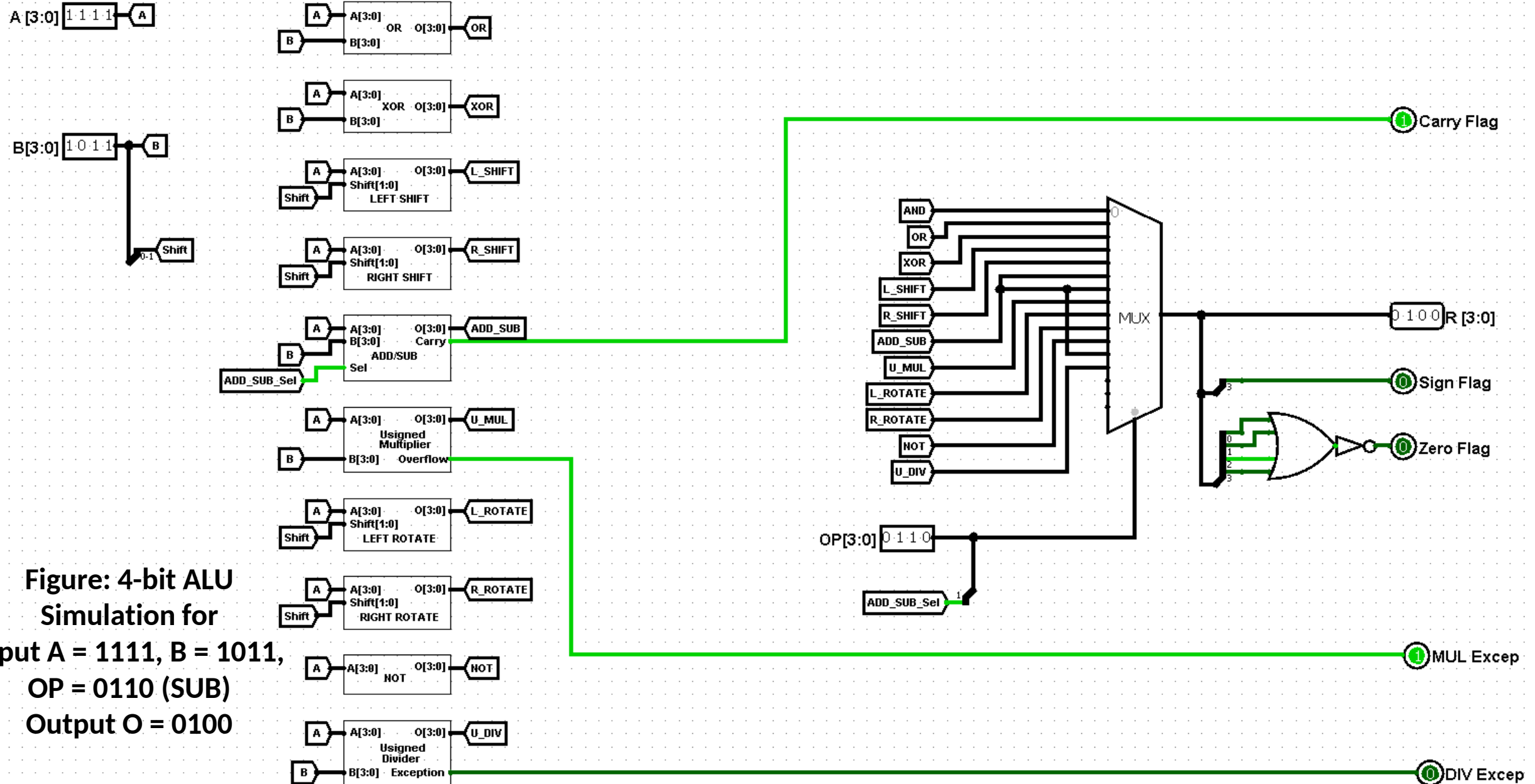



Thank You 😊